

ELECTRONICS

Australia

HiFi, Radio & Computers

DECEMBER 1979

AUST \$1.40* NZ \$1.50



Special Feature:
Giant screen
colour television



- New Compact Loudspeaker System To Build
- Fan Speed Control
- Electronic Bongos

UNIQUE.

Philips Motional Feedback Speakers.

Every now and then a technical breakthrough is achieved and a unique product emerges to set a new standard in its field.

Such is the case with Philips Motional Feedback Speakers.

These electronic masterpieces have been developed after years of exacting research in our European Laboratories and, as a result, we've created a speaker system that comes very close to the ultimate in Hi-Fi reproduction.

Technically speaking, the system incorporates a piezo-electric crystal built into the woofer cone that monitors and converts the acceleration of the cone into an electric signal. The acceleration of the cone is linearly translated back to the original signal driving the loud-speaker. This signal is fed back to a comparator circuit in the amplifier incorporated in the enclosure and compared with the original signal. This enables the loud-speaker to be immediately corrected at the slightest deviation. And, in this way, the acoustic behaviour of the woofer can be completely controlled.

Each speaker contains 3 integrated power amplifiers — a 50W amplifier for bass output, 20W amplifier for mid-range and a 5W amplifier for treble — providing a total power output of 75W. And low-note filters are incorporated in each speaker enclosure for matching the bass response to the location of the box near walls and floor.

Listen to Philips Motional Feedback Speakers. They'll speak for themselves.

Technical specifications: Model AH 5875

Type of enclosure:	Motional Feed Back box with three amplifiers
Internal volume:	19 litres
Total power of amplifiers:	75W cont. sine wave power
Loudspeakers:	AD81671/MFB4, 8" woofer AD21160/ST 8.15 combi dome squawker/tweeter
Cross-over frequencies:	650 Hz and 3500 Hz
Frequency characteristic:	27-20,000 Hz
Input sensitivity:	variable; impedance up to 3V: 100 kohm above 3V: 1 kohm switchable

Low-note filters:

Amplifier for woofer

Output power:	50W cont. sine wave power
---------------	---------------------------

Amplifier for squawker

Output power:	20W cont. sine wave power
---------------	---------------------------

Amplifier for tweeter


Output power:	5W cont. sine wave power
---------------	--------------------------

Also available Model AH585

Output power:	35W cont. sine wave power
---------------	---------------------------

Subject to modification without notice

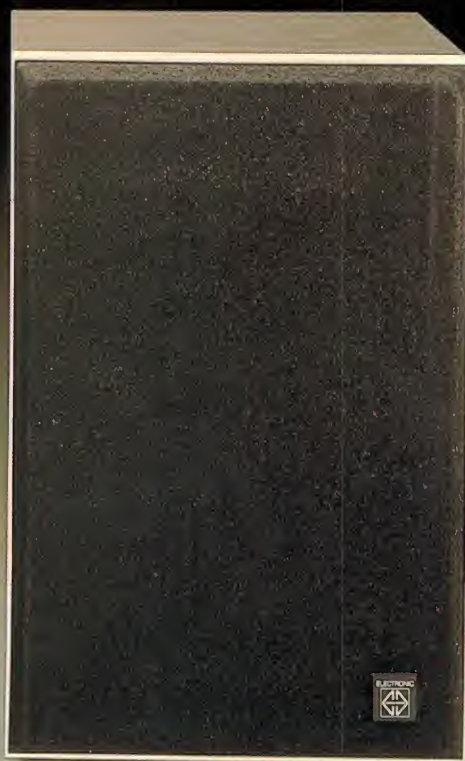Philips Motional Feedback Speakers.
A step closer to sound perfection.



PHILIPS

367 2219

We want you
to have the best




ELECTRONICS

Australia

Volume 41 No. 9

December, 1979

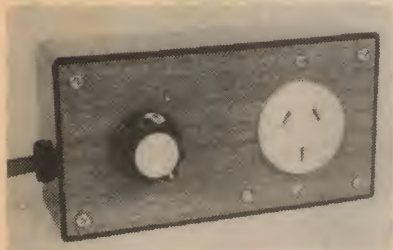Australia's largest selling electronics magazine



Summer is with us and the nights are hot and sticky. Our new fan speed control will help you sleep by slowing your fan to a whisper-quiet breeze. See p68.



Pushed for space but still want big sound? The new Playmaster 3-13L compact loudspeaker system should fill the bill. Find out more on p54.

COMING NEXT MONTH! — find out what's coming by turning to p44.

On the cover

NATIONAL'S "CinemaVision" TC-6200A video projection system gives a theatre size image in relation to your home living room. A report on the latest developments in giant screen colour television begins on p10. (Photo courtesy National Panasonic).

SIMULATED on-screen picture: you could save money and petrol by building our new electronic ignition system for your car. Details on p60. (Drawing by staff artist John Peterson).

FEATURES

GIANT SCREEN COLOUR TELEVISION <i>The latest developments</i>	10
CURRENT — WHICH WAY DOES IT FLOW? <i>Clearing the confusion</i>	18
HOME MOVIES '79, PT. 2 <i>The projectors</i>	25
POWER LINE INTERFERENCE <i>Another approach</i>	32

HIFI TOPICS AND REVIEWS

NEW GENERATION DYNAMIC SPEAKERS <i>Oil-cooled voice coils</i>	39
HIFI REVIEW <i>Audio Reflex EQ-1 10-band graphic equaliser</i>	47
HIFI REVIEW <i>Peerless PAS-50 loudspeaker system</i>	49
WORLD'S SMALLEST FULL SIZE PHONO PLAYER <i>Courtesy of Matsushita</i>	50
AUDIO TALK <i>Which kind of disc is best?</i>	52

PROJECTS AND CIRCUITS

PLAYMASTER 3-13L COMPACT LOUDSPEAKERS <i>Build your own & save</i>	54
TRANSISTOR-ASSISTED IGNITION SYSTEM <i>Save petrol by keeping you car in tune</i> ..	60
FAN SPEED CONTROL UNIT <i>Keep your cool on hot summer nights</i>	68
PRECISION POWER SUPPLY <i>Gives mV accuracy without a meter</i>	72

SPECIALLY FOR THE NEWCOMER

ELECTRONIC BONGO DRUMS <i>Low in cost and easy to build</i>	103
EXPERIMENT WITH DIGITAL COUNTERS <i>And learn about flipflops</i>	110

MICROCOMPUTERS

AN RS-232C INTERFACE FOR YOUR COMPUTER <i>Easier, than you think</i>	81
HOW TO USE YOUR 2650 SYSTEM TO GENERATE RANDOM MORSE	86
ADAPT YOUR D2 KIT TO RUN CHIP-8 PROGRAMS <i>Use Dream 6800 software</i>	89
MICROCOMPUTER NEWS & PRODUCTS	96

AMATEUR RADIO, CB SCENE, DX

CB SCENE <i>First US-style REACT team set up in Sydney</i>	123
AMATEUR RADIO <i>Amateur radio clubs — their aims and activities</i>	125
SHORTWAVE SCENE <i>Test transmissions from Africa Number One</i>	128

COLUMNS


FORUM <i>Repair, up-date or throw it away?</i>	34
THE SERVICEMAN <i>First aid (and last gasp) for an old TV set</i>	74
RECORD REVIEWS <i>Classical, popular and special interest</i>	118

DEPARTMENTS

EDITORIAL 3 — NEWS HIGHLIGHTS 4 — CIRCUIT & DESIGN IDEAS 77 —	
LETTERS TO THE EDITOR 116 — NEW PRODUCTS 131 — BOOKS & LITERATURE	
134 — INFORMATION CENTRE 138 — MARKETPLACE 141 — INDEX TO	
ADVERTISERS 144 — NOTES & ERRATA 139.	


SOANAR CAPACITORS

RP PCB Can Electrolytic

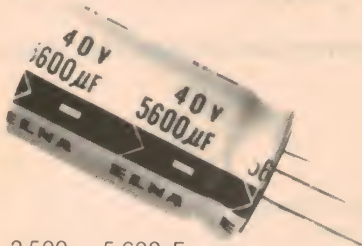

2,500 — 5,600µF
35V — 80V DCW

RB Radial Electrolytic

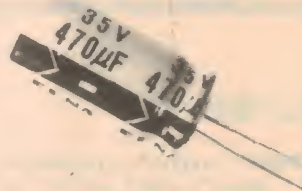

.47 — 2,500µF
6.3V — 450V DCW

RG/RD Lug Terminal




90 — 8000µF
15V — 450V DCW
SINGLE, DOUBLE, TRIPLE

DT Polypropylene Film




.01 — .47µF
200V — 630V DCW

RBP Bi-Polar Electrolytic

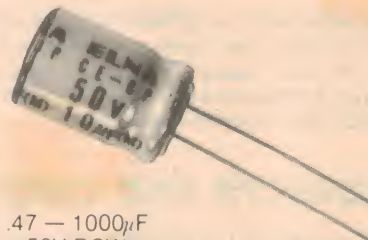

.47 — 1000µF
50V DCW

Computer Grade Electrolytic

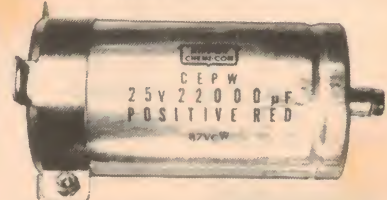

2900 — 68000µF
16V — 40V DCW

TL/TH Ceramic Disc.



1.0PF — .47µF
63V + 630V DCW

TAD Tantalum Electrolytic




.1 — 100µF
3.15V — 35V DCW

NL/NH Polyester Film




.001 — 10µF
100V — 630V DCW

RT Axial Electrolytic

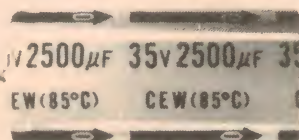

.47 — 4,700µF
6.3V — 500V DCW

PS Polystyrene Film

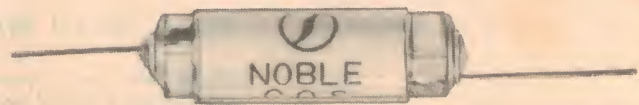

10PF — .01µF
125V DCW

Available ex-stock in all states.

Technical literature available on request.

SOANAR Electronics Pty Ltd

A MEMBER OF THE A+R-SOANAR ELECTRONICS GROUP

30-32 Lexton Road, Box Hill, Vic., 3128, Australia. Telex: 32286.



SALES OFFICES PHONES

VICTORIA: 89 0661
N.S.W.: 789 6733
Sth. AUST.: 51 6981
QUEENSLAND: 52 5421
WEST. AUST.: 381 9522



Editorial Viewpoint

EDITOR-IN-CHIEF

Neville Williams
M.I.R.E.E. (Aust.) (VK2XV)

TECHNICAL EDITOR

Leo Simpson

ASSISTANT EDITOR

Greg Swain, B.Sc. (Hons, Sydney)

TECHNICAL PROJECTS

Ron de Jong, B.E. (Hons, NSW), B.Sc.
Ian Pogson (VK2AZN/T)

John Clarke
Gerald Cohn

GRAPHICS

Robert Flynn

PRODUCTION

Danny Hooper

ADVERTISING MANAGER

Selwyn Sayers

CIRCULATION MANAGER

Alan Parker

How about being frank for a change . . .

Just before this issue went to press, it was revealed that the reactor at Lucas Heights near Sydney had been shut down for periodic major overhaul; that certain glands were to be replaced, which had begun to seep heavy water coolant — an innocuous occurrence that had been foreseen and provided for when the reactor was commissioned more than 20 years ago.

But it was too innocuous for some sections of the media, still mindful of the mileage they had got from the nuclear mishap at Harrisburg, USA. We had our very own nuclear "incident", "accident", "leak", "escape", right here on Sydney's doorstep. Our own Harrisburg, with posters and banner headlines to match!

In vain, scientists protested that there was nothing unsafe about the situation. They were challenged, rather, to give an unequivocal undertaking that there could never be an accident in the reactor. When they couldn't, it was interpreted as admission of a tangible risk. This was picked up by TV crews who toured the district and questioned residents about fears that had thus been heightened.

Positive feedback indeed!

I wonder whether the self-same news teams sought an unequivocal guarantee from their driver that they would not be involved in an accident on the way back to the studio? Of course not; they accepted the statistical likelihood that they would arrive safely at their destination. Literally, everything we do is based on that kind of judgement, so why the exception about a modest research reactor?

If some sections of the media stand condemned, what about the Premier of NSW? He made further headlines by allegedly rejecting an assurance from the Deputy Prime Minister, not on scientific grounds, but because it was qualified by "I am advised . . ."

I ask you: how else would the Deputy Prime Minister — a grazier/politician — have an opinion, unless it was based on advice from scientists who understand the workings of a nuclear reactor?

It is difficult to escape the conviction that, right across the political spectrum of Australia, frankness, commonsense and even truth itself is being sacrificed to personal and political point scoring. Blame the press, blame the politicians, blame who you like, but the spirit of honest inquiry, honest debate and honest consensus is a casualty of our present era.

I also happen to believe that the public is becoming heartily sick of the humbug. Maybe they — we — are ready to respond to leadership at all levels which lays a little more emphasis on frankness and truth.

— Neville Williams

Registered for posting as a publication —
Category B.

Printed by Magazine Printers Pty Ltd, of Regent Street, Sydney and Masterprint Pty Ltd of Dubbo, NSW, for Sungravure Pty Ltd, of Regent St, Sydney.

Editorial Office

57 Regent St, Sydney 2008.
Phone (02) 699 3622
Postal Address: PO Box 163, Beaconsfield 2014.

Advertising Offices

Sydney — 57 Regent St, Sydney 2008.
Phone (02) 699 3622
Representative: Narciso Pimentel.

Melbourne — 392 Little Collins St, Melbourne 3000. Phone (03) 602 3033
Representative: Keith Watts

Adelaide — Charles F. Brown & Associates Ltd, 254 Melbourne St, North Adelaide 5006
Representative: Sandy Shaw, (08) 267 4433.
Perth — 454 Murray Street, Perth 6000
Representative: Ashley Croft. (09) 21 8217.

Subscriptions

Subscription Dept, John Fairfax & Sons Ltd, GPO Box 506, Sydney 2001.
Enquiries: Phone (02) 20944, ext 2589.

Circulation Office

21 Morley Ave, Rosebery, Sydney 2018
Phone (02) 663 3911

Distribution


Distributed in NSW by Sungravure Pty Ltd, 57 Regent St, Sydney; in Victoria by Sungravure Pty Ltd, 392 Little Collins Street, Melbourne; in South Australia by Sungravure Pty Ltd, 101-105 Weymouth St, Adelaide; in Western Australia by

Sungravure Pty Ltd, 454 Murray Street, Perth; in Queensland by Gordon and Gotch (A'asia) Ltd; in Tasmania by Ingle Distributors, 93 Macquarie St, Hobart; in New Zealand by Gordon and Gotch (NZ) Ltd, Adelaide Rd, Wellington.

Copyright. All rights reserved

Devices or arrangements shown or described herein may embody patents. Information is furnished without responsibility for its use and without prejudice for patent rights. All manuscripts, photographs and other material submitted to Electronics Australia for publication must be accompanied by a stamped, addressed envelope. Contributions are submitted at the sender's risk, and responsibility for loss cannot be accepted by Electronics Australia.

*Recommended and maximum price only.

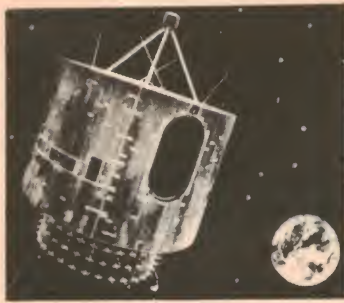

News Highlights

IBM to make video disc player!

The news that International Business Machines (IBM), the \$21 billion US computer giant, is moving into consumer electronics will send a shiver down the spines of some competitors.

by Max Wilkinson
Financial Times

IBM has announced a joint venture with MCA of the US to make video disc players. These are expected to be compatible with units jointly developed by MCA and Magnavox, a subsidiary of Dutch Philips, and launched recently onto the US market in Atlanta, Georgia.

However, the race to perfect and market a viable video disc system is still at first base. Several other large corporations, including RCA of the US and JVC (a subsidiary of Matsushita), are at an advanced stage of development of their own product, using a completely different system of recording and

playback from that of the Philips/MCA laser system.

The Philips/MCA laser system has many potential advantages over its rivals: the disc can be protected by a plastic coating and should last indefinitely; individual picture frames can be "frozen"; and, most important, it has very large capacity. The main drawback is that the disc is expensive to produce and there have been production problems with the cutting of the discs.

This is where IBM comes in: it has also been researching video disc technology for a completely different purpose. It would like to use discs for high density storage of computer data. Philips has also been interested in this possibility.

The reason that the computer industry and the home entertainment industry can make use of a basically similar machine is that video discs are recorded in the computer language of digital pulses. From the point of view of

the machine, it makes very little difference whether the millions of digits on a video disc are encoding data or represent a moving picture.

The joint development with IBM has therefore a number of interesting implications for the future of both industries.

Firstly, it has been estimated that sales of video players to the computer industry could outnumber consumer sales by perhaps 10 to one. This means that high development costs could be more rapidly amortised, so that consumers could get a cheaper product more quickly — very important in the take-off phase of the market.

In the longer term, the advantages of digital techniques for sound only recordings are expected to be exploited by high fidelity manufactures. The largest size disc could hold more than 12 hours of continuous music, but more important, the sound quality would be better and less prone to deterioration than with conventional recordings.

British windmill is hurricane proof

A new generation of windmills developed in Britain are self-starting, unaffected by changes in wind direction — and will automatically adjust their aerofoil sails to withstand even hurricane winds. They can be used for electrical generation or for water pumping.

Most modern wind turbines revolve around a horizontal axis — as did their original and traditional counterparts — but the new British turbine rotates around a vertical axis. One major advantage of this design is that it does not matter from which direction the wind blows, the turbine will always rotate.

In high winds, conventional turbines must shut down to avoid destruction by the huge forces exerted on the structure. This new British turbine will shortly be used to power a lighthouse in the

Leeward Isles and the manufacturers are confident that it will operate successfully even in hurricane conditions.

The turbine has straight aerofoil blades each of which is attached to its supporting crossarm by a hinge. In average wind speeds of 5-7 metres per second the blades are near the upright position, but as the wind increases the ends of the blades cone outwards — due to centrifugal force — preventing damage caused by bending.

A further advantage of the vertical windmill is that as the rotor gives direct drive to the vertical shaft there is no need for complex, energy-absorbing gearing at the top of the turbine.

There are two versions available at present: a six metre version, seen here, producing 3200 watts shaft power in a 10m/s wind and a 500W 4.5 metre version specifically designed for generating electricity in remote areas.



Further information may be obtained from PI Specialist Engineers Ltd, The Dean, Alresford, Hampshire, England.

Speech aid for handicapped

At first sight "Splink" looks like one of the new electronic games played on a television set, but is in fact a new communication aid for the deaf and speech handicapped. Invented and developed in Britain, Splink is a microprocessor controlled device linked to an ordinary television set and has a keyboard on which there are 950 basic words and phrases.

The user presses the appropriate words on the keyboard and these appear as complete sentences on the screen. The keyboard includes some basic phrases such as "I want a . . ." and "What did you say?" Words that are not

on the keyboard can be built up from the initial letters of some of the words that are available. Splink has a constantly available visual memory of about 110 words enabling the user to see on the screen not only what has been said, but how it was worded.

The keyboard can be used up to 6m from the TV set and has no trailing wires connecting the two. The secret is an infra-red datalink between the board and the microprocessor unit.

You can obtain further information on Splink from Medelec Ltd, Manor Way, Old Working, Surrey, GU22 9JU, England.



US award for Australian "talkies" pioneer

The man who put sound into the first Australian talking movies, Mr Arthur Smith, has been elected a fellow of the Society of Motion Picture and Television Engineers.

Mr Smith, who is 77, becomes only the third Australian to be accorded one of the greatest honours of his profession. He developed the sound recording equipment used by Cinesound in the thirties, and was the company's chief recording engineer from 1931 to 1958.

He first became interested in the

recording of sound for films in 1929, and was involved with some of the earliest systems using tungston arc discharge tubes and, later, mercury vapour discharge tubes. The American-based society made its award to Mr Smith because of his outstanding career as an innovator.



Video recorders are lawful says US court

A US District Court judge has ruled that the non-commercial use of home video recorders to record television broadcasts is lawful, clearing the way for further expansion of a rapidly growing segment of America's consumer electronics industry.

The decision upheld the right of the Sony Corporation and, indirectly, other companies, including RCA Corporation, to market such recorders.

The suit, which has been widely followed in the electronics industry, was brought three years ago by Universal City Studio Inc and Walt Disney productions. They asserted that the sale of the recorders unlawfully facilitated the theft of copyrighted materials and would result in millions of dollars in lost sales.

Lawyers for Sony argued that use of the recorders was legal, and asserted that the major factor in Universal Studio's decision to bring the suit was the planned introduction of the videodisc playback system developed by MCA Corporation, Universal's parent company.

Spacecraft to probe Sun's polar regions

Man is expected to take his first look at the polar regions of the Sun as a result of a combined European-US space project planned for 1983.

These regions cannot be seen from Earth or from satellites in earth orbit. Now, under an agreement signed between the European Space Agency (ESA) and the US National Aeronautics and Space Administration (NASA), two spacecraft will travel in orbits passing directly over the Sun's poles.

NASA and the 11 country ESA will each provide a spacecraft and Britain, Germany, France and Switzerland will supply experiments for the craft.

The two spacecraft will be launched together, probably in February 1983 from the American space shuttle vehicle. They will be directed towards Jupiter along similar trajectories by booster rocket and then swing round the giant planet, using its gravity to redirect their paths into orbits passing directly over the Sun's north and south poles.

Scientists believe that by sending one craft over each pole simultaneously they can compare solar and interplanetary phenomena affected by the differences in activity between the northern and southern solar hemispheres.

SHAWMUT®

Electronic
Components
and Materials



STATE OF THE ART FUSES

Electronic products are becoming increasingly sophisticated, and Shawmut engineers work closely with "state of the art" circuit designers to meet and exceed the protective needs of their products.

The Form 101 series of current limiting rectifier fuses protects semiconductor power diodes (rectifiers), thyristors, triacs and other solid state devices against short circuit faults to which they are particularly susceptible because of their intrinsic low overload capability. Short data is listed below.

These Shawmut fuses are available off-the-shelf in a range which can meet your most critical specifications.

The popular "One-time" switch and panel fuses and the "Trionic" dual-element motor starting and protection fuses are also listed. Many other fuse series are available for electrical applications.

For details of the full and comprehensive range of Shawmut fuses contact:
Philips Electronic Components and Materials,
P.O. Box 50, Lane Cove, N.S.W. 2066
Ph: (02) 427.0888



SHAWMUT FUSE DATA


Fuse Type	Amp. Ratings	A.C. Volts	Dimensions	U.L. Class	Interrupting Rating A.C. RMS Amps	Where Used
ONE-TIME	1-600	250 600	N.E.C. Holders	K-5	50,000	Switches, Panelboards fusible equipment
TRIONIC Dual Element	1/10-600	250 600	N.E.C. Holders	RK5	200,000	Motor starting and protection.
AMP-TRAP Form 101 Rectifier fuses	1-10,000 1-5000 1-2000 35-1600 20-1600 20-1600 20-800 20-800 20-600 20-600	130 250 600 500 700 1000 1200 1500 2000 2500	Clip or Bolt Mounting	*N.A.	200,000	Semi-conductor, rectifier, diode, SCR protection. D.C. power supplies Inverters U.P.S. systems Controls Variable speed drives Mine power supplies Special applications, A.C. or D.C.

*Not applicable

AVAILABLE THROUGHOUT AUSTRALIA FROM



AND

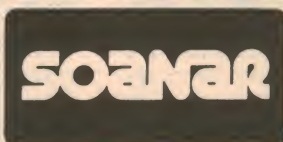

PHILIPS

153.0241

NEWS HIGHLIGHTS

Meteor trail communications feasible

Menlo Park, CA — The hundreds of millions of meteors that enter the Earth's atmosphere every day leave in their wake a very inexpensive communications medium — the meteor trail. This naturally occurring band of ionized particles can be used instead of man-made satellites to relay brief radio messages up to 2000km.

Using these "natural satellites" could reduce the cost of communications systems for a wide range of applications according to Charles P. Mason, a senior

consultant at SRI International. The meteor trails could be used as an effective alternative to satellites for ship-to-ship, ship-to-shore, and even air-to-ground communication systems. They could also be used to relay data on icebergs, pollution, earthquakes and weather.

Meteor burst transmission systems work in several stages. Sensors at remote sites gather and store data, such as temperature or precipitation measurements. Meanwhile, a

microprocessor-controlled central station emits a continuous radio signal, which bounces off a meteor trail whenever one occurs within range. When this signal reaches a transceiver at the remote site, it triggers the transmission of the stored data, via the meteor trail, to the central station.

The meteor trails last up to a few seconds — ample time to transmit the message. And the frequency of meteor showers allows for up to 100 message exchanges an hour!

Meteor burst transmission technology has enjoyed limited use since SRI pioneered its development in the 1950s. Now, says SRI, microprocessors have reduced hardware costs and improved reliability to the point where far greater exploitation of the medium is possible.

Electronics courses at Newcastle Tech.

Newcastle Technical College wishes to advise readers that it provides a wide range of electronics courses for residents of Newcastle, the Hunter Valley, and northern NSW.

These courses include the Electronics Trade Course, which replaces the older Radio Trades Course. The course has recently been broadened to include both analog and digital techniques, and offers a range of optional subjects in stage 3 in specialised areas of industry. It can be taken either as a full-time pre-

apprenticeship course, or in block release pattern.

Others courses offered include Post Trades Television, Radio Transmission, Industrial Electronics, Basic Electronics, Two Way Radio Users Course, Technical Principles of Two Way Radio, and Television Studio Techniques.

Further information is available from The Senior Head Teacher, School of Applied Electricity — Electronics Division, Newcastle Technical College, Maitland Rd, Tighes Hill, NSW 2297.

Pollution-free thermal power plant

Menlo Park, Calif. — Led by scientists at SRI International, formerly Stanford Research Institute, an industrial team has designed a solar power plant which could produce electricity more cheaply than coal.

The SRI scheme envisages 440 small, clean 100MW solar thermal power plants serving the southwestern US states within 30 years. The design concept is said to represent a major advance in the generation of cheap electricity from solar energy.

SRI calls its design a "line-focus" system because its sun reflectors (heliostats) are arranged in rows. Each heliostat, a long mirrored panel backed by fibreglass-reinforced cement, tilts upward to reflect sunlight toward a long receiver raised on steel towers. Sunlight concentrated in the receiver cavity heats salt, which is used to generate steam for a conventional turbine generator. The plant can store extra heat to generate electricity through the night.

Several features beside possible cost savings make the plant attractive. Additional groups of heliostats can easily be attached to the existing system to increase its capacity. And, as soon as the storage system and generator are in place, the first group of heliostats can start reflecting sunlight to generate electricity. Thus, unlike other solar plant designs that cannot operate until fully built, the line-focus system can produce solar energy while it is still being built.

In addition, solar power plants pose no pollution threat and could be placed close to communities, thus keeping transmission costs down. Traditional fossil fuel stations would provide back-up for the solar stations during extended periods of cloud cover.

Business Briefs:

D. D. Webster Electronics Pty Ltd has appointed Anderson Digital Equipment Pty Ltd (ADE) as its sole sales representative for Australia, New Zealand, and Papua-New Guinea. Under the agreement, ADE will be responsible for sales and service of Webster's Computex Spectrum-11 range of small business computers. This includes Spectrum models A, B, C, D, E, F and Z with disc capacities ranging up to 2.52 megabytes. Further information on the Spectrum-11 range from Anderson Digital Equipment Pty Ltd, 1 Expo Court, Mt Waverley, Vic 3149.

Mr B. R. Goddard, Regional Managing Director of the **Plessey** group, has announced the resignation of Mr David Towey from the position of General Manager of Plessey Data Systems. Mr Malcolm Humphreys has been appointed acting General Manager of the division.

Fairchild Australia Pty Ltd has moved to new premises at Suite 1, First Floor, 366 Whitehorse Rd, Nunawading, Victoria 3131 (telephone 877 5444). The company's NSW branch office is at Third Floor, FAI Insurance Building, 619 Pacific Highway, St Leonards 2065 (telephone 439 5911).

Sanyo Australia Pty Ltd has moved to new national headquarters at 225 Miller St, North Sydney 2060 (telephone 02 436 1122). The move completes the transfer of Sanyo's corporate headquarters from Melbourne and marketing head office from Lane Cove.

National Semiconductor Corporation, California, has reported first quarter fiscal 1980 sales of \$US242, up 31% over 1979. Earnings were put at \$12.5 million, or 93c per share, up from 65c a year ago, a 43% increase.

UNIQUE GIFT IDEAS FROM TANDY



TANDY
ELECTRONICS

A. Tandy AM Telephone Radio (12-1921)	19.95	H. Tandy Hand-Held Rocket Pinball Game (60-2140)	39.95
B. Radio Shack TRS-80 4K Level I Computer (26-9051)	699.00	I. Micronta Indoor/Outdoor Electronic Thermometer (63-651)	29.95
C. Lotus English Formula I Racecar AM Radio (12-960)	19.95	J. Tandy Portable Electronic Golf Game (60-2148)	29.95
D. Slot Machine, Cordless electric fully automatic (60-2119)	6.95	K. Tandy Electronic Portable Baseball Game (60-2147)	36.95
E. Draw Poker Cordless Electric Fully Automatic (60-2118)	6.95	L. Micronta Electronic Fever Thermometer (63-652)	39.95
F. Micronta Electronic Blood Pressure Tester (63-660)	89.95		
G. Radio Shack Rolls Royce AM Radio (12-963)	19.95		

May be obtained from any Tandy Electronics Store or Participating Dealer

EEEMC'79 a success

Equipment from more than 130 companies went on display at the 5th Electrical Electronic Engineering Measurement and Control (EEEMC) Exhibition and Convention held in Sydney last October. On show were items ranging from electronic components through small business computer systems to heavy industrial equipment.

A number of seminars were held in conjunction with the exhibition, and dealt mainly with the use of microprocessors and computers in industrial plant. Energy needs and conservation measures were also considered.

Contributing sponsors included the Institute of Instrumentation and Control Australia (NSW Branch); the Microprocessor Group of the Institute of Radio and Electronics Engineers; the Institute of Engineers, Australia; the Australian Electrical and Electronic Manufacturers' Association; and the Micro-Computer Enthusiasts' Group.



Vicom International showed Leader test instruments and a range of professional communications equipment.



Roger Ellis (right) and Nick Fondas (centre) were on hand to demonstrate TI's 5T1 Programmable Control System.



The latest test equipment from Hioki Electric Works was displayed by H. Rowe & Co. Pty Ltd.



John F. Rose showed a range of business computer systems.



Computerland displayed the 16K Apple II Plus computer.

Three new ways to low-cost,
super-bright

Giant screen colour television

Things are really looking good when it comes to projection-type big screen colour TV sets. The latest generation of sets provides brighter, crisper pictures than ever before, and the systems currently being developed look like producing even better results again — at lower cost.

by C. P. GILMORE

I have just returned from a trip to a small laboratory/factory in the shadow of MIT in Cambridge, Massachusetts, to a plant just outside Cape Kennedy, Florida, to a plastic-lens factory in the rolling hills east of Cincinnati. In these diverse facilities, a new generation of projection television is being readied for production. Some of these units will be on the market before the end of this year. I am convinced that they will launch a new age of giant-screen projection TV for the home.

Of course, projection TV has been around for some time. Advent put a high-quality set on the market back in 1972. Other three-tube sets using both Schmidt and refractive optics (see diagrams) have come on the market since then, and are now available in the \$3000-\$5000 range. Also available are a number of "one-eyed monsters" — small television sets in a box with a projection lens in front of the screen. They project a considerably dimmer image (though some are okay in sub-

dued light), and most fall in the \$1000-\$2000 range.

Two of the three new approaches I've just seen are similar to current three-tube sets: One is a Schmidt; the other, refractive. But they feature advances that make them dramatically cheaper and at the same time brighter and sharper. The third is totally new. All three produce high-quality, super-bright projection TV at a price substantially below anything remotely comparable in quality today.

The Novatron

Henry Kloss started Advent Corporation 12 years ago to make a projection-television set with a mirror inside the tube — a Schmidt projection system. "It was quite an effort to get this system, with parts that had to be kept to tolerances of within a couple of thousandths of an inch, in the tube and stabilised," he told me recently. "So I chose a heavy-handed way that I knew would work." The inner structure was composed of more than 20 steel parts, which had to be carefully assembled and aligned before being sealed in the glass envelope.

Two years ago, Kloss left Advent and retired to his basement for a year. "I had the luxury of having the time to see if I could find a more elegant way to make the tube," he continued. "If you want to reduce things to a minimum, you've got to have a mirror. You need a vacuum enclosure. You need a window for the light to get out, and a place to put the phosphor."

"Now suppose you make the mirror as part of the tube (which had been suggested, but I don't think ever done



ROGER HOWE of US Precision Lens holds revolutionary $f/1.0$ plastic lens that makes possible a refractive system rivalling the Schmidt system in brightness.

commercially before), and let the faceplate carry the phosphor. The mirror and phosphor for optical reasons must have the same centre of curvature. If you separate these two spherical surfaces by an accurately ground cylinder — the barrel — it's got to come out right. The accuracy of the position of the barrel isn't important. If it has spherical curves ground into its end, then the two end pieces will automatically be held in perfect alignment."

Kloss showed me what he meant. He set up a tube neck with a mirror, a cylinder, and an end plate containing phosphor. Then on an optical bench he shot a beam of laser light through the axis of the system. As he moved the barrel around, the laser beam showed that the two optical elements remained in perfect registration.


Once the basic concept was hatched, there remained the problem of seeing if it could be built. "Here is a little research furnace that came from my basement," he said, walking through a laboratory at his new Cambridge firm, Kloss Video. It was a 90-litre stainless-steel lobster pot enclosing a smaller pot and fitted with an elaborate array of Calrod electric heating elements. "The key was to be able to differentially heat the mirror, different parts of the cylinder, and the face-plate to appropriate temperatures. I had four Variacs for controlling heater temperatures, and night after night I sat down there trying different temperature schedules so that when the glass came out it was free of strain."

The new Novatron tube has many advantages. Because of its simplicity and ease of manufacture, it's cheaper than other Schmidt-type tubes. It's also brighter. "The electron beam has a better focusing system on it, so you can put higher beam current in," says Kloss. "And the phosphor can be kept cooler because we can get to the back of that glass and put a heat sink on it."


When I went into a lab, all fluorescent lights were on. But the picture at the far end of the room was bright and sharp. "You can measure 120 foot-lamberts in highlights on that picture," said Kloss. "We may run it slightly below that — say, in the 100 foot-lambert range. At that level, we've learned, we can get many thousands of hours of life out of the tubes; we don't know where the actual end of life is." Kloss is setting initial production plans at 100 a month, and planned to show his first commercial set with Novatron at the Consumer Electronics Show in Chicago last June.

The refractive-optics system

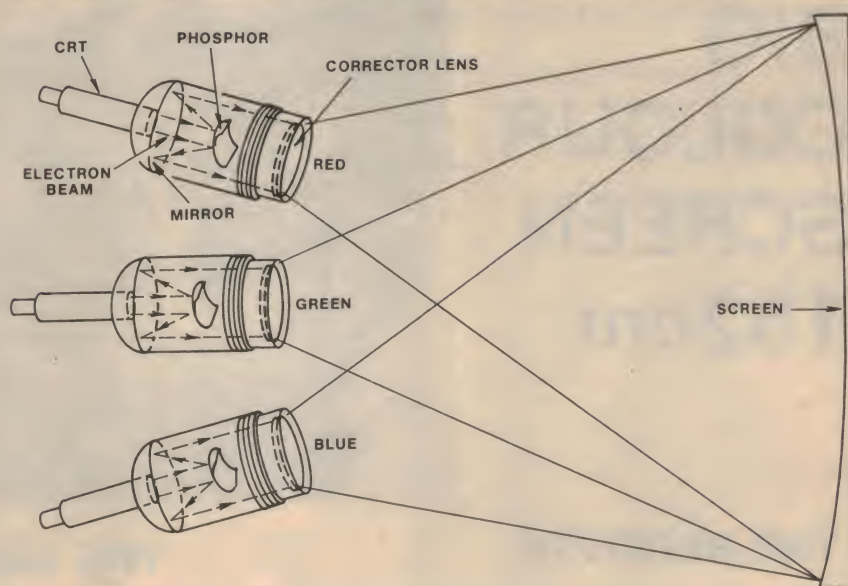This approach is now being championed by Roger Howe, chairman of the board of US Precision Lens, which makes the revolutionary lenses that really put refraction systems in the super-bright category. But oddly, this approach, too, was launched by Henry



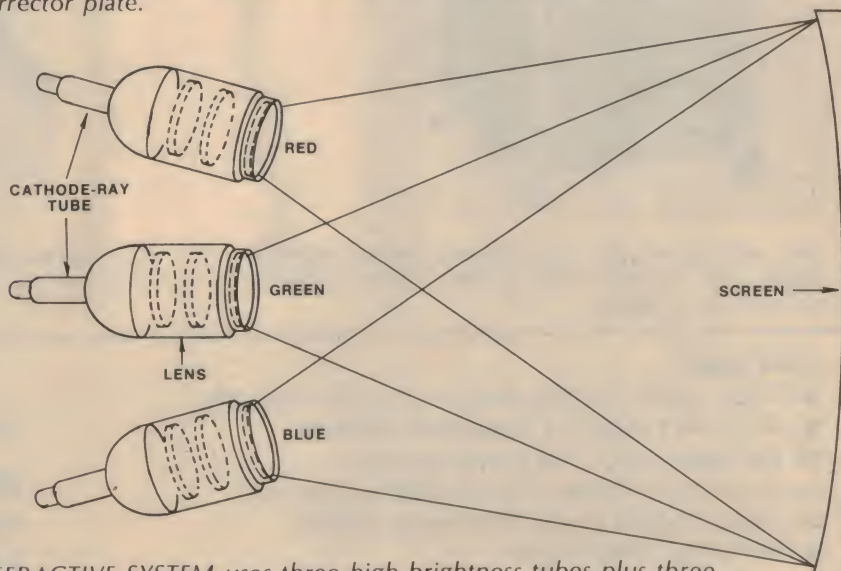SCHMIDT SYSTEM uses an electron beam to form an image in each tube, and telescope optics to project enlarged colour pictures onto the screen. New, simple construction developed by Henry Kloss cuts costs and reduces parts to a minimum: neck with integral mirror, barrel, faceplate with phosphor target, and corrector plate.




REFRACTIVE SYSTEM uses three high brightness tubes plus three fast lenses to project red, blue and green images. The images combine on the screen to form the colour picture.

A NEW DIMENSION IN TELEVISION VIEWING GRUNDIG CINEMA 9000

**BIG
COLOUR
SCREEN
152cm**



THE RECEIVER

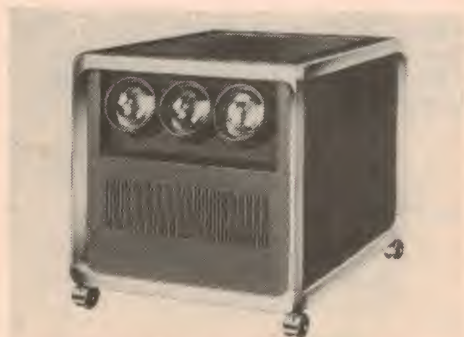

THE RECEIVER OF THE CINEMA 9000 SYSTEM WITH ITS THREE PROJECTION LENSES SEEN FROM THE SCREEN.

THE REMOTE CONTROL



THE INFRA-RED REMOTE CONTROL TELE-PILOT 310 FOR 30 PROGRAMMES.

FEATURES:

- 152cm TOP CLASS LARGE COLOUR PICTURE
- HIGH REFLECTION CONCAVE SCREEN
- OPTIMAL WIDE VIEWING RANGE
- TELE-PILOT INFRA-RED REMOTE CONTROL
- TELE-PILOT 310 PROGRAMME TUNER
- STATION COMPUTER
- HI-FI AMPLIFIER

Distributed By:

BREWO ELECTRONICS


104 BATHURST STREET,
SYDNEY 2000 TEL: 233 3266
61 2867

Kloss. The principle is simple. Put a lens in front of any light source and you project a picture. Many of the projection-TV sets on the market now — the one-eyed monsters — use a lens and a regular TV set to project a bright enough image to see in a darkened room.

Can that simple system be improved? Henry Kloss began to wonder about that in the mid-1970s, after the Advent Schmidt-optics system was on the market. "Electrohome in Canada had some higher quality circuitry than other places and was interested in projection TV," he recalls. "Roger Howe at US Precision Lens was willing to try to make faster, cheaper lenses. There is an oversupply of tube-making equipment. These elements began to come together in my mind."


Kloss decided to make a system using three regular monochromatic tubes — one blue, one green, and one red — then combine them optically to make the full-colour image. With three tubes each giving off light, the total light output could be high. If a fast lens (one that transmits a lot of light) could be found, that would make it brighter still. So Kloss asked Clinton Electronics Co to develop a brighter, more accurate version of its monochromatic tube; Electrohome to work on circuitry; and Roger Howe to build a fast lens.

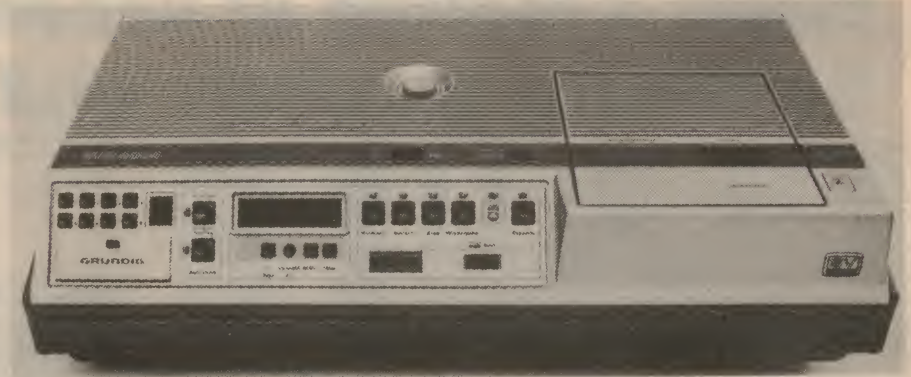The lens US Precision developed was an f/1.4, injection-moulded of acrylic. Kloss used it to make the Advent 750, which has since been repackaged to become the 760. It was a successful product, and the first three-tube refractive home set on the market. Although



ABOVE: Grundig SVR 4004 video cassette recorder — an optional extra with Grundig's "Cinema 9000" giant-screen projection TV system. It can be remotely controlled.

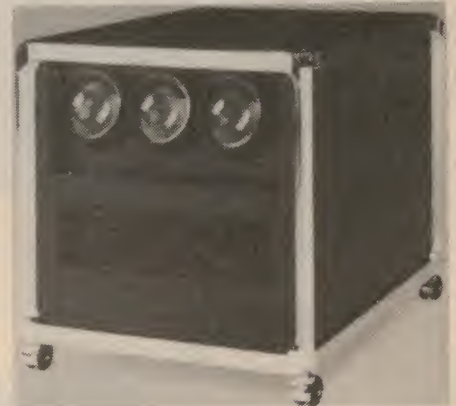RIGHT: the receiver of Grundig's Cinema 9000 system. It uses three in-line projection tubes: one red, one green, and one blue.




not quite as bright as the Schmidt optics set, it was still bright enough for comfortable viewing.

The technical trick that made this possible was the development by US Precision of a way to make large, thick plastic aspheric lenses with optically acceptable surfaces.

This development not only made lenses cheaper, but it had an additional advantage. It freed lens designers from the constraint of having to use lenses with spherical surfaces, as they must do

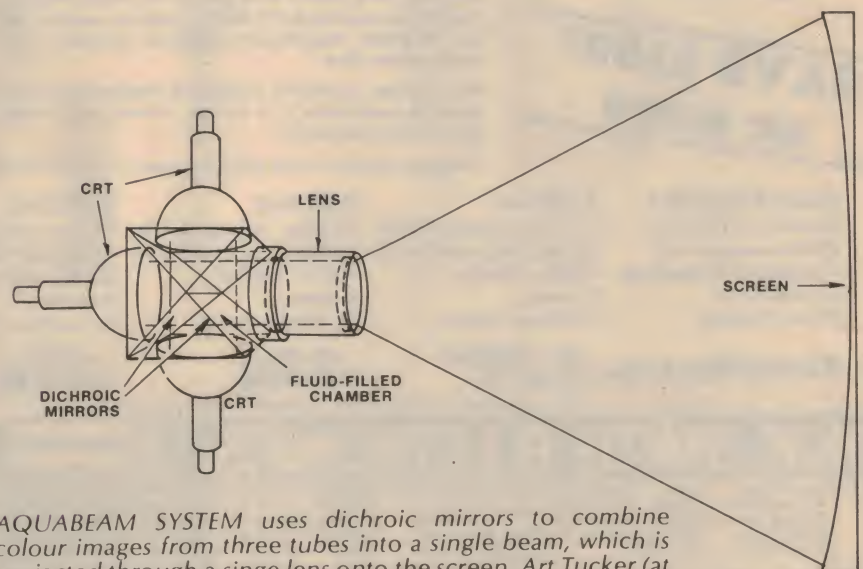with glass. By calling for aspheric lenses with complex shapes, designers could make extremely fast, simple lenses with fewer elements. And since the US Precision process is so much simpler than grinding glass lenses, the lenses could be far cheaper than those made of glass by the traditional method. Once US Precision had made the f/1.4 lens for Kloss, the company decided to



AQUABEAM SYSTEM uses dichroic mirrors to combine colour images from three tubes into a single beam, which is projected through a single lens onto the screen. Art Tucker (at left) is shown holding the housing for the 3-tube assembly.

The rewards for 2 hours of your time: a feeling of accomplishment, beautiful speakers and YOU SAVE



Photograph shows speakers without front grilles.

By assembling these speakers yourself you'll own far better speakers than you could have otherwise afforded (you save high labour costs) and you end up with a superb system that will delight you and your family.

Each of the three Playmaster speaker kits were acoustically designed by Neville Williams (MIREE), Editor-in-chief of Electronics Australia magazine. They are precision manufactured by Dick Smith so that everything just about 'falls into place'. The four side panels are pre-joined to the vinyl cladding - they simply wrap around the front baffle board. Even if you've never built anything before, you can make a pair of these magnificent speakers in about 2 hours construction time.

The 6 page, profusely illustrated instruction brochure explains everything in a simple, step-by-step manner. Even a child can do it!

*Based on the price of the 300mm system in ready built form.

Playmaster

**SAVE \$100*
or more**

Specifications

Speaker Enclosure: 200mm
Dimensions in cm: 53.5(h)x32(w)x22.6(d)
Frequency Response: 45Hz - 20kHz
Impedance: 8 ohms
Power Rating: 40 watts music

250mm
53 litre, infinite baffle
62(h)x39.3(w)x29.3(d)
35Hz - 20kHz
8 ohms
60 watts music

300mm
75 litre, infinite baffle
71.7(h)x47.5(w)x29.3(d)
28Hz - 20kHz
8 ohms
80 watts music

Total System \$149⁵⁰

\$224

\$284

Sent anywhere in Australia for only \$6.00 per pair freight.

DICK SMITH ELECTRONICS

NSW 125 York Street,
147 Hume Highway,
162 Pacific Highway,
30 Grosvenor Street,
283 Keira Street.

SYDNEY Phone 290 3377
CHULLORA Phone 642 8822
GORE HILL Phone 439 5311
PARRAMATTA Phone 883 1133
WOLLONGONG

ACT 96-98 Gladstone Street,
VIC 389 Lansdale Street,
858 Bridge Road,
QLD 188 Logan Road,
SA 203 Wright Street,
WA 414 William Street.


FYSHWICK Phone 80 4844
MELBOURNE Phone 87 8834
RICHMOND Phone 428 1814
BURANDA Phone 381 8233
ADELAIDE Phone 212 1882
PERTH Phone 328 8944

bankcard
welcome here

SHOPS OPEN 9AM to 5.30PM
(Saturday 9am till 12 noon)
BRISBANE Half hour earlier
ANY TERMS OFFERED ARE TO
APPROVED APPLICANTS ONLY
RE-SELLERS OF DICK SMITH
PRODUCTS IN MOST AREAS OF AUSTRALIA



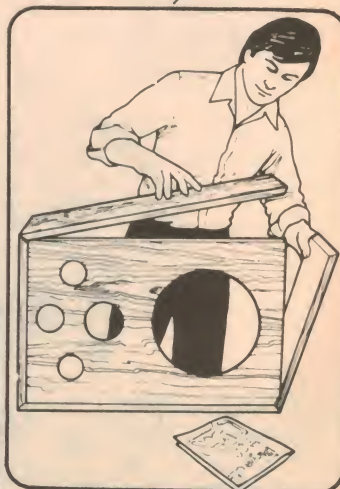EXCEPT WHERE NOTED, ALL ITEMS SHOWN IN STOCK AT PRICES GIVEN AT TIME OF GOING TO PRESS
MAIL ORDER CENTRE: PO Box 747, CROWS NEST NSW 2065 Ph 439 5311 PACK & POST EXTRA



TERMS are available to approved personal shoppers from a low 10% deposit and low monthly repayments.

DSE586

Large-screen projection TV from Grundig



ABOVE: "Tele-Pilot" 310 infra-red remote control — supplied as standard.



THE GRUNDIG CINEMA 9000 is a two-piece unit consisting of a separate screen and a receiver with a high-brightness, in-line, 3-tube optics system. It is supplied complete with a multi-channel infra-red remote control unit.

An impressive feature of the remote

control unit is the in-built digital clock which allows the unit to act as a time-switch. It will also automatically switch the TV to stand-by mode after about 35 minutes if no remote control commands are issued.

The mobile receiver is fixed to the

floor about 2m from the screen which is normally wall mounted. Screen size is 125 x 96cm (or 152cm diagonal) — about eight times larger than the picture area of a 48cm TV.

Further details from Brewo Electronics, 104 Bathurst St, Sydney

see if it could push the technology still further. So it developed an f/1.0 lens, which has twice the light output.

Suddenly new possibilities loomed. A refractive set could be made with the new lens that could be twice as bright as before. "So now it's a real horse race between our technology and the Schmidt technology," says Howe.

The lenses sharply reduce the cost of projection television. Much slower glass lenses, such as are now used in the Japanese sets, cost as much as \$200 each in quantity. But Howe says that any manufacturer who buys his new f/1.0 lenses at the rate of a thousand a month (a small number for a mass-market product) can get them for \$155 for a set of three — enough to make a television set.

Howe led me into a viewing room with a projection set using the new f/1.0 lens. It produced a beautiful, bright, sharp, clear picture in a well-lit room.

Howe's lenses could be an important factor in projection TV. They're now available off-the-shelf. So are superbright monochromatic tubes from Clinton and other manufacturers. TV electronics can be bought as a package. So anyone who wants to can now put together an ultra-bright, relatively low-cost television set by simply buying all of the parts and putting them into a case.

The Aquabeam system

Back in the early days of projection television, many of the sets seen in US theatres, hospitals, military installations, and other commercial and industrial applications were built by an electro-optical expert named Art Tucker. Although Tucker had built many Schmidt-type systems (including a \$28,500 system that produced a 12-metre picture for use in theatres in the late 1950s), he was concerned with several problems inherent in the design. For one thing, a Schmidt system must be engineered for a fixed picture size and a fixed projector-to-screen distance. And getting the three beams from the three colour tubes to converge is complicated.

Tucker had also built and sold several thousand refractive optics systems using glass lenses back in the '60s. They cost \$6800 and were sold mostly to schools. But he decided a couple of years ago that this was not the ideal approach either and that a new kind of system was needed.

So he set about to try to develop a system that would combine the three beams of light before the lens, so they could be projected as a single beam through a single tube. This would allow a single system to produce an image of any size. Just move it toward or away from the screen, focus like a slide projector, and the image size changes. But

to work properly, a lens must be close to the face of the cathode-ray tube whose picture it is projecting. "So how do I get the tubes to think they're close to the lens and still stuff the mirrors in between?" asked Tucker.

He did it in an ingenious way. Tucker made a plastic box with windows on all four sides (see diagram). Inside, he mounted two dichroic mirrors. A dichroic mirror reflects light of one colour or wavelength, while passing most of the light of different wavelengths. When the mirrors were arranged properly, the result was a head that combined the images from the three tubes into a single beam, which could be projected by a single lens.

But there was still one problem. When a light beam goes from glass to air or vice versa, it is bent sharply by a phenomenon known as refraction. Since various images were travelling through varying numbers of glass-air surfaces, refraction seriously distorted some of the images.

So Tucker devised another solution. He filled the box with a liquid with very special properties. It has precisely the same refractive index as the glass used on the face plates, for the internal mirrors, and at the exit pupil. Thus the glass effectively disappeared, there was no refraction of light internally, and refractive distortion was eliminated.

Tucker has just set up his new company, The Big Picture, Inc, in Titusville, Florida. When I was there, he was setting up production facilities: heavy injection-moulding equipment for the optical elements and housing of the projection head, electronics assembly areas, and so on. Initial plans call for him to manufacture 2000 sets that will sell for about \$5000 and be placed in institutional settings — bars, hospitals, auditoriums.

Tucker figures that once he gets that many out in the field, he'll get enough practical experience to impress major TV manufacturers who might want to license his equipment. Ultimately, he hopes to manufacture only the projection head, selling it to the big home-TV makers for inclusion in their sets.

His units are impressive. He showed me sets that produce pictures considerably brighter than those from either the Kloss Schmidt system or the Howe refractive system. The liquid refractive agent directly in contact with the tube face helps keep the phosphor cool, so higher driving power can be used, which produces a brighter picture.

Home sets

What will it take to make a successful home set? The makers disagree — and each outlines a set of desirable qualities clustered around his individual approach. Kloss thinks the two-piece set with projector in the middle of the room and screen on the wall, much like the various Advent models he designed, will be most desirable. Many thousands of that kind have been sold.

Tucker thinks it has to be a one-piece unit. "It can't stick out from the wall more than 28 inches," he says. "Preferably, it should disappear when you're not looking at it. It can't have exposed wires running to it (that eliminates a projector in the middle of the room). It's got to look presentable as furniture. And you've got to be able to get it upstairs and through doors."

Howe has an ideal product in mind, too. "It should be comparatively unobtrusive, should be in one piece, and should sell for under \$2000." While there is a difference of opinion as to whether a one-piece or two-piece system is most desirable, this does not necessarily make one approach more likely to succeed than another. Any of the three systems can be built into either type of unit.

How about brightness?

All three claim they have enough, and after seeing them, I agree. Says Kloss, "We've got enough brightness now, and don't have to talk in terms of



"CinemaVision" TC-6200A from National features one-piece construction, a 153cm (diagonal) screen, and a high-brightness 3-tube Schmidt optics system. A 26 function remote control unit allows the user to turn the set on or off, select up to 16 pre-set channels, and vary brightness and volume. Other features include provision to play either PAL or NTSC video tapes via a VTR, an aluminised screen surface, and an automatic station search facility. Further details from National Panasonic Australia Pty Ltd, 61 Anzac Pde, Kensington, NSW 2033.

foot-lamberts any more. We can be like the Rolls Royce salesman, who, when asked about horsepower, replied, 'It's adequate, Madam'."

Then why is Tucker trying to get more light — perhaps several times as much as the other two? At light levels now used, high-gain screens are also used to make the picture brighter. But the higher the gain, the narrower the viewing angle. Tucker wants to have so much brightness that he can trade some of it off for other desirable characteristics.

What size should a projection set be? Kloss thinks a 1.8-metre picture is desirable. Tucker says his projector will give you whatever size you want — an important point in favour of his set.


Howe says 1.3 metres is ideal, but points out that with the three-tube refractive system the picture can be made any size. (Changing size can't be done by the customer; a set will come adjusted and converged for the size screen with which it is sold. But the factory can use the same package to make sets with any size screen).

What does the future hold? It seems likely that the new systems will launch a new era for large-screen projection TV, both at work and at home!

Copyright 1979 Time Mirror Magazines, Inc, New York. Reprinted from "Popular Science" by arrangement.

LEADER TEST INSTRUMENTS

LBO 508A OSCILLOSCOPE

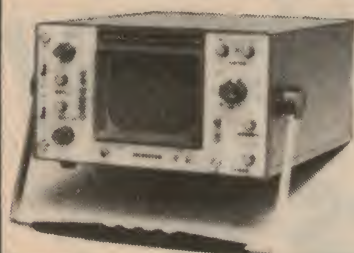

Bandwidth DC-20 MHz.
Sensitivity 10mV/cm.
130mm highly C.R.T.

\$899

LDM 170 DISTORTION METER



20Hz-20kHz 0.3% F.S.
Measures distortion,
signal-to-noise ratio,
signal levels.

\$490

LAC 895 ANTENNA TUNER



Built-in SWR and in-line
Watt meter. 5 bands
from 3.5 to 28 MHz.
500W pep transmitter
input.

\$182

LBO 510A OSCILLOSCOPE



20 mV/4MHz.
FET'S input

BUDGET PRICED
\$399


LSG 16 RF SIGNAL GENERATOR



100KHz-100MHz
Solidstate RF signal
generator. Suited for
aligning the IF circuits
in AM, FM and TV sets.

\$119


LAG 26 AF SIGNAL GENERATOR

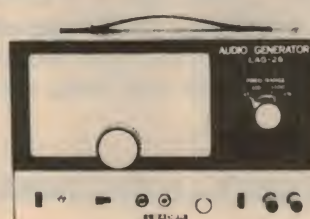

20Hz-200kHz
Stable generator for all
types of audio circuit.

\$166


LFM 39A WOW AND FLUTTER METER

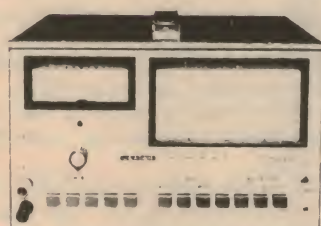

For accurate and easy
determination of the
wow and flutter charac-
teristics of tape
recorders to JIS, CCIR
and DIN standards.

\$699

LMV 181A AC MILLIVOLT METER

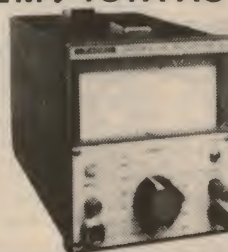

AC Voltages from
100uV up to 300V. 5Hz-
1MHz.

\$189

Distributed by VICOM

VICOM

SOUTH AUSTRALIA
Electronic Components and
Equipment
110 Tynte Street,
North Adelaide
(08) 267 2246

International Communication
System
Dale Street,
Port Adelaide.

NEW SOUTH WALES
Radio Despatch Service
869 George Street,
Sydney.
(02) 211 0816

Custom Communications
Shop 11,
Parramatta Arcade,
Church St.
Parramatta. Ph. 635 6399

Elektron 2000
44 Brown Road,
Broadmeadow
NEWCASTLE, 2292
(049) 69 1222

QUEENSLAND
Delsound
1 Wickham Terrace,
Brisbane, Queensland
(07) 229 6155

Fred Hoe & Sons
246 Evans St.
Salisbury North,
(07) 277 4311

CW Electronics
Cnr Marshall Rd and
Chamberlain St,
Tarragidindi
(07) 48 6601

**WESTERN
AUSTRALIA**
Atkins Carlyle
1-9 Milligan Street
Perth
(09) 321 0101

VICTORIA
Radio Parts Group
Spencer Street,
West Melbourne and
Dandenong Road,
Malvern
329 7888

VICOM International
Pty. Limited.
68 Eastern Rd,
South Melbourne
Ph. 699 6700



Current — which way does it flow?

From the Museum of New York, this Currier and Ives print depicts the 1752 experiment by Benjamin Franklin which established a relationship between lighting and static electricity — altogether a rather hazardous experiment.

Which way does electric current flow in a circuit? From positive to negative, as originally proposed by Benjamin Franklin, or in the reverse direction, as maintained by many adherents of electronics? This somewhat historical survey may help you to get the matter in perspective.

by **NEVILLE WILLIAMS**

Electrical phenomena have been observed and documented over hundreds — even thousands — of years, although not understood at the time. The ancient Greeks, for example, were aware of static electricity, as manifest by the way in which a piece of vigorously rubbed amber would attract particles of dust and lint. In fact, the Greek word "elektron", meaning amber, is the root of our modern term "electronics".

Again, the Romans were aware of the peculiar behaviour of "loadstone", or magnetite, an oxide of iron which provided the key to the early mariner's compass. Even in those far off days, Roman writers were unsure whether their word for the effect had been derived from the island of "Magnesia", the source of the loadstone or "Magnus", the shepherd who allegedly discovered its strange properties. Sufficient to say that, between them, the words provided the root for our modern term "Magnetism".

Much later, from about the 18th century onward, European researchers began to study electrostatic and magnetic effects more deliberately and the conviction grew that there was a link, as yet unresolved, between the

two. In 1752, Benjamin Franklin extended the speculation by demonstrating a further link between static electricity and atmospheric lighting — an experiment that, in retrospect, has been classified as one of the most foolhardy of all time!

Indeed, Franklin postulated that electricity was some kind of intangible fluid. When an object had more than its share of this fluid, it would attract (or electricity would flow into) another body which had less than its share. He also suggested that a body with surplus fluid should be regarded as being electrically positive, and bodies with less than normal fluid as being electrically negative.

A concentration of the "fluid" was seen as "static" electricity. Electrical fluid in motion came to be known as "current" electricity and, in line with Franklin's proposition, current was deemed to flow from positive to negative.

At that point in time, there was no special reason to adopt a contrary view and it was accepted as fact.

So the convention was established.

In subsequent years, Luigi Galvani (1780) and Alessandro Volta (1800) con-

tributed to research which produced the first electrical cells (or "batteries" of cells). In due course, one connection was identified as the source of electrical "fluid" and variously branded "anode", "positive", "plus" or "+". The other connection was called "cathode", "negative", "minus" or "-".

Thus equipped, Hans Christian Oersted began a long series of experiments in 1807, which established a firm relationship between electrical current flow and magnetism:


When current from a battery flowed through a wire (from anode or positive to cathode or negative, of course) it produced a magnetic field around the wire. This could be sensed by a compass and shown to have a north and south polarity comparable with that of the Earth.

Thus, in the early part of the last century, the conventions had become firmly established and interlocked.

In successive decades, many famous physicists and engineers expanded the basic concepts and developed practical equipment, ultimately giving birth to a fledgling electrical industry, with batteries, generators, motors, lighting systems, communications systems and so on.

Associated with it was a growing mountain of textbooks, literature and academia — all conforming to the original assumptions about voltage polarity and the direction of current flow and magnetic flux. These relationships were epitomised in Fleming's classic right-hand and left-hand rules, which have graced electrical textbooks for more years than most can remember.

LOW COST PORTABLE OSCILLOSCOPES THAT DON'T COMPROMISE ON PERFORMANCE!

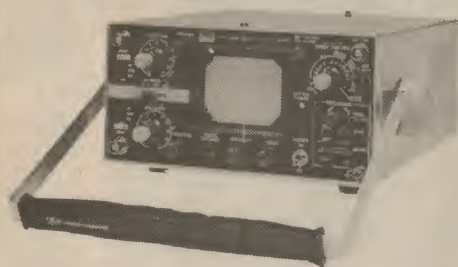

TTM303
15MHz
Battery Operated

TTM303

The TTM Dual Trace Portable Scope Model 303 offers a high sensitivity of 5mV/DIV with DC to 15MHz bandwidth. The 3-inch CRT with 1.5kV regulated accelerating voltage gives a clear bright display.

This Portable Scope operates from standard line voltage (90 to 260V) or from the internal rechargeable Ni-Cad battery, that provides 2 hrs operation before recharging is required. It also operates from any external DC voltages of 11 to 30V, e.g. car batteries, standard 'C' size cells, etc.

SPECIFICATIONS:

SENSITIVITY:- 5mV to 10V/DIV 1-2-5 step with fine control. BANDWIDTH:- DC: DC to 15MHz (-3dB). RISE TIME:- 24nS. OPERATING MODES:- CH-A, CH-B and Dual Trace TIME BASE:- 1µsec to 500 mS/DIV with fine control. EXPANSION:- x5 at all ranges X-Y OPERATION:- X-Y mode is selected by SWEEP TIME/DIV switch. CH-A: Y axis, CH-B: X axis. POWER REQUIREMENTS:- AC: 115/240V DC: 11-30V, 7.2VA. Battery: Ni-Cad Battery (up to 2 hour operation). SIZE: 113 (H) x 223 (W) x 298 (D) mm approx. WEIGHT:- 4.5kgs.



BS310
2mV Sensitivity
Add/Subtract Feature

APPLICATION BS310S

The dual trace Model BS-310 employs a high brightness 95mm CRT and offers a high sensitivity of 2mV/DIV from DC to 15MHz.

The ADD/SUB feature makes this model ideal for measurement and maintenance of computers and peripherals. This scope is recommended for FLOATING Measurements and FREQUENCY/PHASE Measurement (X-Y mode). Rechargeable battery operation makes it ideal for repairing TVs and other consumer and industrial equipment.

SPECIFICATIONS:

SENSITIVITY:- 2mV to 10V/DIV on 12 ranges in 1-2-5 step with fine control. BANDWIDTH:- DC: DC to 15MHz (-3dB). RISE TIME:- 24nS. OPERATING MODES:- CH-A, CH-B, DUAL, ADD and CHOP. TIME BASE:- 0.5µsec to 0.5sec/DIV in 19 ranges and X-Y in 1-2-5 step with fine control. MAGNIFIER:- x5 at all ranges. X-Y OPERATION:- X-Y mode is selected by SWEEP TIME/DIV switch CH-A: Y axis, CH-B: X axis. POWER REQUIREMENTS:- AC: 115/240V DC: 11-30V, 7.2VA. Battery: Ni-Cad Battery (up to 2 hour operation). SIZE:- 113 (H) x 223 (W) x 298 (D)mm. WEIGHT:- 4.5kgs (5.5kgs including battery).

**Now with 95mm
rectangular
tube**



BS610
140mm
No Parallax Display

APPLICATION BS610

The BS-610 employs a high brightness 140mm Rectangular CRT with internal graticule assuring easy and accurate observation of waveforms without any parallax.

External DC-Powered operation expands the versatility of this oscilloscope to FLOATING Measurements as well as field operation.

Other features including TV SYNC and HF REJ. make this scope ideal for research and development, production lines or in-the-field service applications from computers to electrical appliances.

SPECIFICATIONS:

SENSITIVITY:- 5mV to 10V/DIV on 11 ranges in 1-2-5 step with fine control. BANDWIDTH:- DC: DC to 15MHz (-3dB). RISE TIME:- 24nS. OPERATING MODES:- CH-A CH-B DUAL, ADD and CHOP. TIME BASE:- 0.5µsec to 0.5sec/DIV in 19 ranges and X-Y in 1-2-5 step with fine control. MAGNIFIER:- x5 at all ranges. X-Y OPERATION:- X-Y mode is selected by SWEEP TIME/DIV switch. CH-A: Y axis, CH-B: X axis. POWER REQUIREMENTS:- AC: 115/240V DC: 11-30V, 7.2VA. SIZE:- 145 (H) x 280 (W) x 369 (D)mm. WEIGHT:- 6.7kgs.

We STOCK PROBES and ACCESSORIES to suit most makes of oscilloscopes to 150MHz. Contact us for competitive prices.

Available from selected stockists or from:-

P.O. Box 30, Concord, NSW. 2137
13-15 McDonald St., Mortlake, NSW. 2137
Phone: (02) 736-2888, Telex: 25887

P.O. Box 107, Mt. Waverley, Vic. 3149
21-23 Anthony Drive, Mt. Waverley, Vic. 3149
Phone: (03) 233-4044, Telex: 36206

Adelaide: 51 3521, Brisbane: 229 3161, Perth: 398 3362

ELMEASCO
Instruments Pty. Ltd.



NEW!

WHY CUT?
WHY STRIP?
WHY SLIT?

WHY NOT...

JUST WRAP™

Available from

NSW

Radio Despatch, 211 0191
David Reid Electronics, 29 6601
Electronics Distributors, 636 6052
Martin De Launay, 29 5834
Dwell Pty Ltd, 487 3111

VIC

Ellistronics, 602 3282
Arlin Instruments, 569 6984
Stewart Electronics, 277 0622

SA

Protronics 212 3111

WA

Reserve Electronics, 275 2377

QLD

Wilber Sales, 319 5136

- AWG 30 Wire
- .025" Square Posts
- Daisy Chain or Point To Point
- No Stripping or Slitting Required
- ...JUST WRAP™...
- Built In Cut Off
- Easy Loading of Wire
- Available Wire Colors:
Blue, White, Red & Yellow



U.S.A.
FOREIGN
PATENTS
PENDING



DIP/IC INSERTION TOOL WITH PIN STRAIGHTENER



STRAIGHTEN PINS RELEASE PICK-UP INSERT

14-16 Pin Dip IC Inserter INS-1416



ROLLS OF WIRE

Wire for wire-wrapping AWG-30 (0.25mm) KYNAR® wire, 50 ft. roll, silver plated, solid conductor, easy stripping.


30 AWG Blue Wire, 50ft. Roll	R 30B-0050
30 AWG Yellow Wire, 50ft. Roll	R 30Y-0050
30 AWG White Wire, 50ft. Roll	R 30W-0050
30 AWG Red Wire, 50ft. Roll	R 30R-0050



WIRE DISPENSER

- With 50 ft. roll of AWG 30 KYNAR® wire-wrapping wire.
- Cuts the wire to length.
- Strips 1" of insulation.
- Refillable (For refills, see above)

Blue Wire	WD-30-B
Yellow Wire	WD-30-Y
White Wire	WD-30-W
Red Wire	WD-30-R

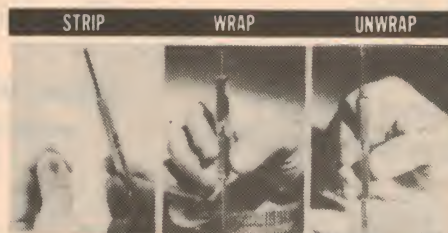

HOBBY WRAP
TOOL



Wire-wrapping, stripping, unwrapping tool for AWG 30 on .025 (0.63mm) Square Post.

Regular Wrap	WSU-30
Modified Wrap	WSU-30M

NEW

HOBBY WRAP
Model BW-630



Battery
wire
wrapping
tool
COMPLETE
WITH BIT
AND SLEEVE

WIRE-WRAPPING TOOL


For .025" (0.63mm) sq. post "MODIFIED" wrap, positive indexing, anti-overwrapping device.

For AWG 30	BW-630
For AWG 26-28	BW-2628

Bit for AWG 30	BT-30
Bit for AWG 26-28	BT-2628

*USE "C" SIZE NI-CAD BATTERIES
(NOT INCLUDED)

DIP/IC EXTRACTOR TOOL

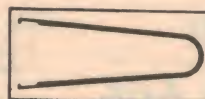

The EX-1 Extractor is ideally suited for hobbyist or lab engineer. Featuring one piece spring steel construction. It will extract all LSI, MSI and SSI devices of from 8 to 24 pins.

Extractor Tool	EX-1
----------------	------

AMPEC ENGINEERING CO PTY LTD

1 Wellington Street, Rozelle 2039

PO Box 132, Rozelle 2039. Phone (02) 818 1166

But, around the turn of the century, Franklin's long-standing electric "fluid" concept began to be questioned by Rutherford, Bohr, Thompson and others, who put forward the then quite revolutionary electron theory. It had enormous implications.

They maintained that atoms were not, after all, the basic building blocks of matter. That atoms, in turn, were made up of still smaller particles (the real building blocks) notably "protons" with a positive electrical charge and "electrons" with an equivalent negative charge.

Each atom was like a miniature solar system with a nucleus of positively charged protons and (usually) an equal number of electrons spinning around it in specific orbits. The number and arrangement of protons and electrons determined the nature of the atom.

In certain substances, electrons in the outermost orbit could migrate from atom to atom. If, for any reason, there was an overall surplus of electrons in a particular area, it was equivalent to a negative electrostatic charge; a deficit of electrons was equivalent to a positive electrostatic charge. A discernable migration of electrons from one region to another was an electric current.

As a logical extension of this, a cell (or battery) could be regarded as a device in which internal galvanic (electro-chemical) action produced a surplus of electrons at one pole (negative) and a lack of such electrons at the other (positive) pole. In a rotary generator, a similar result was produced by magnetic effects. Similarly for an electrostatic generator or any other source of electrical energy.

The current which flowed when the two poles were bridged by an external wire was not some intangible "fluid", but simply a migration of free electrons through the wire.

NEGATIVE TO POSITIVE!

More to the point, this movement was from negative to positive!

The electron theory was not well received at first, partly because it challenged existing physical, chemical and electrical concepts, and partly because it appeared to contradict the "sacred" laws about polarity, current flow and magnetic flux. Indeed, it remained a "theory" for many years, until progressive developments rendered the traditional view untenable.

What gave particular point to the argument was the development of the thermionic valve, better known to the Americans as a vacuum tube or radio tube. As it happened, the operation of this vital new device was relatively easy to depict and comprehend and, of course, it depended on electrons migrating from atom to atom and even across free space.

In a thermionic diode valve, electrons emitted by a heated filament (or cathode) were attracted to an adjacent

THE TEACHERS' DILEMMA ...

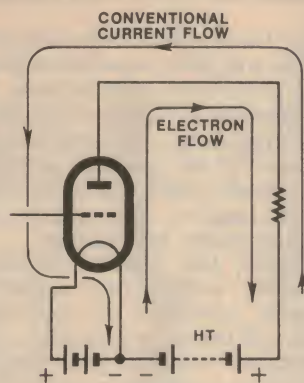


FIG. 1

In a simple triode valve circuit, electrons flow from the negative side of the (HT) high tension supply to the filament or cathode, across the evacuated space to the valve anode, then through the external anode circuit to HT+. This conflicts with the conventional current flow concept from plus to minus.

plate (or anode) within the evacuated glass envelope, whenever the plate was at a positive potential with respect to filament. On this property depended a diode's ability to function as a rectifier or detector.

In a triode valve, electrons were emitted from filament to plate in the same manner, except that the electron stream was subject to further control by an additional electrode (a "grid") mounted between the filament and plate. This made it possible for a triode to act as an amplifier or oscillator.

To understand the operation of wireless circuits using valves, it seemed quite natural to think in terms of electron flow: from the negative side of the supply to the valve filament (or

cathode), thence across to the valve plate (or anode), and on through components in the external circuit back to the positive side of the supply. (Fig. 1.)

In wireless magazines and textbooks, arrows were commonly drawn on circuit diagrams to emphasise this quite fundamental concept.

Over the following decades, as the science and application of wireless expanded (call it "radio" if you like), an inevitable confrontation developed.

The wireless/radio fraternity had no real option but to develop their understanding on the basis of electrons and electron flow. But, to them, electron flow was current flow; how could it be any other way? Indeed, such was the logic of their position that they were confident that, one day, electrical types would have to see it that way!

But, in this, they were disappointed. Possibly because they were less directly concerned with electron physics, the electrical fraternity chose to retain their long established conventions governing current flow and magnetic polarity. What's more, they have never budged from that position.

BASIC CONFLICT

In the centre of things, teachers and lecturers were commonly obliged to explain electron (therefore current) flow in one direction, despite the fact that other members of the staff were talking about current flow in the opposite direction!

Publications like our own were also caught in a bind, particularly as electrical and radio interests began to overlap onto the common ground which is now all part of "electronics". As surely as we gave expression to the electron/current concept, just as surely would readers challenge us with chapter and verse to "prove" that we had our ideas and arrows the wrong way round!


More or less of necessity, we adopted the following practices:

- The word current was used only in a generalised sense; eg, voltage and current.
- If the context required a reference to the direction of current flow, we added the word "conventional", thereby indicating that the statement was in accordance with the established electrical convention.
- In the context of radio (particularly valve) circuits, and where possible, we wrote in terms of electron flow.

This practice, also followed by many other electronics publications, minimised confusion and kept most people happy. Or, perhaps we should say: made them less miserable!

In general, we still follow the practice, but the emphasis has changed again since the advent of solid-state devices: diodes, transistors, integrated circuits, etc.

Unlike valves, their operation is not

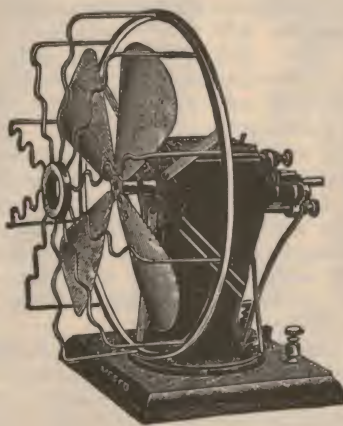

On sale around the turn of the century, this electric fan was a product of the "fledgling electrical industry". One thing it couldn't cool was the then current argument about the nature of electricity: was it a "fluid" flowing in the accepted direction or a massive migration of electrons moving the other way?

ROD IRVING ELECTRONICS

499 HIGH STREET,
NORTHCOTE 3070
MELBOURNE,
VICTORIA.

Ph. (03) 489 8131.

SUPER SPECIALS

COMPONENTS

2114's		\$6.25
2708		11.00
741's	10 up	2.50
555's	10 up	2.90
BD139's	10 up	4.50
BD140's	10 up	4.50
SC141D	10 up	1.10
SC151D	10 up	2.10
Red Leds	10 up	1.40
Red Leds	100 up	11.00
Yellow Leds	10 up	2.90
8 Pin I/C Skts	10 up	2.00
BC 547	10 up	1.00
BC 548		0.15 ea.
BC 549		0.19 ea.
MJ802		3.60 ea.
6800/50V Caps (Lug)		4.50 ea.
5600/40V Caps (PCB)		1.90 ea.
Pots Single Gang Carbon		
All Values Except 100 ohm		0.50 ea.
Quality Single Turn		
Cermet Pots Most Values		0.99 ea.
Quality 10 Turn Pots		
Most Values		7.50 ea.
Computer Cooling Fans		
4 68in Square		27.50 ea.

KITS & PRINTED BOARDS

(KITS OF PARTS INCLUDE QUALITY
FIBREGLASS BOARDS)

SERIES 4000 AMP	
Front Panel	7.99 ea.
ETI 470 60W	19.90 ea.
ETI 480 100W	19.75 ea.
ETI 480 50W	16.50 ea.
(BOTH INCLUDE HEAT SINK BRACKET)	
ETI 470PS	18.50 ea.
(INCLUDES RELAY NOT TRANSFORMER)	
Transformer to suit	22.90 ea.
ETI 471 Preamp	45.50 ea.
EA 79 SF9 Sound Trigger	15.00 ea.
All Parts and Board available for Dream Computer.	
ETI 574 PCB Disco Strobe	2.80 ea.
ETI 549A Metal Detector	2.75 ea.

We are also stockists of audio products, mics,
mixers, speakers (Phillips, Magnavox) Neutrik
Audio Connectors (Cannon Compatible)
Solder, Irons, Car Speakers, etc.
Phillips 12" 3 Way Speaker Kits
(AD12K12) \$295.00 pr.

HEAVIER ITEMS ADD ADDITIONAL POSTAGE.
EXTRA HEAVY ITEMS SENT COMET FREIGHT
ON. PRICES SUBJECT TO CHANGE WITHOUT
NOTICE. SEND 40c & S.A.E. FOR FREE
CATALOGUE.

MAIL ORDERS: PO BOX 135
NORTHCOTE, VIC 3070
MIN PACK & POST \$1.00

CURRENT — which way does it flow?

at all easy to visualise. Depending on the device and the circuit configuration, the potentials applied may be variously positive or negative. Conduction may involve the movement from atom to atom of electrons or so called "holes" or both. The latter move from positive to negative, in line with the traditional electrical convention.

Add further talk about "majority" and "minority" carriers and a variety of other terms invented by solid-state physicists, and the once simplistic argument becomes very confused indeed. So, while the concepts of electron flow and movement remain as valid as ever, the urge to make an issue out of them has greatly diminished.

It may even be said that, if the original positive-to-negative convention was a guess, the view of electronics adherents in the valve era was, itself, an over-simplification of the mechanism of conduction!

No less to the point, solid-state devices are represented, in many cases, by circuit symbols which perpetuate the concept of conventional current flow. Whether he likes it or not, the modern electronics devotee is stuck with them.

It seems almost certain that this came about because the very early rectifiers were allotted circuit symbols which involved an arrowhead for the anode pointing in the direction of (conventional) current flow to a line representing the cathode. For the sake of consistency, this symbol has been maintained for all rectifiers, right through to the modern (?) germanium and silicon diode.

When the transistor arrived, virtually a derivative of the diode, its symbol extended the diode convention. As a result, the emitter lead always points to the negative side of the supply. In an NPN type, the arrowhead points towards the collector, which is fed from the negative rail. In an NPN type, the arrow points the other way.

Faced with this situation, followers of electronics are tending not to argue but simply to adapt to the traditional convention. Where there is the likelihood of ambiguity, they can do as we have already suggested: refer to "conventional" current flow, or talk in terms of electron flow, or both.

It is possible to come up with similes which purport to bridge the remaining gap. Some time ago, for example, we used the example of a nearly-full row of seats in a theatre; by moving the patrons (electrons) in one direction, vacant seats (holes) could be concentrated at the opposite end. A Tandy publication invokes an alternative picture of a tube nearly filled with liquid; as the tube is tilted to and fro, the liquid (electrons) flow in one direction while bubbles (holes) move in the other.

Whether such mental pictures are necessary, or even helpful, at this stage seems debatable. Having come to appreciate the reasons for the apparent confusion, it is probably best to simply accept the situation and conform to it.

Which just about wraps it up, except for one point: why is the cathode of a semiconductor diode commonly thought of or marked as the "plus" end? Traditionally, and in just about every other device, the cathode is regarded as the negative electrode. Why the difference?

In fact, the diode is not an exception. In terms of conventional current flow, its conduction is also from anode to cathode. The markings on a diode follow from the fact that they are most commonly used in rectifier situations, with AC input and DC output.

Consider the basic circuit of Fig. 2, which could represent a diode functioning as either a rectifier in a mains power supply, or as a signal detector, (ie, a signal rectifier) in a radio receiver.

An alternating voltage is typically fed to the diode from a winding, which may be part of a mains transformer or a tuning coil. During the half-cycles when the upper end of the coil is positive, the diode conducts and feeds that positive potential to the filter capacitor and to the upper output terminal. On the reverse half-cycle, the diode does not conduct, since a negative voltage is being applied to the anode.

In short, only positive pulses are

THE DIODE PROBLEM



FIG. 2

In a diode, the anode is represented as an arrow pointing, in the direction of conventional current flow, to the cathode. The latter is sometimes marked "plus" because in a rectifier circuit, as shown, it is at the positive side of the DC output.

applied to the upper output terminal. The pulses are stored and smoothed by the filter capacitor.

Without trying to go any further, the point we want to make becomes apparent. In a rectifier situation, as in Fig. 2, the DC output is derived from the cathode end; hence the marking convention.



If the diode in Fig. 2 was simply reversed, the diode would conduct on the alternative half-cycle and the upper output terminal would become minus — derived from the anode!

sanwa

... the long term reliable multimeter.

N501 Multimeter The executive choice!

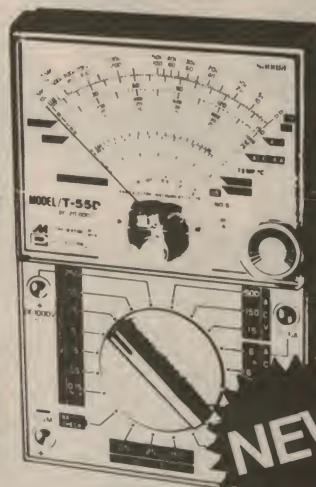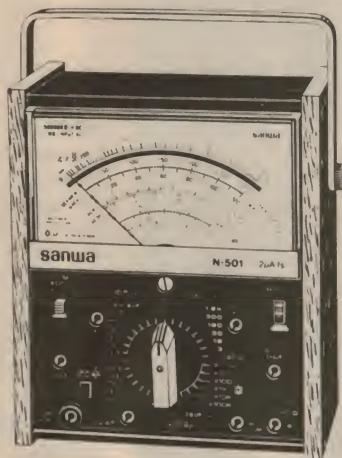- Measurements similar to a VTVM can be taken as the N501 has a constant $1M\Omega$ input impedance on the ACV ranges.
- Widespread coverage of the principal measurements is available as the N501 has AC + DC Volts to 1.2kV, AC and DC Amps to 12 Amps and 6 resistance ranges to 200 $M\Omega$ s.
- Attractive, 9mm thick walnut sideboards help protect the multimeter from accidental damage.



T-55 THD Multimeter (T-55D c/w optional temperature probe)

The latest lightweight
with heavyweight
features!

- Adds a temperature capability ($-50^{\circ}C$ to $200^{\circ}C$) to the newest thin-dimension multimeter. Lets you measure the temperature of industrial and commercial appliances or individual component heat.
- Offers a multi-role multimeter to cover normal requirements plus AC Amps, battery test, LED test and temperature selections.



U-60D UNIVERSAL MULTITESTER

- $44\mu A$ movement—quality performance, diode protected
- Stable ACV measurement—solid-state rectifier & enlarged frequency coverage.
- Linear scale characteristic—common scale reading for DCV and ACV
- Semiconductor test—simultaneous reading of load current & voltage with Ω
- Temperature measurement of $-30^{\circ}C$ to $+150^{\circ}C$ with extra probe



PDM500C INSULATION TESTER

- Easy push button operation.
 - Large easily read scale.
 - No wearing parts (transistorized for long trouble-free life).
 - One-man operation—no handle to crank.
- Specifications**
Rated Voltage 500V.
Resistance 100 Megohm.
Effective scale reading: 0.1–100–200 Megohm.
Continuity Scale: 0–100 ohms.
Including vinyl-leather case with lead pouch, shoulder strap and insulated test leads.



460-ED MULTITESTER THE BEST BUY IN MULTIMETERS

- 100,000 ohms per volt with $\pm 2\%$ accuracy for DC ranges with only 10 microamperes loss at full scale. H.F. current blocking when making DC measurements.
- $10\mu A$ movement— $100k\Omega/V$, varistor protected
 - Polarity reversal switch—negative measurements
 - Equalising transformer—common shunts & jacks for 1.2A & 12A DC/AC



BX-505 MULTITESTER

- Fast-response, $24\mu A$ movement—fuse & diode protected with high resolution factor ($0.4\mu A/\text{scale division}$)
 - Revised scale marking—intermediate readings readily determined
 - Polarity reversal switching—negative measurements
 - Series capacitor terminal (OUTPUT+)—AF output level check
- RANGES: AC & DCV to 1.2kV (30kVDC with optional probe). AC & DCA to 12 amps




WARBURTON FRANKI

• ADELAIDE 356-7333 • BRISBANE 52-7255 • HOBART 23-1841
• MELBOURNE 699-4999 • PERTH 277-7000 • SYDNEY 648-1711
• AUCKLAND N.Z. 77-0924 • WELLINGTON N.Z. 698-272

WF623/78

Home

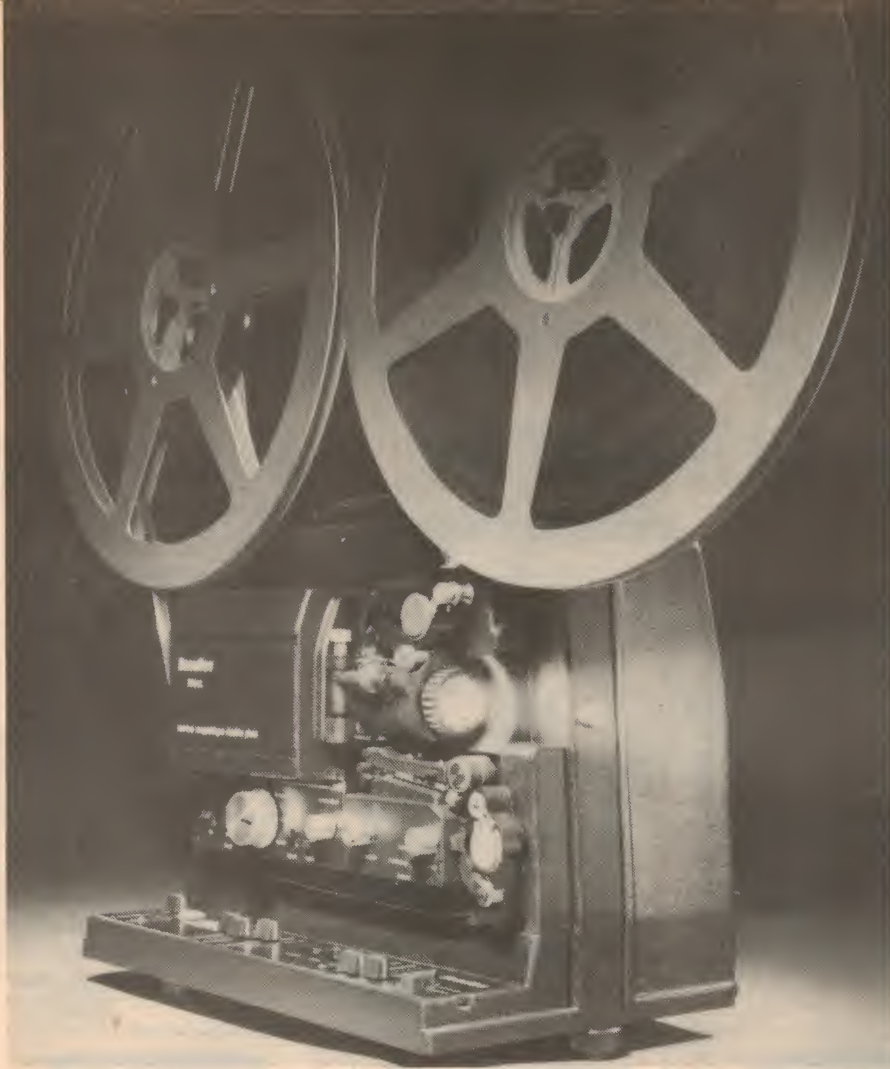

Here is the second part of our rundown on the latest developments in home movie equipment. Having looked last month at the new breed of cameras, we now turn to the features and facilities offered by the new projectors. To round off the subject we also look briefly at developments in animated viewers or "editors".

by JAMIESON ROWE

As you might imagine, while all of these developments have been taking place at the camera end of the home movie market, things haven't been exactly stagnant at the projector end. Perhaps the developments haven't been quite as dramatic, but the latest projectors do offer some interesting new feature and performance advantages.

Probably the most obvious improvement over earlier models is in terms of light output. The output of most of the current projectors is well up on earlier models, due partly to the use of wider-aperture projection lenses and partly to the use of higher-power projection lamps.

Just about every model on the market is fitted with a lens of aperture larger than $f/1.5$, for example. Some of the higher priced machines offer a lens of aperture $f/1.3$ or $f/1.2$, while the top-of-the-line models generally provide an even larger $t/1.1$. Most of these lenses are zoom lenses, with the focal

length variable over a ratio of from 2:1 to 2.5:1 to allow you to fill your screen with the picture over a range of projection distances.

When it comes to lamps, a majority of machines now use a 12 volt 100 watt quartz-halogen lamp which provides a light output considerably higher than the 8V/50W lamp fitted to earlier projectors. A few machines use a more powerful 15V/150W quartz-halogen lamp, giving even higher output, while those at the top of the market (like the Elmo GS-1200) use an even more powerful lamp rated at 24V/200W.


Virtually all of these lamps are fitted with an integral "dichroic" mirror. This is a mirror which fully reflects and concentrates the wanted visible light, but is transparent for infra-red and heat radiation. The idea is to give high light output, while at the same time reducing heating of both the lamp itself and the film.

Many of the projectors with quartz-halogen lamps are also fitted with

high/low switches, so that the lamp may be run from a slightly lower voltage when full light output is not required. This lets you extend the life of the lamp considerably — an important point because many of the Q-H lamps are quite expensive.

In addition to improved light output, many of the newer projectors also offer the ability to accept larger film spools. This lets you project longer without an interruption to change spools. Quite a number of the current models will accept 180m (600ft) spools, for example, in place of the 120m (400ft) or 60m (200ft) provided on most early machines. The 180m spool will let you project for up to 40 minutes at 18fps, or 30 minutes at 24fps.

A small number of projectors take

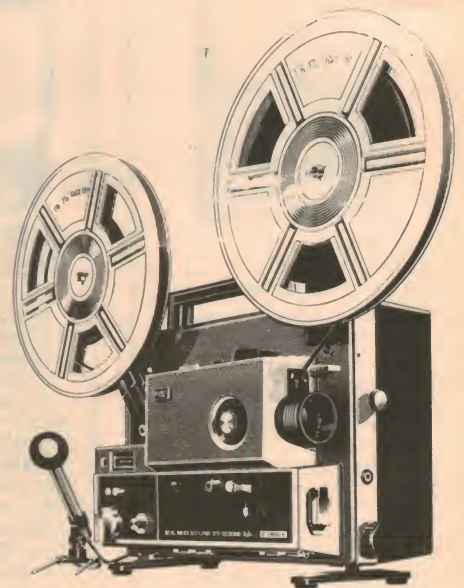

The Elmo ST-1200HD sound projector, which offers a 15V/150W lamp, two-track recording and replay, and 360 metre (1200ft) spool capacity.

TOP LEFT: The Beaulieu 708EL, known as the "Rolls Royce" of super-8mm projectors. Capable of superb results, it takes 720m spools.

Movies '79: the projectors

240m (800ft) spools, while an even smaller number will accept spools of 360m (1200ft) capacity: the Elmo GS-1200 and ST-1200HD, the Chinon SS-1200, and the Beaulieu 708EL. In fact the last of these goes one better again: it will take spools of no less than 720m (2400ft), which will run for no less than 2½ hours (160min) at 18fps, or two hours (120min) at 24fps!

In addition to conventional movie projectors designed to throw the picture up on a separate screen, a number of manufacturers are now making "integral screen" models. These look rather like a small table-model TV receiver, and are designed to project the picture onto the inbuilt screen from the rear. The idea is to reduce the "hassle" of showing your movies — you

don't have to set up a screen and fully darken the room.

Both sound and silent models are made in the integral-screen format, and they have gained some popularity. However they have not really reduced the market for conventional projectors, probably because part of the appeal of home movies for many people is the ability to produce large, impressive pictures.

Actually many of the integral-screen models can also be used to project onto a separate screen, by opening a small flap.

When it comes to sound projectors in particular, probably one of the most obvious features offered by the latest machines is increased flexibility. Many of them are capable of all sorts of fancy


things, with the idea of making it easier to assemble satisfying sound tracks.

Quite a few machines now allow you to record on or play back from either the main magnetic stripe track on the film, or the narrower "balance" track — which was originally intended purely to make striped film lie squarely in the picture gate of cameras and projectors. In most cases you can record on one track while playing back from the other, so you can make transfers back and forth.

This is a considerable help in assembling a sound track, as you don't have to risk the track you have already put together when you add in the next part.

A few projectors extend the two-track idea to provide a full stereo sound

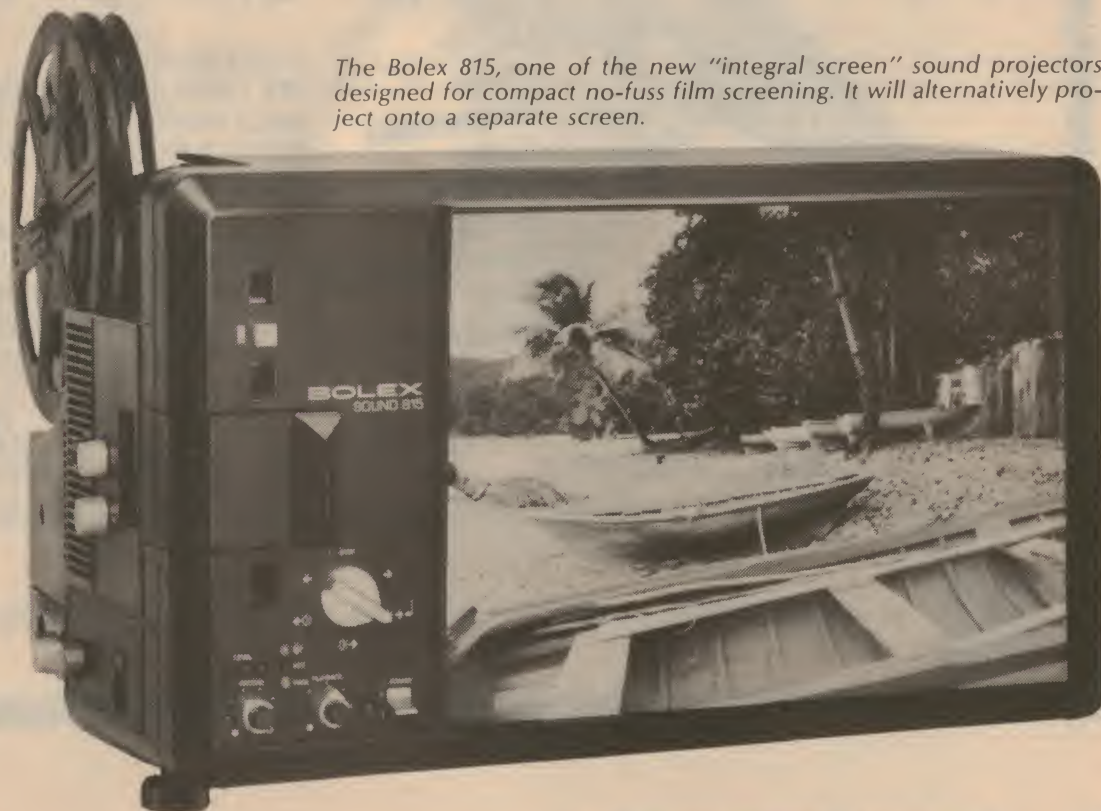The Bolex 815, one of the new "integral screen" sound projectors designed for compact no-fuss film screening. It will alternatively project onto a separate screen.





The Home Talkie Co. of Aust

Choose from over 500
different titles — Colour,
Cartoons, Comedies, Westerns,
Horror, Travel, etc.

Plus many more

STARS
OF
YESTERYEAR
AND
TODAY



THE BIRDS (Hitchcock)
DAY OF THE JACKAL
THOROUGHLY MODERN MILLIE
AIRPORT
WHO'S ON FIRST (Abbot & Costello)

EARTHQUAKE DUEL
JESUS CHRIST SUPERSTAR
SWEET CHARITY
SCIENCE FICTION — MONSTERS
Frankenstein. The Mummy
Dracula. The Creature. More
COMEDIES
Marx Bros. W.C. Fields
Abbott & Costello. Bob Hope.
CARTOONS
Woody Woodpecker
Chilly Willy. Fabulous
Harlem Globetrotters. More
ADVENTURE - ANIMALS - CLASSICS
VON RYAN'S EXPRESS
OUR MAN FLINT
SEVEN YEAR ITCH
CAROUSEL
DESIREE
FRENCH CONNECTION PART 2
CAN CAN
LOVE IS A MANY SPLENDORED
THING

THE PLANET OF THE APES SERIES
FRENCH CONNECTION
M.A.S.H.
PATTON
BUTCH CASSIDY AND THE SUNDANCE KID
THREE MUSKETEERS
TORA TORA TORA
POSEIDON ADVENTURE
SOUND OF MUSIC
STAR WARS



CHOOSE YOUR FAVORITE
STARS
on 60M and 120M reels.

NOW . . .
More
Sensational
Films
Available
For All
Super 8 Magnetic
Sound
Projectors

KING AND I
MY DARLING CLEMENTINE
AND MANY, MANY MORE
AVAILABLE FOR OUTRIGHT
PURCHASE

ENQUIRE ABOUT THIS YEAR'S
NEW RELEASES
FOR ILLUSTRATED COLOUR
CATALOGUE & ORDER FORM
SEND \$1.00 IN STAMPS TO:—

The Home Talkie Co. of Aust.

PHONE:— (Dept. ELEC) P.O. Box M200, Sydney Mail Exchange N.S.W. 2012
(02) 699-8777
698-1758

Retailers & Hirers of Super 8 & 16mm Movies
Photographic Products & Equipment

SHOWROOMS:— 268 Cleveland Street, Sydney (Cnr. Elizabeth Street)



1,000's
OF FILMS
ON DISPLAY

HOME MOVIES '79 — THE PROJECTORS



The SS-1200, a recent addition to the Chinon range. It offers stereo sound and 360m spool capacity.



The Elmo GS-1200, which offers stereo sound, 360m spool capacity, four drive motors and a 24V/200W lamp.

capability. The results can be quite impressive, despite the fact that the two channels are inherently unbalanced. The "balance" track is much narrower than the "main" track, as it was not intended for recording and playback; this

Some projectors also provide a feature known as programmable recording. This works in conjunction with a film counter, which is usually arranged to count in units of 18 frames (one second at 18fps). The idea is that you program the projector with the starting and ending counter readings for a new recording to be added to the film's track, and then it automatically switches the recording circuitry on and off at the right times.

Two of the projectors which offer this feature (the Bauer models T 525 and T 610) use a microcomputer for the

programming, and allow you to set the recording "on" and "off" points "on the fly" — ie, during a preliminary projection. The microcomputer automatically allows for the average human reaction time, setting the start and finish points some seven frames before those at the recording head when you press the buttons.

The microcomputer also rewinds the film automatically, to a point 100 frames before the start of the programmed recording. It can also be used to automatically start an external tape recorder, four frames before the recor-



The Sankyo model 500, which offers an 8V/50W lamp and 180m spool capacity.

means that the stereo channel using this track tends to have a significantly poorer signal-to-noise ratio than the other channel.

Another feature offered by many of the newer projectors is superimposition or "sound-on-sound" recording. This gives you the ability to control recording bias and erase power, so that you can partially record over the top of an existing recording without erasing it.

The firms who distribute them:

Listed below are the importers or distributors of the home movie equipment which is mentioned in this article or shown in the illustrations. In most cases the firms listed will not sell directly to the public; however should you have any difficulty in obtaining a piece of equipment, they will generally be able to advise you of the nearest dealer.

BAUER, MINOLTA: Photimport (Australia) Pty Ltd, 149 Milton Street, Ashfield NSW 2131.

BEAULIEU: Cinema Beaulieu division of International Dynamics, 23 Elma Road Cheltenham, Victoria 3192.

BELL & HOWELL, CHINON, RICOH: Maxwell Photo-Optics Pty Ltd, 55 Murray Street, Pyrmont, NSW 2009.

BOLEX: Wild Leitz (Australia) Pty Ltd, 45 Epping Road, North Ryde NSW 2113.

BRAUN NIZO: George's Camera Store Pty Ltd, 263 Elizabeth Street, Sydney NSW 2000.

CANON: Canon Australia Pty Ltd, 22 Lambs Road, Artarmon, NSW 2064.

COSINA: Tasmanex Pty Ltd, 374-376 Pittwater Road, Harbord, NSW 2096.

ELMO: C.R. Kennedy (Australia) Pty Ltd, 29 Mountain Street, Ultimo NSW 2007.

EUMIG: R. Gunz (Photographic) Pty Ltd, 63-73 Ann Street, Darlinghurst, NSW 2010.

GOKO: Camera Houses of Australia Ltd, 4/2 Harbord Road, Harbord, NSW 2096.

HANIMEX: Hanimex Pty Ltd, 108 Old Pittwater Road, Brookvale, NSW 2100.

POLAVISION: Polaroid Australia Pty Ltd, PO Box 163 North Ryde, NSW 2113.

SANKYO: Camera Distributors Pty Ltd, 108 Old Pittwater Road, Brookvale NSW 2100.

HOME MOVIES '79 — THE PROJECTORS & EDITORS

ding is to start — removing yet another source of error!


Apart from these functional features, most of the latest projectors offer improved sound performance as well. This has been achieved partly through improved stripe heads and amplifier electronics, and partly by a changeover to electronically-controlled DC motors for the film drive.

In place of the single capacitor-run AC induction motor used in most of the earlier sound projectors, many of the latest machines use at least two electronically controlled DC motors: one for the picture mechanism, and one for the sound drive.


This brings a number of advantages, the most important of which is lower wow and flutter. Because the sound capstan and flywheel are driven by their own motor, rather than by the film itself, there is less wow both when the projector starts up and when it is running. Similarly there is less flutter because the sound drive motor is completely isolated from the pulsating load of the projector's intermittent mechanism.

Apart from lower wow and flutter the actual speed regulation also tends to be better, and less dependant upon mains voltage. It also becomes quite independent of mains frequency. The designer can also provide an electronic fine speed adjustment — very handy if you are blessed with "perfect pitch".

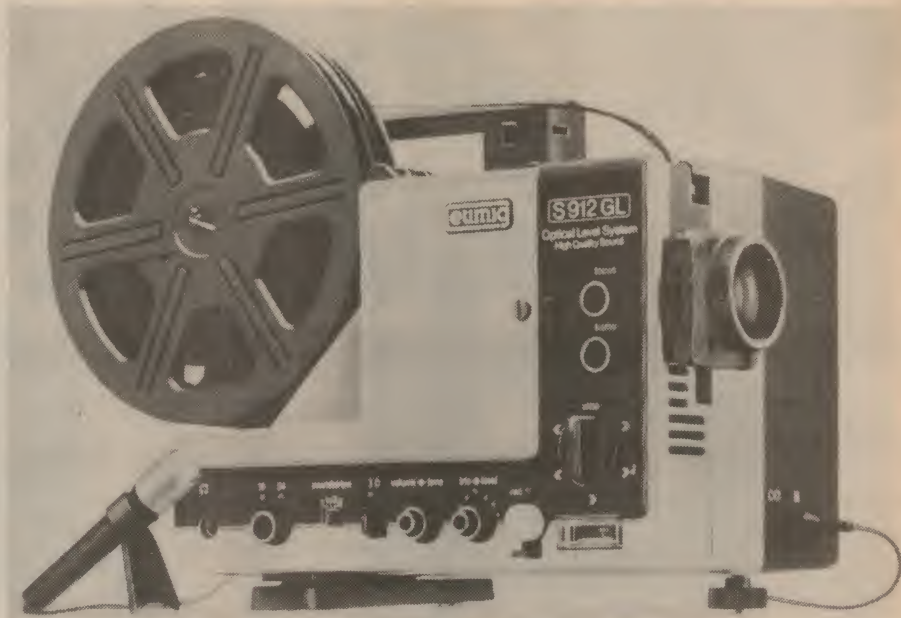The use of DC drive motors also tends to have another benefit: lower hum. Many of the earlier projectors were plagued by hum, due largely to



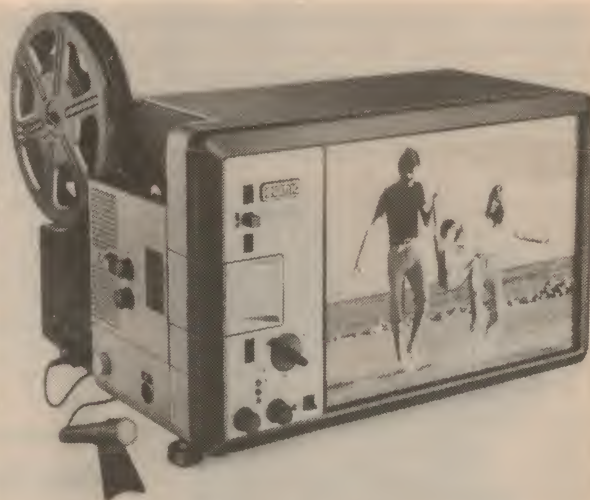The Eumig S912GL sound projector, which offers a 12V/100W lamp, 180m spool capacity and "optical levelling": the front lens element is moved to centre the picture on the screen.



The Eumig RS-3000, another of the new "integral screen" sound projectors. Note the co-axial spool arrangement.



The Hanimex SR 9000 sound projector, a compact unit with a 12V/100W lamp, 120m spool capacity and a sound-on-sound capability.

the sound head picking up leakage fields from the power transformer and induction motor. The changeover to DC drive motors removes at least one of these.

Although perhaps the main developments in the home movie area have been in cameras and projectors, there is another item of equipment which has also been upgraded: the animated viewer, or "editor".

Unlike projectors and cameras, editors do not use an intermittent mechanism to "freeze" the film briefly in the gate. Instead the film moves continuously, with a rotating prism used to freeze the images optically. The early editors use a 4-facet square rotating

HOME MOVIES '79 — THE PROJECTORS



The Goko RM-5000 motorised sound editor, due in Australia by March. It provides full recording and replay facilities.

prism, which gave a good deal of annoying flicker.

Many of the new editors use a 16-facet prism, designed to give almost flickerless pictures. They also tend to have a viewing screen with an integral Fresnel lens, to give a significantly brighter picture as well.

Of course with the advent of sound, movie makers needed some way of listening to the sound track on the editor, as well as viewing the picture. The first response of the manufacturers was to produce small clip-on sound readers for the existing editors, with a pull-through replay head and a small battery-powered amplifier capable of driving an earpiece or headphones.

Unfortunately as most of the existing editors were hand wound, the results from these add-on sound readers were quite poor. In fact one needed to be quite skilled in order to decipher the garbled sound at all! Because of this a new breed of editors has begun to emerge — motor driven, and with the sound head built in.

At this stage there seems to be only two of these motorised editors available in Australia: the Elmo 912/S and the Goko PM2. Both of these allow the user to wind the film back and forth manually in the traditional fashion, as well as providing steady motor drive at either 18fps or 24fps. The Elmo viewer also allows you to vary the motor speed continuously between 10 and 30fps. Both units have an inbuilt loudspeaker.

The next step is to have an editor with full recording and mixing facilities as well. Such an editor is already on the

way: the Goko model RM-5000, which is expected to be available in Australia by March 1980. It will provide full recording facilities, with VU meter, mixing between two inputs, provision for headphone monitoring, manual or automatic recording level control, and fine speed adjustments.

In short, it will provide just about everything you could want — a comment which seems to apply to just about all of the latest home movie gear.

Of course all the fancy equipment in the world won't guarantee professional results. You still need to devote a lot of time and effort into planning what you're going to film, and ensuring that your equipment is used to its full potential. But the right equipment can certainly help.

Finally, a few words about packaged films. Once you have a super-8 sound projector, you aren't just limited to showing your own home movies. You can also entertain your family and friends by screening super-8 prints of commercial movies, in the comfort of your own home. There are now many hundreds of such films available, for either hire or outright purchase.

Full-length features can be rather expensive to buy, running as high as \$350 for a lengthy colour film. But many enthusiasts collect condensed or "digest" 20-minute versions, costing around \$50-60 each.

One of the largest distributors of packaged films in Australia is the Home Talkie Company, of 268 Cleveland St, Sydney.



Cambion Low-Profile Solder Tab Sockets feature solid engineering... plus KAPTON™ film!

- all contacts sealed tightly on board side with Kapton—DuPont's polyimide film which inhibits solder or flux entry. Temperature resistance: -269°C to +400°C. Flame retardant, resists organic solvents.

- unique inverted spring design overcomes insertion force resistance.

- dual leaf spring for redundancy of contacts means four times the reliability.

- excellent DIP retention (low insertion, high extraction forces).

- all popular pin types in tin or gold plating: 8, 14, 16, 18, 22, 24, 28, 40 and 64-pin.



Available from:

**ELECTRONIC DEVELOPMENT
SALES PTY. LTD.,**


92 Chandos Street,
ST. LEONARDS, N.S.W. 2065.
Telephone: 438-2500
Telex: AA25963

CAMBION
The Right Connection.

Kapton—Trademark of Dupont Corporation

CHRISTMAS PRICE TUMBLE...

was
\$29.50
NOW
ONLY
\$14.50!

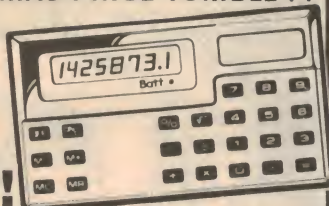

Yes, we've sacrificed these incredible mini-card liquid crystal display (LCD) calculators just in time for Christmas. Out they go at less than half price! They have memory, square root, percentage keys, etc., and the batteries last for around 2000 hours (has auto shut-off). Ideal for the kids at school, you in the office or mum shopping. **WHILE STOCKS LAST! (Cat Q-3022)**

SAVE \$10 ON CLOCK RADIO

Great for Xmas giving, or for yourself! AM/FM radio with digital clock. Wake up to music or buzzer. Was selling for \$45.00, now reduced \$10.00. Save now!

\$35.00



PLAY WITH YOUR COMPUTER!

Try some of these program tapes. They're interesting and exciting. Compare our prices and be pleasantly surprised. For the Sorcerer AND the TRS-80. Call in soon!

FOR THE SORCERER:

MAGIC MAZE: A challenging maze game with ten levels of play. Hold your lantern and wander through the maze. How good are you? Cat X-3620 **\$14.95**

PLOT: Cat graph graphics on your Sorcerer with this one. Super high resolution mode and quick low resolution on one cassette. Cat X-3621 **\$17.95**

Z-80 DISASSEMBLER: Decodes machine language programs, including Sorcerer's monitor and ROM-PACs. Or use in ASCII mode which converts machine language to ASCII. Cat X-3622 **\$17.95**

SHAPE MAKER: Construct special characters and fancy shapes with ease using this on-screen character editor. Detailed 12 page book. Cat X-3623 **\$17.95**

DEBUG: Debug machine language programs by stepping through one instruction at a time. Several display options, etc. Cat X-3624 **\$17.95**

FASTGAMMON: Backgammon players love this program. It provides a skillful opponent. Eight page instruction manual includes rules. Cat X-3625 **\$22.95**

FOR THE TRS-80

Hey, TRS-80 owners: Absorbing and interesting program cassettes miles cheaper than theirs. Look at these:

TIME TREK: (Cat X-3650) A version of the popular Star Trek or Space War.

STIMULATING SIMULATIONS: (Cat X-3652) Ten original games — art auction, forest fire, monster chase, nautical navigation, lost treasure, business management, game fishing, rare birds, space flight & diamond thief.

ELECTRIC PAINTBRUSH: (Cat X-3654) More than just a picture drawing tool, lets you paint patterns at machine language speeds.

BRIDGE CHALLENGER: (Cat X-3656) For all players from novices to experts, who would like to practice and improve their play.

ALL ABOVE:

\$17.95 ea

Compare our prices to you-know-who!

AMICROCHESS 1.5

Always ready for a quick blitz game, or a slow thoughtful one.

ONLY

\$22.95 ea

NEW!

Dick Smith cassettes have been up-graded. Brilliant new packaging tells you they're different — find out for yourself just how good they really are! Try a couple of these quality tapes: better still, try ten (types can be mixed) to obtain the bonus book below!

The inside story on cassettes

C60 LN: \$1.50 ea (Cat C-3350)

C90 LN: \$2.00 ea (Cat C-3352)

C90 EDR: \$2.75 ea (Cat C-3354)

BONUS:

Buy any ten 'Dick Smith' cassettes; or any Dick Smith cassette deck or recorder and receiver FREE a copy of our new book 'The inside story on cassettes'. Tells you all about this incredibly versatile recording medium, and how to get the best from your tapes and tape recording equipment. Also available separately: Cat B-6035 @ \$5.00

DON'T GET CAUGHT

(at about 8AM on Tuesday, 25th December as the kids unwrap their presents...)

Imagine! All those battery operated toys and no batteries. Wouldn't you be popular?


Remember to stock up now on budget Hi Watt batteries from Dick Smith. Cheaper by far than most brands, yet they're fresh and ready to go to work immediately. All popular sizes:

UM-1 ('D') size	Cat S-3001	25c ea
UM-2 ('C') size	Cat S-3002	20c ea
UM-3 ('AA') size	Cat S-3003	15c ea
'AAA' size (tiny)	Cat S-3004	25c ea
'006P' size (9V)	Cat S-3006	45c ea

ALKALINE BATTERY PACKS:

If you prefer, we have famous Mallory Alkaline extra-long-life batteries available. (Two in each pack except 9V type).

'AA' size	Cat S-3280	\$1.60 pack two.
'C' size	Cat S-3282	\$2.15 pack two.
'D' size	Cat S-3284	\$2.15 pack two.
9V (006P) size	Cat S-3286	\$2.50 each.

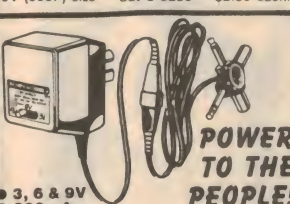

POWER TO THE PEOPLE!

- 3, 6 & 9V @ 200mA.
- 4-way connector & reversible polarity
- Fully Approved!
- WAS \$9.50 NOW

\$6.90

Cat M-9575

Every home should have one — or more. This battery eliminator gives 3 voltages, is ideal for most small appliances. Another bargain from Dick — just in time for all these Christmas gifts!

AMATEURS

DON'T FORGET: Dick Smith will match or better ANY GENUINE ADVERTISED PRICE on Yaesu or Hy Gain amateur equipment!

MORE OF DICK'S BONZA BULK BUY BARGAINS — BEWDY!



FERRITE RODS:

How's this one — 194 x 9mm ferrite rods normally sell for \$2.00 or more. Our normal retail price is \$1.50. But as a bonza bulk buy for a short time only: **90c ea!!!**

Yes, way under price, with dozens of uses for the electronics hobbyist: aerials, chokes, filters, audio suppressor circuits, etc. etc. While our super special lasts; first come first served. Don't miss out on this one!

Cat L-1401

90c ea!!!

YOU REAP THE BENEFIT!

A manufacturer of CBs went broke, so we bought the cases he had made. Must have cost double what we're selling them for! Hundreds of uses for the hobbyist, heavy aluminium case with punched panels as shown. Quick!

Cat H-2507

STRICTLY WHILE STOCKS LAST:

\$7.95!

HELP! Calling manufacturers, importers, liquidators, agents, etc. etc. etc.

If you've any bonza bulk buy bargains similar to the lines on this page, we're interested. You know what we're after: components, etc., which we can offer our hobbyist customers at big savings over normal retail prices. Turn your excess stock into cash by phoning Mark Sim or Gary Johnson on (02) 888 3200.

SAILING SAILING... MIDLAND MARINE RADIO FOR SAFETY AT SEA...



Cat D-1408

This is the marine radio they're all talking about. Mighty Midland. It comes already fitted with the four marine channels, and has provision for extra channels in the future — no crystals to buy! No matter what your craft, you need the security that only the Midland 857M 27MHz marine radio can give you. At \$115.00, you save nearly \$25.00 (was \$139.50). Buy now and save!

\$115 INCLUDING ALL FOUR BOATING CHANNELS!

But that's not all!

Each purchaser of the Midland 857M receives, as a bonus, our unique go-anywhere carry case, which allows you to remove the transceiver from the boat to prevent theft. With the addition of an optional battery pack and whip antenna, you can also use your Midland as a 'walkie talkie'. And this case is free with your Midland (normally \$25.00 extra!)

MARINE ANTENNA TO SUIT:

The Dick Smith 'White Swallowfish' with exclusive 'any-which-way' base. Strong fibreglass construction, complete with cable and tuning coil. Mounts on any boat (glass, steel, wood, etc. etc.) Cat D-4071

\$25.00 VALUE FREE!

EXCLUSIVE TO DICK SMITH: **\$49.90**

'CHANNEL F' CARTRIDGES — Large shipment of cartridges just arrived — here's your chance to grab some before they disappear again! And you can save money on some!!!!


A lot of people were disappointed when we ran out of the popular Fairchild 'Channel F' video entertainment computer cartridges. Now the good news: a large shipment has just arrived, putting good stocks of cartridges back in the stores. We've even cut the price on some of the more popular games! Don't delay: stocks won't last long! The following are back in stock:

- Dodge it (Cat X-1216)
- Hangman (Cat X-1218)
- Maze (Cat X-1204) And a brand new cartridge: BOWLING (Cat X-1221) all above cartridges: **\$24.50 each**

Save a massive **\$9.50** on the following:

- Desert Fox (Cat X-1203)
- Blackjack (Cat X-1201)
- Magic Numbers (Cat X-1210) and • Torpedo Alley (Cat X-1211)

\$15.00 ea

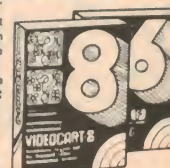

CAR \$\$\$\$ SAVERS

COMPRESSION CHECKER:

Compression levels tell you a lot about your car's engine, without going into the 'works'. This model has rotary dial, calibrated to 1800kPa, and simply pushes into spark plug holes.



Cat A-8506

\$7.50

THIS ONE SOLD FOR \$13.50

NOTE: As our prices are so far under normal retail, stocks are very limited. Don't miss out! Strictly first come, first served.

NEON TIMING LIGHT:

If your timing is off, you're wasting fuel — and money. Check your timing easily and reliably with this neon timing light. Pistol grip for ease of use, pre-focused super bright neon flash tube. Works with all ignition systems: just connect in series with No. 1 plug.



Cat A-8507

\$9.95

THIS UNIT SOLD NATIONALLY FOR \$13.50 — SAVE \$3.55!

UHF TV IS COMING!

Get ready for it with a new UHF TV antenna from Dick Smith. High gain, easy to install, great value.

Cat L-4028

\$19.95

How about a go-anywhere TV ant?

Dick has this little beauty ideal for mounting on caravans, campers, etc, or clip to the gutter of the holiday house.

Suits all Australian channels.

Cat L-4026

\$23.95

SOMETHING TO PLAY WITH OVER THE CHRISTMAS HOLIDAYS?

Try a TV game IC. We've bought an entire shipment of the famous AY-3-8500 IC from a major manufacturer and we're practically giving them away! Yes, we supply a data sheet to show you how to make a TV game, but at this price you could just about use them as fishing lures! They were selling for \$17.75 each. Here's your chance to save a massive \$16.00, while they last! **NOW ONLY \$3.75 each!**

Cat M-6448 Not \$19.75

Update your car hi-fi — for a new year of sound!



\$149.00

\$49.95



We've searched the world to bring you this beauty. An AM, FM and stereo cassette player that will make your music come alive — whatever your taste! Suits in-dash fitting in the same space taken by a normal car radio (replaces the garbage car manufacturers often give you!) and operates from 12 volts, negative earth. 4 ohm speakers suit this unit (not supplied). Also has: • tape fast forward • local/d switch for radio • mono/stereo switch (great for noise reduction on FM in difficult areas.) Cat Z-6480

Want a new set of speakers for the car? Dick has a huge range of car speakers, from around \$2.00 to our superb co-axial and dual cone car speakers at around \$30.00 pair. Call in soon — or check them out on page 23 of our catalog.

You can REALLY make your music sing with this car stereo power booster amplifier. It features a 60 watt (peak) circuit (30W per channel), with a frequency response of 25 to 20000Hz. You can use this with virtually any car stereo (it simply connects in series with the speaker leads; instructions provided) and operates from 12 volts. It's powerful enough to overcome road and other noises in virtually any car. Incredible! Cat A-6680

SEASON'S GREETINGS!

Dick Smith and staff wish a happy Christmas and a safe and prosperous new year to all.

And we hope to be of service to you again in 1980.



BUYING BY MAIL?

It's so easy! Simply list the items you want, with their catalogue numbers, and post it off with your cheque to our mail order centre (address at right). Don't forget to include post & packing (charges apply to total order value as per table at right). Then watch your letterbox!

ORDER VALUE:

\$5 (min) to \$9.99	\$1.00
\$10.00 to \$24.99	\$2.00
\$25.00 to \$49.99	\$3.00
\$50.00 to \$99.99	\$4.00
\$100 or more	\$5.00

NOTE: These charges apply to goods sent by post in Australia only. Large and bulky items cannot be sent by post.

If you prefer, we will despatch your order by Comex Road Freight to anywhere in Australia for only \$6.00 — that's below what it costs us! Large and bulky items are normally sent by Comex unless you specify differently (eg by rail or air — you pay freight on delivery.)

CHRISTMAS GIFT IDEAS...


for technical people; for thinking people; for someone who's got everything!

SOLAR EXPERIMENT KIT - 25-IN-ONE

The science of the 21st century - solar power! Help them learn more about this fascinating field with our budget 25-in-1 solar experiments kit.

\$16⁹⁵

COMPLETELY SAFE!

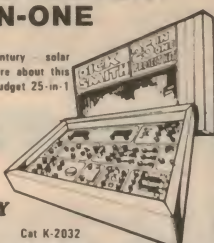

Cat K-2032


150-IN-ONE KIT

150 electronics projects - enough to keep even the laziest person busy for a long, long time. No soldering required with this simple kit - and it is battery operated so it is SAFE! Great value.

\$53⁵⁰

Cat K-2030

Comes in beautiful carry case, too!

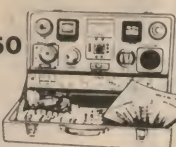

INCREDIBLE PRICE CUT!

Was selling for **\$59.95**!!!!

Yes, we've made a scoop purchase of manufacturer's excess stock - at below manufacturer's cost price! Unit supplied with one channel (27.125MHz) and has provision for second channel (also available). All these units are brand new, and work - but are worth our price in parts alone! Use in conjunction with CB transceiver for paging system!

Cat D-1100

ONLY

\$12.50!

Plus batteries

LOOK! NO WIRES!



Cat F-1010

WIRELESS INTERCOM

Improve communications around the home, office, factory, etc with this easy to install intercom. Easy! It's easier than that! Just plug them into a power point! That's all. Home to garage, office to factory, kids room to kitchen - the uses are endless!

\$49.50 pr

A CB FOR XMAS?

The CB scene has quietened down: it's now really worthwhile. If you've been put off by press reports, think again. CB for safety.



MIGHTY MIDLAND AM 1280 \$129.50 **\$89.50**

Midland 882: Australia's most popular CB. Great range, great performance. Easy to operate, too. Makes a good 'start-up' set. Cat D-1436

RIGHT: Popular magnetic base CB antenna. No holes to drill, sticks to roof of vehicle. Cat D-4412 \$19.50 **\$16.50**


Mighty Midland SSB - for when you're really serious. Tremendous range and performance, unique features. Midland SSB: the Rolls Royce of CB radio. Cat D-1700

SUPER SSB \$239.50 **\$199.50**

DON'T FORGET! We have a huge range of CB radios and CB radio accessories. For anything in communications, see the experts at your nearest Dick Smith Electronics store.

6 LEVEL COMPUTER CHESS

VALUE!

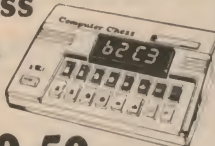

\$99.50


Plus batteries

DICK BREAKS THE \$100 BARRIER!

Yes, this incredible chess computer gives 6 levels of play from basic beginner through to very expert, large, easy-to-read LED display makes easy play. Battery or mains operated (optional) will give lasting enjoyment to the chess players in your family. Cat X-1250

PUSH BUTTON PHONE DIALS

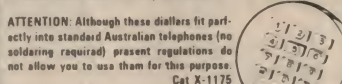We've sold hundreds of these - push button phone dials, ideal for experimenters systems. They remember the last number dialed (up to 16 digits) for easy re-call if the number is engaged. 4 colour coded wires for easy installation.



\$49.95

ATTENTION: Although these dials fit perfectly into standard Australian telephones (no soldering required) present regulations do not allow you to use them for this purpose. Cat X-1175

IN A WORD: BRILLIANT!

3-way light: fluoro, spot and flasher for campers, in the car, home; wherever you need a portable lamp. Hand held or use shoulder strap supplied. Cat X-1084

24 TUNE DOOR BELL

Remember the 'Chromachime'. We sold thousands! Here is a fully built up version of this popular circuit. 24 tunes, fully selectable. Comes complete with push-button for external mounting, so you don't have to buy one! Smart wood grain finish, ideal for mounting on or near door. Incredible value at our super introductory price.

(The Chromachime was \$49.50, in KIT form, and without a front door push button! Incredible!!!!)



Cat X-1130

\$35.00

IT'S ABOUT TIME...

STOPWATCH/TORCH

Incredible! A stopwatch that can do splits, lap timing, etc down to 1/100 second, in a tiny case that also includes a torch! LCD readout for long battery life, highly accurate. Note: due to demand stocks may be low until mid month! Cat X-1043



\$39.50

VALUE FOR THE MOTORIST:

Quartz chronometer accuracy, large, easy-to-read fluorescent digits. Operates from 12 volts, takes less power than your dash lights. Easy to install, bracket supplied. As shown, with case. Cat X-1047

\$24.50

Unit without case (for installation in dash) Cat X-1045 **\$19.50**

STILL THE BEST VALUE!

THE IMPROVED DICKTRACER Mk II

Australia's greatest value in a radar detector! Why spend \$100 and more when all you need is a Dicktracer. Internal batteries recharge overnight from the cigar lighter so there's no trailing leads. Value!

\$49⁵⁰

Cat A-8500

TOOLS MAKE GREAT CHRISTMAS GIFTS!

40PC SOCKET SET:


Ideal for the mechanic, home handyman, etc. Metric and SAE sizes. Set all sizes, with ratchet driver tool. You'd pay dollars more elsewhere! Cat T-4670



\$16⁵⁰


NIBBLING TOOL / TOOL/HOBBY BOX

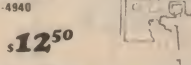Hands up if you've ever wanted to cut holes in thin sheet metal, PCB's, etc. Here's the answer: a handy nibbler. Cuts out holes, shapes, lines, etc in thin metal or plastic, etc. No handyman should be without one. Cat T-4940



\$12⁵⁰

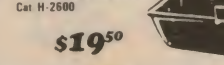Talk about handy! This strong tool or hobby box locks for security (padlock not supplied) and opens out to reveal generous storage area with two storage trays for bits and pieces. Ideal for the electronics enthusiast especially, but also great for a host of other hobbies. Cat H-2600



\$19⁵⁰

Just a few of the hundreds of great gift ideas from our tool and hobby centres at your store!

DICK SMITH ELECTRONICS

NSW 125 York Street, SYDNEY Ph 290 3377
147 Hume Hwy, CHULLORA Ph 642 8922
162 Pacific Hwy, GORE HILL Ph 439 5311
30 Grose Street, PARRAMATTA Ph 683 1133
263 Keira Street, WOLLONGONG Ph 28 3800
ACT 96 Gladstone St, Fyshwick Ph 80 4944

VIC 399 Lonsdale St, MELBOURNE Ph 67 9834
656 Bridge Road, RICHMOND Ph 428 1614
QLD 166 Logan Road, BURANDA Ph 391 6233
SA 203 Wright St, ADELAIDE Ph 212 1962
WA 414 William St, PERTH Ph 328 6944

EXCEPT WHERE NOTED, ALL ITEMS SHOWN IN STOCK AT PRICES GIVEN AT TIME OF GOING TO PRESS.

MAIL ORDER CENTRE: PO Box 321, NORTH RYDE NSW 2113. Ph 888 3200. PACK & POST EXTRA.

NEW KITS

(and new kit components)

Remember: parts for most kits in most of the electronic magazines are normal stock lines. So even if a kit isn't listed, we may be able to help you anyway. Call in and ask us!

TRANSISTOR ASSISTED IGNITION (See EA December)
Complete kit including instructions Cat K-3300 \$32.50
Printed circuit board Cat H-8367 \$2.20
BUX80 power transistor Cat Z-2150 \$10.95

FAN SPEED CONTROL (See EA December)
Short form kit (PCB components, no hardware) Cat K-3090 \$11.50
Printed Circuit Board Cat H-8368 \$1.60
SC141D Triac Cat Z-4510 \$1.28
(rippy box, etc, normal stock lines - or build it in to appliance.)

NEW METAL LOCATOR (See EA November)
Complete kit (excluding dowell & former) Cat K-3504 \$19.50
Printed Circuit Board Cat H-8366 \$2.40

INFRA-RED REMOTE CONTROLLER (See EA October)
CQY8A infra red diodes Cat Z-3235 \$1.50
BPW34 photo transistors Cat Z-1954 \$3.50
Printed circuit boards (pair) Cat H-8365 \$5.95

PROCESS TIMER (See ETI October)
Printed circuit board Cat H-8623 \$3.95

DISCO STROBE Mk 11 (see ETI September)
Complete kit, including instructions Cat K-3152 \$34.50
Printed circuit board Cat H-8572 \$1.95
Flashtube Cat S-3882 \$2.95
Trigger transformer Cat M-0104 90c
Discharge capacitors (each) Cat R-2855 \$3.75
Reflector Cat K-6016 \$4.50

WINDSCREEN WIPER DELAY (See EA September)
Printed circuit board Cat H-8364 \$2.50
Other components for this project are normal stock lines.

AUTO CHIME (See EA September)
Complete kit Cat K-3502 \$29.75
Printed circuit board Cat H-8363 \$3.70
TMS-1000 Integrated Circuit Cat Z-6825 \$16.50

INDUCTION BALANCE METAL DETECTOR (See ETI)
Short form kit (not inc. dowell or former) Cat K-3100 \$36.50
Printed circuit board Cat H-8578 \$1.50

MASTHEAD AMPLIFIER (See EA August)
Complete kit Cat K-3232 \$29.50
Printed circuit board Cat H-8362 \$2.50
OM350 integrated circuit Cat Z-6185 \$9.95
Diecast box Cat H-2221 \$3.00
Zippy box Cat H-2751 \$2.50

9KHz WHISTLE FILTER FOR TUNERS (See Feb EA)
Complete kit, including instructions Cat K-3496 \$19.75

MAJOR DICK SMITH RESELLERS

Listed below are re-sellers who stock a large range of our products. However, we cannot guarantee that they will have all items in stock or at the prices we advertise.

A&M Electronics
78 High Street, Wodonga, Vic. Ph 244 588
Advanced Electronics
5a The Quadrant, Launceston Tas. Ph 317 075
Aero Electronics
123a Bathurst Street, Hobart Tas. Ph 348 232
Peter Brown Electronics
9 Doveton Street North, Ballarat Vic. Ph 323 035
Crystal TV Rentals Pty Ltd
66 Crystal Street, Broken Hill NSW. Ph 6897
Decro Electric
Cnr Magellan St & Brunner Hwy, Lismore NSW. Ph 214 137
Elektron 2000
44 Brown Road, Broadmeadow, Newcastle NSW. Ph 691 222
D & M Harrington
6/1 Machinery Drive, Tweed Heads South, NSW. Ph 364 589
Hutchesson's Communications
5 Elizabeth Street, Mt Gambier SA. Ph 256 404
Keller Electronics
218 Adelaide Street, Maryborough, Qld. Ph 214 559
M & W Electronics
48 McNamara Street, Orange NSW. Ph 626 491
Mellor Enterprises
Shop 2/15 Forsythe St, Whyalla Norrie, SA. Ph 454 131
Power & Sound
147 Argyle Street, Traralgon, Vic. Ph 743 638
Purely Electronics
15 East Street, Rockhampton, Qld. Ph 021058
Stevens Electrical
42 Victoria Street, Mackay, Qld. Ph 511 723
Summer Electronics
95 Mitchell Street, Bendigo, Vic. Ph 431 977
Sound Components
78 Brisbane Street, Tamworth NSW. Ph 661 363
Trilogy Wholesale Electronics
40 Princes Hwy, Fairy Meadow, Wollongong, NSW. Ph 831 219
Tropical TV Services
249 Fulham Rd, Vincent, Townsville Qld. Ph 791 421
Variety Discounts
113 Horton Street, Port Macquarie NSW. Ph 835 486
Wagga Wholesale Electronics Sales
82 Forsyth Street, Wagga NSW
Wellington Electrical Services
110 Lee Street, Wellington NSW. Ph 325

bankcard
welcome here

SHOPS OPEN 9AM TO 5:30PM
(Saturday: 9am till 12 noon)
BRISBANE: Half hour earlier
ANY TERMS OFFERED ARE TO APPROVED APPLICANTS ONLY
RE-SELLERS OF DICK SMITH PRODUCTS IN MOST AREAS OF AUSTRALIA.



Power line interference —

The problem of power line interference to TV sets has been discussed in two recent articles; the Serviceman's notes for April 1979 and an article on an ultra-sonic detector (for pole hardware) in the September 1979 issue. This comment, by the engineer who inspired both articles, suggests other approaches, including an interference-immune TV set.

by R. G. AUTARD

For those who missed the Serviceman's article in the April issue it was a precis of a paper written by myself in the December 1978 Monitor — Proceedings of the IREE Australia-titled "Interference to VHF TV Services from Overhead HV Power Lines".

Naturally enough, the Serviceman's views reflect the thoughts of technically minded readers, bewildered by the fact that we have not cured this interference after 20 odd years of TV.

This attitude towards power lines and electricity authorities is perfectly understandable. However, the technical side of the subject, which is much bigger than most of us imagine, is only part of the story. Its importance rates well below the financial aspects, or to put in bluntly, your power bill. Rightly or wrongly, elimination of interference is financed by the vast majority of consumers who have never experienced power line interference.

Much to the annoyance of some people, supply authorities are not authorised to handle complaints direct from the public. The diagnosis and location of interference requires a great deal of expertise and equipment. The proper authority is the Postal and Telecommunications Department, who locate the source of interference and pass on the location of the troublesome pole to the electricity authority concerned.

The bulk of complaints are about TV interference with only a handful of radio complaints. Bonding the ball and socket joints of adjacent disc insulators as mentioned by The Serviceman and myself would probably halve the complaints, but the cost would be considerable. The remaining TVI would be much harder to find and cure.

A frequent suggestion is to put overhead voltage lines underground. Here again the cost may be prohibitive. In general, any big changes to the electrical distribution systems are so costly that alternative schemes come into favour. The following scheme would reduce power line interference to below car ignition and other competitors:

(a) Re-allocate TV channels to UHF in capital and large cities. This would

reduce city TVI complaints to a very low level.

- (b) Abandon channels 0, 1, 2 and 3. This would reduce the remaining complaints in country areas by a large amount.
- (c) The loss of these channels could be made up by allocating UHF channels and using co-axial cable distribution of TV programs.
- (d) Increase the use of repeaters, translators and community antennas in difficult areas.
- (e) Reduce interference generated by slack span power lines in country areas by redesigning or bonding the metal parts of adjacent disc insulators.

Another scheme for reducing the effects of TVI is a kind of video noise limiter. Interference from high voltage lines consists of short pulses of RF which die away in a few μs . While the pulse exceeds the peak black level the picture tube is cut off, but during the decay period which follows, the picture tube displays the mutilated colour, modulated by a mutilated luminance signal.

In the next scan line of an interlaced PAL system, the mutilated chrominance signal is modulated by normal luminance and displayed for the full


another approach

duration of the interference pulse. (Monochrome and NTSC system receivers are both luckier because they display the interference pulse once only; as it occurs.)

The proposed limiter, which shows more promise than its audio counterpart, could overcome ignition, commutator, and power line interference. Its basic principle is to borrow a piece of good picture from another line, each time interference is received.

By delaying the signal by two lines, or $128\mu\text{s}$, we have a choice of switching between the delayed signal and the present signal. Supposing we choose to display the delayed signal on the screen for normal viewing. The arrival of an interference pulse would then be arranged to switch the picture display to the present signal for a few micro-seconds while the interference persists. (It would be better if we could borrow information from another frame because the differences would be much smaller.) A basic block diagram of the two line delay system is shown.

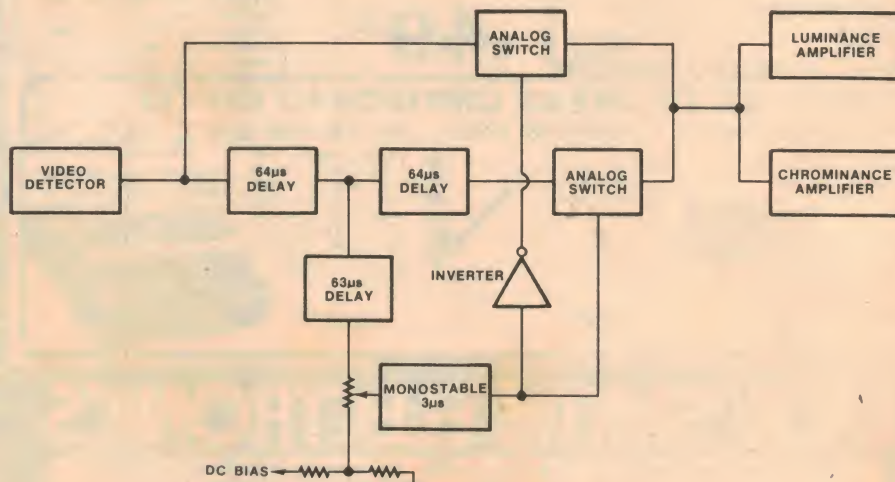To sum up: Rearranging the TV spectrum is a drastic and expensive way of overcoming TV interference from power lines but stopping the interference at its source is much more so. The development of an interference immune TV set seems to me to be the best solution. In the long run I suppose we will just put up with things the way they are — but it makes you wonder, doesn't it?



A block diagram of the proposed video interference suppressor. The displayed signal passes through two delay lines but the analog gates switch the delay out just before an interference pulse is due to be displayed on the screen.

Star Trek:

the motion picture is coming!

"Star Trek — The Motion Picture" climaxes the enormously popular TV series and is probably the most expensive motion picture produced. It is the story of the defence of Earth by the "Enterprise" against alien invaders.


THE MOVIE goes national across Australia and New Zealand on December 21st. An article on the making of "Star Trek" is currently at an advanced stage of preparation, and we hope to present it in the January issue. Watch for it!

Commander Decker
and Ilia ▼



The alien invaders ▲

Mr Spock ▼

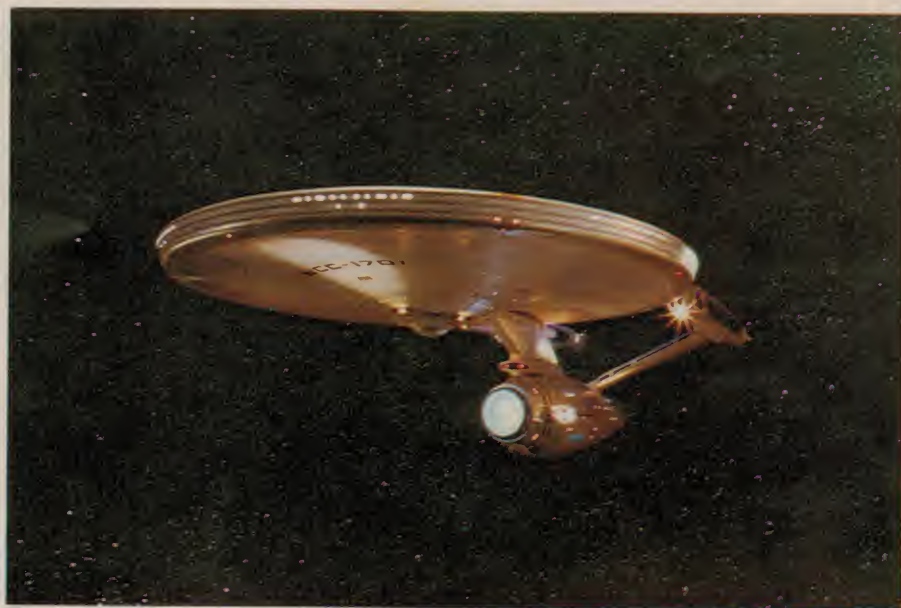

USS "Enterprise" — defending Earth ▲

A MORE COMPLETE CASSETTE DECK WOULD BE HARD TO IMAGINE.



Technics Model RS-641

Technics has gone to great lengths to bring you the RS-641 cassette deck. And it shows.

A glance at the front panel reveals such sophisticated features as a long life, highly accurate FL (fluorescent) bar graph peak/VU meter which makes conventional needle-type meters obsolete.

The distinct advantage of the FL meter is that there is no moving parts, as control is electronic so response time is instantaneous. Also there is no overshoot, a characteristic of the needle-type meter. The FL meter itself emits light, so there is no difficulty in reading and the left and right channel displays are aligned in parallel for easy viewing and comparison.

The RS-641 employs a vertical hold front-loading system with the cassette compartment boasting an indicator for tape left


to run and a back projected light. There's also a music selector switch which allows you to locate the beginning of your favourite track . . . automatically.

What you can't see will impress you just as much. As with any quality deck today the Technics RS-641 has Dolby* noise reduction. Heart of the tape transport system is an IC-controlled FG servo DC motor which maintains unwavering speed accuracy. The result is low wow and flutter rating of 0.05% WRMS.

The impressive wide frequency response is due to the exclusive Technics HPF recording and playback head. So durable that it carries a limited 10-year warranty.

Technics cassette decks offer a lot more than you would expect. See for yourself at your Technics dealer.

For a National Technics catalogue, please write to:
National Technics Advisory Service, P.O. Box 278, Kensington, N.S.W. 2033


 DOLBY SYSTEM * Under licence from Dolby Laboratories Inc.

 **Technics**
hi-fi

SCOOP PURCHASE OF MANUFACTURER'S EXCESS STOCK — BELOW COST PRICE!! INCREDIBLY SMALL WALKIE TALKIE

SAVE
OVER
75%!!

ORIGINALLY
\$59.95 EACH!

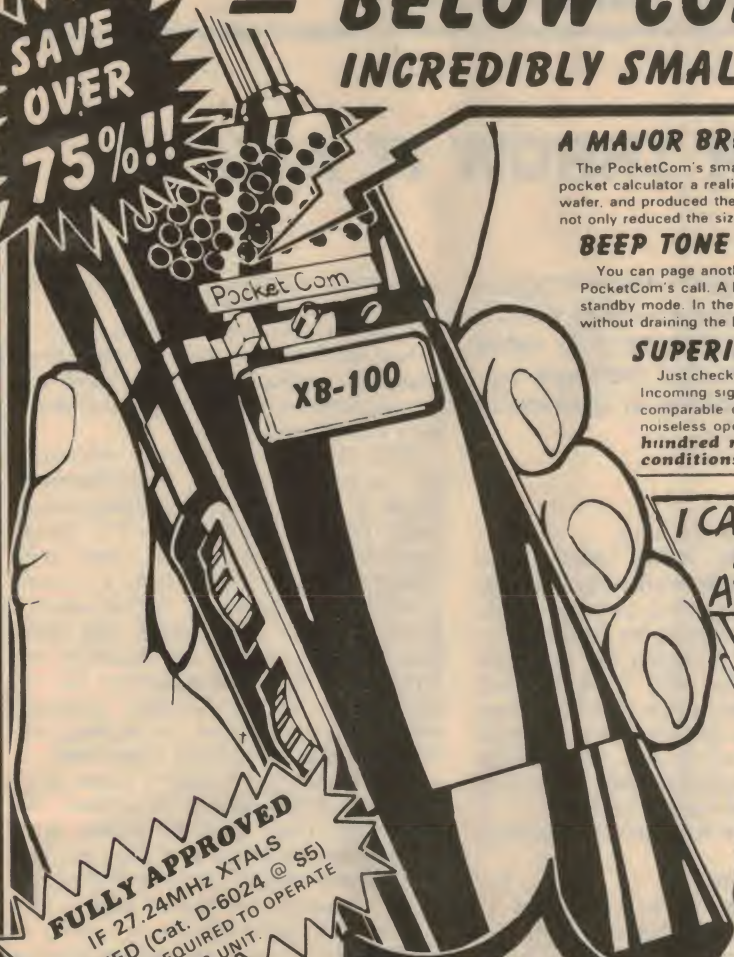

A MAJOR BREAKTHROUGH

The PocketCom's small size results from a breakthrough in the solid-state device that made the pocket calculator a reality. Scientists took 112 transistors, integrated them on a micro-silicon wafer, and produced the world's first transceiver linear integrated circuit. This major breakthrough not only reduced the size of radio components but improved their dependability and performance.



BEEP TONE PAGING SYSTEM

You can page another PocketCom user, within close range, by simply pressing the PocketCom's call. A beep tone sounds on the other unit if it has been left in the standby mode. In the standby mode the unit is silent and can be kept on for weeks without draining the batteries.

SUPERIOR FEATURES

Just check the advanced features now possible because of this new circuit breakthrough 1) Incoming signals are amplified several million times compared to only 100,000 times on comparable conventional systems. 2) A high squelch sensitivity (0.7 microvolts) permits noiseless operation without squelching weak signals. 3) **Range- works from a few hundred metres in the city areas to many kilometres in line of site conditions in country areas.**

I CAN SEE THE
ENEMY,
ATTACK NOW!

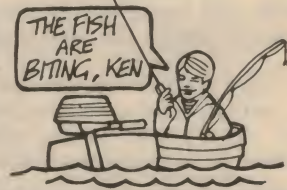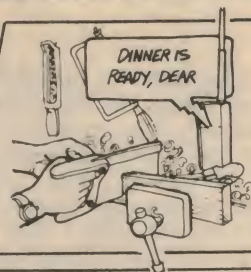

FULLY APPROVED
IF 27.24MHz XTALS
FITTED (Cat. D-6024 @ \$5)
LICENCE REQUIRED TO OPERATE
THIS UNIT.

ONLY
\$12.50
EACH
WAS \$59.95

2 BATTERIES REQUIRED
Cat. S-3005 @ 25c each

Cat. D-1100

Post and Pack \$2.00

HUGE SURPLUS (DISTRESS STOCK) PURCHASE!! YOU REAP THE BENEFIT FROM MANUFACTURER'S MISFORTUNE. . . .

- OVER 200,000 SOLD IN U.S.A. ALONE!
- ALL BRAND NEW!
- ALL ACTUALLY OPERATE BUT ARE WORTH IT FOR THE PARTS ALONE!!
- UNIT SUPPLIED WITH ONE CHANNEL (No.10) CRYSTAL FITTED. PROVISION FOR ANOTHER CHANNEL.
- IDEAL FOR SPORTING EVENT CONTROL, RADIO CONTROL PROJECTS, GARAGE DOOR OPENERS, PAGING RECEIVERS ETC. THOUSANDS OF USES!
- USE AS A PAGING RECEIVER FROM A 5 WATT BASE STATION FOR LONG RANGE.
- FULLY P&T APPROVED IF 27.240MHz XTAL FITTED (\$5.00).

DICK SMITH ELECTRONICS

NSW 125 York Street,
147 Hume Highway,
162 Pacific Highway,
30 Grose Street,

SYDNEY. Phone 290 3377
CHULLORA. Phone 642 8922
GORE HILL. Phone 436 5311
PARRAMATTA. Phone 683 1133

263 Keira Street, WOLLONGONG Phone 28 3800

ACT 96-98 Gladstone Street,
VIC 399 Lansdale Street,
856 Bridge Road,
QLD 168 Logan Road,
SA 203 Wright Street,
WA 414 William Street,

FYSHWICK. Phone 80 4944
MELBOURNE. Phone 87 9834
RICHMOND. Phone 428 1814
BURANDA. Phone 381 6233
ADELAIDE. Phone 212 1982
PERTH. Phone 328 8944

EXCEPT WHERE NOTED, ALL ITEMS SHOWN IN STOCK AT PRICES GIVEN AT TIME OF GOING TO PRESS.

MAIL ORDER CENTRE: PO Box 321, NORTH RYDE NSW 2113. Ph 888 3200. PACK & POST EXTRA

bankcard
welcome here

SHOPS OPEN 9AM to 5:30PM
(Saturday 9am till 12 noon)
BRISBANE Half hour earlier
ANY TERMS OFFERED ARE TO
APPROVED APPLICANTS ONLY
RE-SELLERS OF DICK SMITH
PRODUCTS IN MOST AREAS OF AUSTRALIA





FORUM

Conducted by Neville Williams

REPAIR, UP-DATE OR THROW IT AWAY?

One of the mounting pressures in our modern technological society is to develop, exploit and adopt what is new — and simply to discard the old. Inevitably, there are those who tend to rebel against this philosophy, preferring to maintain and perhaps update what they already have. But is this a proposition, at least in the realm of electronics?

What triggered the question was a couple of letters from readers who were obviously keen to take advantage of recent technological developments, without having to scrap otherwise satisfactory equipment. It was with no great displeasure that I had to discourage them from cutting loose with screwdriver and soldering iron — but their letters did cause me to think at greater length about the whole question.

In the 1930s, when I first entered the industry, radio receivers were relatively expensive, due largely to the cost of components and after-sales back-up. Factory labour at the time was cheap, with much of the work being done by under-21s, who could be hired and fired without ceremony, according to seasonal needs. In my first job as an assembler/wirer, I worked a genuine 48 hours per week for the grand sum of £1 (\$2.00) gross. When railway fares went up, I had to plead for a rise; otherwise it would have cost me 2/- a week to remain employed!

Later, I was promoted to testing and servicing and, while this carried a salary margin, it was not such as to prevent me from spending as much time as necessary to salvage disasters — even to completely stripping and re-building sets that had been fouled by a burned-out power transformer!

To discard a receiver, in those days, was unheard of. They were traded-in, patched up and re-sold, until they became a total liability. After that, they would be taken over and stripped for parts by some impecunious enthusiast.

That was in the 1930s. Since that time, the relative cost of labour has risen enormously and this has affected manufacturing and servicing quite differently, radically changing the

balance between the two.

In the factory, rising labour costs have been more than offset by automation to the extent that portable radio receivers can currently be bought over the counter in Australia for less than \$10. Allowing for 15:1 inflation, that would have been equivalent to about 6/- (60c) in the early thirties — much less than we had to pay for a single valve and about one-sixtieth the cost of a budget-priced mantel radio.

No wonder we were at pains to keep them talking!

But repair work, by its nature, has always been labour intensive and its cost has simply followed wages up. Today, if you summon a tradesman to do anything at all, his bill is likely to start at \$15-\$20, plus so much an hour thereafter. It simply means that there is now a whole range of gadgets and appliances — including small radios — that it is uneconomic to repair. It is quicker and cheaper to buy a new one. And, if the new one fails under

guarantee, it is cheaper for the supplier to replace it than fix it!

It seems odd but that's the way it is.

Not surprisingly, attempts have been made to reduce the skill level and labour content of servicing but with not very convincing results.

With the arrival of colour television, for example, various manufacturers made a great song and dance about supplying replacement PC board assemblies. Servicemen, they said, would need to carry only a certain number of standard factory-tested boards. When a set failed, the faulty board would simply be replaced and later returned to the factory for re-processing and re-testing. Australia would be the home of smiling servicemen and contented customers!


Unfortunately, it didn't quite work that way. For a variety of reasons, the planned few boards grew into prohibitive numbers and the unit cost multiplied with the logistics of shuffling them around. In many cases, servicemen found it simpler to revert to the time-honoured method — diagnosing and fixing the trouble themselves, leaving only the "dogs" for the factories.

With colour receivers still relatively young and still relatively costly to replace, it is economical to repair them — but it won't always be that way. Sooner or later, they will begin to make their appearance on council tips, along with discarded refrigerators, stoves and washing machines.

In some other areas of electronics, the stories one hears about back-up "service" are nothing short of staggering.

The most recent to come our way concerns a friend who installed a new industrial camera for use in the manufacture of PC boards and panels. When trouble developed with the electronic exposure control, he lodged a call for service. Yes, the camera could be fixed by changing over a (not too complicated) PC board assembly for a mere \$560!

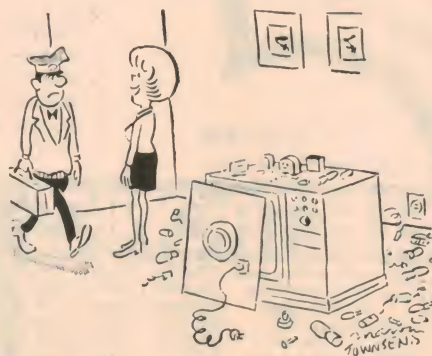Taken completely aback, he stalled for a couple of days to consider the situation. It appeared almost certain



"Harry started to change it over to colour, then decided against it!"

"Radio-Electronics"

that the trouble involved a couple of components on the board, worth about as many dollars but the supplier was quite adamant in his attitude:

We are not set up to repair boards. All we can do is to supply a changeover board as quoted. If you fiddle with it yourself, we will not recognise any future obligation to provide service!

Not very nice.

If it is costly (or uneconomical) to repair many items of equipment, it is likely to be even more so to modify or up-date them — at least on a commercial level.

Arrangements for after-sales service are normally built into the original marketing plan, with spare parts coming from the original production overrun. The mechanics of repair are concerned mainly with correction of the outstanding fault and return of the item in its otherwise existing condition. Morally and officially, that's where the manufacturer's obligation begins and ends.

UP-DATING? UGH!

By contrast, any undertaking to up-date a piece of equipment carries the implication that it is being re-processed to ensure a higher order of performance or convenience. New parts may be involved, plus the man-hours necessary to install them and to ensure that the re-worked equipment meets the higher performance expectations. In the majority of cases, the effort is simply not worthwhile on a cost/benefit basis.

For the owner who is also a competent technician, the situation may be quite different. If the time involved is ignored, equipment can often be maintained, re-built, restored or up-dated with not too much cash outlay — but cases like this are the exceptions rather than the rule. Not too many consumers have the qualifications, the time and the patience to tackle such a task.

Curiously, a great deal of such expert activity has to do with nostalgia and trendiness, rather than any kind of anti-throwaway philosophy. Period homes, period furnishings, period cars and period bric-a-brac are "in" — as a conscious departure from what is modern.

But the cars that are most lovingly restored are very old vehicles that are not in any sense competitive with the present-day family car. The ones in between tend to be passed over as second-hand, clapped-out, rusted bombs! Some time in the future they will regain respectability — when most of them have long since been buried or melted down.

And in the radio/TV sphere, there is no great interest in old valve sets and the "passing parade" of veneered plywood cabinets. Nostalgia ignores them in favour of "wireless" from the twenties era.

But I digress.

A more immediate problem involves those typified by the correspondents mentioned earlier. They have equipment which is still currently in use, they want to up-grade it to include a recent development but they lack the expertise to cope with the job on their own. Can the magazine provide the necessary information by way of a project?

Unfortunately, the general response to such a proposition has to be in the negative. Most electronic equipment comes in a wide variety of brands, models, nationalities, shapes, sizes and circuit configurations. It would be a Herculean task to determine whether a proposed internal modification would be practical for them all, and/or the number of variations that might have to be allowed for.

It would be most unlikely that any one model could serve as a representative example of what precisely needed to be done. Almost inevitably, some enthusiasts, motivated to "have a go", would find themselves in deep trouble. It would be all too easy to end up with equipment which was unserviceable in the old form and unworkable in the new!

We would certainly not want to be a party to that kind of situation.

Take, for example, the case of the reader who is keen to modify his present cassette deck to take the new metal-coated tapes.

TYPICAL LETTER:

Dear Sir,

It has occurred to me that the imminent vogue for metallic cassette tapes will leave a great many of us with decks fitted with quite adequate tape transport systems but with obsolete tape heads and circuitry.

Would conversion be viable? If so, how much would be involved and would it be within the capabilities of a mediocre home constructor? (Another Playmaster project, perhaps.)

Thanks for the comprehensive mag and don't be bluffed into scrapping your "newcomer" articles. We aren't all qualified technicians you know!

Regards, T.T. (Doyalson, NSW)

If I were to offer the short answer, I would simply say to T.T.: "Forget it!"

To be more explicit, there is not much future for a magazine like "Electronics Australia" in trying to tell readers how to modify commercial equipment. This would be especially true for "mediocre home constructors" (your phrase) and for equipment with as many makes and models as cassette decks.

Conversion of a cassette deck for metal-coated tape would present a whole array of problems. For starters, one would require a higher powered bias/erase oscillator and a higher powered recording output stage, plus

PLESSEY COMPONENTS

For stocks of

DRALORIC



Ceramic RF Power
Capacitors

- Tubular Capacitors
- Pot Capacitors
- Plate Capacitors
- Feed-through Capacitors
- Water-cooled Capacitors
- High Voltage Capacitors

GENERAL COMPONENTS

Stocks held of

- Connectors
- Rotary Switches
- Lever Keys
- Reed Relays
- Neon Lamps
- Panel Lamps
- Switches
- Potentiometers
- Integrated Circuits
- Sonalert Devices
- Indicator Tubes
- Photodiodes
- Photo Voltaic Cells
- Nickel Cadmium Batteries
- Loudspeakers

*Try us for hard-to-get
components such as:-*

- Silver Mica
- Transmission Mica
- Transmission Ceramics
- Computer Grade Electrolytics




**PLESSEY
COMPONENTS**

PO Box 2 Villawood, NSW 2163.
Telephone 72-0133

Adelaide 269 2544 ● Melbourne 329 0044
Brisbane 36 1277 ● Perth 458 7111

LATEST IMPORTS AT REDUCED PRICES

TRANSAIR® TRANCEIVERS

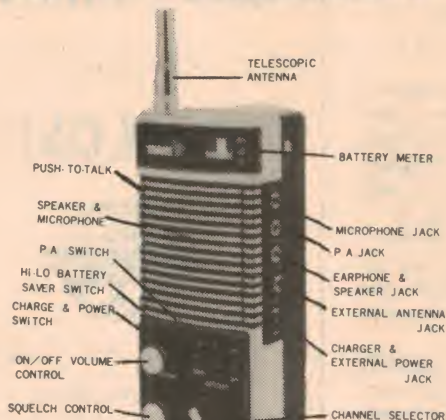

***\$95.00**
EACH

MODEL TNC-506
5 WATT 6 CHANNEL TRANSCEIVER
WITH 4 CHANNELS OF CRYSTALS
FITTED. CARRY CASE INCLUDED


MODEL TC-10 ***\$47.92 EACH**
1 WATT 2 CHANNEL MODEL WITH TONE CALL
EXTERNAL POWER & EARPIECE SOCKETS

Handheld Transceiver ***\$58.63 EACH** **WT273**

A powerful (2 watt), hand held marine transceiver which gives longer range and greater reliability.

- Built-in condenser microphone for exceptional voice clarity.
- 3 channel capability.
- Lightweight (50gms).
- Squelch control to cut down background hash.
- Super one hand operation.
- Earphone facility.
- Carry case.

AFP SCIENTIFIC CALCULATORS

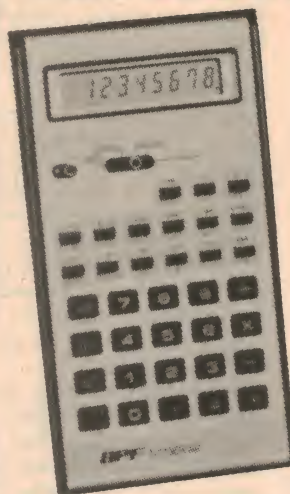

AFP
M5602 ***\$28.95**
SCIENTIFIC
SLIDE RULE
LCD CALCULATOR

- TRIGONOMETRIC FUNCTIONS
- STATISTICAL FUNCTIONS
- FULL SCIENTIFIC NOTATION
- 35 KEYS

SPECIFICATIONS:

1. Display: 8-digit liquid crystal display.
2. Capacity: 8-digit with sign.
3. Memory: 1 accumulating memory.
4. Calculation modes:
 - a. $+$, $-$, \times , \div
 - b. $()$, $\{ \}$, $[]$
 - c. π , e^x , \sqrt{x} , $1/x$, x^1
 - d. Log, Ln, 10^x , e^x , \sqrt{x} , $\sqrt[3]{x}$
 - e. Sin, Cos, Tan, \sin^{-1} , \cos^{-1} , \tan^{-1}
 - f. Σx , Σx^2 , \bar{x} , σ , σ^2
 - g. Constant and repeat operation.
 - h. DMS (degree-minute-second) to degree, degree to DMS.
 - i. Mode select switch selects degree, grad, radian or statistical mode.
5. Notation: Automatic selection for scientific or floating point notation.
 - a. Result x is displayed as floating point notation when $0.01 < |x| < 10^4$
 - b. Otherwise x is displayed as scientific notation.

AFP

MARK 8601

LCD advanced scientific calculator

- TRIGONOMETRIC FUNCTIONS
- STATISTICAL FUNCTIONS
- FULL SCIENTIFIC NOTATION



***\$39.95**

FEATURES:

- * Advanced LCD scientific calculator.
- * 10 digit with sign, or 8 digit mantissa + 2 digit exponent display.
- * 1 independent memory.
- * Calculation range: 10^{-99} to 10^{99}
- * Mode key for Degree/Radian/Grad/Statistical function selection.
- * Two level parenthesis.
- * Scientific functions: x^2 , \sqrt{x} , $1/x$, π , $x!$, 10^x , e^x , \ln , \log , y^x , $\sqrt[y]{x}$, nPr , nCr , \sin , \cos , \tan , \sin^{-1} , \cos^{-1} , \tan^{-1} , \sinh , \cosh , \tanh , \sinh^{-1} , \cosh^{-1} , \tanh^{-1}
- * Statistical functions: \bar{x} , σ , Σx , Σx^2 , $P(x)$, $Q(x)$, $R(x)$
- * Exchange functions: CN , $P \rightarrow R$, $R \rightarrow P$, $\sigma \rightarrow \sigma^2$, $D \rightarrow R$, $R \rightarrow G$, $G \rightarrow D$, $R \rightarrow D$, $G \rightarrow R$, $D \rightarrow G$.
- * Long battery life - over 2000 hours' operation.
- * Super thin size with deluxe aluminum case.

QUALITY MULTIMETERS AT REDUCED PRICES



RAPAR MODEL 200H
20,000 OHMS PER VOLT
14 RANGES

SENSITIVITY: 20,000 Ohms/Volt DC
DC VOLTS: 0.5, 25, 125, 500, 2500
AC VOLTS: 0.10, 50, 250, 1000
DC CURRENT: 0-50mA, 250mA
RESISTANCE: 0-50K, 0-5M Ohm
DECIBEL: -20 to +22

NORMALLY *\$15.94

SPECIAL *\$11.95



RAPAR SK120
NORMALLY ***\$39.85**

SPECIAL *\$29.88

RAPAR SK120

SPECIFICATIONS:-

SENSITIVITY: 20K Ω /Volt DC
10K Ω /Volt AC
DC VOLTAGE: 0.3V, 3V, 12V, 60V, 300V, 1200V
AC VOLTAGE: 6V, 30V, 120V, 300V, 1200V
DC CURRENT: 60 μ A, 6mA, 60mA, 600mA
RESISTANCE: 8K Ω , 80K Ω , 800K Ω , 8M Ω
DECIBELS: -20 to +63dB
DIMENSIONS: 146 x 95 x 38 mm

DISTRIBUTED BY:

Radio Parts GROUP

562, SPENCER STREET, WEST MELBOURNE, VIC. (03) 329 7888.
1103, DANDENONG ROAD, EAST MALVERN, VIC. (03) 211 8122.



FORUM: Repair, up-date or discard?

erase and recording heads capable of handling the additional energy without magnetic saturation. It would be unrealistic to expect substitute components to be made available for a significant number of decks, and equally unrealistic to expect "universal" conversion kits.

Nor would the problem end there. The circuitry in existing decks will have been peaked and tweaked to get the best out of the original heads and the then-available tape. It may not be optimum for new heads and new tape.

In short, the amplifier circuitry, including response, compensation and bias, would have to be reworked in an effort to realise the potential of the new tape. It would also have to be reworked (with appropriate switching) so that the deck would perform correctly with conventional tape!

Finally, we return to the matter of mechanics. As frequency response is pushed up, head alignment and tape travel become progressively more important. It does not follow that mechanics adequate for a top response of 12-15kHz will cope with 20kHz.

As I see it, metal-coated tape is not an end in itself. It is an important forward step in technology which has challenged manufacturers of cassette equipment to effect an across-the-board upgrading of specifications — right through to reduced wow and flutter and hifi at half speed. In achieving this, they are pushing the cassette system technology to new limits.

It makes interesting reading, it's nice to own it and something to brag about. But I suspect that the majority of cassette users, with access to a good conventional deck and good conventional tapes, can already make recordings which match up pretty well to their subjective acuties.

My advice to T.T. is to settle back and enjoy what he has until such times that he can trade it in on something obviously better.

NOISE IN FM RADIO

In rather similar vein comes a letter from a reader in Padstow, NSW, who says:

Dear Sir,

I have read with interest the two brief snippets you published about stereo FM noise and how it is easily overcome by fitting "a little black box".

Having been plagued by this impulse noise problem on my FM mono car radio, I can imagine how much worse it must be in stereo. I am sure that many readers would welcome a constructional article on such a noise reduction system.

I believe that impulse noise suppression ICs are available overseas and an

article by your magazine could encourage suppliers to import them here.

B. F. (Padstow, NSW)

I am not sure how much of the discussion B.F. may have seen but a letter in "Forum" in May (N.H. North Carlton, Vic, p.25) is very relevant. Reacting to earlier correspondence, N.H. makes the following points: impulse suppression devices are basically palliatives, not cures; they may require internal modification to the receiver; they call for critical setting up

procedures.

As with cassettes decks, there are so many makes and models of automotive FM receivers, so many different vehicles, and so many different listening situations, that we have little inclination to encourage readers to get involved in electronic surgery. External, add-on units are one thing; "black boxes" which have to be wired into the innards of existing commercial receivers are quite another.

We would be much happier if our current exercise with inductive ignition cable resulted in a cure for ignition impulse noise, at least from the parent vehicle. But even that hopeful cure is proving rather elusive. ☺

A poor lookout for television

It is mildly annoying when an aircraft, flying nearby, causes television pictures to flicker and dance. However, few people get up-tight at present because the effect may last for only 10 or 15 seconds. But Thomas B. A. Senior of the University of Michigan in Ann Arbor, and research colleague Depak L. Sengupta warn that similar video modulation caused by giant windmills will not be so obliging. The interference will persist while ever the blades are turning and it will be particularly bad if the TV broadcast happens to be on the UHF band.

Sengupta believes that the annoyance level could be such as to inhibit the installation of giant wind turbines on some otherwise suitable sites. But, more than mere annoyance, he sees windmills as a positive hazard in locations where they might affect the signals from airport guidance and landing aids.

Research by Senior and Sengupta has centred around a 100kW windmill, with 37.5m blades, which has been constructed by NASA near Sandusky, Ohio. If the USA is to exploit wind power on a large scale, it is imperative that the potential for RF propagation interference be understood and allowed for.

Lafayette)) TWO-WAY RADIO

FOR INDUSTRY, FARMS BOATS, SPORTS, ETC.



1 WATT 3 CHANNEL
LAFAYETTE HA-310



1000's of Lafayette HA-310 Walkie-Talkies in use in Australia. 100,000's throughout the world, attest to their superior qualities. A professionally designed, sturdily constructed, commercial quality unit for top performance and long term reliability. Rechargeable Nicad battery packs and large range of accessories available.



Pinnacle PE-920, 6 channels, 5 watts, transceiver for 27MHz marine, within premises and limited area services. Ideal mobile or base station unit. Design eliminates unwanted image interference from CB stations. Up-to-the-minute design with all wanted features.



P & T Dept Approved (Licence Required)

Lafayette are 2-way specialists. Large range of crystals, antennas, auxiliary equipment available!

Dealer enquiries invited.

Lafayette)) the Communicators

LAFAYETTE ELECTRONICS Div. of ETD Electronics Pty Ltd
94 ST KILDA ROAD, ST KILDA, VIC 3182. Tel 534 6036.

SPECIAL PURCHASES

NEW B.S.R. RECORD CHANGERS-PLAYERS



MODEL C197
\$47.50

This is a new model just released and is fitted with a ceramic cartridge & diamond stylus. Auto or manual operation: Three speed 33, 45 & 78rpm. Cueing control and bias compensation: Changer & player spindles supplied: 11" turntable. Post & packing extra, NSW \$2.75: Vic, Qld \$3.75: WA, NT & Tas \$4.75.

SPEAKER GRILLE FABRIC AT 1/2 PRICE

AVAILABLE IN BLACK, BLACK WITH GOLD FLECK, LIGHT & MID BROWNS. WIDTH 60in.

\$4.80 Per YARD. Post & Pack \$1.75.

Send two 20c stamps for samples.

GARRARD CC10A RECORD CHANGER

\$15.75

Fitted with a Sonatone Garrard Ceramic Cartridge Sapphire Stylus supplied with template & instructions. Posts & Packing: NSW \$2.50. Inter. \$3.50.

MODEL C142R

HI-FI UNIT WITH ADC MAGNETIC
CART & DIAMOND STYLES



\$55.00

A precision automatic and manual record-playing unit fitted with 4 pole motor to provide constant speed conditions for the 11 1/2 inch turntable. The low resonance tubular pickup arm is counter-balanced with a resiliently mounted weight to permit light sensitive tracking, and the slide-in cartridge carrier enables styles inspection and the interchange of replacement of cartridges to be carried out simply and quickly. Fine stylus force adjustment and bias compensation are both calibrated for accurately setting the arm to given optimum playing conditions for the chosen cartridge.

The fluid-damped level-type cue and pause control ensures gentle lowering of the pickup to the surface of the record. A short spindle is supplied for single record play records. Precision engineering is reflected in the styling of the 142R, which is elegantly finished in black and silver.

POST AND PACKING EXTRA

NSW \$3.75

Tas, WA & NT \$7.00

Vic, SA & Qld \$5.75

(Reg. post \$2.00 extra)

NEW RANK-ARENA F.M.-A.M. TUNER AMPLIFIER

MODEL RA402. Output 24 watts RMS. (12+12). Response 50HZ to 50KHZ. Mag or ceramic inputs. High & low filters. Loudness control. Provision for 4 speakers.

Freight Extra.

\$147.00

NEW AWA HI-FI SPEAKER KITS 8" 2 WAY 3 SPEAKER SYSTEMS

AT LESS THAN 1/2 LIST PRICE

POWER RATING 20 WATTS R.M.S.
IMPEDANCE 8 OHMS
FREQUENCY RANGE 46 TO 18000 CYCLES

Supplied in kit form (less cabinet) each kit comprises: One AWA 8WAC 8in. bass unit, two AWA 4MBC 4in tweeters with ceramic magnets & curve-linear cones, crossover components, grille cloth, innabond lining and cabinet plans.

CABINETS AVAILABLE
Post & packing extra, NSW
\$2.50. Interstate \$3.50

\$18.50
Per Kit

NEW E.M.I. AND HITACHI RECORDING TAPE AT BARGAIN PRICES

HI-DYNAMIC EMITAPE — HIGH OUTPUT — LOW NOISE — HI-FIDELITY

HLP18 7" reel 1800ft. long play \$5.95 P & P — \$1.00

HDP12 5" reel 1200ft. double play \$3.95

Hitachi LN 8-track 90 minute cartridge. 5 for \$10. P & pack \$1.50.



NEW GOODMAN-FOSTER 3-WAY

4-SPEAKER HI-FI SYSTEM

\$39.00 PER KIT

Frequency Range 45 to 22,000 cycles. Power rating 25 watts. RMS Imp-8ohms. Supplied in kit form (less cabinet) each kit comprises two English Goodman 8" bass units. Foster 5" mid range. Foster 1" dome tweeter crossover components Ocodensers and inductance innabond, speaker fabric and plans of cabinet. Cabinet dimensions 23" x 13" x 10" CABINETS AVAILABLE.

Post & packing extra: NSW \$2.70: VIC, SA, QLD, \$4.70: WA \$5.70. (REGISTERED POST \$2.00 EXTRA IF REQUIRED) cabinets available.

NEW HOKUTONE HI-FI SPEAKER KITS AT A FRACTION OF LIST PRICE

NEW THREE WAY HIGH FIDELITY SPEAKER SYSTEM
WITH A FREQUENCY RANGE OF 35 TO 20,000 CYCLES.
POWER RATING 50 WATTS.

Supplied in Kit form (less cabinet) Woofer HFW-302, 12". Mid range HM-24 dome. Tweeter HT-60 dome. Three way crossover with separate controls for mid range & tweeter. Innabond lining, grill fabric & cabinet plans supplied Cabinet dimensions 668 high, 435 wide, 310 deep.

\$69.00 per kit

Freight extra by
rail, air or road transport.

NEW GARRARD 6-200 CP RECORD PLAYERS

Fully automatic turntable automatically or manually as required. 11" turntable. Cue & pause control. Record speeds 33 1/3, 45 and 78 rev/min. Finished in black with silver trim. Fitted with ceramic cartridge. Post & packaging extra NSW \$2.70: Vic, Qld, SA \$3.70: WA \$4.70 (registered post \$2 extra if required).



\$34.00

RANK-ARENA 2 WAY SPEAKER

- 10 Watts RMS
- 8 ohm impedance
- 8" woofer with tweeter
- Supplied with lead and plug
- Teak finish



\$42.00
PER PAIR

Dimensions 18"H, 11"W, 9 1/2"D
Freight extra per rail air or road transport

NEW MAGNAVOX — MV50 — 50 WATT SPEAKER SYSTEMS


COMPLETE KIT OF PARTS (LESS CABINET) COMPRISING MAGNAVOX 10240 IN 10" BASE UNIT. 625 MID RANGE 6" TWO XJ3 DOME TWEETERS, CROSS OVER NETWORK, INNABOND, SPEAKER SILS AND PLANS OF CABINET. ALSO 6 1/2" AND 4 1/2" TUBES.

\$89.50 PER KIT

Freight extra per rail or air freight.
Cabinet available 830 System also available.
Range of Magnavox Speakers stocked.

CLASSIC RADIO

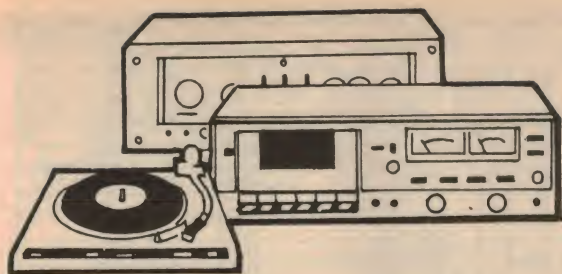245 PARRAMATTA RD, HABERFIELD 2045. PHONES 798-7145, 798-6507.



Hi Fi Topics

A NEW GENERATION OF DYNAMIC SPEAKERS FEATURES OIL-COOLED, OIL-DAMPED VOICE COILS

Every now and again, one comes across a reference to loudspeakers which use a "magnetic fluid" in the air-gap surrounding the voice coil. What is magnetic fluid and in what way can it contribute to the ultimate performance of a dynamic driver? Is it an important technological development or a gimmick?

If one were to accept at face value the claims in advertisements and publicity hand-outs, the answers to such questions would never be in doubt:

Magnetic fluid simplifies assembly of drivers with tight tolerances, and reduces the number of rejects; it helps protect the voice coil from overheating; it increases power handling capability; it improves damping of the voice coil and cone assembly; it suppresses contortions of the voice coil; it cuts distortion, controls resonances, improves performance, flattens peaks, reduces transient ringing. It allows given power requirements to be met by smaller drivers, and simplifies crossover network design.

And so on.

The claims sound so impressive that the reader might almost wonder how we have possibly managed, to date, without this magical fluid!

Up till fairly recently, the idea of putting any foreign substance in the voice coil air gap of a dynamic driver was a technical "funny", if only because there was no way in which it could be retained. It would very smartly be sprayed or smeared all over the place by the rapid to-and-fro movements of the voice coil and cone.

Well ... almost anything would! The writer recalls an experience from younger days, when he was called out to service a receiver which had become mysteriously silent for no apparent reason. There were no faulty components, no short circuits, and no open circuits. It ultimately transpired that the handyman set-owner had traced a rattling noise to the paper cone in the loudspeaker "that seemed loose". He had laid the speaker on its


back and dribbled glue "down into that space there". Immediately following the treatment, the speaker sounded "much smoother and sweeter" but, next morning, the set wouldn't work at all!

How could it, with the voice coil glued solidly to the pole faces?

While the story has its funny side, there is also a point to it. While the glue was still viscous, it would undoubtedly have inhibited "rattling", whether due to loose turns or to contact between the voice coil the pole face. It may also have improved speaker damping — a property that was lamentably deficient in many early radio receivers. Unfortunately the cure, while prophetic, was also rather short-lived!

The idea behind the current generation of magnetic fluids was originally developed by NASA as a possible means of controlling rocket fuel in part-empty tanks under the weightless conditions in space. In the absence of gravity, fuel might be induced to aggregate and flow in response to magnetic fields — provided it could be given appropriate magnetic qualities.

It was found that liquids could be

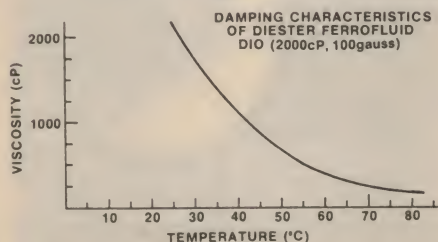

Variation of viscosity with temperature is a problem which remains to be solved, if damping is to remain constant.

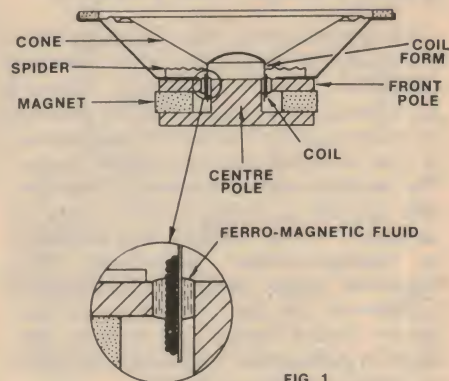


FIG. 1

Not drawn to scale, the sketch shows how ferromagnetic fluid is retained within the normal air-gap by the magnetic field between the pole faces.

given this unlikely property by mixing into them minute particles of a magnetically sensitive solid — particles so small that they would remain in permanent colloidal suspension. Under the influence of a magnetic field, the particles would move in a particular direction, shuffling the liquid molecules along with them. It was as if the liquid itself was magnetically responsive.

In the event, NASA found other ways around their fuel problem and, for a while, magnetic fluid was largely an interesting idea in search of an application. Then, around 1969, the Ferrofluidics Corp (Burlington, Mass., USA) began to promote it in connection with special purpose seals, bearings and dampers.

Ordinary fluids tend, in the long term, to creep out of bearings and past seals and may cause troublesome contamination in critical equipment. But by using a "magnetic" fluid (hydraulic fluid, lubricant, etc) and by setting up a magnetic field between the bearing faces, the fluid can be retained much more effectively, by magnetic attraction.

In due course, it was realised that this very property would enable a magnetic fluid to be retained within the voice coil gap of a dynamic loudspeaker,

without any kind of physical containment. The liquid would simply distribute itself between the inner and outer pole faces and the voice coil structure, resisting any tendency to be carried away from the intense magnetic field. As such, it would have the potential to lubricate, cushion and damp the mechanical movements of the voice coil, with possibly beneficial results. (See Fig. 1).

In addition, it could be expected to conduct heat from the voice coil to the magnetic structure and frame, thereby offering some protection against voice coil damage under conditions of near-overload.

IRON OXIDE PARTICLES

As developed for loudspeaker purposes, a magnetic fluid typically contains tiny, irregularly shaped particles of iron-oxide (Fe_3O_4), ground to a dimension of about 100 Angstroms, or one millionth of a centimetre across. The particles are so processed that they also acquire a molecular-thin layer of surfactant which inhibits the tendency to coalesce when magnetised. This, together with random (Brownian) movement of the molecules of the carrier liquid, keeps the ferrous particles in permanent suspension, even in an intense magnetic field.

Contrary to what might be expected, the actual concentration of solid matter in the carrier fluid does not need to be very high (eg 2%) so that the physical properties of the fluid remain substantially unchanged.

Needless to say, the characteristics of the carrier liquid are vital if it is to fulfill its role in the overall driver design:

- It should exhibit the greatest possible heat conductivity. At present, six times the conductivity of air is a typical bench mark.
- The shear/viscosity characteristics must be such as to apply the appropriate amount of damping to the voice coil of particular drivers. Manufacturer's data indicate that typical magnetic fluid can be adjusted in the range 100-10,000 centipoise at 27 degrees C, according to requirements.
- The particle loading must be low enough so as not to prejudice the shear characteristics when subject to a magnetic field. At the same time, loading must be high enough to ensure that the liquid is retained in the gap under all possible signal drive conditions, or under any likely handling (even accident) stress.
- It must not evaporate or harden during the anticipated service life of the loudspeaker.
- It must not interact with adhesives, finishes or other materials involved in the magnet/voice coil assembly.
- All the above properties must be

Pouring oil on troubled tweeters!

With magnetic fluid in the air gap of a cone tweeter, a troublesome 1kHz resonance (upper curve) was eliminated (lower curve). See text.

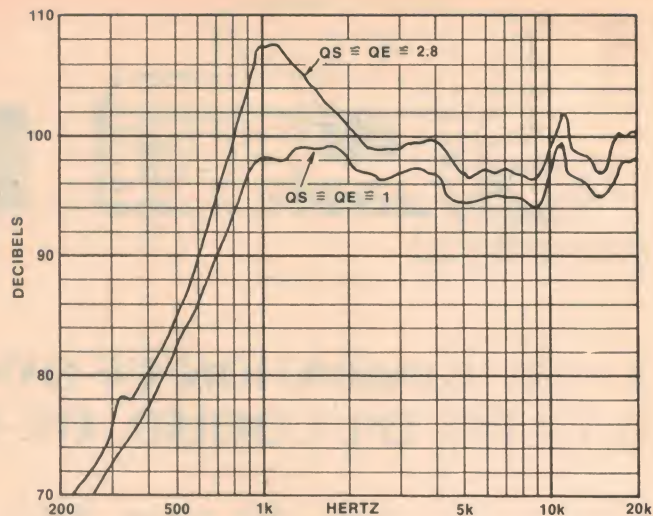


FIG. 3

maintained as far as possible over the full range of ambient and working temperatures. Fig. 2 suggests that considerable further work needs to be done in this area.

Ferromagnetic fluids are available involving various carriers, such as diesters (probably the most widely used) fluorocarbons (more costly) and synthetic hydrocarbons. Silicones are also under consideration.

At present, magnetic fluids suitable for use in loudspeakers are all quite

expensive. A typical brochure from the Ferrofluidics Corporation lists 100-Gauss Ferrofluid on diester base at \$US1075 per litre. The equivalent 200-Gauss Ferrofluid is \$US1612 per litre, with other fluids exhibiting higher Gauss levels, lower viscosity, etc, available on special order.

Fortunately, the amount of magnetic fluid required in any one driver is quite small and therefore the cost, while significant, is not prohibitive — provided there is no waste. To this end,

AR systems use ferromagnetic fluid



According to Max Roberts, Managing Director of Acoustic Research Australia, the tweeters and (upper) mid-range drivers in all current AR loudspeaker systems use magnetic fluid in the voice coil gap for purposes of damping and heat conduction.

At the expensive end of the AR "Vertical Series", the AR9 and AR90 are four-way systems in which the tweeter and upper mid-range drivers rely on magnetic fluid for damping — and more importantly for heat conduction. AR say that, at the power ratings involved (400W and 300W respectively) compact, wide dispersion drivers are only practicable by reason of the magnetic fluid.

The AR91 (pictured) and the AR92 are three-way systems in which the mid-range driver has to work down to 700Hz and this posed a potential problem with the back of the unit sealed and with the magnetic gap also sealed with fluid. AR overcame the problem by using fluid only between the voice coil and inner poleface, thereby combining the benefits of damping and heat conduction with adequate air movement.

For further details of the AR range of loudspeaker systems: Acoustic Research Australia, 3 Ford St, Greenacre, NSW 2190. Tel: (02) 642 3993.

The new generation of factory-built or kit-set Peerless loudspeakers



It's true most speakers *look* alike and that price alone never tells the whole story. But now the new generation Danish-built Peerless loudspeakers give you a recognizable difference in sound quality—a difference that has set Peerless a notch above the others for over 50 years.

The range of new generation Peerless loudspeakers includes the fully assembled *PAS series* plus the money-saving *PLK kit-sets*. Both series contain drive units with the following characteristics.

Peerless 'X' Line Woofers

- ☐ Large ceramic ferrite magnets for high power handling.
- ☐ Specially coated cones reduce colouration to a minimum.
- ☐ Cones are supported by a single-roll foam or rubber surround to maintain excellent linear motion.
- ☐ Bass response is clean and tight at all listening levels.

Peerless Midrange Units

- ☐ Sealed back units prevent interaction with the woofer. Distortion and colouration are reduced to a minimum.
- ☐ The rear side of the cone is coated with a special damping material to eliminate colouration.
- ☐ Specially impregnated polyurethane cone rim provides high degree of linearity.

Peerless Tweeters

- ☐ Dome tweeters designed for the highest accuracy of reproduction with low distortion flat response and wide dispersion.
- ☐ The sealed back isolates the tweeter from interference.
- ☐ Specially developed dome fabric ensures no degradation of performance even after prolonged heavy loading.
- ☐ Assembly mounted on a precision diecast plate where rigidity ensures permanent alignment.

Peerless Dividing Networks

- ☐ Peerless crossovers use air-cored chokes for maximum power handling, and special electrolytic capacitors to ensure long term reliability.
- ☐ All components are mounted on fibreglass printed circuit boards for maximum durability, while coded clip connectors eliminate the need for soldering.

Power handling

The power handling capacity is high and conservatively rated at 100W RMS, however, due to the high efficiency of Peerless speakers, the recommended amplifier power is between 25-100W RMS.

Whether you settle for the smart timber-veneered *PAS* assembled series or the *PLK* kit-set, you're getting the same Danish-made Peerless quality—a quality selected by many of the world's most reputable names in loudspeakers, for inclusion in their own speaker systems.

Contact us now, and discover where you can hear Peerless loudspeakers—then let your ears make up your mind.

Danish-built Peerless loudspeakers, Orthodynamic headphones and unique car speakers are imported by the sole Australian agents,

G.R.D. GROUP Pty. Ltd.

698 Burke Road, Camberwell. 3124. Telephone (03) 82 1256. Telex 31712

Please send me descriptive literature and dealer list:

BO1294

Name

Address

Postcode

HIFI TOPICS — continued

the Ferrofluidics Corp. has evolved dispensing equipment for use on assembly lines, which meters the required amount of fluid to both sides of the voice coil former, rapidly and with high repeatability. Depending on the grade of liquid and size of speaker, the cost might range from something under 10c per unit to something over 40c.

Naturally enough, the initial application of magnetic fluids has been to existing designs, mainly of quality mid-range drivers and tweeters, where the cost increment is not likely to be prohibitive. However, as already mentioned, close attention has to be paid to other chemicals or substances which may come in contact with the magnetic fluid and with which it may interact.

In any case, magnetic fluids are not suitable for use in drivers which have voice coils wound on paper or on other even partially absorbent materials. Over a period of time, such material will absorb the fluid, gradually "wicking" it out of the air gap, despite the magnetic attraction. The end result may be only residual fluid in the gap and a voice coil assembly that has grown heavier than it should be!

TYPICAL BENEFITS

Where an existing design is compatible, or can easily be made so, beneficial results may well be achieved. For example, recurring problem exists with tweeters, which commonly exhibit a system resonance in the vicinity of 800-1000Hz. To protect tweeters and to prevent them from "colouring" the sound of a multi-way system, it is more or less essential to use an inconveniently high crossover frequency, or a very high slope filter, or a special trap circuit tuned to the resonance.

Practical tests have demonstrated that the problem can be alleviated significantly by the use of a magnetic fluid in the air gap. The viscous drag, right on the voice coil itself, can provide an essentially resistive damping which can dramatically reduce the Q of the major resonance mode. Fig. 3 shows the response of a 7cm cone tweeter with and without ferromagnetic fluid damping; note that the Q has been dropped from a troublesome 2.8 to unity. The information comes from a paper by John King (Essex Group Inc., Cleveland Ohio) presented to the AES Convention, Los Angeles, in May 1977.

It seems highly likely that some dome tweeters, which exhibit a very high Q system resonance, would stand to benefit even more from magnetic fluid damping.

These curves for a 13cm mid-range driver show how its natural resonance at 140Hz is progressively damped by adding magnetic fluids of higher viscosity. With the 10,000cP mix it is obviously over-damped.

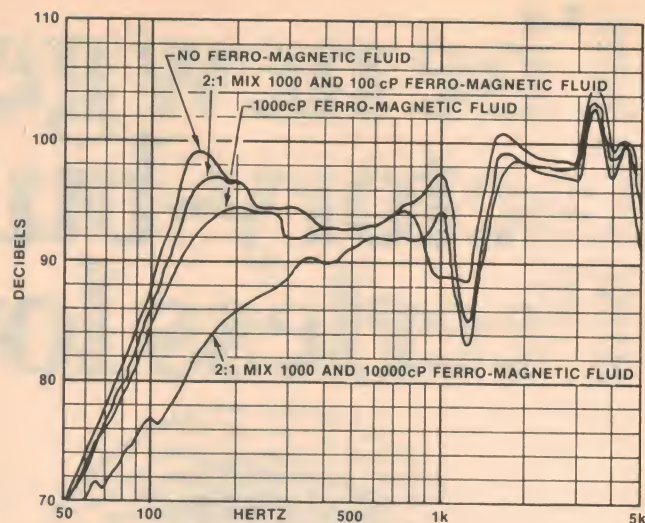


FIG. 4

Sealed mid-range drivers tend to suffer a similar problem in the 150-200Hz region and this is also amenable to magnetic fluid damping. A second set of curves from the same paper (Fig. 4) shows how such a resonance can be controlled by the choice of fluid with a suitable viscosity; this for a 13cm mid-range driver.

Yet another curve for this, or a similar driver, shows that the addition of magnetic fluid reduces the voice coil temperature to about 0.6 of what it would otherwise be. (Fig. 5). This could be seen as offering a wider margin of insurance against possible voice coil burn-out. Alternatively, and in some cases, it might permit an increase in actual power rating.

The use of magnetic fluids with woofers and full-range drivers is less attractive, partly because of the amount of fluid involved, and partly because the system resonance is subject to control by the drive amplifier and by the enclosure design. However, the advantage remains of greater heat conduction from the voice coil and the protection which that offers.

In terms of power sensitivity, the addition of a magnetic fluid to an existing driver has only minor effect, the loss due to extra damping being partly offset by greater (permeability) magnetic conduction across the gap. A loss of 1dB is suggested as typical.

As distinct from "retrofitting" or adapting existing designs, it would

You'd like a nice, new mixer?



This most impressive mixing console is just one of a comprehensive range manufactured by Ward Beck Systems Ltd for use in recording studios, television and radio stations, auditoria, etc. Ward Beck Systems Inc are represented in Australia by Vital Electronics (A'Asia) Pty Ltd. Managing Director is Mr Claude Grech and the postal address is PO Box 72, Blackburn, Vic 3130; telephone (03) 529 1542. Vital Electronics (A'Asia) also represent their parent company, which specialises in video, audio and machine switching systems. As a further activity, they represent Datatron Inc, who are manufacturers of computer based editor systems.

After you experience our equalizer at work, unequalized sound just won't seem like music anymore!

1 **Bad rooms become good rooms**
The listening room is the final link in the audio chain. It determines, as much as any component, the sound that will reach your ears. Most homes are designed for comfort, not for acoustics. An equalizer can let you have it both ways by transforming a comfortable living room into an excellent listening room.

2 **Good speakers become great speakers**
An equalizer can improve speaker balance and ideally blend, according to your taste, the character of your speaker with the character of your room — thus your speaker performance is greatly improved.

3 **Highlight an instrument**
A musical instrument, a band of instruments, or a vocalist can be emphasised on a recording to aid in learning a specific tune or admire and enjoy the playing of a particular instrument.

4 **Optimise system balance**
An equalizer will be able to eliminate any incompatibility between your cartridge/pre amp combination and your speakers by levelling any of the-peaks or dips.


5 **Improve source material (records etc)**
An equalizer can upgrade the sound of your source material by reducing record rumble and surface noise, hushing tape hiss and stiffling radio static.

6 **Improve your recording**
Get professional quality effects by shaping the sound of the program material to achieve the results that you want on tape.

7 **Make you own music**
Listen to the music the way you want to hear it — not the way the recording engineer felt like hearing it when he mixed it down. Bring up the vocals or fade the guitar. It's your choice. An equalizer can make music anyway you want to hear it.

An equalizer is the final component, the catalyst which will tune today's advanced components to each other, to your room and most importantly, tune the music to your ears.

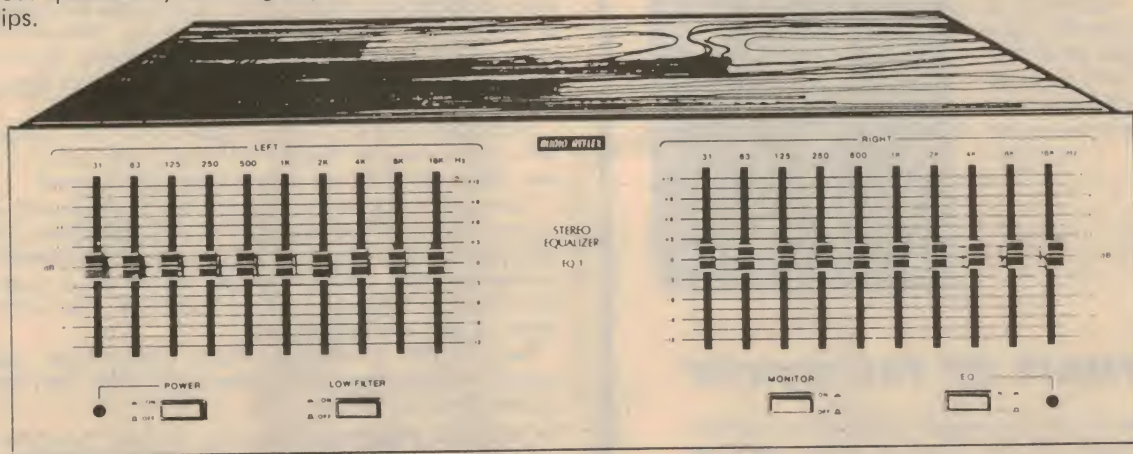3 year parts and labour warranty.
Available in anodized black or brushed aluminium



What the critics say

HI-FI & MUSIC, May 1979 — "The Audio Reflex equalizer has been carefully designed for general use in systems owned by audiophiles who require that 'something extra' in hi-fi systems."

CANADIAN STEREO GUIDE, Winter 1979 — "Separation between the two channels was excellent, being better than — 64dB across the range. THD was also exceptionally low, as was equipment generated noise."

THE FM GUIDE (Canadian) 1979 — "Quality, that was only hinted at with the original material, can be brought out through proper use of this well-designed, modestly priced, and simple-to-operate frequency equalizer."

(Copies of full reviews available upon request.)



AUDIO REFLEX

You'll hear more from us

Australian Distributor: Audio Reflex (AUSTRALIA) PTY. LTD.

● **SYDNEY**

7 Orchard Road, Brookvale 2100
(P.O. Box 208, Brookvale 2100)
Telephone: (02) 938 4188

● **N.S.W.**

NEWCASTLE (049) 69 2733
WOLLONGONG (042) 29 3762

● **INTERSTATE**

MELBOURNE (03) 267-1655 GEELONG (052) 21 6934
BRISBANE (07) 52 4074 ADELAIDE (08) 250 4617 PERTH (09) 321 6865
CANBERRA (062) 82 1388 LAUNCESTON (003) 31 7188

Next Month

Don't miss our article on buying a Cassette Deck ...

Our article gives a rundown on just about every feature you are likely to find on any cassette deck. Which features do you really want? Get hold of the January issue for the answers. And on the same theme, check out the hifi reviews!

FLASH EXPOSURE METER

Take the guesswork out of flash photography with our new Flash Exposure Meter. Based on a silicon solar cell, it measures the light available from the electronic flash so you can compute the right exposure setting.



"PLAYMATE OF THE MONTH"

Little sister to the Playmaster series of fine performance equipment, our Playmate stereo amplifier has a power output of about three watts per channel and mates with a ceramic cartridge — just right for an economy stereo system.


PLUS MUCH MORE

As always, the issue is full of interesting features. So don't miss out. And why not treat yourself to a 12-month subscription while you think about it. See page 144.

Our planning for this issue is well advanced but circumstances may change the final content. However, we will make every attempt to include the articles mentioned above.

HIFI TOPICS — continued

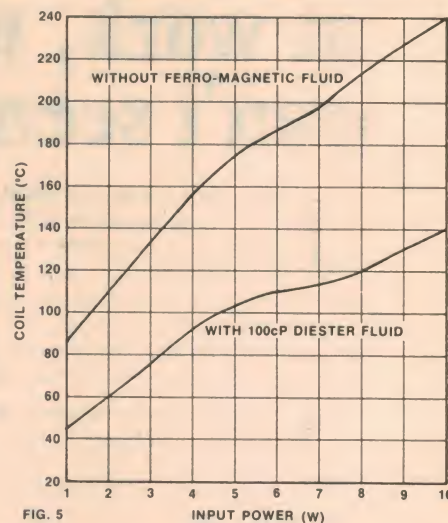Voice coil temperature rise for a typical mid-range driver with and without magnetic fluid in the gap. As indicated earlier, AR take full advantage of this effect in their latest high-power systems.



seem that a whole new design approach is open to loudspeaker manufacturers, particularly in respect to tweeters and mid-range drivers, where high power handling has to be combined with small physical dimensions.

To date, dynamic drivers have relied on the outer suspension and "spider" to maintain the voice coil centred in the magnetic gap. This sets a limit on minimum design clearances, makes heavy demands on assembly techniques and is a potential cause of buzzes and rattles if there is any subsequent sagging.

When magnetic fluid is used, magnetic attraction will ensure that there is a layer of liquid on the pole faces. Since the liquid also happens to have very commendable qualities as a lubricant, the voice coil tends to operate more like a piece of machinery, sliding in a bath of oil. Without the same reliance on purely mechanical suspension, tolerances can be tightened, assembly can be simplified, and failures due to voice-coil problems reduced.

Manufacturers of the fluid claim that the savings on this new generation of drivers will more than offset the cost of the magnetic fluid on which they will depend.

How promptly and how positively loudspeaker manufacturers react to the challenge remains to be seen. Designers will have to adapt to a whole new set of parameters and be convinced that promise in the laboratory is going to be matched by long-term performance in the field under a wide variety of conditions.

But, in the meantime, there seems little doubt that magnetic fluids have the potential to fulfil the claims made in the sales literature.

ACKNOWLEDGEMENT: The writer would like to acknowledge the assistance of Mr Stuart Barton, Chief Engineer of Magnavox (Aust) Pty Ltd, in providing copies of references used in this article. Magnavox are currently investigating the use of magnetic fluids in new, locally produced drivers.

SURROUND SOUND FROM IBA

Although conventional quadraphonic systems are very much a non-event, research continues in Britain as an extension of the original "Ambisonic" concept.

On September 23, the Independent Broadcasting Authority broadcast a two-hour "surround-sound" concert from the Portsmouth FM transmitter, as originally recorded in the Winchester Cathedral.

IBA's latest surround system is a three-channel matrix system which has excellent stereo compatibility and much better definition than the earlier "2½ channel" method.



CONCEPT AUDIO PTY LTD advise that the supply position for the Hafler DH-101 preamplifier should begin to improve from the Christmas period onwards. It was released in Australia during July, but demand has consistently exceeded supply since then. While presenting a rather plain face to the world, the new preamplifier lays claim to a very high order of performance and utility.

Recommended retail price for the DH-101 is \$375 in kit form and \$475 fully assembled. For a further \$135, Hafler provide their DH-102 pre-preamplifier, designed to fit inside the DH-101 and to provide the additional gain necessary to operate directly from the output of a low impedance moving coil cartridge.

A companion unit is the DH-200 power amplifier, rated to deliver a generous 100W per channel (continuous) and with highly commendable characteristics in other respects. It comes in kit form for \$655 and ready built for \$755. For further information on the Hafler range: Concept Audio Pty Ltd, 22 Wattle Rd, Brookvale NSW 2100. Phone (02) 938 3700.

HIFI INDUSTRY ASSOCIATION office bearers for the current year are:
Chairman — Les Black of Pioneer Electronics Aust. Pty Ltd.
Vice Chairman — Peter Lee of National Panasonic (Aust.) Pty Ltd.
Promotions Executive: John Watts of Superscope (Asia) Pty Ltd.
Treasurer — Graham Timmins.

The Hifi Industry Association currently represents about 25 member companies, marketing more than 60 major brands.

PHILIPS have introduced a new family of round-frame 8-inch woofer speakers intended for use in sealed enclosures not exceeding 25 litres, and with impedance values of 4 and 8 ohms. The AD80601/W and AD80602/W have a resonance of 42Hz and typical ratings in a 25 litre enclosure of 50-4000Hz, 50W, and a sensitivity of 96dB at 1m with 5W drive. The AD80651/W and AD80652/W have a resonance of 39Hz and ratings of 50W, 50-5000Hz in a 25 litre enclosure; sensitivity 3.8W. The AD80671/W and AD80672/W are rated at 60W, 40-3000Hz, sensitivity 9W. Power ratings

for all three can be doubled under appropriate conditions. For further details: Bruce Druery, Philips Press Office, 15 Blue St, North Sydney, 1092.

BASF AUSTRALIA PTY LTD say that a linear video recording system (LVR) is in an advanced stage of development with mid-1980 as a likely release date. The system will offer a 3-hour playing time on a small cassette, with good picture quality. A feature of the LVR system is high quality sound, giving it a distinct advantage over currently available video cassette recorders. BASF see the role of their new LVR as not only for recording off-air TV, but for making home movies with quality sound.

TOSHIBA (AUSTRALIA) PTY LTD have built up their line of Micro HiFi components to a total of 10, giving them a claimed leadership in this growing field.

Latest additions include the 30W + 30W "12" series, comprising the SC-M12 stereo power amplifier, the SY-C12



stereo preamplifier, the ST-10 stereo tuner and the PC-D10 "metal position" cassette deck. The "10" series comprises the 20W + 20W integrated stereo amplifier SB-A10, combined with the tuner and cassette deck as above. Toshiba (Australia) Pty Ltd are at 16 Mars Rd, Lane Cove, NSW 2066.

Rapar

PUBLIC ADDRESS AMPLIFIERS YOU CAN DEPEND ON



TPA 50

Specs.

RMS power, 25 watts. Frequency response: 50Hz to 15kHz (+3dB at 8 ohms). Multiple outputs: 4, 8 and 16 ohms. 70 and 100 volt lines. Inputs: Mic. 1, 47k ohms, Mic. 2, 600 ohms. Aux. 300mV, Phono 2.5mV.

Size: 310mm (width), 230mm (depth), 80mm (height). Weight 3.8 kilos. Finish: Durable two-tone baked enamel.

***\$146.97**



MODEL TPA 70

Specs.

RMS power, 50 watts. Frequency response: 50Hz to 15kHz (+3dB at 8 ohms). Multiple outputs: 4, 8, 16 ohms, 70 and 100 volt lines. Inputs: Mic. 1, 47k ohms, Mic. 2, 600 ohms, Aux. 300mV, Phono 2.5mV.

Size: 310mm (width), 230mm (depth), 80mm (height). Weight: 4.3 kilos. Finish: Durable two-tone baked enamel.

\$183.60

**TRADE AND DISTRIBUTOR
ENQUIRIES WELCOME**

MANUFACTURED BY:



RADIO PARTS GROUP

562 SPENCER STREET,
WEST MELBOURNE, VIC. 3003.
TEL. (03) 329-7888.

1103 DANDENONG ROAD,
EAST MALVERN, VIC. 3145.
TEL. (03) 211-8122.

INCREDIBLE HI-FI OFFER

DICK'S FANTASTIC 55 WATT SYSTEM ONLY \$799

Terms available to
approved applicants

For the first time, Dick is offering the superlative performance of his top Hi Fi system, incorporating the superb Dick Smith 55 watts rms per channel stereo amplifier, the 12" Playmaster 3-way speaker system with in-built control for the midrange and tweeter and the Sanyo belt drive turntable with servo control, magnetic cartridge, base and cover - at a price that will astound you **PLUS** a matching stereo AM/FM tuner (worth \$239) absolutely **FREE!**

BUT THAT'S NOT ALL!
THIS TUNER WORTH \$239
ABSOLUTELY (When you buy the system)


FREE



Post & Packing
\$5.50 anywhere
in Australia

DELUXE AM/FM TUNER

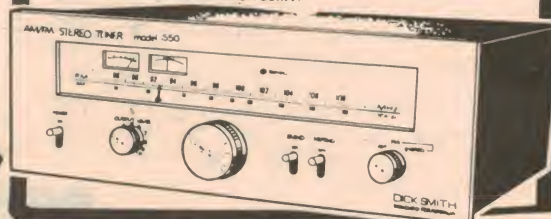SPECIFICATIONS: 1 FET, 1 stage RF amplifier, 3-gang variable capacitor, 5 stage limiter, PLL MPX ★ Frequency range 88-108MHz ★ Sensitivity IHF 1.9uV ★ S/N ratio 70dB (mono) ★ Total harmonic distortion 0.2% (mono) @ 1kHz, 0.3% (stereo) @ 1kHz ★ Frequency response 30Hz to 15kHz ★ Separation 40dB @ 1kHz. The AM section has a frequency range of 525-1605kHz. Audio variable from 0-750mV.



DIRECT IMPORT CUTS OUT THE MIDDLEMAN - YOU GAIN!

SAME FANTASTIC DEAL ON 30 WATT SYSTEM

And yet another fantastic bargain! The Dick Smith 30 watts rms per channel amplifier matched to the Playmaster 10" 3-way speaker system and Sanyo servo belt drive turntable. Looks good, sounds fantastic and with your purchase you receive the matching AM/FM stereo tuner absolutely **FREE!**

**FANTASTIC
VALUE**

\$683

Terms available
to approved
applicants

Post & Packing
\$5.50 anywhere
in Australia

Prices correct and products in stock at press time



PLUS FREE TUNER WORTH \$189

(When you buy the system)

SPECIFICATIONS FM tuner section Frequency range 88-108MHz ★ IHF sensitivity 1.8uV ★ Selectivity 60dB ★ Stereo separation 40dB @ 1kHz ★ Frequency response 30-15,000Hz AM section Frequency range 530-1605kHz ★ Sensitivity 48dB ★ Selectivity 35dB @ 1kHz ★ Semiconductors 1 FET, 3 ICs, 5 transistors, 3 diodes and 1 LED Dimensions (same as amplifier) 400(w)x135(h)x290(d)mm

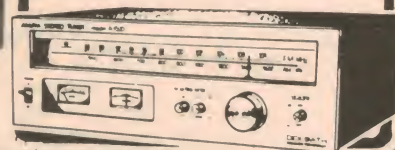


Illustration shows incorrect turntable - this system incorporates the Sanyo as shown in the 55 watt system illustration.


DICK SMITH ELECTRONICS

SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RESELLERS



Audio Reflex EQ-1 10-band Graphic Equaliser

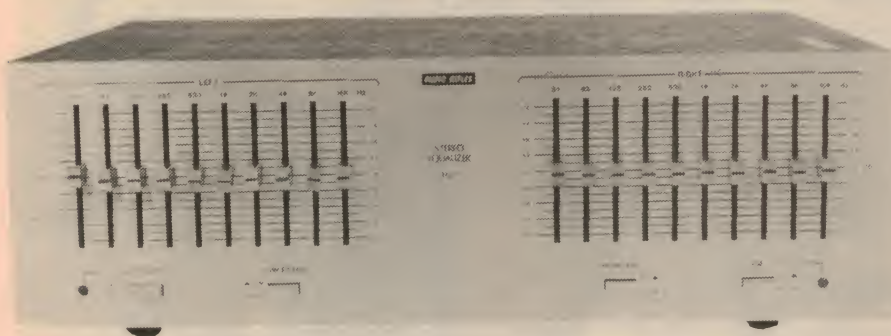These days it is recognised that ordinary tone controls are inadequate to compensate for room and loudspeaker deficiencies. Graphic equalisers are far more suited to the purpose. One such device is the Audio Reflex EQ-1 Graphic Equaliser which has 10 bands and 20 separate controls.



The Audio Reflex EQ-1 splits the audio spectrum into ten bands with centre frequencies of 31Hz, 63Hz, 125Hz, 250Hz, 500Hz, 1kHz, 2kHz, 4kHz, 8kHz and 16kHz which are the usual frequencies for 10-band equalisers. Each band is controlled, boosted or cut, by a separate slider in each channel, making 20 in all.

Each slider control has a quoted range of +12dB at the centre-frequency and has a centre detent to enable a flat response to be obtained.


Normally, a graphic equaliser such as this is connected to the "tape monitor" terminals of a stereo amplifier. If the system includes a cassette deck, this is then connected to the duplicate "tape monitor" terminals on the equaliser. The equaliser has unity gain (nominally) so that it can be switched into or out of the system with no change in overall gain, provided controls are centred.

Dimension of the Audio Reflex EQ-1 are 420 x 138 x 300mm (W x H x D). These large dimensions are necessary mainly because of the large array of slider controls.

Styling and presentation of the EQ-1 leave little to be desired. Our sample has some of the slider knobs crooked and some of the sliders were a little rough in action. We could excuse this as it is probable that our sample was a much-used one.

Inside the large chassis is a lot of unused space with most of the circuitry accommodated on two printed circuit

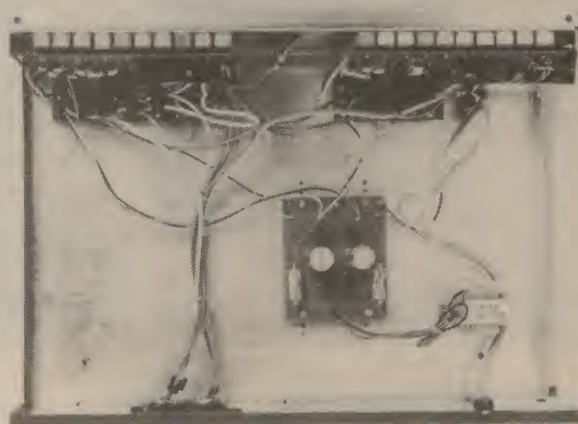As with all graphic equalisers using op amp gyrator circuitry, the inside is virtually empty.



boards which also mount each group of ten sliders. The overall circuit is quite conventional using operational amplifier ICs in gyrator configuration. The "gyrator" is an op amp circuit which effectively transforms a capacitor into an inductor which can then be used in a series-tuned feedback circuit to provide each band.

As such, the gyrator circuit is well proven and has become the standard configuration in graphic equalisers. What is not realised by high fidelity enthusiasts, is that the resulting circuit is inexpensive to produce — much less costly than cassette decks, for example. That is not borne out in the price even

though this particular unit, the EQ-1 is something of a bargain, relatively speaking.

On test, the Audio Reflex EQ-1 performed well. All specifications were met or exceeded: Signal-to-noise ratio with respect to 1V RMS was 93dB unweighted. With the same reference level, separation between channels was 84dB at 100Hz, 76dB at 1kHz and 58dB at 10kHz, measured with 4.7k loading the undriven input. Again, with respect to the same reference, harmonic distortion was .015% at 100Hz and 10kHz and .02% at 1kHz.


When the controls are set at 0dB, the gain of the equaliser is -0.5dB. An 8 volt output signal can be obtained before more than 0.05% distortion is produced. This overload voltage is far in excess of what would be delivered to the equaliser from the amplifier tape out-

put.

Listening tests revealed no performance problems. For the most part, the EQ-1 is virtually noiseless — switching the equaliser in and out of circuit produced no audible increase in noise.

Our summary can be short: The Audio Reflex EQ-1 works as claimed.

Recommended retail price of the Audio Reflex EQ1 is \$299 including sales tax. Warranty is three years on parts and labour. Further information can be obtained from retailers or from the Australian distributors, A.G.S. Electronics (Australia) Pty Ltd, 7 Orchard Road, Brookvale, NSW 2100. (L.D.S. & J.C.)



Hearing is believing with **KOSS**®

Koss have succeeded in creating a new sensation in the private world of stereophone entertainment. A new era in listening begins with KOSS "PRO 4 TRIPLE A" and "Auditor" Series of Headphones. The supreme feeling of weightlessness and the comfort of contoured earcushions which completely exclude outside noises is only surpassed by the magnificent sound. Whether you enjoy hard rock... Bach... Country Western or easy listening, when the deep, rich lows and crisp highs come through you'll have to agree... with Koss... hearing is believing.

**New Pro/4 Triple A
Stereophones by Koss**



ESP/10 Electrostatic headphones with energiser.

NEW KOSS 'AUDITOR' SERIES

Dynamic/10 has exclusive pneumatic ear cushions.



If your Hi-Fi dealer is out of stock contact the distributors.

AUDIO ENGINEERS P/L

342 Kent Street
SYDNEY 2000 N S W

AUDIO ENGINEERS (Vic.)

2A Hill Street.
THORNBURY 3071 Vic

AUDIO ENGINEERS (Qld.)

51A Castlemaine Street.
MILTON 4064 Qld

ATHOL M. HILL P/L

33 Wittenoom Street.
EAST PERTH 6000 W A

Peerless Loudspeaker System

Of all the loudspeaker systems sold today, probably the most popular is a three-way system with a volume of about 50 litres. Right in the middle of that market sits the Peerless PAS50 system which is a sealed enclosure with three drivers. Frequency response is quoted as 30Hz to 20kHz (DIN) and power handling is 100 watts on program signals.

It is not surprising that systems with a volume of around the 50 litre mark are so popular. They are of reasonable size and efficiency and have a good bass response and power handling. This is no accident, as all these parameters naturally come together in this size of enclosure to provide what is possibly the best all-round compromise, for the designer as well as the buyer.

The woofer in this Peerless PAS50 system is a rugged looking unit with an effective diameter of about 170mm and a large foam roll surround. The midrange also has a roll surround and an effective cone diameter of about 75mm. The tweeter is a 25mm dome unit. All three drivers are made by Peerless, of Denmark.


The enclosure is intended to be floor-standing, but it could be mounted on a deep shelf. Overall dimensions are 360 x 660 x 290mm (W x H x D), the cabinet being made of chip-board with a synthetic veneer on four sides. The grille frame is removeable to reveal the three drivers. The enclosure is well-sealed — considerable care has been seen to that. There was no way we could inspect the inside of the enclosure to look at the crossover details or driver construction.

However, according to literature supplied by the distributors, the crossover networks use "air-cored chokes for maximum power handling and minimum distortion and special electrolytic crossover capacitors for long term reliability." Crossover frequency from woofer to midrange is at 400Hz while the crossover to the tweeter is at 5kHz.

On the rear panel there is a recess for a pair of spring-loaded terminals which are colour-coded for polarity (red for positive). However, apart from the Peerless logo on the grille cloth frame, there is no labelling of any kind on the loudspeaker. We think that some labelling, giving the brand, type number, specifications (particularly impedance and power handling) plus name and address of the distributor should be somewhere on the enclosure, back or front, so the information won't be lost. After all, it is nor-

mal for delivery dockets and warranty cards to be misplaced after a few years. (Other loudspeaker manufacturers, please note).

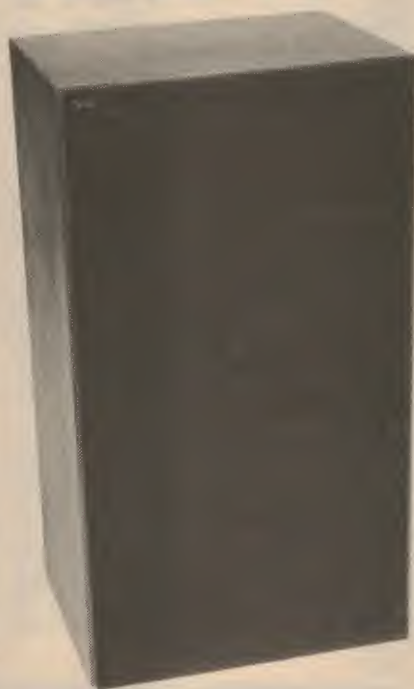The impedance curve is quite smooth and does not present any potential problems of incompatibility with solid state amplifiers. The lowest impedance value occurs at 100Hz, at just over nine ohms. Apart from this, there are virtually no dips at all in the whole curve. The main system resonance is close to 50Hz and is well damped.



smooth, a statement which cannot be made about many three-way systems. And in the treble end, there are certainly no complaints.

On all types of music, we found the Peerless PAS50 eminently satisfactory. It has reasonable efficiency and can be driven to satisfactory room levels with an amplifier rated as low as 25 watts per channel. Or on the hand, it can handle the full output (on program) of a 100 watt per channel amplifier. Bass boosting is unnecessary but modest boost can be handled.

If these units are to be floorstanding, it is probable that they would benefit from the addition of a stand to raise them about 200 to 250mm above floor level.

Most of this review then, is complimentary. The Peerless PAS50s do



The Peerless PAS50 is an infinite baffle system with three drivers.

Peerless quote the frequency response of the PAS50 as 30Hz to 20kHz under the DIN specification. A supplied (typical) third-octave pink noise response indicates that the response is flat from 40Hz to 20kHz within +6dB. Our tests would appear to confirm this latter claim. The bass is very well maintained down to below 40Hz and is fairly smooth over the entire frequency range.

The midrange seems particularly

perform well and should satisfy the needs of most listeners. There is a catch though. At \$574 per pair, these Peerless systems are not cheap. Even so, we concede that buyers will be satisfied with their purchase.

Further information can be obtained from the Australian distributors for Peerless loudspeakers, G.R.D. Group Pty Ltd, 698 Burke Road, Camberwell, Victoria, 3124 or from the showroom at Danish Hifi, of the same address. (L.D.S.)

Matsushita does it again . . .

The World's smallest full-sized phono player!

So you'd like a turntable that doesn't dwarf the rest of your hifi gear? That you can store in your record cabinet when not in use? A compact turntable that employs state-of-the-art technology? Well, be patient. You should be able to buy one within a few months!

by NEVILLE WILLIAMS

The turntable in question is the new "Quartz, Linear Tracking Direct Drive" Technics model SL-10. At the time of writing, there are no samples in Australia, or perhaps in any country outside Japan. But press release kits have been supplied to technical magazines around the world and, on Matsushita's usual form, it won't be too long before production units will be available for evaluation.

The SL-10 will mate naturally with the new generation of compact hifi amplifiers, tuners, etc, which Japanese manufacturers have released during the past year or so. While this may have been a motivating thought, it seems likely that the SL-10 is also a by-product of fresh thinking generated by consideration of computer disc systems, video disc players and digital audio systems. All of these have broken right away from the traditional phono playing deck.

But while, as a package, the SL-10 is new, even revolutionary, many of the ideas which it brings together have been around for a long time, in one form or another.

FOLD-UP, STOW AWAY: This idea is

about as old as the pre-electric phonograph but the SL-10 wins hands-down in the matter of size. In plan view it occupies about the same area as a record sleeve and should stand upright in most ordinary record shelves.

ULTRA-COMPACT: Small turntables and scaled-down pickups have been featured in portable record players for decades but the clearance dimensions, when playing a 30cm (12in) record are likely to be greater than for the SL-10, full-size turntable and all.

DC OPERATION: Electronically controlled DC motors for disc and tape decks are no longer news as such but the SL-10 provides deliberate access to the circuitry so that it can operate directly from a 12V car battery!

DYNAMIC PICKUP BALANCE: Fifteen years ago, we were using an All-Balance arm which could be set up to play a record in any attitude, even upside-down. The SL-10 features complete dynamic balance. It can play a record quite happily while still standing on end in the record

cabinet!

LINEAR TRACKING: Quite a few players have dispensed with radial arms, with their inherent tracking error, in favour of a linear tracking system: Beogram, Harman Kardon, Revox, Technics, etc. The SL-10 follows suit, but with special claims about the accuracy and smoothness of the microprocessor-controlled linear transmission. The system eliminates tracking error and the need for anti-skating force correction.

AUTOMATIC OPERATION: Old hat, featured on all prestige turntables! The SL-10 has it, too but carried a logical step further in being interlocked with an acoustically sealed lid.

So the list goes on: a quartz-locked, direct-drive motor; optical sensing for the presence of a record, its size, and the position of start and finish tracks; automatic speed setting; moving coil cartridge; in-built moving coil preamplifier; pressure device to hold the disc firmly on the turntable, etc.

As I said earlier, the story of the SL-10 is not so much the novelty of the in-



The new Technics SL-10 phono deck (left) ranged alongside other units in the Technics "Bonsai" range. In the centre is the AM/FM tuner, resting on the cassette deck. On the right is the power amp (top), control unit (middle) and power

supply. There is no reason, of course, why the SL-10 should not be used with an existing system, where space is at a premium.

dividual features, but in the fact that they are all brought together in the one unit — a unit which is about as small as it's ever likely to be, while still being able to get the best out of a present-day 30cm analog recording.

Whether by accident or intent, the SL-10 has been announced just 10 years after Matsushita/Technics released the World's first direct-drive turntable, the SP-10. According to the manufacturers, the SP-10 exhibited less wow and flutter and a more constant speed than cutting lathe motors of the era. It was followed, six years later, by the SP-10MKII and by the high-torque quartz-locked SP-02, designed to fit Neumann cutting lathes. In the meantime, direct drive turntables have become almost a way of life for quality-conscious audiophiles, with most manufacturers featuring them in their range.

The new Technics SL-10 is no longer presented as a playing deck with a lift-up perspex dust cover. It comes as a complete die-cast cabinet which opens into two halves. The lower half, as expected, contains an integral platter/DD motor, together with its quartz phase-locked control circuitry. The upper half contains the linear tracking tonearm, its drive control system and a dedicated microcomputer which monitors and controls the arm travel.

Also built into the lid is a record stabiliser which holds the disc firmly against the centre of the turntable, instead of relying on gravity. The stabiliser turns with the disc and carries a stroboscope, which is visible through a dark perspex window in the lid.

To use the SL-10, one places a record on the turntable and closes the lid, sealing the record into a chamber which is acoustically much more isolated than normal from the listening environment. Internal damping provides a further barrier against outside vibration.

On pressing the play button, an optoelectronic sensor checks for the presence of a record and then checks its size. If it is a standard 30cm (12in) album, the sensor sets the speed at 33rpm, unless a manual over-ride is operated. Similarly, 18cm (7in) records are played normally at 45rpm.

The optoelectronic sensor also identifies the start groove and later the finish groove, lowering and raising the playing head without imposing any mechanical loading on the groove or stylus. If, for any reason, the lid is lifted during play, the mechanism automatically returns the pickup to its rest position and switches off, allowing the record to be removed, without any other intervention.

While normal operation of the player is about as simple as it can possibly be, additional facilities are available for those who may need them.

Buttons with left-pointing and right-pointing arrows allow the arm to be shuffled in either direction above the surface of the disc, a calibrated scale on top of the cabinet indicating just where



The SL-10 phono player compared with an ordinary record sleeve. Details are rather obscure but the record stabiliser, arm and tracking system are in the lid.

it is. The arm can be moved slowly or rapidly, depending on how hard the buttons are pushed, but it will not travel beyond the playing groove area.

On pressing a cue button, the arm lowers and begins playing at that point.

In this turntable, the user never touches the playing arm. All cueing is done by means of the external buttons, thus minimising the risk of mishandling, and of physical damage to cartridge or groove. An electronic muting circuit silences the system at the moment of lift-off and until the stylus is properly seated in the groove, thereby eliminating all cueing noise.


Facilities are available to provide automatic repeat playing of a disc, or to repeat that part of the disc which has

already been played.

The SL-10 is supplied complete with a new slide-in moving coil cartridge, developed from the Technics MC305. It features a core-less, twin-ring coil structure and a pure boron pipe cantilever to produce what the makers as "an extremely linear, flat frequency response and superb tracing ability".

The built-in MC preamplifier allows the SL-10 to be used with conventional magnetic input systems, but the preamplifier can be bypassed, if desired, to access directly the output from the cartridge.

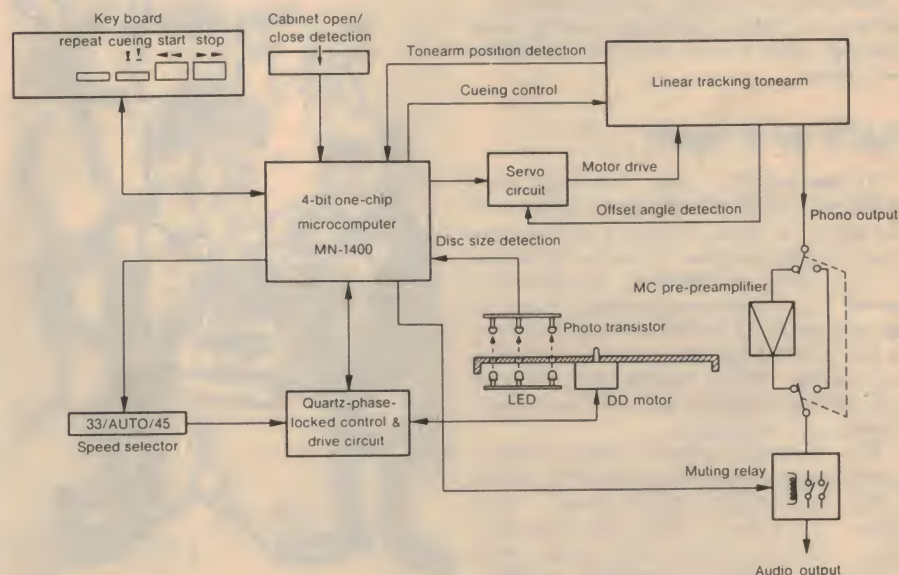When available, the Technics SL-10 turntable will be distributed through National Panasonic (Australia) Pty Ltd, 57 Anzac Parade, Kensington 2033.



The internal circuitry and "brains" of the SL-10. Note the LED system which checks for the presence and size of a record to set speed and enable the play system.



AUDIO TALK

by NEVILLE WILLIAMS

Which kind of disc is the best?

Fact is — there isn't any best!

Until such time that digitally encoded domestic discs take over (assuming they will some day) audiophiles are faced with three distinct technologies competing for their dollar:

- Discs transcribed from top quality analog tape equipment;
- Discs transcribed from digitally encoded tape masters;
- Direct cut discs, where the signal has been derived directly from the console, with no intermediate recording.

Which is the best?

In fact, there is no simple answer to the question. One can only respond with the time honoured phrase: it all depends ...

If there were no other considerations, one might have to come down in favour of direct cut, because it minimises the number of processes through which the signal must pass, en route to the consumer. That should be a big plus.

But there are other considerations — dozens of them. We'll be modest and mention just a few, in order to make our point.

"Let's do it again ..."

Undoubtedly, the number one problem of the direct cut technique is the strain it puts on artists and recording engineers alike. There is no scope for patching or editing. Everyone is aware that imperfections either have to be tolerated, or else the whole side has to be recorded again. It can be tedious, frustrating, even maddening. Worse still, whole projects have to be abandoned, on occasions.

The tensions don't always show, some artists and groups seeming to be quite uninhibited. Real Time's "For Duke" is a case in point. But there are other albums where one senses that everyone is being frightfully careful, lest they mess it up — again!

After a few minutes of that, the

"direct to disc" endorsement on the jacket loses its trendy charm, particularly if it has cost the best part of \$20!

Tape mastering obviates much of this tension, with modern digital encoding way ahead of the older analog method on the basis of performance figures. There is virtually no wow or flutter, negligible frequency error, negligible distortion, a very wide dynamic range, and no degradation from editing, dubbing or storage. The risk of degrading the signal would seem to be very small indeed.

No less important, having the recording on master tape allows the levels to be observed to the last decibel, for the best possible "fit" to the dynamics of the lathe and the disc. Cutting can be done at half-speed and the groove spacing computer-controlled to pack the grooves towards the outside of the disc, while still giving the clearance needed for crescendo passages.



"Cheer up Claude, we're on overtime!"

"Telarc", for example, seem to exploit this advantage to the full. Looking at the clearance they leave around heavily modulated grooves, you wonder how they're going to fit all the rest in, without scribing grooves in the label!

An engineer, recording a signal direct off line, has none of this flexibility and none of this assurance. He needs a lot of skill, and "a little bit 'o luck", for everything to come out spot-on.

Well then, are digitally mastered discs the best?

No, scream the direct-cut enthusiasts. Those with sufficiently keen ears can sense a certain subtle this, that and the other, which betrays the fact that the analog signal has been chopped up into bits and then put back together again. Digital discs are good but they're not like the real thing!

It's difficult to assess such highly subjective statements, particularly if some of the people with super-sensitive ears also happen to have a vested interest in direct cut! All I can say is that, along with a lot of other audiophiles, I remain blissfully unaware of any such intrinsic limitation, either in digitally sourced analog discs, or complete digital systems.

"It ain't necessarily so"

Personally, I find it difficult to escape the conclusion that digital mastering offers the most practical and satisfying way to produce an analog disc. Certainly, some superb records have been made in this way, but there have been some very ordinary ones too — I suspect for a variety of very ordinary reasons. Once again, the "Digital" endorsement is not much comfort, if you don't like what you finally hear.

But while there is a lot of competitive emphasis on direct and digitally sourced discs, it is noticeable that many conventional analog system recordings still earn enthusiastic reviews, overseas and locally.

How is this possible with an often-insulted, "out-dated" system? Easy!

The fact is that a top quality analog master tape can also be most impressive, with negligible wow and flutter, good frequency response, low distortion, low noise and good dynamic range. If it is transcribed directly and carefully to a disc, its desirable qualities are substantially preserved and you get a top-flight disc as a result. Indeed, many labels seen during the past few years have been based on this "tender loving care" approach.

An inherent problem with analog tape mastering is that the latitude for error is relatively small. Too much signal on peaks can overload the tape; too low a recording level overall allows the softer passages to sink into the noise region. The problem can be alleviated by a variety of signal processing techniques but these tend to be anathema to the purist consumer.

A great deal depends, of course, on the nature of the material to be recorded. If the dynamic range is characteristically small, fitting the signal to the dynamics of analog master is no great hassle. In these circumstances, the advantage offered by direct or digital technology may be subjectively quite small.

Time and again, in reviewing ordinary catalog releases, I've commented favourably on the quality but added a remark to the effect: "it's not surprising, considering the tightly controlled dynamics of the original performance". It's when one strikes a disc with very clean sound AND wide dynamics that the proverbial hat can be removed in deference to those responsible!

However, to argue only about the recording system is to omit other factors no less significant to the end result. Consider, for example, the recording venue and the microphone techniques used to intercept the sound.

The classic "purist" approach is to use a single stereo microphone to gather the total sound with, preferably, as little interference as possible with the signal en route to the recorder. At best, it can yield an authentic, spacious sound; at worst, solo voices and instruments can almost be lost in the remoteness and ambience, unaided by the visual clues that someone present at the actual performance would have. A record like this can be utterly frustrating, irrespective of supportive argument in the jacket notes.

"I got plenty o' nuttin"


At the other extreme are those engineers who are not happy unless they are working with 20 or 30 microphones and as many channels in a massive mixer. The result can vary all the way from startling intimacy of sound to an acoustic mess!

All these qualities can — and do — appear irrespective of the recording method, and they'll undoubtedly continue to do so as we move into the era of the digital disc. We'll simply be able to hear the rights and wrongs of the performance, the venue and the miking more clearly than ever!

Just to complicate things further, the established record makers, at the moment, have a substantial monopoly on the most experienced artists and the appropriate venues, together with an army of highly experienced technical personnel. Those, who have thus far pioneered the direct cut and the digital market, have had to do so on a shoestring budget — and it sometimes shows.

What it all adds up to is that the "best" records for any given listener are those which afford him/her the greatest listening pleasure. If that, for you, rests only on the way in which the signal has been transcribed, one thing is certain: you're hung up on technology!

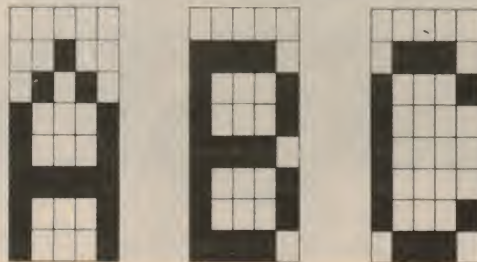IF YOU WANT TO UNDERSTAND MORE ABOUT MICROPROCESSORS



APPLY HERE...

One of the fastest growing sections of the electronics industry is microprocessing and its associated technology. A sound basic knowledge and a constant up-dating of that knowledge is necessary to stay informed of the developments within this exciting new technology.

Stott's Technical Correspondence College has produced an up-to-the-minute home study course specifically designed for people interested in this subject.

This Stott's home study course has been meticulously prepared by experts in this field and takes you through the stages necessary to reach a basic understanding of micro-computers and the processing techniques needed for their application, whether for consumer or industrial use. To this basic training you can add further knowledge and gain more experience.

The course is prepared in three stages. It begins with initial training in basic electronics, goes on to digital electronics and then proceeds to an in-depth study of microprocessors.

For further information on Stott's Microprocessors Course or other courses which interest you, mail the coupon below.

Stotts



TECHNICAL CORRESPONDENCE COLLEGE

The name to trust in correspondence education.

Melbourne, 159 Flinders Lane, 3000. Tel: 63 6212
Sydney, 383 George Street, 2000. Tel: 29 2445
Brisbane, 290 Adelaide Street, 4000. Tel: 31 1627
Kent Town, 66 King William Street, S.A. 5067. Tel: 42 5798
Perth, 140 St. Georges Terrace, 6000. Tel: 322 5481
Hobart, 1st Fl. 29 Argyle Street, 7000. Tel: 34 2399
Singapore, P.O. Box 3396, Singapore 1.

Please send me free and without obligation full details of the following courses:

(PLEASE PRINT) _____

MR MRS MISS _____

AGE _____

ADDRESS _____


POSTCODE _____

Stott's undertake that no sales counsellor will visit you

The Stott's range of courses in Electronics are:

Radio for Amateurs
 Introduction to Electronics
 Digital Electronics
 AM Radio Receivers
 Radio/TV Servicing
 Colour Television
 Amateur Radio Operators' Certificate
 A full range of Hobby and Business courses also available.

ALA/ST//70/EA1279

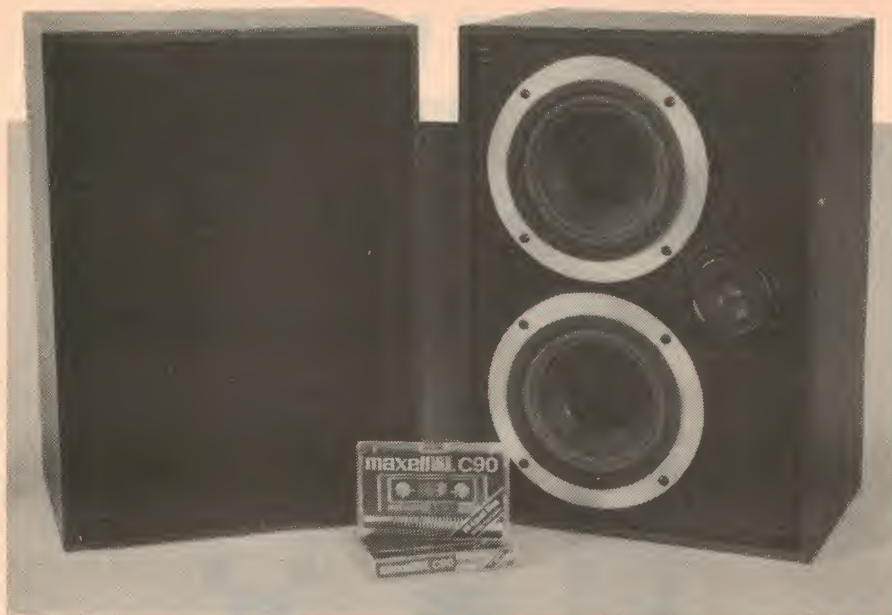

The prototype Playmaster 3-13L enclosures, with and without grille and compared in size to a compact cassette. At the top is the woofer-thru mid-range driver and, below it, the passive radiator. To the right is the tweeter, crossing over at 1500Hz: three cones and a cubic content of just over 13 litres. Dimensional and constructional details are shown on the facing page.

by NEVILLE WILLIAMS

A BIG SOUND FROM TWO SMALL ENCLOSURES

So you are pushed for space, with no room to stand large loudspeaker enclosures? But you still want big sound, be it for jazz, orchestral or classical organ? Then read on: this brand new build-it-yourself Playmaster loudspeaker system may be the solution to your problem — without costing you a fortune! We've called it the Playmaster 3-13L.

What immediately impresses about the new system is its modest overall size: in round terms 390mm x 270mm x 195mm or 15 x 11 x 7½ inches. As such, a pair of 3-13Ls can rest easily on a mantel shelf or book shelf, or be attached directly to a wall or partition.

But, despite their modest dimensions — and their modest weight — the new 3-13Ls can produce agreeably big sound, with rumbling bass and crisp transients. During some of our listening tests, we had them standing on top of a couple of full-size enclosures and it was hard to believe that the small systems alone were making all the noise!

How were they being driven? We'll get around to that a little later.

The new Playmaster 3-13Ls are the outcome of an approach made to us, a few weeks back, by the Australian manufacturers of ETONE loudspeakers. In recent years, the company has built up quite a connection in the field of public address and music loudspeakers, as well as supplying local drivers for big-name imported music systems.

However, they have been keen to diversify into the Australian do-it-yourself hifi market.

This is understandable, considering the huge numbers of systems which are assembled by local hobbyists every year. Topping the list easily is the still-current Playmaster 3-75L, followed by its smaller counterparts, the 3-53L and the 3-26L — the figure in each case indicating the approximate internal volume of the enclosure in litres.

These still-current systems are based on imported drivers and cross-over networks, all so solidly entrenched and so economically priced that it seemed pointless to encourage a local manufacturer to mount a head-on challenge. Well then, was there some other approach that would be worth looking at?

Yes there was: a system that would meet the needs of music lovers who want big, full-range sound from even smaller enclosures. Such systems are available from specialist hifi dealers — at a price — but they are not represented, to any extent, on the do-

it-yourself market. Perhaps it's not surprising.


The fact is that there is far more to producing a full-range compact system than merely scaling down a successful large one. The usual result of such an approach is an equivalent scaling down in performance, particularly at the bass end, with a severe reduction in bandwidth and power handling, and a sharp increase in distortion at anything but a very modest level. It can be very disappointing indeed.

If one is to obtain good bass response and a good power handling capability from a compact enclosure, it is essential to treat it as a distinct exercise — and one logically based on work on vented systems done right here in Australia by Thiele and Small. Cutting across decades of guesswork and folklore, the two aforesaid engineers have set down firm relationships between bass driver parameters, enclosure volume, system efficiency and bass roll-off. Results using their methods are predictable and reliable.

Amongst other things, they pointed up the weakness of starting with an off-the-shelf driver and then hopelessly trying to devise an enclosure to suit it. Failure to understand the attendant problems, in past years, has largely been responsible for vented systems being dubbed "boom boxes".

They needn't be and shouldn't be!

The proper approach is to make an

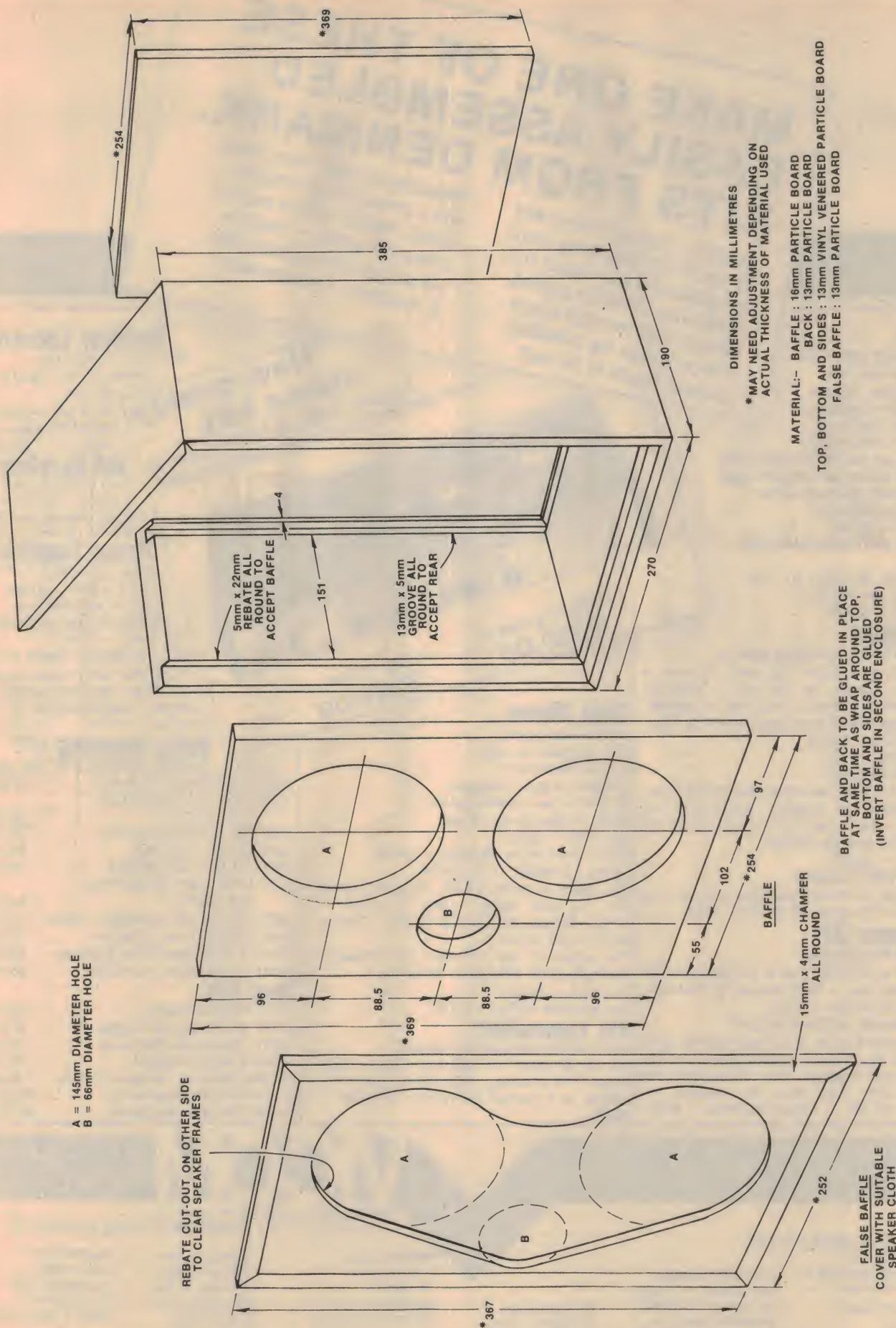

PLAYMASTER 3-13L LOUDSPEAKER SYSTEM

MAKE ONE OF THESE EASILY ASSEMBLED KITS FROM DENMARK.

JostyKits... Denmark's finest, offer the kind of innovative design inside and outside that you'd expect from Scandinavia. Created by qualified electronic engineers, they feature solid-state space age technology advanced enough for the most

demanding kit builder. Each comes with a comprehensive instruction booklet. Whether you're a novice or experienced builder — JostyKits will give you hours of satisfaction in construction and performance!

Audio

AF300 AUDIO AMPLIFIER

A real work-horse, this universal power amp has a wide range of applications such as car radio, record players and small receivers. Due to its well designed electronic circuit, the AF300 can be used over wide voltage ranges without deterioration of the specification parameters.

Kit AF300 — \$25.00

AF340 40 WATT AUDIO AMPLIFIER MODULE

High quality 20-20,000 Hz, 37w RMS with low distortion.

Kit AG340 — \$35.00

FM Tuners

HF325-2 QUALITY FM TUNER MODULE

The HF325 is a complete high quality FM tuner of professional standing. The tuner unit is ready-made and pretrimmed, making it child's play to assemble. Tuning range 88-108 MHz, operating voltage 12-55 ac. Kit HF325 — \$79.00

Stereo decoder HF 310

HF310 FM RECEIVER

The HF310 is a very reasonable priced HF FM tuner. Fully trimmed, the sensitivity according to IHF standards is better than 10uV. Features 60 dB S/N ratio and low harmonic distortion.

Kit HF310 — \$49.00

HF330 STEREO DECODER

Gives 40-45 dB channel separation, just add to a good quality FM receiver. Kit HF330 — \$24.00

Pre-amps (RF)


HF395 RF PREAMPLIFIER

Gain 30dB to 20 MHz, 10 dB to 100 MHz and 5 dB to 226 MHz. Ideal to boost reception on short-wave receivers. Kit HF 395 — \$6.00

HF385 VHF/UHF ANTENNA PREAMP

Superb quality with two aerial inputs and one down lead which simultaneously supplies current from the power supply. Frequency range 40-250 MHz and 400-820 MHz. Gain 9-18 dB, depending on frequency. Kit 385 — \$30.00. Box B850 — \$6.00.

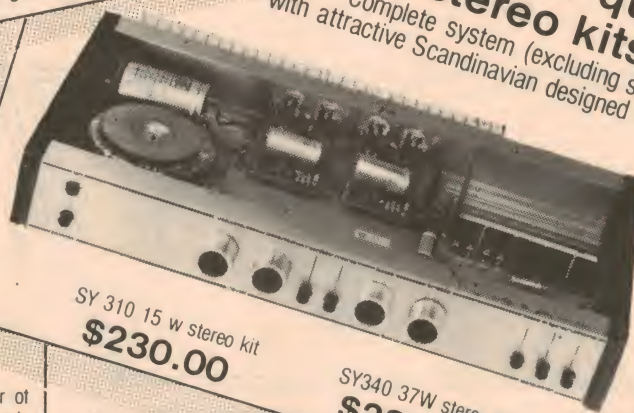New quality stereo kits Complete system (excluding speakers) with attractive Scandinavian designed cabinet



Light Shows

AT465 LIGHT SHOW

Turn your music into light. Simply connect this 3 channel light show to the audio terminals of your amplifier and this quality kit does the rest for you!

Kit AT465 — \$64.00

Attractive box and knobs B6065 — \$25.00

AT468 4 CHANNEL LIGHT SHOW

This superb kit drives 4 lights (400w per channel) from the audio amplifier output. Kit AT468 — \$75.00. Attractive box and knobs B3265 — \$48.00

AT365 LIGHT SHOW

This quality kit uses microphone input instead of connection to the audio output. 1599w max.

Kit AT365 — \$69.00

Box and knobs B3265 — \$48.00

FM Transmitter

HF65 FM TRANSMITTER 60-148 MHz

Will run 5w output with heat sink. Ideal for signal testing of for a miniature transmitter which could be received on a standard FM receiver. Kit HF65 — \$9.00.

Receiver Converter

HF305 VHF CONVERTER

Converts FM 105-148 MHz to 105 MHz.

Kit HF305 — \$28.00

Box B3405 attractive chassis kit — \$24.00

AM Receiver

HF61 MEDIUM WAVE RECEIVER 540-1600 KHz receiver complete with ferrite coil antenna. Kit HF61 — \$9.00

Power Supplies

NT415 LAB POWER SUPPLY

0-30V 1 amp well-regulated supply for professional use. Complete with box and transformer. Kit NT415 — \$128.00

NT300 LABORATORY POWER SUPPLY

2-30V High quality supply, regulated 2-30V dc at 2 amps with overload protection. Complete with box and transformer. Kit NT300 — \$110.00

Quick assembly kits

JK01	GENERAL PURPOSE AMP 0.5w	\$18.00
JK02	MICROPHONE AMPLIFIER	\$18.00
JK03	SINE WAVE GENERATOR 20-20,000 Hz.	\$30.00
JK04	FM TUNER 88-108 MHz	\$30.00
JK05	27 MHz RECEIVER	\$33.00
JK06	27 MHz TRANSMITTER	\$29.00
JK07	DUAL TONE DECODER FOR R/C MODELS	\$43.00
JK08	330Vac LIGHT OPERATED RELAY	\$19.00
JK09	SIREN KIT inc. SPEAKER	\$19.00
JK10	PHOTOGRAPHIC TIMER 240 Vac	\$23.00
JK101	CAR BURGLAR ALARM KIT	\$55.00

New Kits

AT347	Electronic Roulette	\$54.00
AT350	2 amp triac light controller	\$12.00
AT357	Touch-control light dimmer	\$33.00
AT356	6 amp AC regulator	\$27.00
MI-360	Multivibrator, sq. wave to 10MHz	\$6.00
SY-310	15w stereo amplifier kit	\$230.00
SY-340	37W stereo amplifier kit	\$289.00

VICOM

Mall Orders: Direct to VICOM, 68 Eastern Rd, Sth. Melbourne, Vic. 3205. Enclose \$1 extra for handling and postage costs

JostyKits are available now from:

Sydney: Custom Communications, 6 Orchardleigh St. Yennora. Ph. 631-3544.

Radio Despatch Service
869 George St
Sydney Ph. 211 0816

Adelaide: Hamtronics,
Gardner Rd. Kilsnoy

International Communications Systems, 75-77 Dale St, Port Adelaide. Ph. 47-3688

Melbourne: Eastern Communications, 898 Riversdale Rd Camberwell. Ph. 836 8635.

Tasman Electronics,
12 Victoria St. Coburg.
Ph. 354 5062
J.H. Magraths & Co. P/L.
208 Little Lonsdale St.

Brisbane: Delsound,
1 Wickham Tce.
Ph. 229 6155.

Launceston: Advanced Electronics, 5A Quadrant, Ph. 31 7075, Tasmanian Hi-Fi Company, 87A Brisbane St. Ph. 31 5815

Sydney 681 3544
Adelaide 43 7981
Gold Coast 32 2644
Melbourne 836 8635
Perth 321 3047
Geelong 78 9660
Rockhampton 28 2843
Wagga 21 2125

Hobart 43 6337
Cairns 54 1035
Launceston 44 3882
Brisbane 38 4480
Wellington (N.Z.) 28 7946

BIG SOUND — cont

initial decision about the desired bass roll-off and the permissible enclosure size, and then to work forward to the type of driver that will be necessary to complement the stated requirements. If the driver parameters turn out to be impractical for one reason or another, you modify the requirements and try again.

And that is where we started with Etone engineer Nick Kay. Knowing that many commercial compact systems roll off around 80Hz, we suggested that the "corner" frequency (-3dB) should be at 50Hz or below. This should ensure good, foundational bass, particularly as the system would be further assisted, in a listening situation, by the proximity of walls, etc.

As a further requirement, we wanted an enclosure considerably smaller than for the existing 3-26L, and certainly well below 20 litres. We would accept the Thiele/Small dictum that acoustic efficiency would have to be sacrificed to reconcile small size and extended bandwidth. After all, we were after a special-purpose system and if it needed a few more watts to drive it, that should not be too great a problem these days.

Etone's first response was an on-paper design which involved a specially made 6-inch woofer and a matching enclosure having a large port formed by a partial shelf across the lower end. We didn't like it very much, partly because of the volume added by the port, and partly because it would not lend itself to simple fold-around enclosure assembly. Why not a conventional port tube, of more modest dimensions?

Unfortunately, that seemed not to meet the requirements of the Thiele/Small formulas, relative to the driver/enclosure combination envisaged.

Out of the seeming impasse came the suggestion to use a passive radiator instead. In essence, this usually involves the housing and cone of a woofer, minus magnet and voice coil, mounted in a second hole in the baffle. It serves the purpose of a vent or port, except that the mass and springiness of a physical cone assembly substitutes for that of the air within a port.

We liked the idea immediately. It would conserve space, allow a simple cabinet structure to be retained, and offer the visual advantage of an extra (and very active) cone. And this is what we settled for, after the appropriate amount of calculation and experiment. The bass driver would be a specially designed unit, to be designated Etone type 608; it would be mated with a passive radiator type 600 and accommodated in an enclosure with a volume in the range 13 to 14 litres — half the size of the 3-26L! Estimated corner fre-



Although illustrating a somewhat larger enclosure, the diagram emphasises the extreme simplicity of the fold-around method of construction.

quency would be 50Hz, as originally envisaged.

So much the bass end.

Consideration of the 608 cone assembly suggested that it should not be expected to perform too high up and a crossover at about 1500Hz was indicated — meaning that the tweeter had to operate down to at least this region. This tended to rule out the usual dome tweeter, unless we were prepared to specify an accurate high-slope filter or trap to counter possible tweeter resonance around 800-1000Hz.

Rather than get involved in an exer-

Circuit details of the crossover network. The capacitors shown are non-polarised electrolytics. Note speaker polarity, involving a plus sign or a red dot.

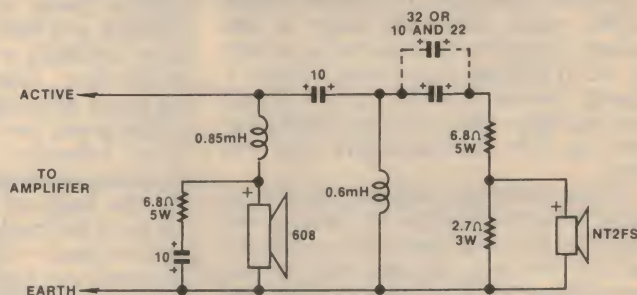


FIG. 2

cise that would have added markedly to the cost of a stereo pair, we settled for an Etone cone tweeter type NT2FS and a straightforward crossover network giving a nominal 6dB/octave roll-off for the woofer and a nominal 12dB/octave roll-off for the tweeter.

When the units were actually interconnected, it became immediately obvious that the output from the tweeter would have to be reduced drastically to match that of the woofer. In fact, it is fed from the active line through 6.8 ohms and shunted by 2.7 ohms, giving a loss of about 13dB.

Even allowing that the tweeter may be more than usually sensitive, the figure does indicate the kind of sacrifice that must be made in woofer sensitivity, in the interest of bigger bass from smaller enclosures. The fact is that

most modern enclosures trade sensitivity for bass response, on the grounds that adequate drive power is available from modern solid-state hifi amplifiers.

What does this mean in practice?

In a typical, not-too-noisy home situation, a pair of 3-13L enclosures will provide adequate, even loud volume when driven by an amplifier delivering a genuine 20 + 20 watts on program material.

If you want to "show off" a bit and/or turn up the bass a notch or two, then a twin-40W or a twin-50W rating would be more appropriate. In fact, it should meet all ordinary requirements for domestic listening.

But for the "big" sound we spoke about earlier, go for an amplifier in the twin-70W to twin-80W grouping. That would be about their limit, running with the bass and treble controls set for "level". With drive of this order, compact systems like the 3-13L will not cope with artificially boosted bass — nor will they cope with spurious cone excursions caused by turntable rumble or eccentric grooves.

What if you don't have even a 20+20W amplifier? Well, the options are fairly straightforward:

- Build the 3-13L and settle for wide-range listening at a very modest level;
- Search out a compact loudspeaker system that emphasises sensitivity rather than bass response. Drivers in low-cost radiograms usually exhibit this approach.

- Settle for a larger loudspeaker system which may well combine adequate bass with higher sensitivity. The Playmaster 3-26L, for example, offers 3dB higher sensitivity, equivalent to a 2:1 increase in amplifier power output. The 3-53L and the 3-75L are somewhat more sensitive again.

The prototype enclosures which appear in the lead photograph were produced for us by H.S.C. Timber Industries Pty Ltd, of 25 Pritchard Place, Peakhurst, NSW 2210. (Phone 02 534 1746). They have a simulated wood finish, a black lacquered baffle face and a removeable grille of black open weave fabric stretched over a particle board frame.

The dimensions shown in the drawing of Fig. 1 were taken off the

BIG SOUND — cont

prototypes and should be representative, in that they were selected by a cabinet manufacturer to ensure economical use of particle board sheets.

We envisage, however, that 3-13L enclosures will be handled by various suppliers throughout Australia and New Zealand, in both kit form and built up. They will doubtless be produced by various cabinet makers, with their own ideas about details and finishes. We would not want to prejudice their discretion but certain points must be stressed:

- Panel sizes may be varied slightly to suit available materials but the internal volume of the enclosure must not be reduced below the 13.2 litres provided for in our drawing. Equally, it should not exceed 14 litres.
- Materials should not be lighter than specified. The construction must be rigid, airtight and rattle-free, with the drivers held snugly and securely against the baffle face.
- The drivers, passive radiator and crossover network must be as specified.

And here a further word about the loudspeaker mounting arrangements:

Assuming the baffle is of particle board, use screws which are of no heavier gauge than necessary, and drill a suitable pilot hole for them, angled slightly away from the edge of the cutout. If screws are too heavy, or are driven in without a pilot hole, there is a strong chance that the particle board will crumble. Nip them just tight, but not too tight, otherwise the hole will strip.

In the prototype cabinets, the drivers were mounted against the face of the baffle, protruding about 5mm from the surface. This way, the mounting screws can utilise the full thickness of the particle board to hold the drivers firmly in place. However, it does mean that a frame grille must be used to keep the cloth clear of the cones.

Alternatively, some manufacturers may choose to recess the baffle to accommodate the drivers flush with the surface. This permits the use of a foam grille but it can also reduce drastically the thickness of material available to the mounting screws. In such a case, it may be desirable to mount at least the main driver with bolts and nuts, using access through the passive radiator hole to secure them. Better still, cement nuts on the rear side of the baffle, so that bolts can be used for all three.

However mounted, it is absolutely essential to provide some kind of a gasket between the speaker frames and the baffle surface to ensure a continuous airtight seal. Air leaks produce



Plan ahead so that the join will be out of sight when each cabinet is placed in position on a shelf.

a dissipative energy loss, which can defeat the whole function of the passive radiator. No matter how good it looks, surface/surface contact between drivers and baffle is not reliable.

As on past occasions, we used Engels 5C adhesive-backed foam strip, sold by hardware merchants as a draught excluder. Alternatives are adhesive backed felt, or resort to non-hardening caulking compound, or a liquid silicone rubber.

Such details aside, it is likely that all kits will be presented and assembled in much the same way. The sides, top and bottom come already cut and pre-grooved, and held together only by the other surfacing material. Lay them flat on the floor, finished side downwards, but avoid stressing or flexing the outer covering any more than necessary.

The intention is that, when the segments are folded around the baffle and the back of the cabinet, the join will be at the bottom — or where it will be seen least — when the enclosure is ultimately put into use. That is why our drawing is shown upside-down, with

the bottom flap yet to be closed.

If the enclosure is to be used in an upright position, plan to have the main driver at the top and the tweeters to the outside (in the case of a mirror pair) so as to gain as much separation as possible. If to be used on its side, have the tweeter towards the top and the main drivers to the outside. On this basis, plan how the baffle and back are to fit.

We would recommend that most of the inside surfaces of the enclosure be padded with ordinary Innerbond, of nominal thickness about 2cm. A piece measuring 1m x 0.5m cut into strips 1m x 45cm, would just about cover the sides, top and bottom of each enclosure, with a couple of strips left over to attach to the back, clear of where the divider network will sit.


Attach the Innerbond securely to the relevant surfaces with thumb-tacks before the enclosure is folded up. It must not be stuffed into the box as an afterthought, as it would then become space filling.

When all is ready, run PVC glue ("Aquadhere" etc) into all V-grooves and slots and smear it to wet all the mating surfaces. Also wet the edges of the baffle and back plate. Slip them lightly into position and carefully fold the sides and bottom up around them, bumping them into position with the ball of the hand. With the final joint firmly closed, hold it tight with straps of adhesive tape and leave overnight.

Before proceeding further, carefully examine the enclosures to ensure that the glue has filled and sealed all corners and joints. If you detect a possible leak, prop up the cabinet as necessary, run glue into the space and leave to harden long enough to ensure that it will stay put.

Also check the output terminal arrangement. Provide a gasket if a plate or fitting is involved and seal any other possible leaks with caulking.

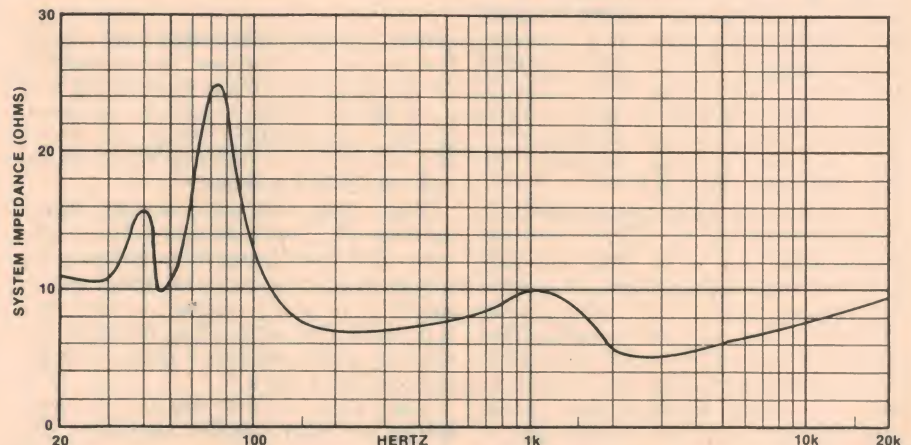This done, the crossover network can be attached to the inside rear of the cabinet, working through the aperture for the passive radiator. Attach the leads to the respective drivers, and to



The impedance V frequency curve of the 3-13L. It falls below the nominal 8 ohm figure in some areas but not enough to be unusual. Note the double-hump centred around 50Hz — characteristic of a vented (or passive radiator) system.

Helps save petrol by keeping your car in tune

Transistor-assisted Ignition System

with dwell extension and full protection!

Electronic ignition is in but CDI systems are out. Our new transistor-assisted ignition system with dwell-extension has all the advantages of CDI without the disadvantages. Our new circuit results in a hotter spark at high engine speeds and is directly compatible with electronic tachometers.

by **LEO SIMPSON** and **RON DE JONG**

Some four and a half years ago in July 1975 we published the circuit of a Capacitor Discharge Ignition system which has proved extremely popular and with the recent surge in petrol prices is selling more strongly than ever in kit form. However, even back in 1975 and even prior to that we were unhappy about some aspects of CDI.

Now, in December 1979, the time has come to close the book on CDI systems

and present a viable and appealing alternative — a transistor assisted ignition system with dwell extension. But let us state that while this new circuit is more satisfactory in every respect than CDI systems, it and other automotive add-ons are not the ultimate answer to obtaining best economy, performance and minimum pollution from car engines.

The ultimate answer, as far as the


petrol engine is concerned, will undoubtedly involve some sort of microprocessor circuitry (which will have the high falutin' term of "on-board computer") controlling a breakerless electronic ignition system together with fuel injection. That answer is probably a few years off yet, so let us revert to the present.

Well, why is Capacitor Discharge Ignition now "beyond the pale"? The first problem regards reliability of the circuit itself. It seems that, even now, some people are troubled with malfunction of the circuit we published back in July 1975 (File No 3/TI/12). It is not possible for us to judge whether these few cases are due to poor assembly, normal component failures or a fault in the original design. But, for the record, some constructors have had trouble.

Apart from reliability of the circuit itself, the most severe problem with CDI systems is "crossfire". For those not familiar with this phenomenon, crossfire is the result of the higher energy and very fast rise-time of CDI systems combined with the normal stray capacitance and leakage resistance across the distributor cap and between spark plug leads.

Every time a designated spark plug fires there is the possibility of a weak spark occurring in other cylinders due to the high energy available from the coil. The engine behaviour when crossfiring is occurring can range from slight "pinking" behaviour to very rough running, particularly when accelerating or lugging up hills.

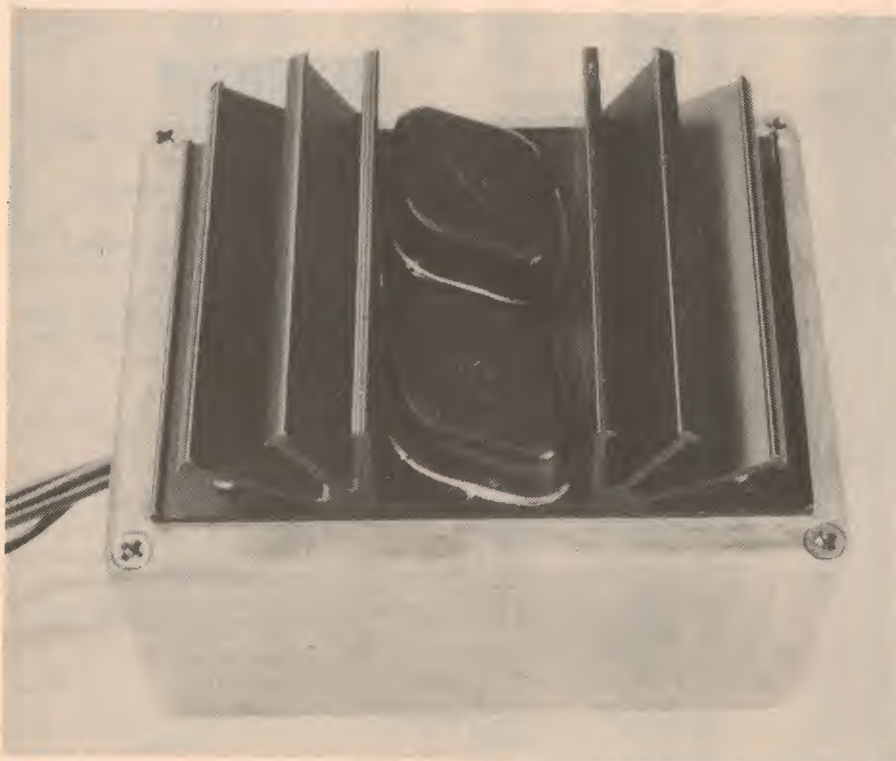Looks are unimportant, utility is the name of the game. That hefty heatsink helps dissipate the heat generated by the constant current source, Q3.



TRANSISTOR-ASSISTED IGNITION

in normal running. Add a CDI system and they might run "like a hairy goat".

Recently, there have been more complex CDI circuits which have attempted to overcome this problem of misfiring due to short spark duration. Various terms "multiple spark discharge" or similar, they produce a series of high energy sparks for each plug firing. Perhaps these systems do indeed overcome the problems of firing less than optimum mixtures but it could be that they have even worse problems with crossfiring.

A final bugbear, particularly as far as the keener auto enthusiasts are concerned, is that CDI systems are generally not compatible with tachometers. This problem is just as applicable to commercial CDI systems as well as our design. The manufacturers blithely ignore this problem, as far as we can see, and have even referred dissatisfied customers to our magazine for a suitable preamplifier circuit to enable the tachometer to be used. For the record, we have not published such a circuit.

CDI does have a place but not with the four-stroke engine. They are more applicable to magneto-based ignition systems as used on two-stroke motors for lawnmowers, motorcycles and outboard motors. There, the ability of capacitor-discharge ignition to fire fouled plugs is a significant feature and crossfiring is not a problem.

Our new transistor-assisted ignition system offers significant advantages over the conventional Kettering system and our previous transistor system described in August 1975 (3/TI/13). For a start, as with other electronic systems, it relieves the points of the heavy burden of coil current switching while still passing enough current through them to keep them clean.

This means that once the system is initially set up it will not be necessary to readjust the system until wear of the rubbing block becomes significant. In practice, this means that every 15,000 kilometres or so, the points should be regapped and the timing readjusted. So, in essence, the car will stay at peak tune for much longer periods than would otherwise be the case and long term economy will be improved.

Starting performance of the new transistor assisted ignition system can be expected to be on a par with a freshly tuned Kettering system. However, in the conventional Kettering system starting performance normally deteriorates as the points become worn, so as time goes on, the transistor system is superior.

At low engine speeds, the spark energy of the transistor system will be comparable with a freshly tuned Kettering system with new points fitted.

This is because the voltage drop across the main switching transistor is less than 300 millivolts when turned on. This is comparable to the voltage drop across a typical set of points when they are reasonably new. As points become worn, the voltage drop may increase to one volt or more at maximum coil current.

As engine speed rises, the spark energy of the conventional Kettering system is reduced due to the relatively

We estimate that the current cost of parts for this project is approximately

\$35

This includes sales tax.

slow build-up of current in the coil primary. Our transistor-assisted system maintains spark energy at a high level even up to very high engine speeds by using "dwell extension".

DWELL EXTENSION

The term "dwell" refers to the time the points are closed and is measured in terms of degrees of distributor camshaft rotation. Our circuit provides for dwell extension by switching on the coil 0.6 milliseconds after the points open. This means that we have artificially determined spark duration at 0.6 milliseconds.

By comparison, the typical spark duration of a capacitor-discharge ignition system is about 0.2 milliseconds.

The photographs of the oscilloscope waveforms shows the performance of the system. The first photograph shows the coil waveform without dwell extension.

At the instant of points opening the coil voltage rises very quickly until the spark discharge occurs, at which the voltage falls to a relatively low level while the coil secondary resonates with its distributed capacitance at about 10 to 15kHz. When the spark is extinguished, the remaining coil energy is dissipated by resonance in the primary circuit at a much lower frequency.

In practice then, the spark lasts for less than one millisecond. Our circuit takes advantage of this fact by fixing the spark duration at 0.6 milliseconds. In the second oscilloscope photograph, the effect of the dwell extension can be seen. Since the main coil transistor is turned on again 0.6 milliseconds (approximately) after the points open, there is no time for the low frequency coil primary resonance to occur.

But notice that the amplitude of the coil primary voltage is much increased.

This clearly shows the useful advantage of dwell extension. These photographs, by the way, were taken at the very high spark repetition rate of 300 sparks per second. This corresponds to 4500rpm in a V8, 6000rpm in a 6-cylinder and 9000rpm in a 4-cylinder motor! That also explains why the coil energy is so low for the system without dwell extension.

MORE SPARK ENERGY

Lest readers think that we are featuring this circuit merely for the hotfoot fraternity, let us state that compared with the conventional ignition system, our transistor assisted ignition system gives a useable increase in spark energy from idle speeds and up. Whereas the normal system begins to taper off the spark energy from idle speed upwards, the transistor system with dwell extension does a much better job of maintaining spark energy up to spark rates far beyond the capability of normal engines. Fig 1 illustrates this.



This great improvement in spark energy comes about in two ways. Consider the fact that a normal coil and ballast resistor system takes about 15 milliseconds for the current to rise to saturation (and thus provide maximum spark energy). Since in a 6-cylinder motor the points provide an approximate 50% duty cycle, this means that if sparks are required less than 30 milliseconds apart, the coil current will not reach saturation level. And a 30 millisecond period coincides with a spark rate of only 33 sparks/second or only 667rpm for a 6-cylinder motor.

COIL NOT FULLY DISCHARGED



The main reason for the improvement is not so much the extra time for the coil current to build up but the fact that the coil transistor is turned on before the spark extinguishes naturally and primary coil resonance occurs. The fact is that when the coil transistor is turned on again the coil energy has not been fully dissipated. In fact, after the spark extinguishes there is considerable energy remaining in the coil which is usually dissipated in useless primary resonance.

One benefit of a high energy transistor ignition system which has not so far been mentioned is its ability to refire a spark plug after the spark has been blown out by a turbulent mixture. So not only does this system have an advantage over CDI with longer spark duration but it is also able to re-ignite a spark that is blown out (provided it all happens within 0.6 milliseconds).

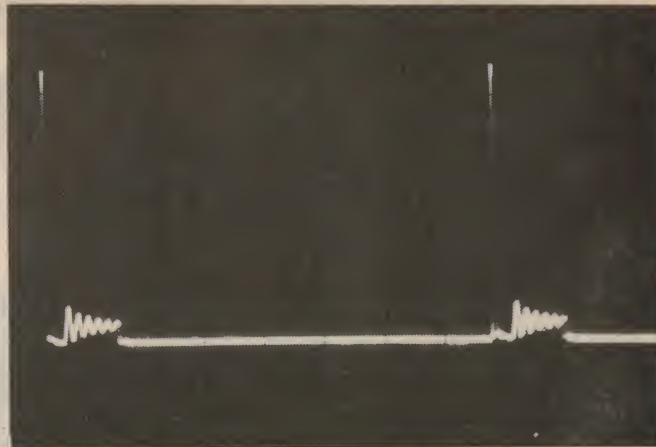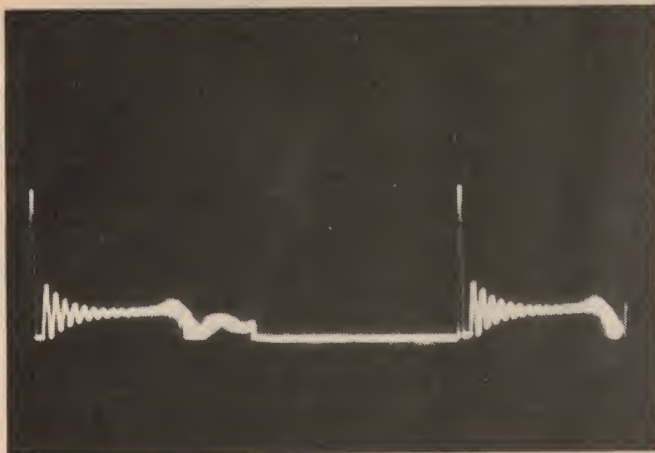Other features of this transistor assisted circuit are comprehensive protection of both the ignition system components and the electronic circuitry itself and the ability to drive a standard tachometer without any modifications.



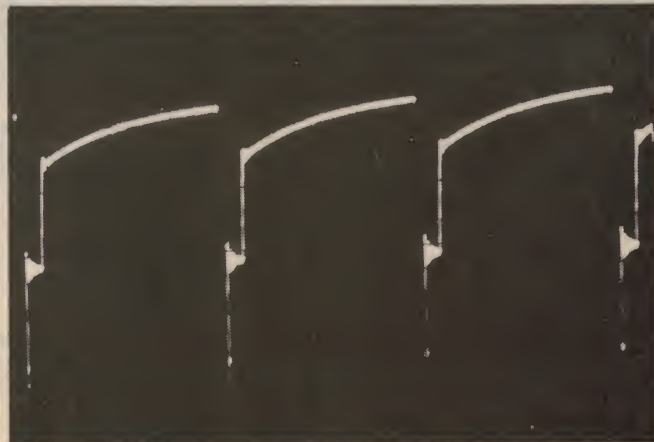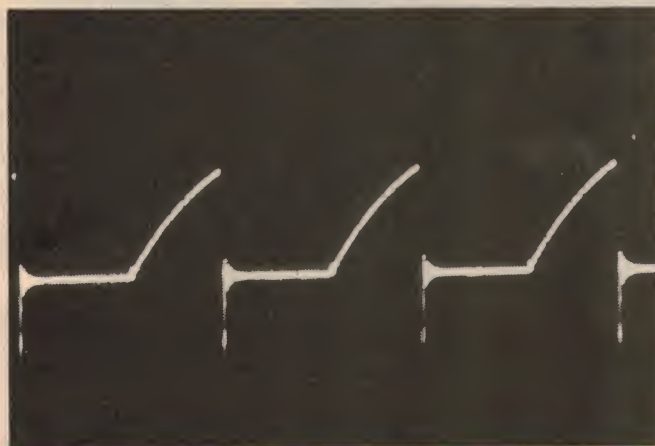These two photos show the coil primary voltage from the circuit without (left) and with dwell extension. Cro settings: 50v/div and 0.5ms/div.



These two photos show the coil current without (left) and with dwell extension. Cro settings: 2 amps/div and 2ms/div.

Is there a catch to all this? Are there no disadvantages of this new transistor ignition system compared with conventional or CDI systems? Well there are a few side-effects of the new system but you could hardly class them as major drawbacks.


For example, because of the dwell extension feature, the coil is maintained in saturation for a much higher proportion of its operating time. So the average current passing through the coil is about 80% higher. Or, to put it another way, the coil current is increased from about 2.5 to 4.5 amps.

In addition, the transistor drive circuitry draws about 1.5 amps so the total current drain of the transistor-assisted system is around six amps versus 2.5 amps for the conventional system.

The extra current drain is unlikely to pose much of a problem for the car electrical system but the extra coil current does mean that the coil runs hotter. This should not be a problem for the oil-filled coils on modern cars. Even so, the coil should ideally be placed so that it receives some of the cooling air from the fan.

On the plus side, because of the

Fig 1 (left). This shows how the dwell extension feature maintains coil current and, therefore, spark energy up to very high engine speeds (in this case, for a 6-cylinder motor).

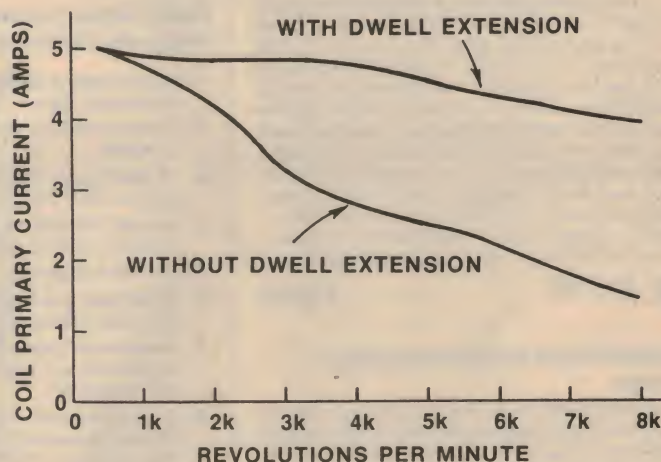

comprehensive protection features of the circuit, the transistor assisted system is unlikely to cause catastrophic failure due to voltage breakdown which can occur with CDI systems.

As far as most enthusiasts are concerned, the only drawback of our new transistor-assisted ignition system is the necessity to gain access to the battery side of the ballast resistor. This can be difficult on cars which have the ballast resistor incorporated into the wiring harness, as on Holden cars, for

example. More about this later.

Well that explains some of the thinking behind this new transistor-assisted ignition system. You can refer to the section on circuit description to find out the details of operation. It is a fairly complicated circuit but it should be reliable as all components are operated well within their ratings and are able to sustain high temperatures.

MORE →

Heathkit Continuing Education Series— the fast, easy, low-cost way to learn electronics!

These four basic programmes provide an excellent overview of contemporary electronics—they'll provide you with the fundamentals you need to follow your interests wherever they may lead you. The programmed learning text is clearly written, with technical material fully explained as it is introduced. Built-in quizzes let you test your knowledge at each step. The records give you a "personal" outline of text material and additional information, and electronic parts are included for use in the experiments. Each course leads logically into the next, and when you complete all four, you'll have a thorough knowledge of basic electronics.

Part 1: DC Electronics— electrical fundamentals, theory and practice—

- | | | |
|---------------------------|-----------------------------------|--------------------------------------|
| 1. <i>Electron Theory</i> | 4. <i>Ohm's Law</i> | 7. <i>Network Theorems</i> |
| 2. <i>Voltage</i> | 5. <i>Magnetism</i> | 8. <i>Inductance and Capacitance</i> |
| 3. <i>Resistance</i> | 6. <i>Electrical Measurements</i> | |

Includes all texts, records, 56 parts for 20 experiments.
Average completion time, 20 hours.

Programme EE-3101

\$68.00

Part 4: Electronic Circuits Learning Program

Brings the knowledge you've gained in the first three programs to bear on the latest circuits used in solid-state electronics. This program covers the operation of common solid-state electronic circuits. It shows you how to analyse and design simple amplifiers and oscillators. You learn about pulse circuits, multivibrators, SSB and how to use a voltmeter and oscilloscope to analyse the operation of electronic circuits. Included are texts, records, and 110 electronic components for 18 different experiments.

Programme EE-3104

\$83.00

Part 3: Semiconductor Devices— transistors, zeners, SCR's, FET's, digital and linear IC's, LED's, opto-electronics

- | | |
|--|------------------------------------|
| 1. <i>Fundamentals</i> | 7. <i>FET's</i> |
| 2. <i>Diodes</i> | 8. <i>Thyristors</i> |
| 3. <i>Zener Diodes</i> | 9. <i>IC's</i> |
| 4. <i>Special Diodes</i> | 10. <i>Opto-electronic Devices</i> |
| 5. <i>Bipolar Transistor Operation</i> | |
| 6. <i>Bipolar Characteristics</i> | |

Includes all texts, records and 27 parts for 11 experiments. Average completion time, 30 hours.

Programme EE-3103

\$68.00

Part 2: AC Electronics— sine waves, inductive and capacitive reactance, impedance, phase shift, transformers and filters

1. *AC Fundamentals*
2. *AC Measurements*
3. *Capacitive Circuits*
4. *Inductive Circuits*
5. *Transformers*
6. *Tuned Circuits*

Includes all texts, records, 16 parts for 8 experiments. Average completion time, 15 hours.

Programme EE-3102

\$68.00

Heathkit Experimenter/Trainer

For the Heathkit DC, AC and Semiconductor programs—helps you perform each project quickly and easily. And after you finish the programs, it's ideal for "breadboarding" your own design projects. Has solderless breadboarding sockets, 2-range variable sine and square wave signal source, dual-variable power supplies for positive and negative voltages (both variable over 1.2 to 16 volts, 120 mA, both regulated and short-circuit protected). Built-in 1k and 100k linear potentiometers. Center tapped power transformer secondary provides 30 V rms, 50 Hz for line experiments.

Kit ET-3100

\$114.00

Heathkit Digital Design Experimenter/ Trainer

Use it to perform all the experiments in the Heathkit Digital Techniques Programme, also to develop projects, build and test prototypes, verify circuit operation, check digital IC's. Has solderless breadboard sockets, four binary data switches, 2 "no-bounce" switches to pulse logic circuits, 3-frequency pulse clock generator, 4 LED's for visual indication of logic states. Three regulated power supplies: +12V, 100 mA current limited; -12V, 100 mA current limited; +5V, 500 mA, overload protected. Accommodates up to eight, 14 or 16-pin dual-in-line IC's, also 24, 28 and 40-pin DIP's.

Kit ET-3200

\$138.00

HEATH
Schlumberger

Digital Techniques Program—For the advanced experimenter, technician, hobbyist or engineer.

Learn digital fundamentals, circuit design, TTL, ECL, CMOS, PMOS, NMOS integrated circuits; SSI, MSI and LSI; ROM's, PLA's; microprocessor theory

- | | |
|--|--|
| 1. <i>Introduction: techniques and uses, binary numbers, digital codes.</i> | 10. <i>Digital Applications: counters, computers, microprocessors.</i> |
| 2. <i>Semiconductor Devices for Digital Circuits.</i> | |
| 3. <i>Digital Logic Circuits: AND gates, OR gates, NAND / NOR logic, etc.</i> | |
| 4. <i>Digital Integrated Circuits: TTL, ECL, CMOS, nMOS, pMOS, how to choose.</i> | |
| 5. <i>Boolean Algebra.</i> | |
| 6. <i>Flip-Flops and Registers: latches, D & JK flip-flops, storage registers, applications.</i> | |
| 7. <i>Sequential Logic Circuits: binary, BCD, modulo N, up / down counters, dividers, shift registers.</i> | |
| 8. <i>Combinational Logic Circuits: encoders, decoders, exclusive OR, comparators, multiplexers, ROM's, PLA's.</i> | |
| 9. <i>Digital Design: combinational and sequential circuits, procedures.</i> | |

Programme EE-3201

\$90.00

ORDER BY COUPON NOW OR COME TO OUR SHOWROOM

Please rush me the programme of my choice. My cheque for \$ _____ is enclosed plus \$7.00 for package & post.

Name


Address

..... P / Code


Send to: W. F. Heathkit Centre,
220 Park St., South Melb. 3205. Phone: 699-4999

- ☐ Programme EE-3101
☐ Programme EE-3102
☐ Programme EE-3103
☐ Programme EE-3104
☐ Kit ET-3100
☐ Kit ET-3200
☐ Programme EE-3201

TRANSISTOR-ASSISTED IGNITION

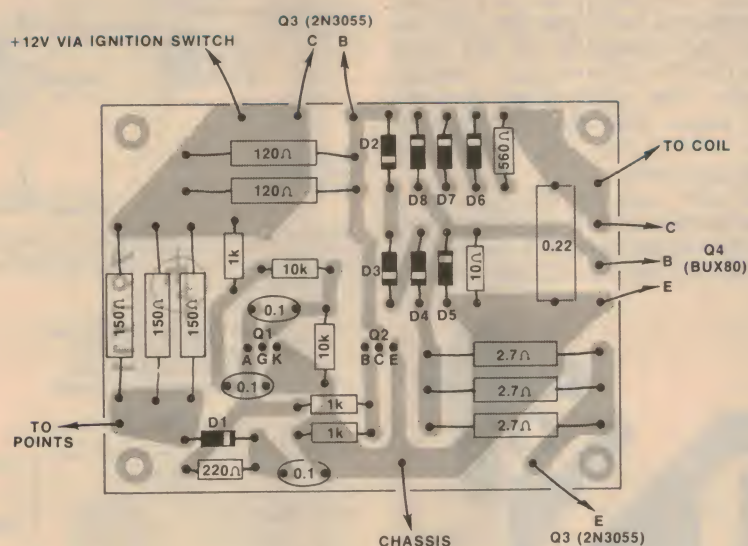

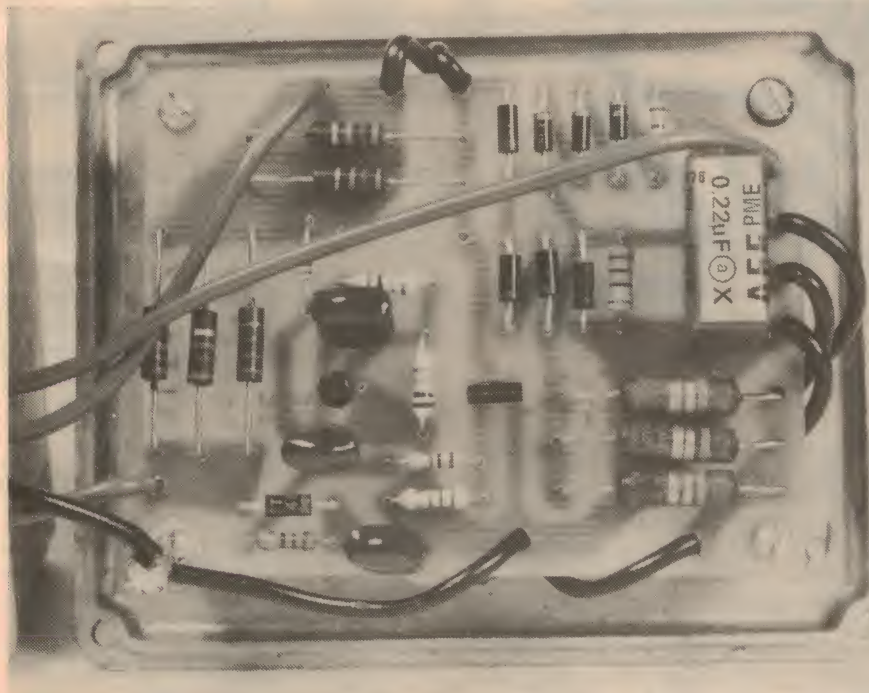The 150-ohm, 120-ohm and 2.7-ohm resistors are all 1W units; the 0.22μF capacitor across the BUX80 (Q4) should be rated at 630VDC or 250VAC.



CONSTRUCTION

The entire transistor ignition circuit is housed in a rugged diecast aluminium box. We used an Eddystone box measuring 93 x 56 x 119mm; but any diecast box which can comfortably accommodate the PC board and power transistor heatsink would be suitable. All the components except for the power transistors are mounted on a small PC board measuring 91mm x 68mm and coded 79T111.

The two power transistors are mounted on the lid of the diecast box together with a suitable heatsink. The

heatsink we have used is available from Dick Smith Electronics. Actually almost any heatsink which can accommodate two TO-3 devices is suitable provided it can fit comfortably on the lid of the diecast box and has a reasonable thermal resistance; ie a radiating area at least as large as that of the heatsink we have used.

If the heatsink does not come pre-drilled you should first drill it using a TO-3 mica washer as a template. After drilling, remove any burrs by using a large diameter drill. Next, position the heatsink on the lid of the diecast box in

such a way that it does not interfere with the lid-securing screws and then punch suitable drill centres in the lid and drill and deburr the holes in the previous manner.

With the heatsink free of any metal shavings or other grit, a thin layer of thermal conducting compound or silicone grease can be applied in the area underneath the transistors and on the mica washer. Some heatsink compounds may contain beryllium, a highly toxic substance, so apply the compound carefully with a cotton bud and avoid skin contact with it. Mount the transistors with the mica insulating washers and plastic bushes in position

PARTS LIST

- 1 PC board coded 79T111, 91mm x 68mm
- 1 diecast aluminium box, 118 x 93 x 56mm, Eddystone 6908P or similar.
- 1 dual TO-3 heatsink (see text)
- 3 metres red 4mm auto cable
- 1 metre black 4mm auto cable
- 4 25mm brass standoffs
- 2 sets of TO-3 mounting hardware, ie. mica washers insulating bushes, screws and nuts.
- 2 TO-3 transistor insulating caps
- SEMICONDUCTORS**
- 1 BUX80 transistor
- 1 2N3055 transistor
- 1 BD139 transistor
- 1 2N6027 PUT
- 5 1N4002 diodes
- 3 1N4761 75V zener diodes
- CAPACITORS**
- 1 0.22μF 630VW or 250VAC
- 3 0.1μF metalised polyester (greencap)

RESISTORS (½W or ¼W)

- 2 x 10k, 3 x 1k, 1 x 560 ohm, 1 x 220 ohm, 1 x 10 ohm, 3 x 150 ohm (1W), 2 x 120 ohm (1W), 3 x 2.7 ohm (1W).

NOTE: Resistor wattage ratings and capacitor voltage ratings are those used for our prototype. Components with higher ratings may generally be used provided they are physically compatible.

and then check that the case of both transistors is insulated from the heatsink and lid using a multimeter or other continuity checker.

We used plastic TO-3 transistor covers on both transistors. These are essential both to eliminate the possibility of short circuits and also to isolate the rather high voltages which are present on the case of the BUX80 transistor.

Now the components can be soldered onto the PC board. The only problems which might be encountered here are with the orientation of the


diodes, the PUT and BD140 transistor, so pay special attention to the wiring diagram. Note that parallel combinations of 1 watt resistors have been used in some cases. This was done because they are cheaper than equivalent 5 watt wirewound resistors and their surface temperature rise is not as great. Even so the 1 watt types can still become quite hot so mount them slightly off the board to avoid the possibility of charring the PCB.

Wires to the transistors and to the various external connections are heavy gauge 4mm auto cable. This won't fit easily into a standard PC hole so we suggest that you could either redrill the


from the box using a cable clamp; if necessary build up the cable thickness with insulation tape to give a tight fit. The cable should exit via a grommited hole at the side of the box.

The only remaining task is to install the completed unit into the car. For reliable performance of the unit choose a well-ventilated spot — ideally well away from possible splashing by mud or water. Near the front grille or on the wheel housing would be suitable positions.

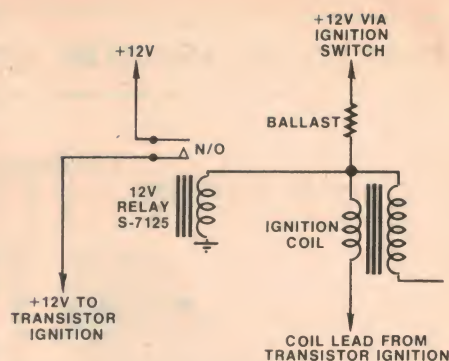Install the case by the use of a suitable bracket or drill several holes in the bottom of the case and secure it to the vehicle by means of 12mm x No. 10



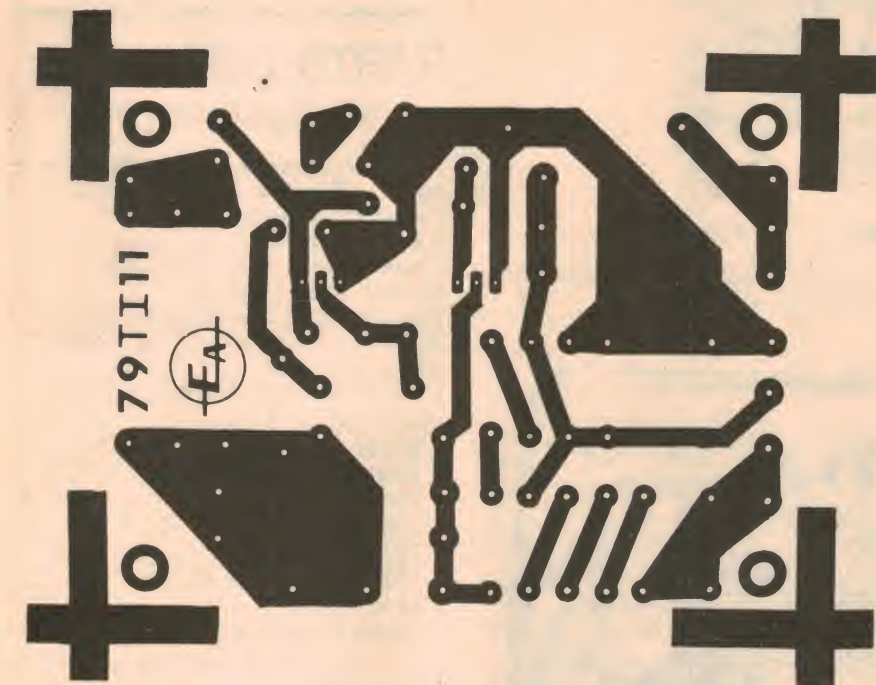This circuit is suggested as a method of connection in cars with ballast resistor in the wiring harness.



Actual size artwork for the PCB.

holes to an appropriate size or use PC stakes. If PC stakes are used make sure they fit tightly into the PC hole so they can't fall out when a wire is soldered onto them.

Mounting holes for the PC board should now be drilled. The PC board is mounted on the lid using brass or plated standoffs, screws, nuts and shake-proof washers. The holes will pass through both the lid and the heatsink, so ensure that the mounting screws don't interfere with the fins on the heatsink first. Before installing the PCB, wire up the leads to the power transistors. Use one-metre lengths of wire to provide the chassis, points, coil and battery connections to the PCB.

When the unit is actually installed these lengths can be trimmed down and suitable lugs or connectors attached. The earth cable is also connected to a lug on one of the standoffs so that the circuit will be earthed via the case as well.


Clamp the cables before they exit

self-tapping screws. With the unit mounted, the various connections to the car electrical system can be made.

For this purpose we recommend that you use two eyelet/solder-lug assemblies, attached to the ignition coil. This allows the connection of the coil and points leads to be readily made and it allows quick changeover between transistor ignition and conventional ignition should this be necessary. Some systems make use of a slide switch or octal plug to facilitate changeover but poor reliability of these methods led us to opt in favour of the lug assemblies.

We understand that Watkin Wynne Pty Ltd will be able to make these eyelet assemblies available to parts suppliers. Alternatively, they are available from Dick Smith Electronics.

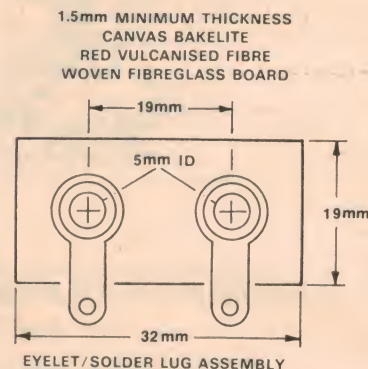Apart from the connections to the ignition coil and points it is also necessary to connect the +12 volt lead to the battery via the ignition switch. Some circuit designs actually obtain power via the ballast resistor, which



Use two of these lug assemblies to make the connections to the ignition system.

means that the circuit would probably be easier to install but it also has the disadvantage of reducing coil current and so reducing spark energy.

If your car has a separate ballast resistor then it is a simple matter to connect to the ignition switch side of the resistor. Some cars though, use a ballast wire, which complicates the situation because it is then necessary to guide the +12 volt lead from the transistor ignition through an appropriate hold in the firewall to the actual ignition switch itself. Alternatively, if you do not wish to drill through the firewall then you can use the circuit shown elsewhere in this article. It consists simply of a relay connected to the coil side of the ballast resistor which switches the +12 volt from the battery directly. The relay can be installed inside the box.

With installation complete, the system can be tested. The points gap should be set exactly as specified by the car manufacturer. Note that if a "dwell meter" is used to set the points gap, then it is probably best to do this adjustment when the vehicle is running with conventional ignition.

Well, now that all those readers have been disillusioned about CDI, what are they going to do with them? We have thought of that too. The answer is to make use of the inverter in a strobelight for auto tune-ups. Refer to our article on a "Power Timing Light" of February 1976. (File No 7/SC/5).

GREAT NEW KITS


to build over the holidays



**AUSSIE
KITS
FOR
AUSSIE
ENTHUSIASTS**

SEE EA
DEC '79

TRANSISTOR ASSISTED IGNITION

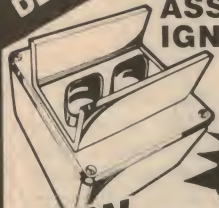

NEW


K 3300

\$32⁵⁰

At the present time, D.I. is the only way to get a transistor assisted ignition system. This kit is a complete system for a car. It is a complete system for a car. It is a complete system for a car.

SEE EA
SEPT '79

AUTOCHIME

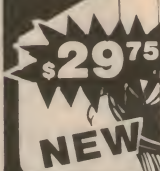

\$29⁷⁵

NEW

This simple to build kit utilizes a microprocessor with a repertoire of 24 tunes. Each time the doorbell is pushed it will automatically move on to the next tune! Full instructions supplied.

K 3531

SEE ETI
SEPT '79

MARK II DISCO-STROBE



K 3152

\$34⁵⁰

**NEW
UPDATED
KIT**

The ever popular ETI Disco Strobe has been updated. Improvements in the electronics are essential. Now PCB and this plus the all new case makes this an essential kit for parties. The kit comes complete with instructions and these instructions include details on extending the kit to include two flash tubes.

SEE EA
NOV '79

METAL DETECTOR



K 3504

\$19⁵⁰

Economy PLUS! Latest digital IC circuitry for top performance from a budget kit. Easy to make and get going - you could find a fortune! (Note: does not include dowel rod or coil former!)

SEE EA
AUG '79

MAST HEAD AMP

NEW

\$29⁵⁰

Not Illustrated

K 3232

If you are plagued with TV reception problems then this masthead kit could solve them for you! Designed for TV plus FM and UHF - it is simple to build and includes power supply and full instructions.

PLAYMASTER 40/40 STEREO AMPLIFIER

(E A December 76)
Our most popular kit ever. Thousands sold.
Cat. K-3411.....\$129.50

PLAYMASTER TWIN 25 AMPLIFIER

(E A May 76)
Similar to above, but less power. A great kit.
Cat. K-3410.....\$105.00

PLAYMASTER AM/FM TUNER

(E A Nov Dec 78)
Matches Playmaster amplifiers - with a built-in digital clock.
Cat. K-3494.....\$129.50

PLAYMASTER GRAPHIC EQUALIZER

(E A June 79)
Aids depth and dimension to your Hi-Fi system.
Cat. K-3500.....\$99.50

LED LEVEL METER

(E A June 76)
Easy to make. Fully solid state.
Cat. K-3370.....\$13.50

CAR STEREO BOOSTER

(E A January 79)
Boosts power output of your car stereo to 12 watts per channel.
Cat. K-3493.....\$29.50

MUSICOLOR Mk111 COLOUR ORGAN

(E A September 76)
Turns your music into light! Just add the lights.
Cat. K-3140.....\$65.00

ETI601 MINI ORGAN

(E T I August 76)
You can play your favourite tunes in style.
Cat. K-3430.....\$26.50

LOUDSPEAKER PROTECTOR

(E A June 76)
Eliminates burnout and turn-off surges from most amplifiers.
Cat. K-3425.....\$13.50

PRICES CORRECT AND STOCK AVAILABLE AT TIME OF GOING TO PRESS

C.D.I. SAVES ON PETROL

This kit will pay for itself over and over. Installed in your car, it will give easier starting from cold, keep your points & plugs in better condition thereby keeping your car in tune for a longer time.



K 3280

\$32⁵⁰

DRILL SPEED CONTROLLER

Thousands of these simple to build kits have been sold. Use with your 240V universal brush type motor drill to give speeds down to near zero.

E A July 76



K 3080

\$13⁵⁰

DICK SMITH ELECTRONICS


SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RESELLERS



DSE652

Fan Speed Control

ELECTRONICS Australia, December, 1979

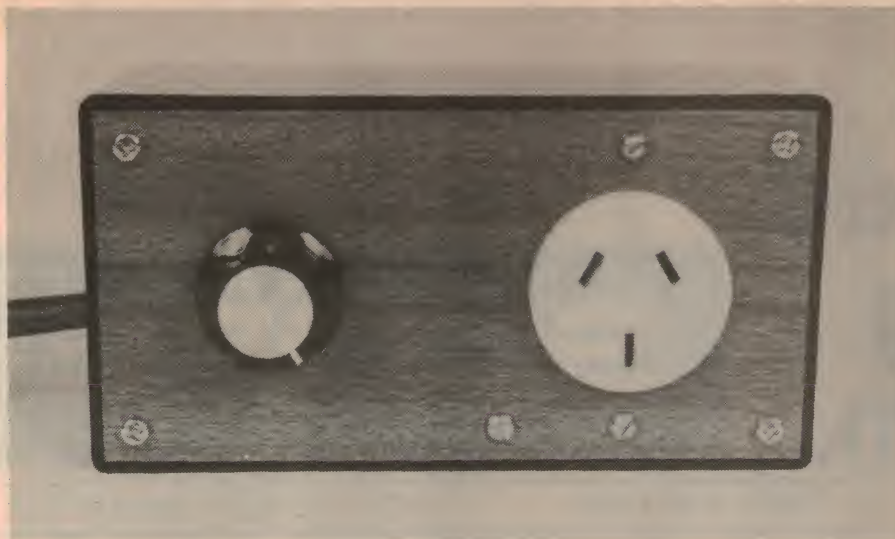

An economical plastic box makes an attractive case for the fan speed control.

quence is repeated. If the pot is set to a low resistance value, C1 is charged quickly and the Triac is fired early in each half-cycle, which thus feeds a relatively high voltage to the load.


Alternatively, if the pot is set for a higher resistance value, C1 charges slowly and the Triac is fired later in each mains half-cycle, which means a lower voltage is fed to the load.

In practice, there are two limitations on the range of pot settings which can be used with typical domestic fans. The first of these has to do with the starting torque of the motor itself. Because the starting torque of a "shaded pole" motor is quite low even with the full mains voltage applied, a much reduced input voltage may result in the fan not starting at all.

This type of circuit also suffers from the "hysteresis" characteristic which was displayed by early single time-constant light dimmers. In the present circuit, it is possible that this hysteresis may result in the circuit failing to trigger reliably at very low settings. However, the effect is unlikely to be noticed because of the constraint set by the first limitation. In practice, a setting which causes the fan to spin just fast enough to cause a noticeable breeze (by this we mean a gentle breeze rather than a draught) will also be the minimum setting for reliable starting of the motor.

Inductive loads such as fans present a particular problem when controlled by Triac circuitry. Because the current tends to lag the voltage waveform, the Triac turn-off (when the current drops to zero) occurs not at the end of the AC half-cycle but well into the beginning of the next half-cycle. This means that when the Triac turns off, the voltage across it will not be zero but reversed in polarity.

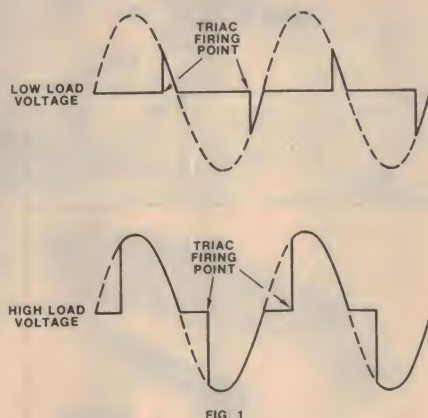Thus, at turn-off, the voltage across the Triac will rise from near zero at conduction to whatever is the instantaneous value of the mains waveform



These diagrams show how the Triac can vary the speed of the fan.

We estimate that the current cost of parts for this project is approximately

\$15

including sales tax.

which may be as high as several hundred volts. This rapid rise in voltage across the Triac may cause it to turn on again in a phenomenon known as "dv/dt switching".

R1 and C2 are incorporated into the circuit to control the rise time of the voltage across the Triac at switch-off and so prevent "dv/dt switching". The values selected for R1 and C2 are adequate for typical fan motors. This RC network is commonly referred to as a "snubber circuit".

We have not included RF suppression components in this circuit. These are necessary in light dimmers because of the very fast rise time of the current waveform at the time of each Triac fir-

PROJECT BUILDERS DON'T RISK IT!

For safety's sake use transformers designed to Australian Standard Codes like Ferguson Transformers

TWO POPULAR RANGES

20/40/60VA Low Profile

A compact range with ratings from 6 to 40V and a 20VA multi-tap.



5VA PCB Mounting

Designed to standard 0.1" grid. Double insulated, very compact with ratings from 4.5V, 1.11A upto 40V at 0.13A.



MADE IN
AUSTRALIA
TO AUSTRALIAN
STANDARDS

Available from Electrical and Electronic Stores or write to;


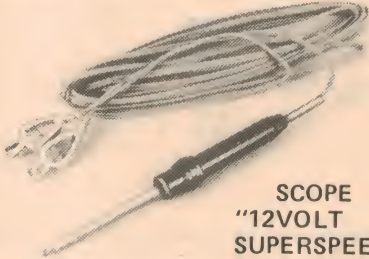

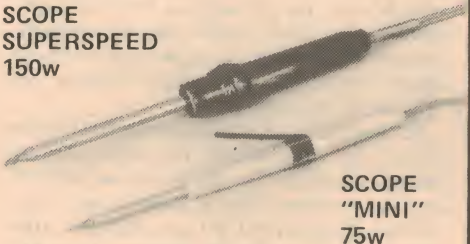
FERGUSON

FERGUSON TRANSFORMERS PTY LTD
331 High Street, Chatswood N.S.W. 2067

SERVICE TECHNICIANS!

Specialised Soldering Tools from...

SCOPE


SERVICE SITUATION	TAKE THIS TOOL	GET THIS USER ADVANTAGE
<ul style="list-style-type: none"> ● No power ● No time to get power ● Must work on live gear 	<p>SCOPE "CORDLESS"</p> 	<ol style="list-style-type: none"> 1. 40-200 Terminations depending on conductor size. 2. Recharges overnight. 3. Heats in 6 seconds. 4. 60 watts - Controllable temperature.
<ul style="list-style-type: none"> ● 12 volt. Battery power available only. ● Outdoor and bad weather expected. ● Service vehicle can get within 6 metres. 	 <p>SCOPE "12VOLT SUPERSPEED"</p>	<ol style="list-style-type: none"> 1. 5 Second heating. 2. 200 watts if needed. 3. Controllable temperature. 4. You can replace tip or element anywhere in minutes.
<ul style="list-style-type: none"> ● Modern sophisticated PCB equipment. ● Accurate & automatic temp. control wanted. ● Components are heat critical. 	<p>SCOPE "TC60"</p> 	<ol style="list-style-type: none"> 1. Heats in 45 seconds. 2. Dial any temp. 200°-400°. 3. Plugs direct to mains. No transformer needed. 4. Accept iron plated tips from 0.8mm to 6.4mm.
<ul style="list-style-type: none"> ● Unpredictable soldering situation. ● Maybe electrical or electronic or mechanical. ● You can't come back to base for a bigger or smaller iron. 	<p>SCOPE SUPERSPEED 150w</p>  <p>SCOPE "MINI" 75w</p>	<ol style="list-style-type: none"> 1. 5 second heat up. 2. Controllable temperature. 3. Reserve heat for any normal job. 4. 4 volt safety in the hand.

Available from your normal trade suppliers in Australia and New Zealand.


SCOPE LABORATORIES

Box 63 Niddrie Vic., 3042.
Phone: (03) 338 1566. TLX 34382.

FAN SPEED CONTROL

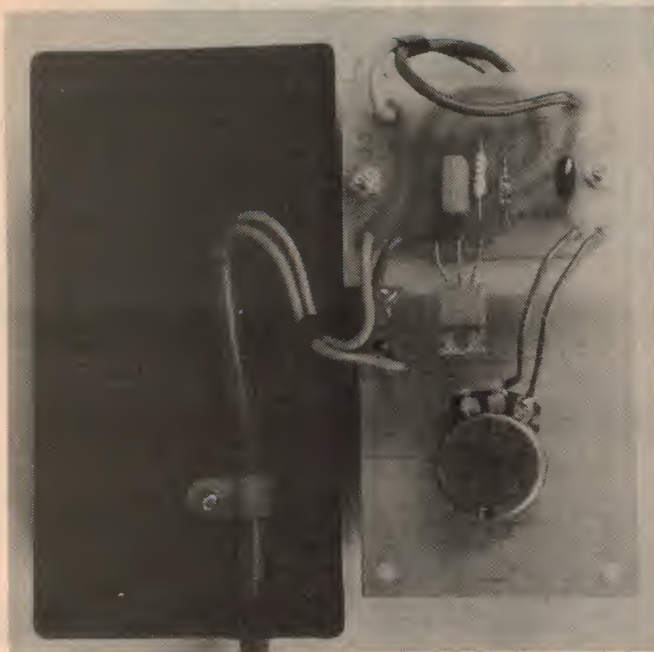

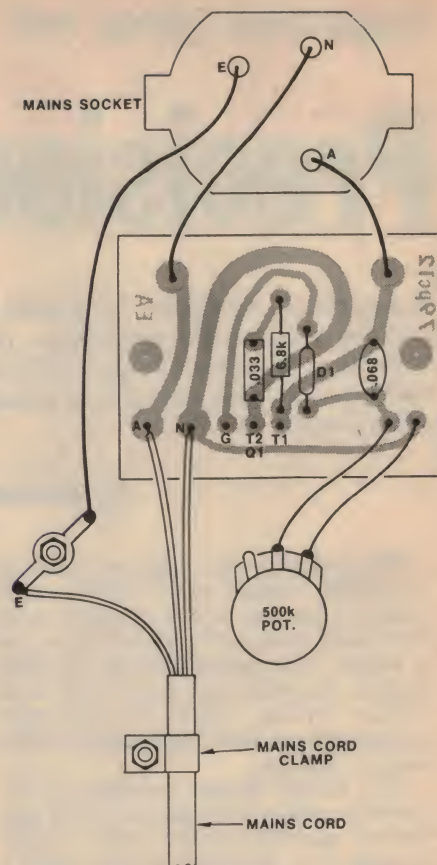Assembly of this circuit will take only half an hour to have it working. The Triac is wired directly to the PCB. At lower right is the full size artwork of the PCB.



PARTS LIST

- 1 plastic box 130 x 68 x 41mm
- 1 three-pin mains plug
- 1 length 3-core mains cable
- 1 mains cord clamp
- 1 grommet
- 1 panel mount mains socket
- 1 steel front panel 130 x 68mm
- 1 PC Board 79pc12
- 1 knob
- 1 SC141D Triac

- 1 V413, BR100 Diac
- 1 500k (1in) potentiometer
- 1 6.8k 1W resistor
- 1 .033uF/630VW or 240VAC polyester capacitor
- 1 .068uF/100VW polyester capacitor

MISCELLANEOUS:

solder lug, connecting wire, screws and nuts, lockwashers, spacers for PCB, solder.

ing point. However, the inductance of typical fan motors inhibits this fast rise time, making RF suppression components less important.

So the complete circuit comprises just six components, two active and four passive. Which means that it is a simple task to put together.

Our version was made up in a plastic utility box measuring 130 x 68 x 41mm. These boxes are supplied with a light-gauge aluminium lid but this is too flimsy to accommodate a flush-mounting three-pin mains socket. Accordingly, a stiffer lid made of Marvplate steel or thicker aluminium should be made up to replace it.

The circuitry is accommodated on a small PC board measuring 61 x 46mm (coded 79pc12) which is mounted on the back of the mains socket using long mounting screws.

Before mounting this PCB, install the five components on it. The Diac can be installed either way around but make

sure the Triac is put in correctly. The Triac does not need a heatsink.

Make sure the capacitors have the voltage ratings specified. No skimping here.

With the components soldered to the PCB, put it aside and work on the plastic box. Drill a hole to take a grommet for the mains cord and a smaller hole for the cord clamp securing screw and nut. Now install the mains cord. The earth wire (green) is connected directly to a solder lug on the control panel and thence to the earth terminal on the AC socket.

Active and neutral wires of the mains cord are terminated directly onto the PCB. Two insulated wires of the same gauge are connected from the PCB to the relevant terminals on the AC socket. Then connect the pot to the PCB and you are finished. Check all your wiring carefully against our circuit and wiring diagram.

Connect a fan to the speed control



and apply power. With the pot set fully clockwise the fan should run at normal speed. Now reduce the pot setting and the fan speed should reduce accordingly, allowing for some flywheel effect of the fan blades. You should be able to control the speed over a fairly wide range, subject to the limitations that we mentioned above.

Do not leave the fan in a stalled condition otherwise it may overheat due to the lack of cooling air passing through the motor.

Well there it is. A handy little accessory which will make your fan more useful on these hot summer nights. Sleep well.

Regulator gives mV accuracy without a meter:

Precision power supply

A precision, variable, regulated power supply can be a very useful device around the workshop. As a power supply it can be set to deliver a precise voltage without the need to tie up a voltmeter, while it may also serve as a voltage reference for checking other instruments.

by BRIAN DANCE


The simple circuit shown will provide an output voltage which can be set to within a few mV of any required value between 0 and +20V without the use of a meter. The output device provides built-in thermal shut-down and short circuit limiting, whilst the reference source ensures ultra high stability of the output voltage.

The REF-01 device provides an extremely stable +10V across the 10 turn helical potentiometer, VR1. In the prototype a Beckman Helipot with a 0.1% linearity was used so that the voltage tapped off by VR1 was within a few mV of the dial reading. (Editorial note: The REF-01 is made by Precision Monolithics, of California, USA, and is available in Australia from Cema Distributors, either direct or via normal suppliers. The Beckman Helipot may not be available in Australia, but units of similar style and quality are available, one of which is illustrated. This has a linearity of 0.25%, but 0.1% units are available at a higher price).

The LM295K alone has a gain of about one million but, as fed from one amplifier of the 358 inside a feedback loop it has a gain of two ($1 + R1/R2$). The output voltage is thus twice the voltage tapped off by the slider of VR1. The LM295K must be mounted on a heat sink; the output current is limited to about 1.5A, but more current can be obtained by paralleling a number of LM295K devices. (The LM295K is available from NS Electronics, either direct or via normal suppliers).

VR2, shown dotted, is an optional trimming device. Even without it, the voltage at pin six of the REF-01 will be within 50mV of 10V (or within 100mV for the REF-01C) and if R1 and R2 are close tolerance resistors, no trimming may be needed. However, VR2 can be included to trim this output voltage at the middle of the range to accurately match the readings of the VR1 dial.

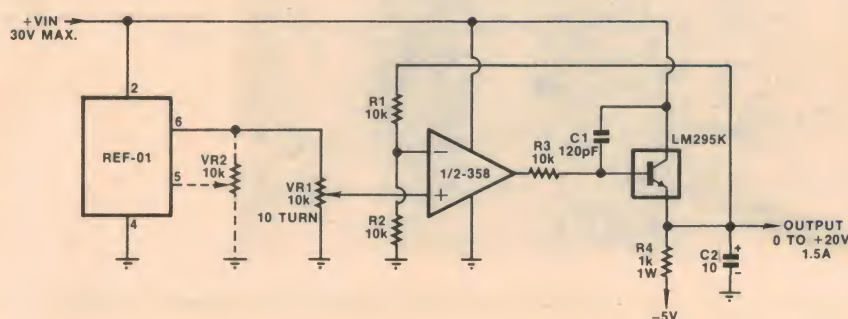The LM295K will operate correctly only if its quiescent current can pass to the output or to R4. If R4 is omitted and the output current is zero, the output voltage will float upwards to about +9V



The precision regulator circuit, which can be added to any power supply delivering up to 30V at 1.5A. Better immunity from line voltage variations can be obtained by pegging the voltage to pin 2 of the REF-01 with a zener diode. Apart from the electronic details, the most important aspect is the mechanical accuracy of the pot and dial used for VR1.



A typical 10-turn pot fitted with a 10-turn dial. Note the small window above main dial, in which is displayed the number of revolutions, and the lever which can lock the dial at any setting. Both pot and dial are made by Bourns of USA. (Photo by courtesy Radio Despatch Service.)

when VR1 is set for any smaller output than 9V. The use of the -5V supply can be avoided by connecting R4 to ground, but the minimum output voltage will then be approximately equal to the LM295K quiescent current (typically 1mA, maximum 5mA) multiplied by the value of R4.

If a dial calibrated from 0 to 20 cannot

be obtained, a dial calibrated from 0 to 10 can be used for VR1 and the reading doubled to give the output voltage. If R1 is shorted out, the output voltage of 0 to +10V can be read directly from a dial calibrated from 0 to 10.

The 358 amplifier maintains its linearity even when the non-inverting input falls to 0V, but if any other type of operational amplifier is employed, its negative supply should be connected to the -5V line. The two capacitors may possibly be required for stability, although the prototype operated satisfactorily without them.

The REF-01 output voltage is independent of the output current taken from the circuit; a current of 1A taken from the output produced an output voltage change of less than 1mV. A change of 10V in the power input line supply resulted in a 10mV change at pin 6; this could be reduced with a series resistor in the pin 2 line and a 15V zener diode from pin 2 to ground.

It was found the output corresponded with the dial readings to within ± 5 mV. The temperature stability has not been measured, but will be determined by the class of REF-01 device employed — typically three to 20 parts per million per °C. Output noise at very low frequencies was extremely small and difficult to measure.

Choose up to 4 of these software packages...FREE!

- Electronic Engineering
- Civil Engineering
- Mathematics
- Lab Chemistry¹
- Marketing/Sales
- Fluid Dynamics
- Statistical Testing
- Securities
- Oil/Gas/Energy
- Printer Utility²
- Programming Aids²
- Blackbody
- Astrology
- 59 Fun¹
- 3D Graphics
- Production Planning

\$20 value
2 FREE software
Pakettes with
purchase of
a TI-58C
see coupon



\$40 value
4 FREE software
Pakettes with
purchase of
a TI-59
see coupon



Free software from Texas Instruments can help make this year a little easier.

A special offer if you act now! From October 31st, to January 31st, 1980... that's your special opportunity to purchase one of the world's most advanced programmable calculators... and get up to \$40* worth of free software Specialty Pakettes in your choice of 16 different application areas.

TI's Specialty Pakettes are a new way to expand the usefulness of your TI Programmable 58C or 59. The convenient notebook format includes complete step-by-step program listings, applications notes, and sample programs. Just enter the program you need and you can put it to work right away.†

Four FREE SPECIALTY PAKETTES with the purchase of a TI Programmable 59. A \$40* value. Two FREE SPECIALTY PAKETTES with the purchase of a TI Programmable 58C. A \$20* value.

Both the TI Programmable 58C and 59 feature TI's exclusive Solid State Software™ plug-in library modules. Each 5,000 step module contains a wide selection of prerecorded programs. Optional library modules are available in a variety of fields, including engineering, science, statistics, and business.

The TI Programmable 59 has up to 960 program steps or up to 100 memories. Magnetic card read/write capability lets you record your own custom programs, or programs from your Specialty Pakettes. \$349.95*

The TI Programmable 58C features up to 480 program steps or up to 60

memories. And it has TI's Constant Memory™ feature that retains data and program information even when the calculator is turned off. \$164.95*

Act now!

Visit your college bookstore or other TI retailer for more information, and help you select the programmable that's right for you. Use the coupon below to take advantage of this special limited time offer.



- * Suggested retail price.
- † Specialty Pakettes do not require plug-in module or magnetic cards.
- ¹ TI Programmable 59 required.
- ² TI Programmable 59 with PC-100C or PC-100A printer/plotter required

Use this coupon to obtain your FREE Specialty Pakettes

- ☐ I've bought my TI-58C, send me these 2 free Pakettes
- ☐ I've bought my TI-59 send me these 4 free Pakettes

Send to: Texas Instruments Australia Limited,
PO Box 106,
North Ryde, NSW 2113

Texas Instruments will fulfil the offer you have selected above when you return this completed coupon, including serial number, and a dated copy of proof of your purchase verifying purchase of a TI Programmable 58C or 59 (whichever is applicable) between October 31st and January 31st, 1980. Items must be postmarked on or before February 6th, 1980 to qualify for this special offer.

Name _____
Address _____
City _____ State _____
Calculator Serial Number (from back of calculator) _____

Please allow 30 days for delivery. Offer void where prohibited by law.

Texas Instruments technology — bringing affordable electronics to your fingertips.

TEXAS INSTRUMENTS
AUSTRALIA LIMITED



**INTRODUCING
THE
FIRST 15" X 18"
STUDIO.**

Now you can have the essential functions and flexibility of multitrack recording in one compact, self-contained unit. It's called the Model 144 Porta-Studio™ and it lets you record basic tracks, overdub in sync and remix to stereo. On standard cassette tape.

TEAC engineers created a totally unique format for Porta-Studio. Four tracks in sync on cassette tape at 3-3/4ips. It's fast, simple, reliable and economical. Rehearse on it. Learn on it. Create on it. Just plug in a microphone or instrument and go to work on it.

Porta-Studio's versatile 4 x 2 mixer section gives you mic/line/tape switching, trim control, high and low EQ, fader, pan and Aux Send for each input. The failsafe group switching matrix lets you record on up to two tracks at the same time. And there's a master fader that gives you overall level control during recording and mixdown.

The full-logic cue system in Porta-Studio lets you hear everything you're doing all the time.




Input and tape cueing, monitoring for recording or mixdown are all available. And every signal can be metered. Coming or going.

Porta-Studio's drive system is built specifically for the rugged needs of multitrack recording. Transport controls are all solenoid-operated for faster, easier switching. And you get a built-in variable speed control that lets you add special effects, fix a flat note or solve timing and cueing problems.

You can work with Porta-Studio using nothing more than headphones. Or send the output through your home audio system. You'll also find the patch points and controls that let you use Porta-Studio

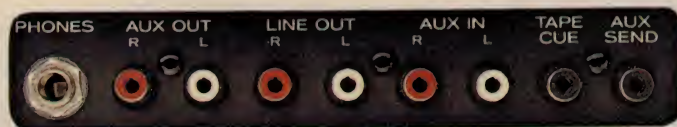with equipment like echo or delay units, equalizers and additional mixers.



So see your dealer for a demonstration of the very affordable Porta-Studio. Nothing else in the world puts so much multitrack function into so small a package.

TASCAM SERIES

TEAC Professional Products Group

* Recommended Retail Price \$1275.

TEACAUSTRAALIAPTY. LTD., 165 Gladstone Street, South Melbourne, 3205. Phone 699 6000. TASCAMDEALERS: VIC. Douglas Hi-Fi, Syntec, Brashs, Klarion. N.S.W. Douglas Hi-Fi, Syntec, Roland Aust. QLD. Stereo Supplies. S.A. Truscott-Electronics, W.A. Audio Centre, Arena Dists. ACT. Kent Hi-Fi. TAS. Audio Services, Burnie; United Electronics, Launceston; Quantum Electronics, Hobart.

(LEA)3370/TEA/EA



The picture was produced by computer of a video image and plotted on a flat bed plotter by John F Rose Graphics Company Pty Ltd.

JOHN F ROSE COMPUTER SERVICES PTY LTD has formed.

JOHN F ROSE GRAPHICS COMPANY PTY LTD to undertake research and development of professional standard low cost computer colour graphics and animation systems.

Although our development has taken definite directions, we would like to hear from outside graphics users as to your needs and requirements.

To this end we are establishing a GRAPHICS DEVELOPMENT GROUP and we invite all interested parties to contact us, in writing, at PO BOX 745, CROWS NEST 2065.

Demonstrations of systems are available, by appointment, at our St Leonards showroom.

JOHN F ROSE COMPUTER SERVICES PTY LTD supply business and special applications systems using equipment ranging from floppy disk to hard disk drives.


John F Rose Computer Services Pty Ltd
are the sole Australian distributors for
NDK S-2000 Dot Matrix Printers
MICROMATION Computers
NNC Electronics Inc

We are stockists of
ALTOS, CROMEMCO, VECTOR GRAPHICS, DIABLO,
HAZELTINE, SIEMENS, MICROPOLIS, SHUGART,
MICRO PRO INTERNATIONAL, DIGITAL RESEARCH,
CO-ORDINATED DESIGN and
STAR SYSTEMS PRODUCTS.

Send for our product/system list.

PO Box 817,
Crows Nest 2065

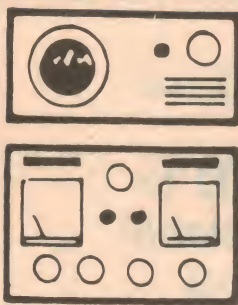Telephone 439 1229, 439 1628
Telex AA27901



The Serviceman

First aid (and last gasp) for an old TV set

By way of a change from my usual run of intermittents, mysteries, and curly ones from the work bench, here is what might best be described as a busman's — or serviceman's — holiday. Or, if you like, how to service a TV set with only the tools from the boot of the family car. (Who needs a soldering iron or multimeter?).

To be honest, this is not a recent story, it has been sitting in my files for well over 12 months now, and it was several months after the incident that I wrote it. I have passed it over on several occasions when more topical stories rated a higher priority. At least it's topical at this time of the year!

It all started when I decided to take Mrs Serviceman and other members of the family for a holiday on the NSW South Coast — to a very small town which boasts some facilities for boating, fishing and swimming, but with no TV serviceman for miles around.

Knowing this, and having a few acquaintances in the area, I quite deliberately omitted to pack even a single item from my own service kit. I have learned from past experience that one can all too easily spend hours on TV service "dogs" for friends instead of spending the holiday in the way it should be spent — "beside the seaside ..."

When I inquired about TV in the holiday cottage, the owner assured me that it contained an old but serviceable black-and-white receiver coupled to an outside aerial. "It takes a while to warm up", he added, "but it goes orright!"

I guess I should have been warned. Sets that "take a while to warm up" are usually sets with a large complement of old, leaky capacitors and off-tolerance resistors — all liberally coated with gunk — which struggle towards some kind of workable state only after the prolonged application of voltage and temperature.

I did consider taking along a portable set of my own but, by the time Mrs Serviceman had packed all the things she regarded as essential, there was barely room for the kitchen sink! When we finally did arrive at our destination and I had time to switch the TV set on, I had

every reason to regret the omission.

The set was an ancient STC model, in a (once) handsomely designed and polished console cabinet, very deep, but with a 21-inch tube that still managed to protrude from the back. In its heyday, it had obviously been someone's pride and joy.

When I switched it on, I was greeted a few moments later, by a sharp crack as something "went over" — presumably due to the high warm-up voltage. Since it was not repeated, I left the switch on and waited for the picture to come up. Unfortunately, the old set was barely able to produce a glow from its screen, with a picture that showed very little inclination to lock either vertically or horizontally. The sound wasn't too hot, either!

Thinking of the landlord's warning, I left it on for a quarter-hour but it was still far from "orright": brightness and contrast had improved a trifle but we watched the news only by dint of riding the two hold controls. Even then, the picture seemed to be pulsating in brightness. Clearly, corrective

measures would have to be taken if we were going to have something to while away the evening hours. But how do you service a TV set without equipment?

At that point, I called round to the local general store to ask about the possibility of hiring a TV set for the next couple of weeks but the inquiry was met by a sad shake of the head. I was on my own!

There was just once chance that some of the troubles might be due to fouled valve sockets so, next morning, I looked out the only two tools from the car kit that were likely to be useful — a pair of long nosed pliers and a screw-driver with interchangeable blades.

Taking the back off the set, I peered inside ready to spot the arc-over and switched on. It went over right on cue inside a valve which turned out to be a 6AQ5 — probably the audio output stage. I switched off, pulled the valve out and tapped it smartly pins-down on the table, hoping to dislodge the cause of the flash-over. When I tried again, I was greeted with quite a pyrotechnic display which fortunately didn't last too long. Obviously there would be no more tapping — the valve would be better left alone!

Turning back to the picture circuits, I identified two or three valves that would most likely include the sync separator and the oscillators. One of them, in a sprung socket, seemed to be virtually frozen in and I had to prise it out carefully, in case too large a pull should remove the socket as well!

This done, I pushed the valves back into their sockets and worked them around a bit to clear poor contacts.

When I switched the set on once again, I was delighted to find that I could now lock the picture for a few minutes at a time, so that it was at least watchable. True, it lacked brightness and contrast, and the tuner didn't seem to make much sense, but at least the picture moved and talked!

Suitably encouraged, I visited the local general store and managed to buy a spray can of WD 40, which could be expected to de-louse and lubricate the sockets and expel moisture.



"You want me to fix it once and for all?
I'll do that, madam. I'll do just that!"
"TV Times")

One by one, I removed the valves, sprayed and wiped between the pins, sprayed the sockets and re-inserted the valves. I stress the "one by one", because it is all too easy to get valves mixed up, in the absence of a circuit and, in some cases, the absence of a decipherable type number on the glass envelope.

While doing this, I noticed that the area around the picture tube's EHT connection was completely fouled and, this too, was treated.

TUNER FIRST AID

And the reward for all this? A picture that had reasonable brightness, contrast and stability and that did seem to improve gradually, the longer we watched it. But, alas, the tuner was far from satisfactory and, to obtain a picture at all, one had to wiggle the switch and fine tune, often ending up with rotor deliberately partly out of its de-tent position. This looked like being a problem indeed because the tuner was inaccessible inside the cabinet and a frozen-on fine tune knob would have prevented the chassis being withdrawn. More immediately, it denied access to the cores through the front. So I sprayed it with WD40 and went for a swim.

That night, I managed to get the fine tune knob off, and, directing the spray through the valve sockets, other holes and now exposed core access holes, I gave the tuner a good drink, meanwhile working the rotor and fine tune controls.

And what a difference it made. Evidence of contact trouble disappeared and, using a screwdriver blade that was fortunately long enough and fine enough, I was able to peak the oscillator cores properly. As I had suspected, they were well out of position and the picture started to look really promising — except that at times it still seemed to oscillate somewhat in brightness. Why?

I woke up to the cause next morning when examination of the aerial showed that the ribbon down-lead had come out of the spacers and was flapping against the steel mast in the prevailing nor-easter. I couldn't climb the mast but a scrap of rope to a nearby nail was sufficient to hold the ribbon clear and steady, and it effectively steadied the picture.

There remained only the sound — somewhat distorted and with an obvious content of frame buzz. Most likely the discriminator core needed touching up — but where was it?

Looking along the valve line-up it seemed likely that a large IF transformer that I could feel but not see, with the chassis in the cabinet, would be the discriminator transformer. I could only hope sincerely that the designer had thought to make the secondary core the accessible

one.

And this seemed to be the case. Working by feel rather than sight, I turned the core in and out by repeatable amounts and found that a full turn in gave the result required — clean sound and no frame buzz. And at that point I called it a day.

I think that the set was still well short of optimum because, despite its generous IF line-up, it still had no contrast to spare, irrespective of the AGC adjustments at the back. But as I settled back and watched the sport, I was thankful for whatever the fates that made it possible to achieve an acceptable result with such limited facilities — screwdriver, pliers and a can of WD40!

But there has to be an epilogue to the story affecting this set and thousands of others of like vintage around Australia.

I was lucky in being able to extract temporary advantage from a superficial treatment but in no sense was the set "fixed". If it was to be put into a reasonably reliable state it would have to be given a complete on-the-bench overhaul. I would expect something like the following:

- Remove and dismantle the tuner, cleaning away the gunk that my WD40 treatment had merely loosened. Check all contacts and biscuits, valve sockets etc and reassemble. Either that or fit a replacement tuner.
- Check the video IF chain, almost certainly replacing off-tolerance resistors and leaky capacitors in the supply and AGC systems. Replace valves as necessary and possibly re-align.
- Ditto for sound IF system and replace the 6AQ5 output valve.
- Replace all off-tolerance resistors and leaky capacitors in the sync separator and vertical oscillator/-output stages to obviate residual vertical rolling tendency.
- Check and clean the entire line output and EHT system and determine why the picture did not come straight up to normal brightness. Perhaps the picture tube itself is reaching the end of its life!
- Check over other components and controls, reinstall in cabinet, set up picture for correct geometry, etc.


Now ask yourself how much all that is going to cost at normal shop rates and you will have some idea of the dilemma which faces owners of ageing receivers and servicemen who have to cope with them. They seem too good to discard but the cost of a complete overhaul equally seems prohibitive. The tendency therefore, is to keep patching them up until client or serviceman gives up.

It's bad enough for sets in the suburbs but what about those like the one I describe — 20 or more miles from the nearest service centre? No wonder new portable TV sets are selling so well! ☺

We've got everything in the heart of electronics



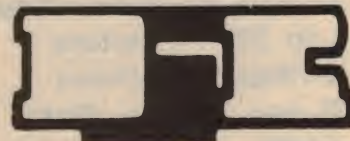Look — we've got most of your electronic components at the one central location. Come on in and inspect our range that includes such things as PC Boards for "Electronics Australia" and "Electronics Today" projects including the ETI 449a metal detector. Drop in anytime and browse through our self service component outlet — only 2 minutes from the Town Hall Station.



**DAVID REID
ELECTRONICS
PTY. LTD.**

127 York St, Sydney.
Telephone 296601

GRADUATE TO *University* TEST INSTRUMENTS

The non-contact EZ-Scan unit gives an immediate visual indication of voltage, with or without current flowing at distances up to 15cm from the source. Battery powered and all solid state, the unit is small enough to be carried in a pocket, and tough enough to leave in a tool box.

To find a break in a cable, a bad earth, a faulty fitting or just to know if its live — use the EZ-Scan. For all unshielded AC electrical systems, 60V and higher.

Available from leading wholesalers or fill out the attached coupon & post to

University Graham Instruments Pty Ltd

PO BOX 204, Enfield, NSW 2136
PHONE (02) 53 0644 TELEX AA21398

Name
Address
Qty Model EZ-Scan Value


Enclose cheque or Postal Note and please allow \$2.00 for packing & post.

EZ SCAN. *The ideal Christmas gift for every safety minded person.*

HANDYMAN — HOBBYIST — TECHNICIAN — PROFESSIONAL — STUDENT
— SERVICEMEN — INSPECTORS.

DEAD OR ALIVE?

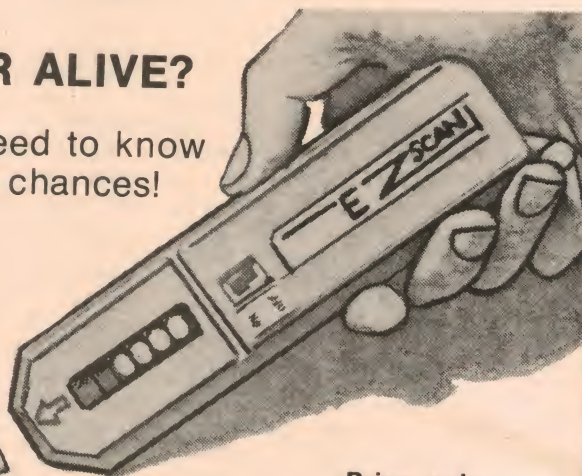When you need to know
don't take chances!



Price only
\$39.00

DISCO — SOUND — LIGHT



XMAS-JAN SALE



USED DISCO CONSOLES

- | | | | |
|--|--------|---|------------------|
| ● Stereo Discos 200 x 200 Watts | \$1500 | ● RCF 100 Watt Bass Speakers | \$90 |
| ● Mono Discos 200 Watts | \$980 | ● Goodman 50 Watt Horns
W/In-built Crossover | \$65 |
| ● Rope Lights 30' 5 Colours: Red
— Blue — Green — Yellow —
Multicolour | \$125 | ● Peizo Bullet Radiators | \$12 |
| ● SAC4 Chasers (New) | \$135 | ● 200 x 200 Watt Soundout Power
Amps | \$540 |
| ● 8 Way Space Beacons (New) | \$500 | ● 200 Watt Mono Soundout
Power Amps | \$300 |
| ● 4 Way Space Beacons (New) | \$380 | ● Disco Mixers 3 Types from \$350
to \$650, 20 Pair Multicore Cable
Twin Shielded/PVC covered | \$5
per metre |
| ● Dry Ice Fog Machines (New) | \$320 | | |
| ● Bubble Machines (New) | \$130 | ● Belt Drive T/TW/Mag Cart | \$54 |
| ● Lito 250 Projectors
W/Radiators (New) | \$250 | | |
| ● Super Freeze Flash Strobes
(New) | \$165 | | |

CASH-MORE ENTERPRISES WISHES YOU A MERRY CHRISTMAS AND A PROSPEROUS NEW YEAR

FOR BROCHURES AND PRICE LIST WRITE OR CALL TO

356 LIVERPOOL ROAD, ASHFIELD, NSW 2131

TEL, 798 6782, 799 3424, 798 5647

CIRCUIT & DESIGN IDEAS

Interesting circuit ideas and design notes selected from technical literature, reader contributions and staff jottings. As they have not necessarily been tested in our laboratory, responsibility cannot be accepted. Contributions to this section are always welcome, and will be paid for if used.

Conducted by Ian Pogson


Accurate motor speed control

I recently built a robot using an on-board 2650. Accurate motor control is essential and I designed a circuit to suit. It may be of interest to other readers. The circuit allows a computer I/O port with a DAC (digital to analog converter) to control motor speed. The output voltage can vary the mark-space ratio of the 555 over the widest possible range.

In effect, the 339 comparator replaces the top comparator in the 555. When the capacitor voltage reaches the analog input voltage, the comparator goes high causing the 555 to time out. The maximum analog voltage is $V_{CC}-1.5$. The 555 is triggered by a very short pulse from a second 555. To prevent output spikes at full mark, the zener ensures that the capacity never reaches an analog input greater than 3.3V. The motor is turned on and off at 200Hz, the speed being proportional to the mark-space ratio.

A second motor needs only one extra 555 as the astable can be shared and the 339 is a quad comparator. Do not forget the pullup resistor on the comparator as it is open collector. For a linear relation between digital word and mark-space ratio, replace the charging resistor with a constant current source.


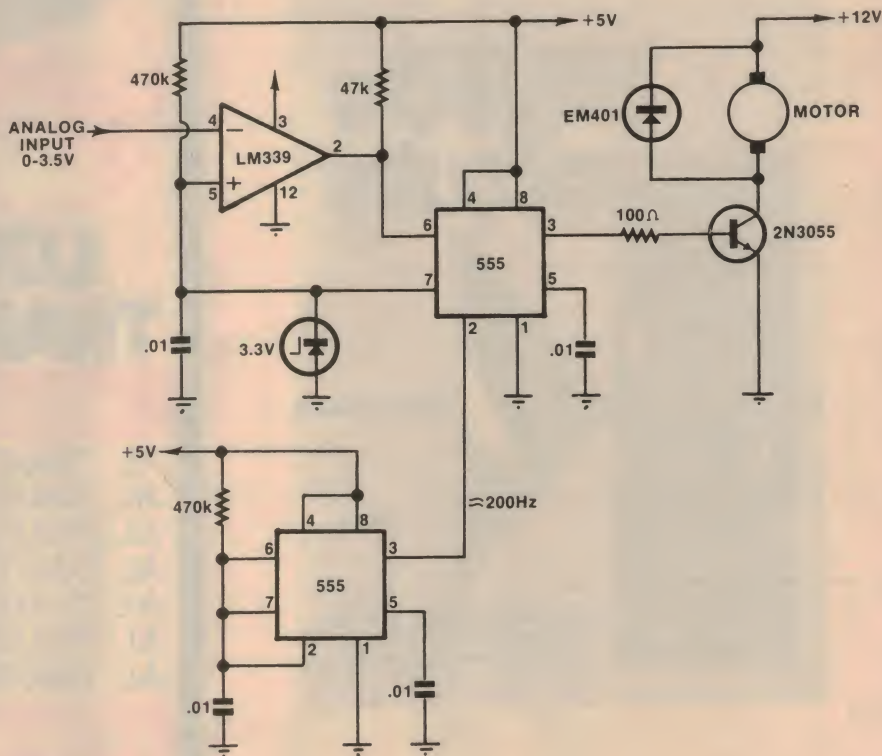
(By Mr A. Peek, 10 Gale Street, Woolwich, NSW 2110.)



A simple frequency doubler

This very simple circuit generates one pulse for each transition of the input from low to high and from high to low. Since one input of the exclusive OR gate is connected directly to the drive and the other is connected via a delay, it follows that after each transition there will be an interval during which one input is high and the other low — ergo, output high.

The delay network components are selected to suit the particular circumstance, typical values being 4.7k and 0.1μF. The CRO photograph was taken with $C = 680\text{pF}$ and $R = 4.7\text{k}$. The input frequency was 125kHz. Although a CMOS device is shown, other logic families could be used equally well if restraints on levels and rise times are observed. Input waveforms other than rectangular could possibly be used.

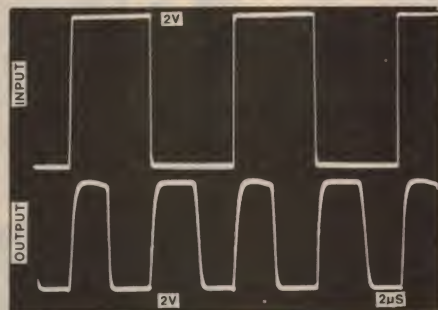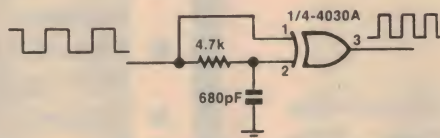

(By F. J. Maher, CSIRO Division of Chemical Physics, PO Box 160, Clayton, Victoria 3168.)


Adjustable power supply up to + or -12V and 800mA

The circuit shows a power supply which is adjustable up to 12 volts with either positive or negative polarity. The current source is also adjustable up to about 800mA and it is short circuit proof. I have used this circuit successfully for an antenna rotating motor to turn in either direction. I have also used it as a power supply for either polarity as the need has arisen.

The output voltage is set by means of the 500 ohm potentiometer, between the limits of + and -12V, with 0V in the mid position. When the potentiometer is turned towards the negative side, the PNP transistor conducts, while the NPN transistor is blocked. The reverse applies when the potentiometer is turned in the opposite

Don't miss this

PROJECTS and CIRCUITS No. 2

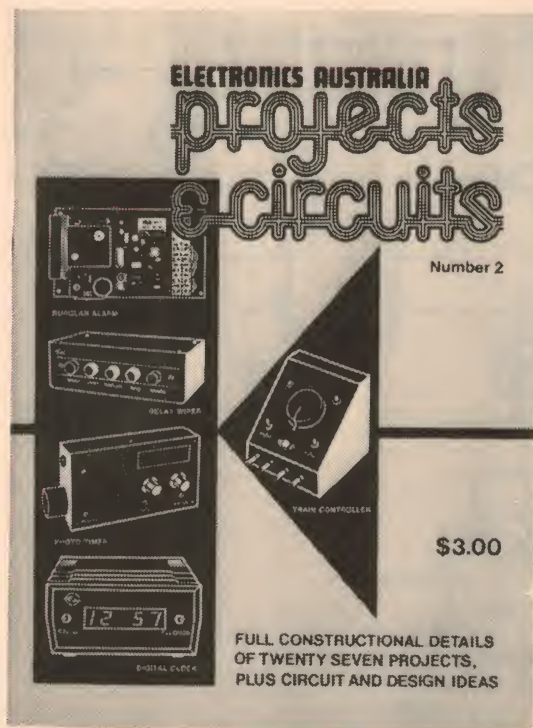

27 DO-IT-YOURSELF PROJECTS FROM "ELECTRONICS AUSTRALIA"

You can't afford to miss out on this exciting new book from "Electronics Australia". Here are just a few of the projects it contains: remote TV headphones, multi-band vertical aerial, roulette wheel, radar burglar alarm, model train control, voice-operated relay, transistor tester, water level alarm ... plus many more. Get your copy now!

Available from:
"Electronics Australia", 57 Regent St, Sydney.
PRICE \$3.00 OR by mail order from "Electronics Australia", PO Box 163, Beaconsfield 2014. **PRICE \$3.60.**

ARLEC



LOW PROFILE TRANSFORMERS with 40% Extra Power

AL 7VA/6	6V C.T. or 3V
AL 7VA/9	9V C.T. or 4.5V
AL 7VA/12	12V C.T. or 6V
AL 7VA/15	15V C.T. or 7.5V
AL 7VA/18	18V C.T. or 9V
AL 7VA/24	24V C.T. or 12V
AL 7VA/30	30V C.T. or 15V

All Models Rated At 7 VA.

Features:

- Insulated to AS C126
- PCB Mounting Pins
- Pin Compatible with other Current Models
- Mounting Clamps available for non PCB applications
- Modern Welded Stack
- Fully enclosed windings
- S.E.C. Certificate of Suitability to A.S.C. 126
- Size L.49mm, W.35mm, H.34mm.
- Weight 0.23 Kg

Also available in 10VA with similar dimensions for O.E.M. Quantities.

ARLEC

A MEMBER OF
THE A+R-SOANAR
ELECTRONICS
GROUP

A+R Electronics Pty Ltd

30-32 Lexton Road, Box Hill, Vic., 3128, Australia. Telex: 32286.

VICTORIA: 89 0661

N.S.W.: 789 6733

Sth. AUST.: 51 6981

QUEENSLAND: 52 5421

WEST AUST.: 381 9522


HONG KONG: (3) 89 1271

direction.

By means of the respective transistor in the current circuit, with its 100 ohm preset potentiometer, the circuit is protected against overload. The voltage drop across the one ohm resistor will block the transistor when the current exceeds the preset value. The circuit works as a constant current source up to about 800mA.

I made the two one ohm resistors from a piece of heater element but one ohm resistors obtained commercially could be substituted. The two-power transistors must be mounted on a heat-sink of adequate proportions.

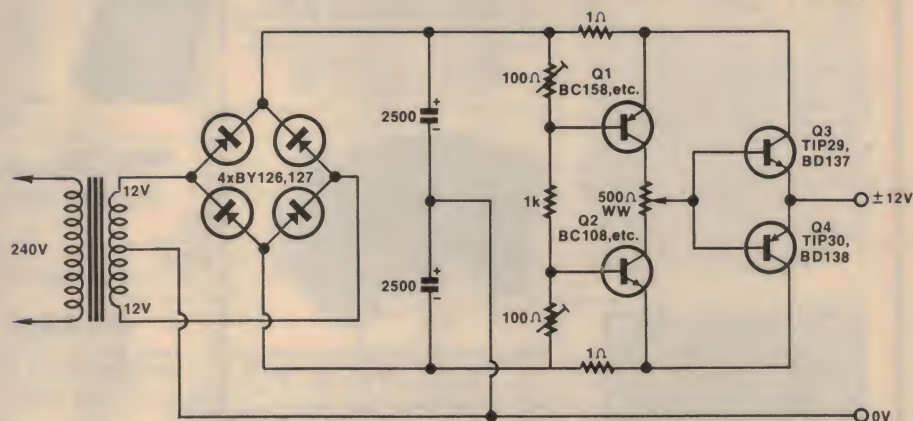(By Mr W. R. Jongeneelen, 463 Hawthorne Road, Bargo, NSW 2574).



A novel vye to make

Pictured is a novel type of "vyce" I have developed for holding pipe, tubing and rod stock. It can be built in a variety of sizes, and can firmly hold anything from large-diameter PVC conduit to 3mm welding rod. It can even hold thin-walled stainless steel pipe, without the pipe being deformed.

As you can see the basic idea is two pieces of steel strip, bolted together with spacers between them. The strips have an identical series of holes bored in them, to suit the stock to be clamped, and are then case-hardened.


A number of "J"-shaped hooks are

used to perform the actual clamping, as shown. The hooks are made from rod of a suitable diameter, and the hook portion radiused to suit the diameter of the stock to be clamped. They are threaded on the straight end to take a hex nut and flat washer. Each hook is used with a short length of steel strip, to couple it to the sides of the main vyce strips. The nut is simply tightened until the stock is held firmly.

I have made up the vyce in a couple of versions, and they seem to work particularly well. As the stock is clamped in balanced shear mode, even thin-walled

tubing may be held firmly without damage. I hope other readers find it as useful as I have.

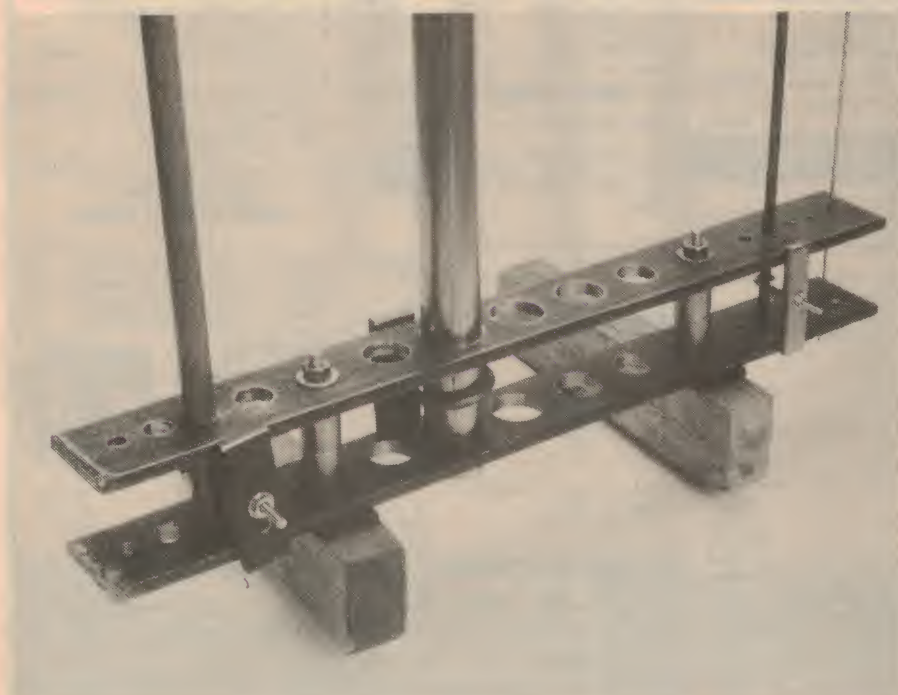(By Mr M. Ronell, 14 Griffen Street,
Surry Hills, NSW 2010.)



NEW EDITION

FUNDAMENTALS OF SOLID STATE



ONLY
\$3.50
+ 60c
p&p

Fundamentals of Solid State has been reprinted, revised and updated showing how popular it has been. It provides a wealth of information on semiconductor theory and operation, delving much deeper than very elementary works but without the maths and abstract theory which make many of the more specialised texts very heavy going. It begins with atomic theory, diode types, unijunction, field effect and bipolar transistors, thyristor devices, device fabrication and microcircuits. A glossary of terms and an index complete the book. Fundamentals of Solid State has also been widely adopted in colleges as recommended reading – but it's not just for the student, it's for anyone who wants to know just a little bit more about the operation of semiconductor devices.


Available from:
"Electronics Australia", 57 Regent St,
Sydney. **PRICE \$3.50** OR by mail order
from "Electronics Australia", PO Box
163, Beaconsfield 2014. **PRICE \$4.10.**

6800**DESIGNER BOARDS
MODULES PROTO BOARDS***Ideal for expanding D2 kits:***STEWART ELECTRONICS
9 SLOT BACKPLANE FOR M6800**

- Double sided board
- Active or passive termination
- Provision for 10 bypass caps
- Exorciser and D2 compatible
- Bare PCB with instruction sheet \$ 39.50
- Completely Assembled \$110.50

EXTENDER CARD

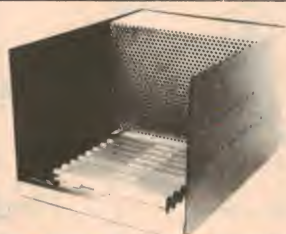6800 — D2 — Exorciser Compatible
43 x 43 way double sided fibre glass board.
Hard gold plated contacts. Gold plated
socket \$26.50



Stewart Motorola D2 Exorciser Compatible
Card Cage with provision for shielded
power supply. See E.A. Feb 1979 for full
details shown with our 9 slot mother board
fitted. Cage complete with 18 card
guides \$39.50

LOW COST VDU**VIDEO DISPLAY BOARD
D2-6800 COMPATIBLE**

- Electronics Australia Aug 1978
- 16 lines 32 characters
- Memory mapped — software controlled.
- Complete Kit \$56.50
- PCB plated through holes \$22.50

6800 16K STATIC RAM

- Uses 2114 1K x 4 STATIC RAMS
- Only 1.2 @ 5 V typical for 15K
- Motorola Exorciser Bus as on D2.
- 8K blocks switch addressable.
- PCB plated through with solder resist + support ICs Kit \$111.00
- 8k kit complete 450nS \$190.00
- 16k kit complete 450nS \$270.00

**MEM2 16K S100 STATIC
MEMORY BOARD**

- Uses 2114 RAMS
- Wait state generation
- Addressed on 4K boundaries
- Complete documentation
- Silk screen parts layout
- Bare board W/- documentation \$39.50
- 2114 450 nS \$ 5.95
- Manual only (refundable with board purchase) \$ 5.00
- Complete Kit (less 2114s) \$95.00

Z80 CENTRAL PROCESSING UNIT**Software:**

The Z-80 CPU will accept most existing 8080 software without modification including Assemblers, Debuggers, Disk Operating Systems, Basic and Fortran.

Support:

The Z-80 CPU is fully S-100 compatible and supported by a full range of peripherals from both Ithaca Audio and other vendors.

Features:

- On-board 2708 EPROM
- Power-on-jump to any 4K boundary above 32K-RAM, ROM, or the on-

Z80 CPU IC \$18.50

Z80 Technical Manual \$8.50 tax exempt.
Z80 Programming Manual 288 pages. One full page on every instruction plus much other data \$12.50 tax exempt Plus \$3 postage.

- Front panel-less operation allowed by on-board run-stop flip-flop and optional generation of MEMORY WRITE.
- Selectable wait states on the following cycles: M1 cycle

Memory Request cycle On-board ROM cycle Input cycle Output cycle

- Selectable 8080 or Z-80 I/O addressing modes
- DMA Grant tri-states all signals from processor board
- 8224 clock generator provides 8080 like 1 and 2 for the S-100 Bus.

PCB with manual \$44.50
Manual only (refundable when board purchased) \$5.00
Kit complete with manual 4MHz \$125.00
Built and tested 2MHz board \$175.00

All items plus 15% sales tax unless otherwise marked. Prices subject to change without notice.
All orders plus packing and freight \$2 small items \$5 large and heavy parts. Registration and insurance extra.

COMPUTER COMPONENTS**Hexadecimal Keypad**

\$17.50/each



19-key pad includes 1-10 keys. ABCDEF and 2 optional keys and a shift key

Ideal For Dream Project

**LEDs Cheaper
by the 100**

Red 100/\$12.00
Green 100/\$18.00
Yellow 100/\$18.00
● 2" dia mounts 3c extra

DREAM**ELECTRONIC AUSTRALIA
MICROCOMPUTER PROJECT**

Kit for main board (including programme 2708)


\$90.00

PCB (fibre glass) only \$14.50
2708 programmed \$15.50
Key Pad 19 keys \$17.50
Kit (less key pad) \$90.00
PCB for power supply \$4.50

DIP SWITCHES

(On-Off Contacts)

4 positions \$1.50
6 positions \$1.70
8 positions \$1.80
10 positions \$3.45

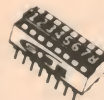**COMPUTER GRADE
CAPACITORS****NEW RANGE ALL EX STOCK**

6.800MF 16V \$ 5
10.000MF 16V \$ 7
10.000MF 25V \$ 8
10.000MF 40V \$ 10
22.000MF 25V \$ 10
22.000MF 40V \$ 18
33.000MF 16V \$ 10
68.000MF 16V \$ 17
100.000MF 10V \$ 17

10 TURN POTENTIOMETERS

Stock resistance values

50R, 100R, 200R,
500R, 1K, 2K, 5K,
10K, 20K, 50K,
100K.

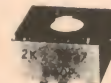
Spectrol model 534 1/4" shaft.

Price 1-9 \$6.75
10 + values may be mixed \$5.75

MULTIDIALS

Dials to suit 10 T Pots

Model 21 1.8" dia \$ 9.50
Model 16 9" dia. \$ 8.50
Model 18 1" x 1.75" dia \$16.50


**CERMET SINGLE
TURN TRIM POT**

Spectrol model 63P
ACTUAL SIZE

STOCK VALUES

10R, 20R, 50R, 100R, 200R, 500R, 1K,
2K, 5K, 10K, 20K, 50K, 200K, 500K,
1M, 2M.
1-9 \$0.85
10-99 \$0.75
100 \$0.65

Values may be mixed.

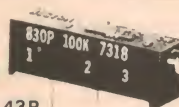**20 TURN
CERMET
TRIM POT**

**SPECTROL 43P
ACTUAL SIZE**


STOCK RESISTANCE VALUES

10R, 20R, 50R, 100R, 200R, 500R, 1K,
2K, 5K, 10K, 20K, 50K, 100K, 200K,
500K, 1M, 2M.
1-9 \$1.10
10-99 \$0.90
100 \$0.80

Values may be mixed.

P.C. EDGE CONNECTORS

S100 gold plated wire wrap \$6.50
S100 solder tail \$5.90
D2 Motorola bus
43/86 solder tail \$6.34
43/86 gold plated wire wrap \$7.40

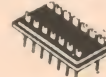DIP PLUGS

Ideal for use with flat
ribbon cable or to
mount components on

14 pin \$0.56 24 pin \$0.94
16 pin \$0.58 40 pin \$2.00

POWER TRANSFORMERS

**SPECIALLY DESIGNED FOR
MICROCOMPUTERS**

- See Feb 1979 EA for full details
- Good regulation Electrostatic shield
- SE 805
8V @ 5A 2x15V @ 1A \$16.50
- SE 810
8V @ 10A 2x15V @ 1A \$19.50
- SE 820
8V @ 20A 15V @ 1A
15V @ 3A \$29.50

**Gold Plated
WIRE WRAP PINS**

Per Hundred

WWT 1 Slotted Head \$5
WWT 2 Single Sided \$5
WWT 3 Socket Head \$15
WWT 4 Double Sided \$5

**COMPUTER
COOLING FANS**

Muffin fan 4 1/2" square

110V \$26.50

240V \$24.50

Sprite fan 3 1/2" square

110V \$26.50

240V \$24.50

Range of larger fans available. Send for
details

STEWART ELECTRONICS**33 SUNHILL ROAD, MT WAVERLEY 3145****Phone (03) 277 0622****Bank Card Accepted.**

**Mon.-Fri. 9am-6pm
Sat. 9am-12noon**

Give your computer an RS-232C interface

Many printers, video terminals and other peripherals are designed to communicate with the computer via an RS-232C interface. This article gives you a quick rundown on the RS-232C standard, and shows how you can provide your home computer with this sort of interface at low cost.

by JAMIESON ROWE

What do you know about the RS-232C interfacing standard for data communication? Perhaps not too much, although most computer hobbyists and personal computer owners have probably seen references to it in advertisements for high speed printers, video terminals and other fancy peripheral devices. But you won't find much about it in textbooks.

Perhaps you've gained the impression that RS-232C interfacing is fairly complicated, and not suitable for small microcomputers. Or you might think that you can't make use of a printer or terminal designed for RS-232C interfacing, because it would be too hard to connect to your microcomputer. If either is the case, you're in for some good news.

The fact is that in the form you'll normally meet it, RS-232C interfacing is really quite straightforward. Not only that, but you can provide your microcomputer with a basic RS-232C interface very easily and at low cost. In this article we're going to tell you how it's done, so read on.

First of all, just what is an RS-232C interface? Well, it's a set of connections between two pieces of equipment,

designed to allow them to "communicate" by exchanging data — numbers, messages and so on. Moreover it's a set of connections which allow the exchange of data according to the specifications set down in Standard RS-232C, published in August 1969 by the Electronic Industries Association (EIA) in the United States.

As a lot of things have happened in electronics since 1969, the RS-232C standard is now regarded as obsolete. The EIA has brought out later standards, like RS-449 (October 1977), which allow better use to be made of modern technology. But a lot of lower-speed data communication still conforms to the basic RS-232C standard, and a lot of modern equipment is made to work at the lower speeds. So from the practical point of view, RS-232C is still quite current.

Basically, RS-232C covers "serial" data communication — where the code bits making up the characters of the message are all sent one-by-one over a single circuit. This is in contrast with "parallel" communication, where each of the bits of the characters is sent on a

separate circuit (although the characters themselves are still sent one after the other).

Although the full RS-232C specification covers both synchronous and non-synchronous or "asynchronous" communication, most of the RS-232C interface circuitry you are likely to come across will probably be designed for asynchronous operation.

All this means is that each group of code bits representing a letter, numeral or other character in the message is preceded by a "start" bit, whose purpose is to tell the receiving end that a new character code is arriving. At the end of each code group there is also one or more "stop" bits, which provide

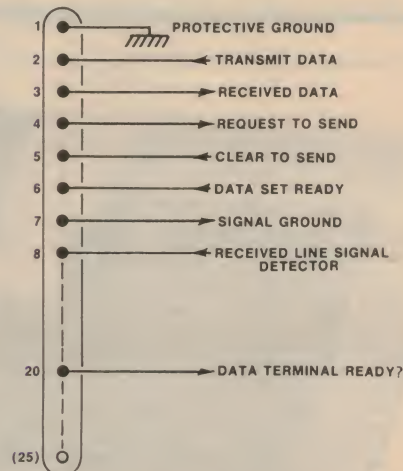


FIG. 1: BASIC RS-232C CONNECTOR SIGNALS

TABLE 1: The basic RS-232C electrical specification

Communication rate	0 — 20,000 bits per second
Driver output voltage levels, maximum no-load	-25V logic 1 +25V logic 0
Driver output voltage ranges for loads between 3k and 7k ohms	logic 1: -15V (7k) — -5V (3k) logic 0: +15V (7k) — +5V (3k)
Driver output current, short-circuited	500mA maximum
Driver output impedance with power off	300 ohms minimum
Maximum driver output slew rate	30 volts per microsecond
Receiver input resistance	7k ohms maximum, 3k ohms minimum
Effective receiver input capacitance	2500pF maximum
Maximum receiver input voltage range	-25V to +25V

a brief pause between characters to allow for any timing differences between the sending and receiving ends.

At this stage, those of you with hobby computers may well be wondering how an RS-232C interface compares with the familiar "20mA current loop" interface, which your system probably has at present. What is the difference?


The main difference is that the RS-232C system uses voltage levels to represent the two digital truth values, rather than current levels. The digital 1 or "mark" level is normally represented by a negative voltage level, while digital 0 or "space" is represented by a positive voltage level.

The voltage levels are not given



Cromemco COMPUTER SYSTEMS

TOMORROW'S COMPUTERS NOW

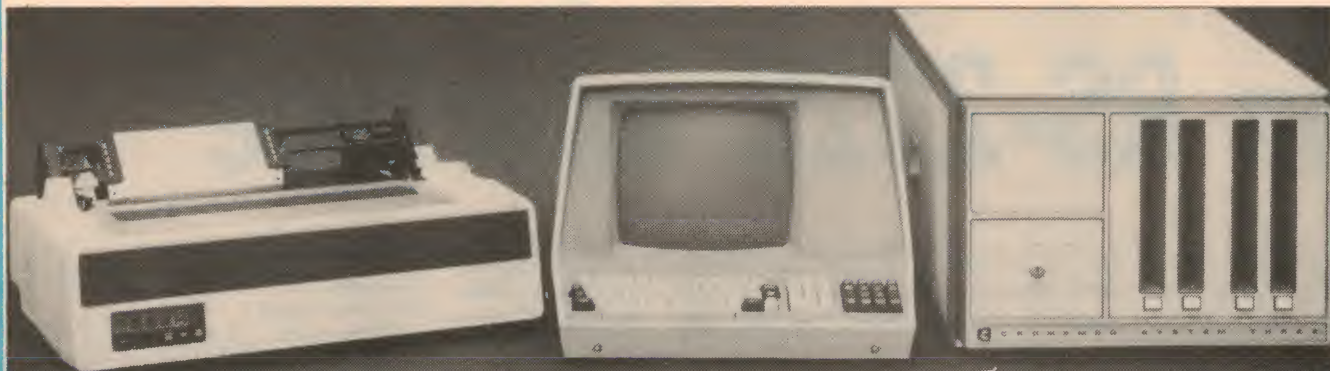

ADAPTIVE ELECTRONICS NOW OFFERS THE SUPERB RANGE OF **CROMEMCO** COMPUTER SYSTEMS, PERIPHERALS AND SOFTWARE, INCLUDING SOFTWARE SUPPORT AND PROFESSIONAL HARDWARE BACK-UP.

SYSTEM THREE FEATURES

- Fast Z-80A microprocessor
- RAM expansion to 512k Bytes
- 2 or 4, 8 inch disc drives
- 21 slot S-100 bus
- Printer interface
- RS-232 or 20mA serial interfaces
- Excellent service access


COMPREHENSIVE SOFTWARE SUPPORT

- Disc operating system (CP/M compatible)
- 16k disc extended BASIC
- Multi-user BASIC
- COBOL compiler
- FORTRAN IV compiler
- Z-80 macro-assembler
- Word processing and Data base management

AE ADAPTIVE
ELECTRONICS P/L

77 Beach Rd, SANDRINGHAM, Victoria,
Australia 3191

Telephone (03) 598 4422. Telex 35666

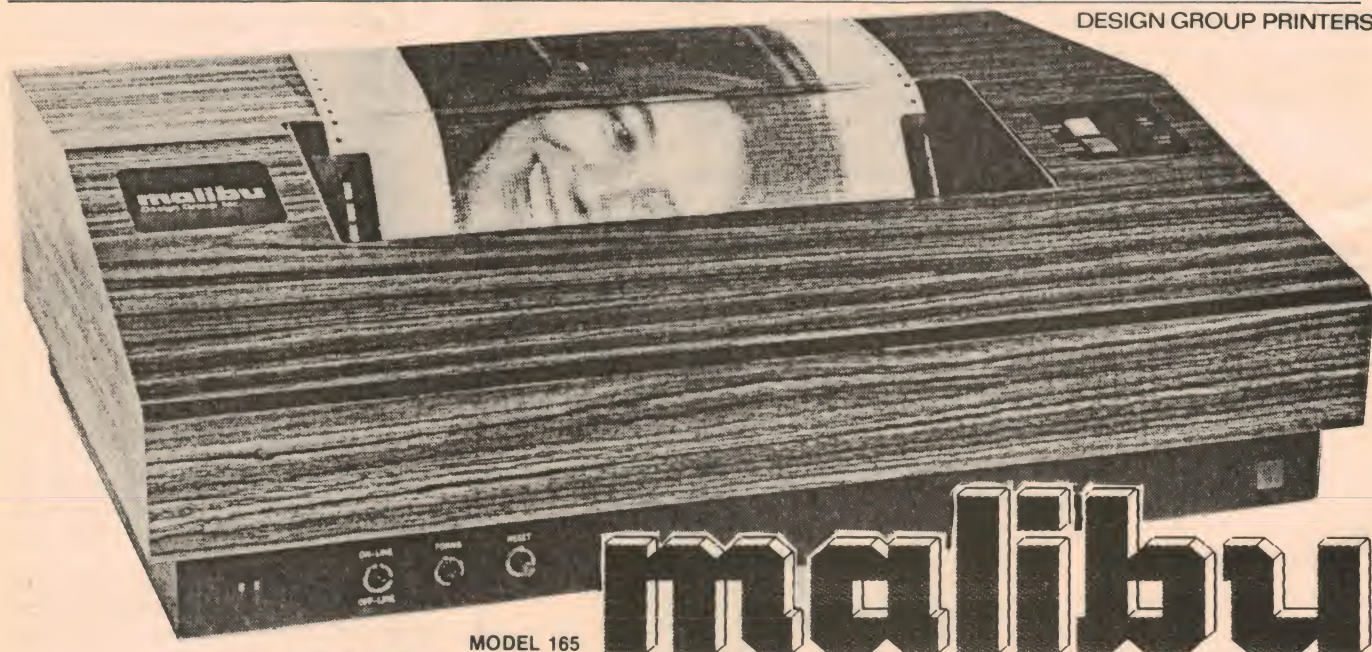

DESIGN GROUP PRINTERS

MODEL 165

SPECIFICATIONS

Features:

- High speed printing: 165 cps full logic bi-directional
- Letter quality printing: 90 cps full logic bi-directional
- Adjustable tractor feed (4 1/2" forms width)
- Paper feeds from front or bottom center
- User adjustable platen
- Forms length from 1 to 99 lines, 15 ips slew rate
- Auto-reversing, re-inking ribbon
- LSI Hydra Ballistic printhead, 9 wire, 12 x 9 matrix
- Line spacing: 6 lines per inch
- Power save circuitry turns off the fan and motors shortly after printing stops and re-energizes them as new characters are received, reducing noise and power consumption

Controls:

- Lighted "Power On" switch
- FORMS Override allows printing to bottom of last form after the "out of paper" switch has been activated
- ADJUST UP ADJUST DOWN provides vertical forms positioning
- LINE FEED advances the paper at the slew rate
- FORM FEED advances the paper to next top of form
- Functional with optional controller card only
- ON LINE OFF LINE
- RESET reinitializes the controller card
- SELECT D=Select with LED indicator
- TEST causes the printer to go into a self test mode printing a rotating character pattern

Software Routines:

- Full 96 ASCII character set, lower case with descenders
- Two type fonts: high speed and letter quality, software controlled automatic speed change
- Expanded characters
- Underlining
- Programmable vertical and high speed horizontal tabs
- Selectable left margin
- Complete dot control graphics (60 x 72 dots/inch)
- Easy custom character installation

Physical:

- Selectable primary voltage (110/240 VAC, 50/60 Hz)
- Dimensions: 27.5 x 19 x 9.25 inches (60 x 47 x 23 cms)
- Weight: 48 lbs (22 kgs)

Optional Interfaces:

- RS-232 serial or ASCII parallel controller
- S-100 buss I/O card
- S-100 buss I/O card with memory
- Apple computer I/O card with Hi-RES screen dump

Proudly distributed
in Australia by:



MICROCOMPUTERS

799 DANDENONG ROAD,
EAST MALVERN 3145
VICTORIA AUSTRALIA

Telephone: 211 8855 211 8344

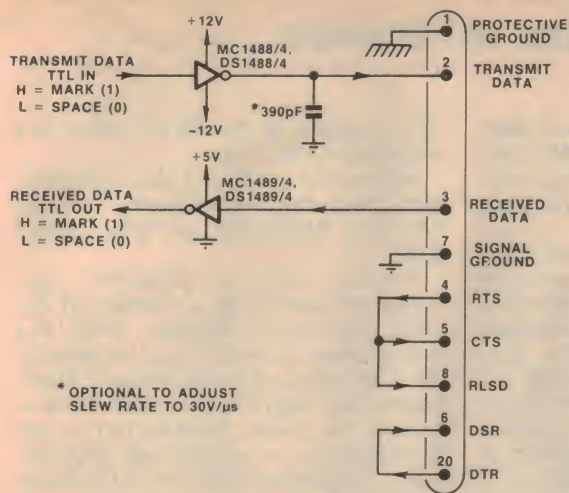


FIG. 2 : TTL/RS-232C INTERFACE USING 1488/1499 ICS

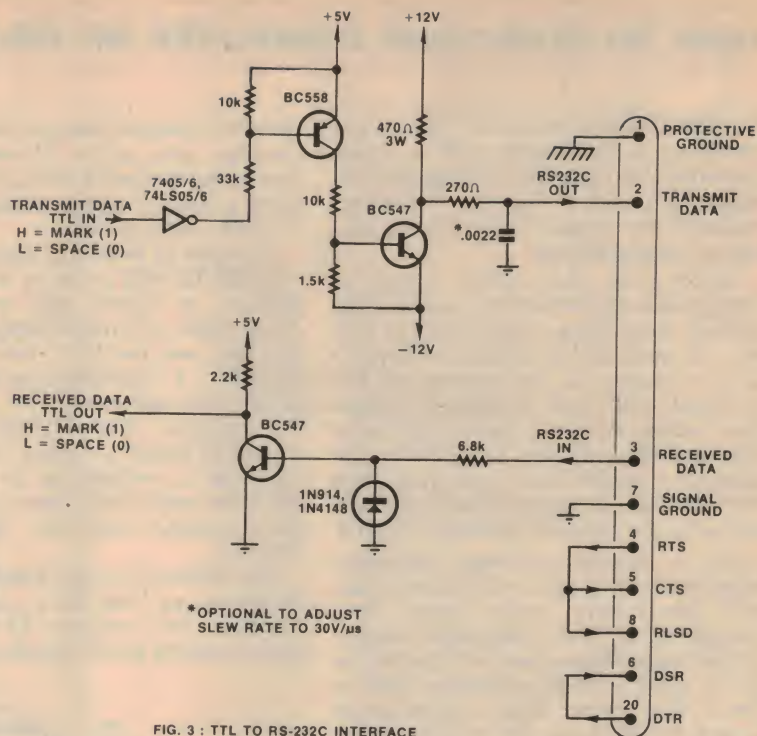


FIG. 3 : TTL TO RS-232C INTERFACE

nominal values, because in practice they will vary somewhat due to component tolerances and line voltage drop. Instead the RS-232C standard simply specifies the limits of the range in which each voltage may vary without causing error. So a digital 1 may be represented by any voltage between -5V and -25V, while a digital 0 may be represented by any voltage between +5V and +25V.

Note that it is not necessary for the voltage levels for 1 and 0 to be symmetrical with respect to signal ground. The only requirement is that each level remains inside its specified range. So a signal swinging between -12V for "mark" and +5V for "space" is quite acceptable, although the +5V level would be regarded as marginal.

A number of other electrical parameters are also specified in the RS-232C standard, as shown in Table 1. An important point is that the RS-232C specification is only intended to cover data communication rates up to 20,000 bits per second, which is loosely equivalent to 20 kilobaud.

Notice that the output impedance of

an RS-232C driver circuit is not specified as such, in the active condition. Rather it is given indirectly, by such parameters as the output levels for loads between 3k and 7k, and the maximum short-circuit current.

The maximum effective receiver input capacitance of 2500pF also includes cable capacitance, by the way.

Why does the specification give a maximum slew rate for an RS-232C driver? Simply because it is designed to minimise cross-talk in multiwire cables. The slower the voltage transitions, the lower the potential cross-talk.

Along with the electrical specification given for individual signals, the RS-232C standard also defines some 21 possible connections or "interchange circuits", which may be included in a standard RS-232C

interface. It also specifies the corresponding pin numbers for each one, on the accepted connector for RS-232C communication: a 25-way "Canon"-type connector, type number DB-25 or equivalent.

By definition, any piece of equipment provided with an RS-232C interface is fitted with a DB-25 socket. Any two or more devices fitted with such sockets are interconnected by cables fitted with a matching plug at each end.

Don't let those 21 defined connections worry you. Many of them are quite esoteric, being used mainly for secondary control functions when devices like modems are involved, connected to the switched telephone network. You can generally forget them for simple one-way or two-way asynchronous communication between a computer and its peripherals.

The main RS-232C connections you are likely to come across are shown in Fig. 1, along with their standard DB-25 pin numbers. Even here quite a few of the connections shown are used only when the interface involves "handshaking".


In fact most of the time you will probably only have to worry about three connections: those associated with pins 2, 3 and 7.

Pin 7 carries the signal ground, the reference against which the other signals are compared.

Pin 2 carries transmit data, or data leaving the equipment via the RS-232C socket.

Pin 3 carries received data, or data arriving at the equipment via the RS-232C socket.

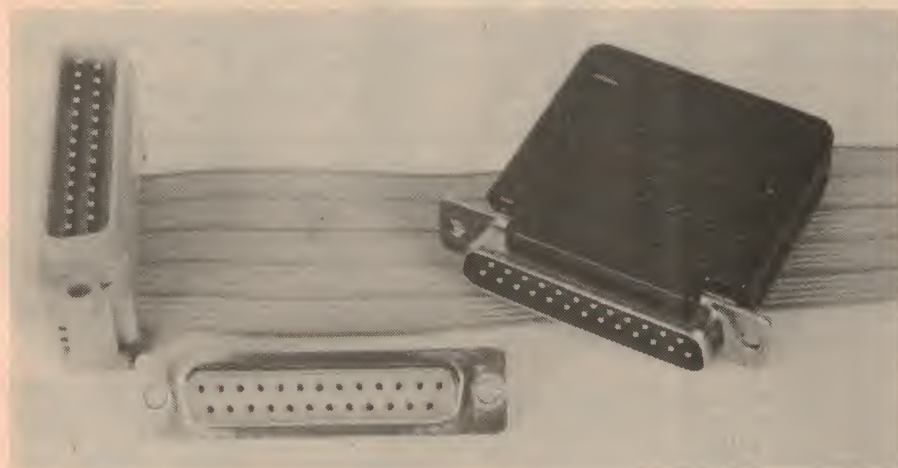These would be the only connections you will normally require for a simple



Typical connectors used for RS-232C interfacing. In front is a standard DB-25 socket, while at right is the matching DB-25P plug for a conventional cable. At left is a compatible plug which crimps onto ribbon cable. (Courtesy Radio Despatch Service)

HOW TO GIVE YOUR COMPUTER AN RS-232C INTERFACE ...

RS-232C asynchronous interface between a computer and a video terminal, for example, although you might also want to use pin 1 to interconnect the chassis earths of the two pieces of equipment.

Note that the cable used to interconnect between the two RS-232C sockets must have a crossover, so that pin 2 at each end is connected to pin 3 at the other. So the socket on the terminal will have keyboard output data leaving via pin 2, and display input data arriving on pin 3. Similarly the computer socket will have data from the terminal arriving on pin 3, and data going to the terminal leaving on pin 2.

For a simple one-way interface between a computer and a printer, you will probably only need two connections. The computer output socket would have transmit data fed to pin 2, along with its reference earth in pin 7. The printer input socket would accept the data via pin 3, again using pin 7 for the reference earth.

What about the other connections and signals shown in Fig. 1 — can you just ignore them? In many cases, you can. However, if you are ever likely to be connecting to a piece of equipment which makes use of some of the handshaking signals, it is possible to interconnect some of the pins so that the signals are simply fed back to the other end. This "fools" the equipment at the other end into thinking that your equipment is responding normally.

To do this you connect the "Request to send" (RTS) input on pin 4 to the "Clear to Send" (CTS) and "Received Line Signal Detector" (RLSD) outputs, on pins 5 and 8 respectively. You also connect the "Data Terminal Ready" (DTR) input on pin 20 to the "Data Set Ready" (DSR) output on pin 6.

An alternative scheme is simply to ignore the RTS and DTR inputs on pins 4 and 20, and tie the CTS, DSR and RLSD outputs (pins 5, 6 and 8) to a positive voltage between +5V and +15V, via a 330 ohm resistor. This sets them permanently in the "true" or 1 state, because the logic convention used for RS-232C control signals is the opposite of the convention for data signals.

So much for the basics of RS-232C interfaces in general. Now let's look at how you can provide your microcomputer with a practical interface, so that you can hook it up to an RS-232C terminal, printer or other device.

The approach that is generally taken by commercial designers is to make use of special RS-232C driver and receiver ICs, as shown in Fig. 2. The most commonly used driver IC is the MC1488 (Motorola), or its equivalent

DS1488 (National Semiconductor). Both devices are quad TTL-to-RS-232C translating buffer/drivers, so you only need a quarter of the device for each RS-232C output socket.

In order to limit the slew rate of an MC1488/DS1488 driver to the specified 30V/us, it should see an effective capacitance of around 400pF shunting the line and load. As the lines used between a microcomputer and its peripherals will usually be quite short, this suggests that a 390pF capacitor should be added as shown. However, as cross-talk is unlikely to be much of a problem with short lines in any case, the capacitor may be regarded as optional.

The drivers in an MC1488/DS1488 are inverting, so that they automatically produce the correct RS-232C data signal polarity from a positive-logic TTL

ACIA device, or the SENSE input of a microprocessor chip.

As you can see Fig. 2 also shows the recommended connections for the RTS, CTS, RLSD, DSR and DTR control pins.

If you want to provide your microcomputer with a number of RS-232C interface sockets, then the arrangement shown in Fig. 2 is probably the easiest way of going about it. Don't forget that each interface will have to have its own computer port arrangements — which will probably mean a separate UART or ACIA device for each one.

You don't have to use special ICs like the 1488/1489 combination to produce a practical RS-232C interface, though. In fact if you only want a single interface for a printer or video terminal, it is probably easier and

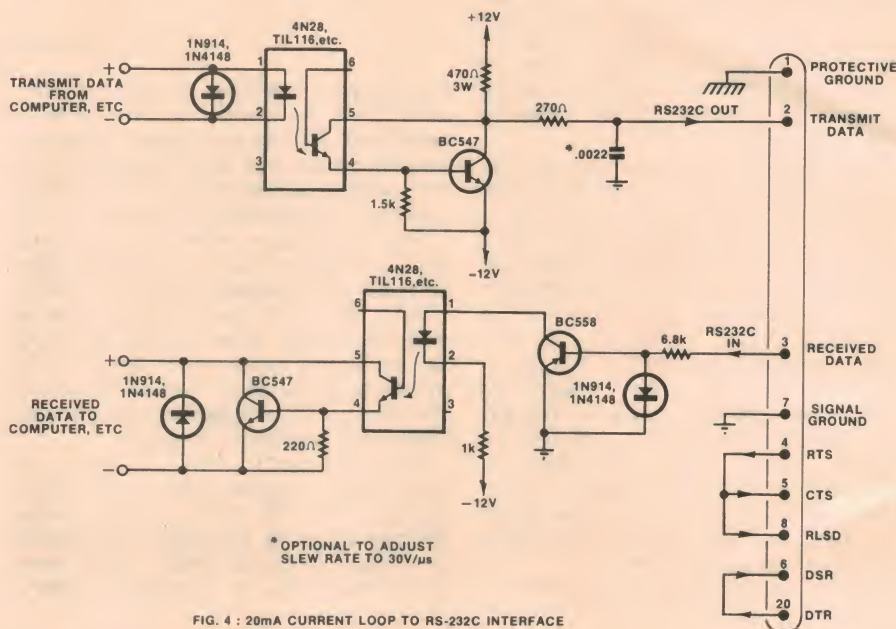


FIG. 4 : 20mA CURRENT LOOP TO RS-232C INTERFACE

input, as shown. This means that the driver input can be fed directly from either the TSO (transmit serial out) output of a UART or ACIA device, or the FLAG output of a microprocessor chip itself.

The most commonly used receiver IC is the MC1489 (Motorola) or the DS1489 (National Semiconductor). These are again quad devices, with four Schmitt trigger type RS-232C-to-TTL receivers in one package. So as before you only need a quarter of a device for each RS-232C socket.

The receivers in an MC1489/DS1489 are again inverting, so they take the RS-232C data signal polarity and automatically produce a positive-logic TTL output signal as shown. The signal from the receiver is thus suitable for feeding directly to either the RSI (receive serial input) of a UART or

cheaper to use discrete circuitry like that shown in Fig. 3.

As you can see, no special parts are required. The receive side is very simple, using a single BC547 or similar general-purpose NPN transistor with a protective diode and two resistors. The transmit side is only a little more complex, with two low-cost transistors and a TTL inverter to allow driving by positive-logic input signals. If the transmit data is available in negative-logic form (L-mark, H-space), the inverter is not required.

Note that to set the transmit output slew rate to the specified 30V/us, there should be an effective line shunt capacitance of around 2200pF. As before this can be regarded as optional.

What if your computer is already provided with a 20mA current loop

Continued on page 139

LARGE AREA LCD

Fairchild's Big Four.




FLB 3511 11 mm character height



FLB 4013 13 mm character height



FLB 3513 13 mm character height

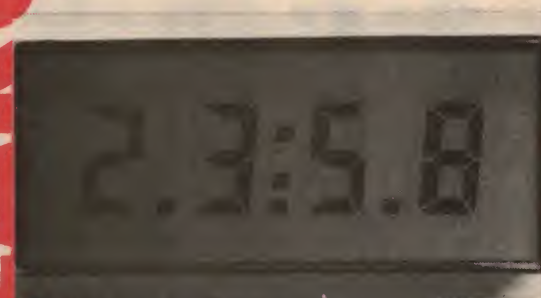

FLB 4018 18 mm character height

More and more industrial manufacturers are using our four most popular standard Large Area LCD displays. In digital panel meters, scales, testing equipment, clocks and gasoline pumps.

They're your best choice due to glass-frit seals that provide reliability, long life and hermeticity.

And thanks to our new fully-automated factory, we can produce our big four in high volume at low prices.

So if you need Large Area LCDs, think Fairchild.

366 Whitehorse Road,
NUNAWADING. VIC. 3131
Telephone: 877 5444

F.A.I. Insurance Building,
619 Pacific Highway,
ST. LEONARDS. N.S.W. 2065
Telephone: 439 5911

FAIRCHILD

Use your 2650 system to generate random Morse!

Trying to learn Morse code? The best way is to have an obliging "old timer" send you random groups of letters and numbers, so that you don't anticipate or "journalise". For those lacking an obliging friend here is the next best thing — a program which turns your 2650 Mini Computer into a random Morse generator.

by **RICHARD ROGERS, VK7RO**

4/439 Huon Road, South Hobart 7000

One of the common errors of beginners in copying Morse code is to "journalise", or write down the end of a word before it has been sent! Random code groups are an excellent practice material to help combat this tendency. Once you are able to copy random groups, plain language will seem easy. Also, with random code there are many more chances to hear the letters which occur infrequently in plain language.

The program described here was originally written for my Central Data 2650 system, but the program as listed has been modified to suit systems using the Pipbug monitor program, like the EA 2650 Mini Computer.

The program generates five-character groups consisting of four letters and one figure, eg ZF90B 8JLUY etc, at speeds ranging from 3 to 25 words per minute. The starting speed is selectable and the speed increases by one WPM every five minutes. The current speed is displayed on the VDU. Below 10WPM, the characters are sent at a 10WPM rate but the spaces between the characters are increased.

As written, the program generates a tone at the 2650 flag output. The tone frequency used is ignored by a 110 baud VDU and nothing is printed on the screen during the morse output. I use a loudspeaker in series with a 1000 ohm resistor, connected between the output of the flag buffer and earth, as a monitor.

The program may be changed to give a voltage suitable for controlling an external oscillator by changing the code at 04A3 from 76 40 C0 C0 to 04 00 F0 C0

Some NOP's are provided within the program to facilitate the use of any other output port. For instance, the use bit 0 of output port D as the tone output, the following code changes are required.

05EB change from C0 C0 C0 C0 to 04 00 F0 C0

049D change from 74 40 C0 C0 to 04 01 F0 C0

04A3 change from 76 40 C0 C0 to 04 00 F0 C0

04AE change from 76 40 C0 C0 to 04 00 F0 C0

The program may also be modified to generate five character groups of

mixed letters, figures and punctuation by changing 04F8 from 18 26 04 1A to C0 C0 04 30.

My thanks to Ron Brown, VK7ZRO, for allowing me to test the program on his system.

```

0440 1F 05 E7 60 88 A8 90 40 28 D0 08 20 78 B0 48 E0
0450 A0 F0 68 D8 50 10 C0 30 18 70 98 B8 C8 7C 3C 1C
0460 0C 04 84 C4 E4 F4 FC 56 CE E2 32 7A 86 94 B4 B6
0470 4A 8C 54 00 00 E5 00 19 15 1A 0F 3B 2F 3B 2D 3B
0480 2B 3B 29 3B 27 3B 25 3B 23 17 3B 0F 3B 0D 3B 0B
0490 3B 1A D1 45 FE E5 80 18 6C 1B 5A 06 00 74 40 C0
04A0 C0 3B 14 76 40 C0 C0 3B 0E FA 72 17 06 00 76 40
04B0 C0 C0 3B 03 FA 78 17 04 5C F8 7E 17 09 14 0D 64
04C0 D3 85 01 E5 17 1A 02 05 00 C9 07 8D 64 D3 CD 64
04D0 D3 17 00 00 01 02 03 04 05 06 07 08 09 0A 0B 0C
04E0 0D 0E 0F 10 11 12 13 14 15 16 07 05 04 05 C8 29
04F0 0A 24 3B 3C C8 20 08 1E 18 26 04 1A C8 1B 0A 17
0500 3B 2E C8 13 C1 0D 64 43 CF 65 1A A7 01 14 08 06
0510 A4 01 C8 02 1B 62 00 00 00 00 00 00 00 00 00 00
0520 04 0A C8 75 0A 72 3B 08 C8 6E C1 0D 64 5D 1B 58
0530 3F 04 8C 82 1A 03 E8 61 16 A8 5E 1B 77 3F 04 EA
0540 07 06 0F 65 19 C1 3F 04 75 3B 90 3B 8E FB 73 04
0550 01 88 07 E4 00 15 C8 02 1B 63 00 04 00 0E 25 97
0560 14 3F 02 B4 1B 77 01 E0 00 00 00 00 77 0E 08 79
0570 05 00 07 11 75 01 D1 B5 01 18 04 E9 6C 1A 06 77
0580 01 A9 66 77 01 06 02 0E 45 6A D0 CE 65 6A 5A 77
0590 FB 64 09 57 75 FF 17 00 0A 0A 0D 52 41 4E 44 4F
05A0 4D 20 4D 4F 52 53 45 20 44 45 20 56 4B 37 52 4F
05B0 0A 0D 30 33 20 2D 20 32 35 20 57 50 4D 0A 0A 0D
05C0 53 54 41 52 54 49 4E 47 20 53 50 45 45 44 3F 0A
05D0 0D 00 0A 0D 20 20 57 50 4D 00 E7 30 1E 00 1D E7
05E0 39 1D 00 1D 47 0F 17 76 40 75 FF C0 C0 C0 C0 06
05F0 00 3F 05 5D 3F 04 BC 12 1A 7A 3F 02 86 C3 3F 02
0600 B4 3B 57 D3 03 D0 D0 83 CC 05 68 3F 02 86 C3 3F
0610 02 B4 3B 46 8F 05 68 CF 05 68 06 3E 3F 05 5D 0F
0620 05 68 E7 19 1D 00 1D E7 03 1E 00 1D E7 09 19 10
0630 A7 02 04 79 06 02 82 FB 7D CC 05 5C 05 30 1B 1A
0640 CF 05 69 0C 05 66 CC 05 6A 0C 05 67 CC 05 6B 3F
0650 05 6C 04 89 CC 05 5C 0D 05 6B CD 04 9C D1 CD 04
0660 AD 0C 05 68 C1 D1 D1 81 CC 05 54 20 CC 05 5A 3F
0670 05 3D 06 37 3F 05 5D 0D 05 68 E5 19 18 02 85 01
0680 CD 05 68 E5 0A 1A 0A E5 14 1A 04 85 0C 1B 02 85
0690 06 3F 02 69 1F 06 1A

```


At right is the full hex listing of the author's random Morse program. It starts at 0440.

REWARD

ACT AS OUR REPRESENTATIVE, PROMOTE OUR RANGE OF TEXAS INSTRUMENTS PRODUCTS AND EARN UP TO 25% COMMISSION ON EVERY SALE.




TI-58C

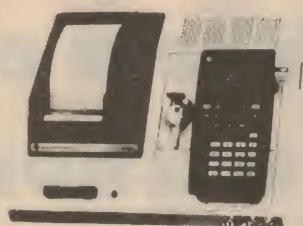


PC-100C with Calculator




Solid State Software

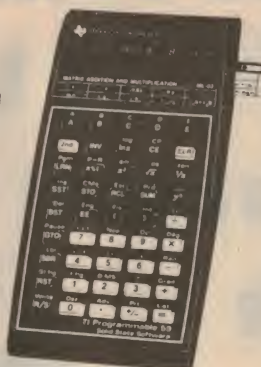


TI-59

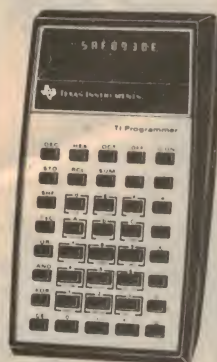


TI Programmer

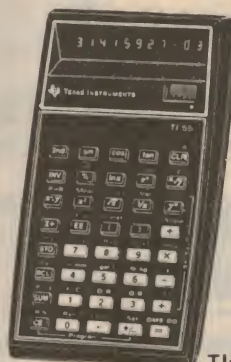

TI-55

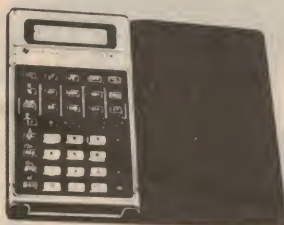

TI-50

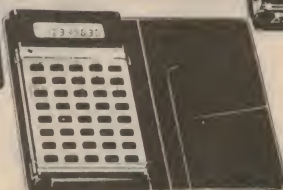


TI-25

TI-35

electronic calculator/clock
with stopwatch and alarm
"DATA-CHRON"



TI-30 Student Pack

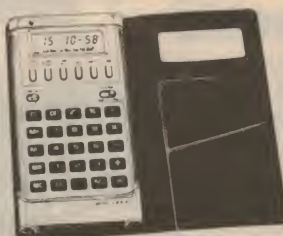

TI-59 Programmable Calculator, up to 960 progr. steps, up to 100 memories, over 175 functions, Solid State Software, Magnetic Cards, etc.

TI-58C Programmable Calculator, up to 480 progr. steps, up to 60 memories, constant memory feature, Solid State Software, over 170 functions.

PC-100C Printer for TI-58/58C/59, turns the calculator into high speed printing calculator that prints, lists, and traces your program.

SOLID STATE SOFTWARE for TI-58/58C/59
Up to 5,000 program steps at your fingertip.
Electrical Engineering, RPN Simulator (converts HP Keycodes into TI-59 Keystrokes), Math Utilities, Business Decisions, Securities Analysis, Leisure, Surveying, Marine Navigation, Aviation, Real Estate, Applied Statistics.

PPX-59 Professional Program Exchange.
Subscriptions are now available from Delta. Members will receive the PPX-59 Software catalogue listing more than 1,000 programs, first 3 programs are free, each extra program \$3.00 plus we keep you informed on new software announcements, programming hints etc.

TI-25 Powerful 52-function scientific calculator, Powers and Roots, Trig Functions, Parentheses, Hyperbolic Functions, Degree-Radian-Grad Conversions, Log and Statistical Functions, Memory, Constant, etc.

TI-30 STUDENT MATH KIT, an extraordinary value, all basic Functions, Parentheses, Power and Roots, Logs, Trig Functions, Memory plus 224-page "The Great International Math on Keys" book.

TI-35 economical scientific calculator for students and professional, all scientific functions plus statistical functions, etc.

TI-50 60-function scientific calculator with powerful statistical functions, and constant memory feature etc.

TI-55 advanced programmable slide rule calculator, with 10 memories, and statistical functions, with rechargeable batteries / charger and 140-page book etc.

BUSINESS ANALYST II, pre-programmed powerful financial and statistical functions, plus special functions,

MBA Powerful programmable business calculator with statistical and financial functions plus 288-page book "Calculator Analysis for Business and Finance", rechargeable batteries & charger free.

TI-PROGRAMMER provides conversions between octal, decimal and hexadecimal number systems, performs arithmetic in any of three number bases, a must for any programming professional, rechargeable batteries & charger included.

Suggested Retail Price Your buying price.


PRODUCT	SUGGESTED RETAIL PRICE	SALES TAX	
		EXEMPT	PAID
TI-59 Calculator	\$349.50	\$240.75	\$269.25
TI-58C Calculator	165.95	115.69	127.39
PC-100C Printer	283.95	197.21	218.21
3 reels Thermal Paper	12.50	10.25	11.36
Solid State Software	35.30	28.80	32.10
Pakettes	9.10	7.46	8.27
40 Blank Mag. Cards	15.95	13.21	14.48
PPX-59 Subscription	18.00	16.10	16.10
TI-25 Calculator	35.95	24.83	27.68
TI-30 Student Pack	25.95	17.89	19.99
TI-35 Calculator	39.95	27.38	30.83
TI-50 Calculator	45.95	31.65	35.40
TI-55 Calculator	69.95	48.41	53.81
Business Analyst II	49.95	36.72	40.77
MBA Calculator	79.95	55.13	61.58
TI-Programmer	69.95	48.41	53.81
Stopwatch/Cal./Clock	44.95	30.68	34.73
TI-5025 Printer	89.95	61.50	69.45
TI-5225 Printer	166.95	141.75	128.70
TI-5230 Printer	399.95	274.65	308.40
Little Professor	19.95	13.84	15.34
Dataman	24.95	19.42	21.52
144 Page Texas Instruments Product Catalogue listing Calculators, Computers etc.			\$2.50
POST, PACK & INSURANCE \$2.50 per Order			

DELTA SCIENTIFIC PRODUCT DISTRIBUTION

RED BANK COURT, ST. ALBANS, VIC. 3021, AUSTRALIA

Phone (03) 366 3742

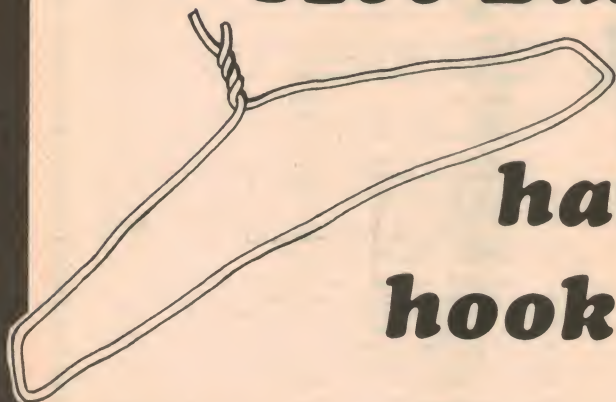a micro computer without S100 Bus compatibility is like a coat hanger without a hook



The Exidy Sorcerer is a complete stand-alone microcomputer, needing only a video monitor or modified TV set to be up and running in full BASIC.

But the Sorcerer is more: change the plug-in ROM PAC™ and it will communicate in other languages, add the S-100 Bus expansion and have access to other manufacturer's peripherals - plus, plus, plus. The Sorcerer is a complete dedicated computer.



**NOTE!
ALL PRICES
INCLUDE
TAX!**

SORCERER


Cat. X-1190
8k Memory

\$1095

P&P \$5.50 per unit

Cat. X-1192
16k Memory

\$1250

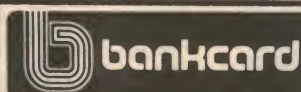

Welcome
here




terms available
to approved applicants
(personal shoppers only)

FROM

\$1095*

look at our prices for peripherals

Video Monitor

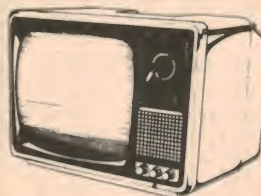

**Suits Sorcerer,
Tandy TRS-80,
Apple etc.**

Why waste money on overpriced monitors? This famous make unit has large 30cm diag. screen plus it simply connects to your computer via an RCA socket. 240V AC or 12V DC operation.

\$149.50

X-1196
P&P \$5.50

S-100 Expansion Unit



Use other manufacturer's peripherals with your Sorcerer & S-100

For the serious computer owner. Contains powerful computer power supply plus buffer/interface circuit to protect the computer in case of damage to the S-100. Plus many more benefits.

\$499

X-3010
P&P \$5.50

Floppy disc drives SINGLE


Micropolis single unit with 143k storage plus improved drive system. Dual density & complete with all bits and pieces.

DUAL DENSITY DUAL

Micropolis drive with 630k storage. Takes hard centre diskette and comes with all bits and pieces.

QUAD DENSITY

X-3210 P&P \$5.50

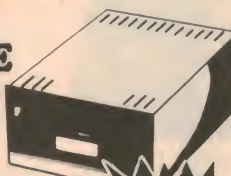


X-3200
P&P \$5.50

\$875



\$1950

C-ITOH PRINTER

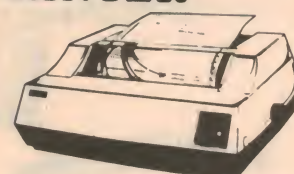

**FANTASTIC VALUE
FOR LESS THAN
\$1,000!!!**

A fantastic dot matrix printer that uses inexpensive fan fold paper. Upper and lower case with 125 character per second print speed and a one line buffer memory and lots more for **LESS THAN \$1,000!!!!**

X-3255
P&P \$5.50

\$970

DICK SMITH ELECTRONICS

SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RESELLERS



Adapt your D2 kit to run CHIP-8 programs

How would you like to run CHIP-8 programs on your Motorola MEK6800D2 evaluation kit system? Here is a memory/video interface circuit which lets you do just that. Build it and you can run just about any program written for the Dream 6800 or the RCA "VIP" systems.

by GRAHAM LEADBEATER*

Michael Bauer's excellent "Dream 6800" computer project as described in the May-August 1979 issues has captured the imagination of many people, enabling them to experiment with a simple high level language like CHIP-8 at low cost. However, there must be many people like myself who did not wish to build up a complete new computer, as they already have a Motorola 6800 D2 kit. If you're in this position, you may be interested in how I modified my D2 kit to run CHIP-8.

When we look at the problem of adapting Michael's interpreter program to the D2, everything drops into place. We already have a Monitor Program (J-Bug). We have the cassette interface and we have the keypad. Once we remove the software associated with these things from the CHIPOS PROM we will have plenty of space for program changes. We also have a PROM socket located at C000 to take our new program.

We will need a 50Hz interrupt input for the timer and an audio "bleeper". These are easily connected to the D2 kit's "User" PIA located at 8004-5.

What we don't have is a block of memory at 0200 for storing CHIP-8 programs, and a video interface. These are best built on a separate board designed to plug into the 86-pin "Exorcisor" bus as is the kit itself.

The prototype was hand-wired on a piece of matrix board for development, but to make a good job of it, an Exorcisor-compatible, wire-wrap board, available from Pennywise Peripherals, is recommended. Fig 1 shows the connections. Whether you use a card cage or just two sockets wired together is up to you.

The D2 kit comes with 256 bytes of memory in two 6810s with sockets provided for another 256 bytes. The last address used is 01FF but images extend

to 1FFF because of incomplete address decoding. It would be possible to make our new memory start at 0200 but since 2114s are the cheapest way to make memory and since they come in 1K blocks, the decoding becomes a bit fiddly if they are not located on the 1K boundaries. It was decided to make a board which would allow for memory expansion and occupy the address range 0000-1FFF, containing up to 7K of 2114s for general purpose memory and

256 bytes in 6810s dedicated to the video display.

The idea is to remove the 6810s from the D2 Kit and open up the bottom 8K of memory for off-board expansion as described in the kit handbook. The 6810s can now be used in the new board.

It is suggested that you build a board with 1K of memory (two 2114s) for a start but leave space for another 12 ICs which can be added later if you have the inclination and the money. Note that CHIP-8 is limited to the first 4K anyway. The Video RAM can be used as ordinary memory when not running CHIP-8 (just switch off your TV set).

Fig 2 shows the circuit. This looks a bit of a monster at first glance, but it is really fairly straightforward. Note that the Video RAM is permanently enabled and is connected to the data bus via tri-state transceivers (ICs 19 and 20). The signals to separately enable their sending and receiving sections are derived from the VRAM decoder output and the R/W and $\phi 2$ lines.

The video circuitry calls for some comment. It was decided not to halt the processor while the picture is scanned, as the D2 Kit has a slow clock to start with (614.4kHz). Instead, the address lines to the Video RAM are normally driven by the scanning counters but are switched over to the processor address bus whenever this part of memory is accessed. This is done with the 74LS157 devices. The 74LS157 is a quad 1-of-2 data selector and can be likened to a relay with four sets of changeover contacts (but a bit faster). Two of them switch the eight low-order address lines. (ICs 11 and 12). The Video RAM looks just like ordinary memory to the processor. The picture is blanked whenever this RAM is accessed.

Since we don't have to compromise between picture size and processor throughput, the picture has been enlarged to better fill the screen. Each dot is now 0.667us wide and six lines high.

The theory of operation remains the same, only the figures have been changed to protect the innocent!

We start with a 3 MHz oscillator, the output of which is divided by two to


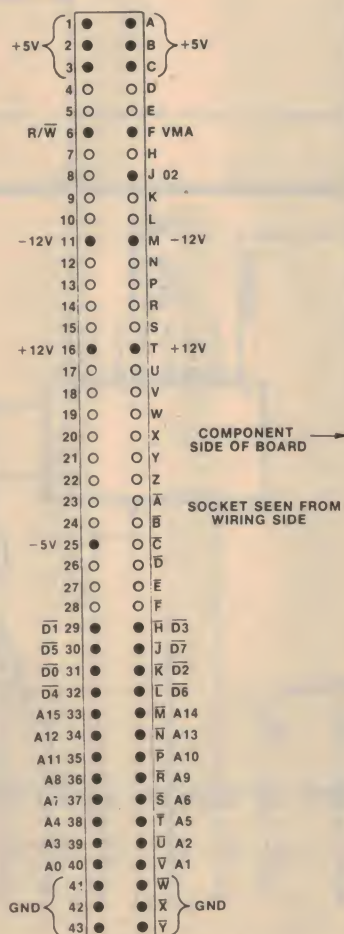



FIG. 1: RELEVANT CONNECTIONS TO THE MOTOROLA BUS

OVERLEAF: The complete circuit for the author's memory/video interface, which lets you run CHIP-8 programs.

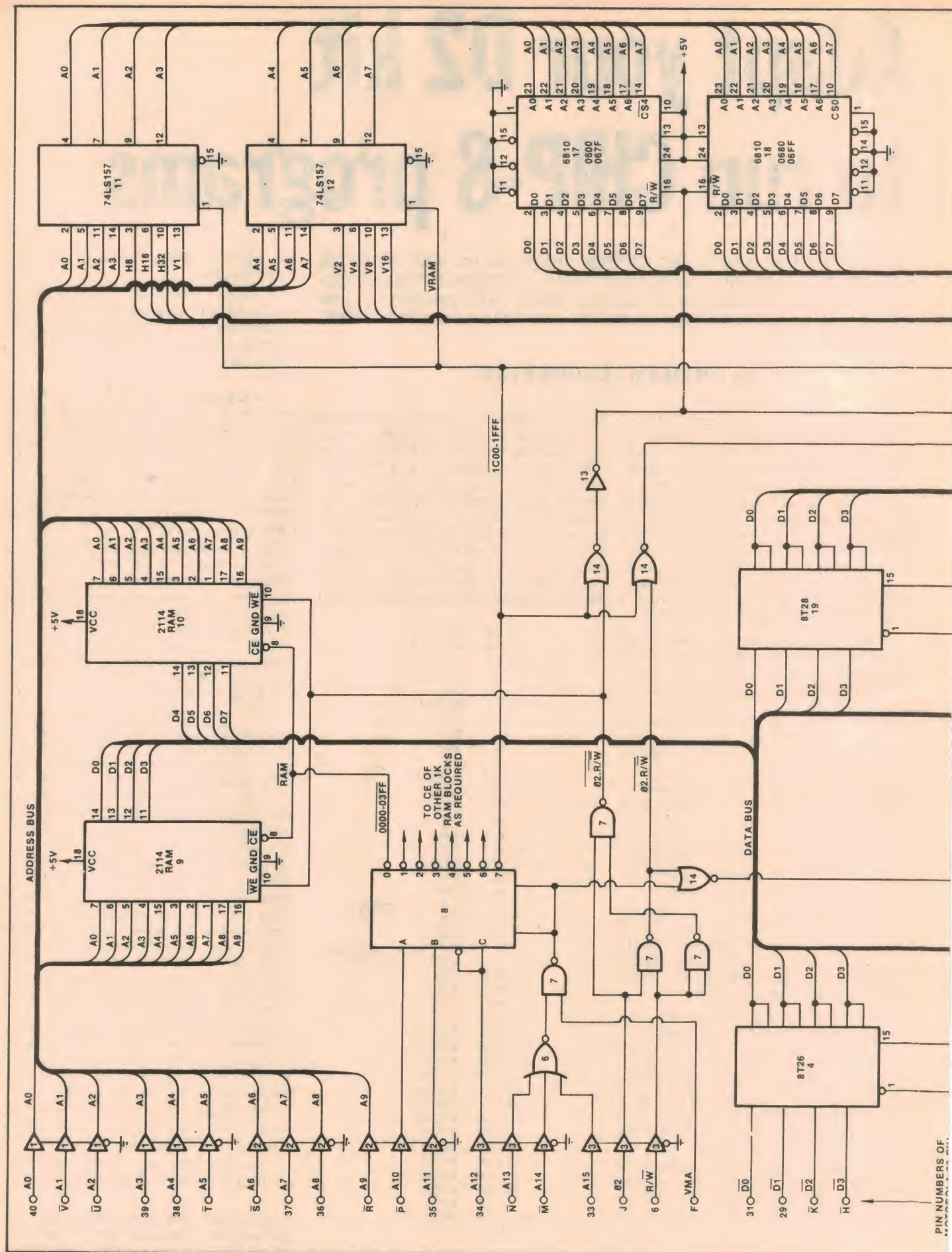*16 Ellison Street, Ringwood, Victoria 3134




PIN NUMBERS OF
RAM CHIPS

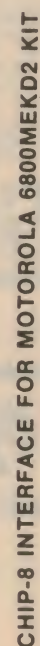

"THE S100 BUS STOP"™

S100 16K STATIC RAM KIT

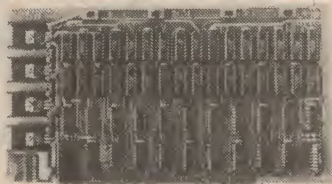

ETI 642

16K, 2114, Low Power 1.2 Amps Typ. for 16K, 300 or 450nS, 4K addressing, 4K write protect switches. Cromemco bank select, wait states plated thru holes, solder mask. See FEB ETI project for details. Assembled and tested \$380.00. \$5.00 P&P Reg. mail. Kit price \$315.00

UV EPROM ERASERS



New product range, LEE/T 15W tube — 120 min. timer — up to 40 eproms — will erase in 10/15 min. Model MEE/T — 8W tube — 120 min. timer up to 10 eproms — will erase in 20/30 min. Model MEE is the same as MEE/T but with no timer. All erasers have safety cut out switch. PRICE: LEE/T \$105.00, MEE/T \$93.50, MEE \$74.00. P&P \$3.00

S100/6800 CHASSIS




11 Slot back plane, 15 amp. power supply, fan, key switch, bench mount, rack mount, fully card guided, anodised alum. 5 sockets in basic unit.

S100 Rack Kit	\$306.00	Assembled	\$406.00
S100 Bench Kit	\$345.00	Assembled	\$445.00
6800 Rack Kit	\$331.00	Assembled	\$431.00
6800 Bench Kit	\$370.00	Assembled	\$470.00
6800 Power Supply	5V at 10 amps, + 12V at 2 amps		
S100 Power Supply	8V at 15 amps, + 16V at 2 amps		

S100 16K Eprom Board Kit	\$98.00
S100 Z80 4 MHz CPU Board Kit	\$156.00
S100 Floppy Disc Controller Kit	\$165.00
S100 Double Density Disc Controller Kit	\$325.00
S100 2708/2716 Programmer Kit	\$175.00
S100 2708/2716 Eprom Board kit	\$115.00
S100 11 Slot Back Plane	\$36.00
Extender Termination Board	\$70.00
S100 Sockets	\$8.00
S100 Wire Wrap Board	\$28.50
S100 Extender Board Kit	\$33.00
Number Cruncher Kit (MM57109)	\$49.50
SBC 100 Single Board Computer	\$260.00
S100 80 x 24 Video	\$330.00

DUAL SERIAL PORT BOARD NEW PRODUCTS

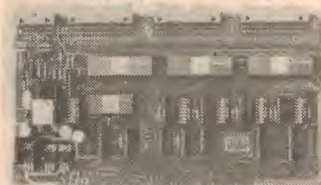

9 Parallel Ports (programmable) 2 Serial Ports TTY RS232 or TTL. Baud rate generator 9600 to 75, full address decoded, low power buffers, plated thru holes, solder mask. KIT PRICE \$189.00. P&P \$3.00. ASS PRICE \$225. Dual serial port version.

DISC DRIVES

Shugart SA400 Mini	\$375.00
Shugart SA801	\$650
Remex 4001 Double Sided	\$750.00

6800 PRODUCTS

6800 11 Slot Back Plane	\$36.00
6800 11 Slot Chassis (Basic Rack)	\$175.00
6800 Extender Board Kit	\$33.00

2708 EPROMS (ceramic)

450nS, guaranteed quality	\$12.00
2716 Eproms (single supply)	\$47.50


2114 RAMS low Power Hitachi, Super Rams

450 NS	\$7.50
300 NS	\$8.50

Send 60c in stamps for computer printout catalogue for full production information and price list.

All products Aust. made and ex-stock (almost). Dealer enquiries welcome.

S ELECTRONICS
MELBOURNE

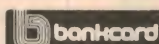

BUILT AND TESTED P.O.A.
ALL PRICES ADD 15% S.T. IF APPLICABLE

Give name, number, expiry date and signature. For mail order sales.

S.M. ELECTRONICS

10 STAFFORD CRT, DONCASTER EAST, VICTORIA, 3109
BOX 19 DONCASTER EAST, 3109. Dealer A.C.T. 81 5011
PHONE (03) 842 3666, 842 3950. SYD. 661 9237.
TELEX AA37213



AIM 65


DWELL
ELECTRONICS



ROCKWELL AIM 65

AIM 65 is fully assembled, tested and warranted. With the addition of a power supply, it's ready to start working for you. AIM 65 features on-board thermal printer and alphanumeric display, and a terminal-style keyboard. It has an addressing capability up to 65K bytes, and comes with a user-dedicated 1K or 4K RAM. Two installed 4K ROMs hold a powerful Advanced Interactive Monitor program, and three spare sockets are included to expand on-board ROM or PROM up to 20K bytes. (4K assembler, 8K basic optional). An Application Connector provides for attaching a TTY and one or two audio cassette recorders, and gives external access to the user-dedicated general purpose I/O lines. Also included as standard are a comprehensive AIM 65 User's Guide, a handy pocket reference card, an R6500 Hardware Manual, an R6500 Programming Manual and an AIM 65 schematic.

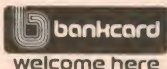AIM 65 1K RAM \$525 TAX PAID
4K RAM \$570 TAX PAID
8K BASIC IN ROM \$125
4K ASSEMBLER IN ROM \$100
CASE TO SUIT \$75



TWO LOCATIONS: 77 Edgeworth-David Avenue, Hornsby NSW 2077;
Shop M17, Level 3 Northgate, Hornsby NSW 2077
Telephone: (02) 487 3111.

DWELL PTY LTD

CHIP-8 FOR THE D2

produce the dot clock. This is divided by eight to give the load pulse to the shift register. These divisions are performed by IC22. IC23 now divides by 12 to produce the line sync frequency of 15625Hz. The pulses from the first stage of this counter are 5.3us wide which is near enough to the required 5us line sync pulse. The 64us per TV line is equivalent to 96 dots, but we only want 64, the remaining 32 represent the horizontal blanking period. Gating is arranged to put the line sync pulse in the middle of this period to centre the display in the screen.

To give square dots we would need 5.3 lines per dot, which is a bit hard to do; so we will settle for six. Line sync pulses are counted by IC26, which divides by six. Unfortunately we can't use the first stages of the 4040 (IC27) as we could if dividing by four or eight. The outputs from the first five stages of the 4040 provide the addresses for the 32 rows of dots. The 312 lines per TV field represent 52 rows of dots so IC27 is reset on the count of 52. We only want 32 rows so the sixth stage is used to provide vertical blanking for the remaining 20. The vertical sync pulse is positioned in the middle of this blanking period, ie at 42.

The 3 MHz oscillator features

IC IDENTIFICATION

IC 1	74LS367	IC15	74LS10
IC 2	74LS367	IC16	74LS20
IC 3	74LS367	IC17	6810
IC 4	8T26	IC18	6810
IC 5	8T26	IC19	8T28
IC 6	74LS27	IC20	8T28
IC 7	74LS00	IC21	74LS00
IC 8	74LS155	IC22	74LS93
IC 9	2114	IC23	74LS93
IC10	2114	IC24	74LS221
IC11	74LS157	IC25	4014B
IC12	74LS157	IC26	74LS93
IC13	74LS04	IC27	4040B
IC14	74LS02		

reliable starting and adequate stability. Keep all leads as short as possible. If you have a 3 MHz crystal it can be connected as shown dotted, omit the trimmer and change the 180pF to 150pF. IC21 must be a 74LS00.

I estimate the cost of the ICs to be around \$60 (\$75 if you include the 2708).

The 8T28s could be replaced by three 74LS367s or any other non-inverting tri-state buffers.

The buffers on the address bus (ICs 1, 2 & 3) could possibly be omitted but I consider the few dollars that they represent to be a good investment to reduce bus loading in big systems and to keep MOS inputs off the edge connector.

Changes to the software are relatively

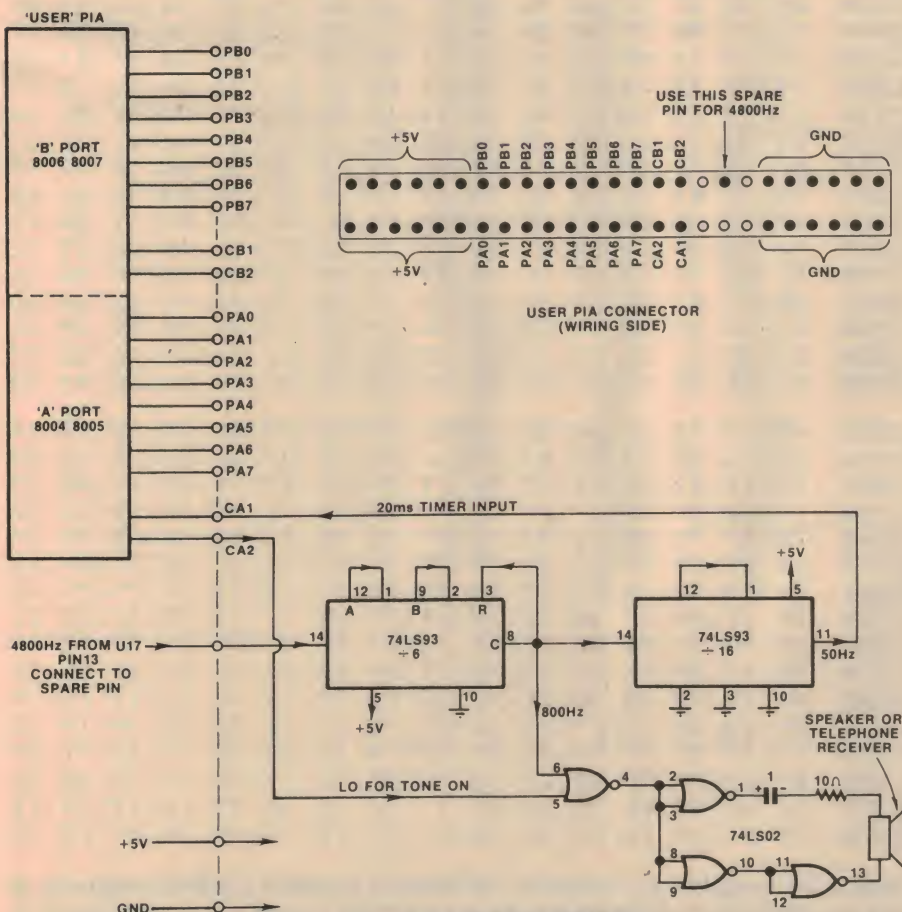


FIG. 3: TIMER AND BLEEPER

\$ THE LOGIC SHOP PTY. LTD.

Discount shopping for your professional Microcomputer and terminal requirements

COMPUCOLOR II



features:

Up to 32K User RAM
Eight-colour display
32 lines of 64 char.
5" Mini Disk Drive
40 Tracks, 48 TPI

Low Cost LOGIC TLS 900



features:

24 lines
80 char. per line
Transmission rates 75-19, 200 Bd.
96 char. ASCII Upper & Lower Case
12" Monitor

DECwriter® Terminals LA-34, LA-36, LA-180



features:

10 or 30 char. p.s.
132 char. per line
Type Font: — 9 x 7 Dot Matrix
Switch-selectable parity

"retail saving on professional products"

\$ THE LOGIC SHOP PTY. LTD.

212 High St. PRAHRAN VIC
3181. Tel 51 1950

91 Regent St. Chippendale
NSW 2008
Tel: 699 4910

(R) Registered Trade Mark
of Digital Equipment Corp.

CHIP-8 FOR THE D2

minor until we get to the keypad routines. The D2 keypad cannot just be read like the DREAM, it must be scanned and decoded. Unfortunately there are few subroutines accessible in J-Bug for this purpose, so we must provide our own.

The PIA initialisation subroutine at C287 is no longer needed. A new Keypad Input Subroutine (KEYINP) is now located at C287. It makes use of some minor subroutines and the look-up table of key values in J-Bug. A new GETKEY subroutine follows at C2C4 (the same address as the old one). It is a bit simpler since we don't need the function key. Tone generating subroutines follow at C2DA and the new interrupt service routine is located at C2F6.

To run CHIP-8 we use the monitor to enter at C300. A set-up routine is located here which writes the start address of the interrupt service routine into the J-Bug pseudo IRQ vector at A000-1. Then it initialises the timer/tone PIA at 8004-5, clears the interrupt mask and jumps to the start of the CHIP-8 mainline at C000.

Nearly a quarter of the 2708 PROM is left over and could be used for extensions to CHIP-8.

The only requirement for the timer is a 50Hz signal into the CA1 lead to the PIA but it must be an accurate 50Hz if the computer is to be used for serious timing applications or even if you just want to "write" a digital clock. The 50Hz could simply come from the mains and the bleeper need only be something that make a noise while CA2 is low.

One approach is shown in Fig 3 which uses the D2's crystal as the timebase and also provides the source of tone.

There is scope for ingenuity here. You could for example, pick other frequencies out of the divider chain and use the PIA outputs to select them. Resistors could also be switched in or out by transistors driven by the PIA to make a crude programmable attenuator.

With program control over frequency, amplitude and duration of tones, you could just about make your computer talk to you. Machine code subroutines for this purpose could be stored in the empty space in the PROM and called via jumps in the accessible area.

In fact, a program to convert ASCII to speech could be the subject of an article for the April issue of EA!

So there you are, D2 owners, the world of CHIP-8 is open to you. Happy programming!

In conclusion, the author would like to thank Michael Bauer for his patience on the telephone, explaining software.

C000	8D	77	CE	02	00	DF	22	CE	00	7F	DF	24	DE	22	EE	00
C010	DF	28	DF	14	BD	C0	D0	96	14	84	0F	97	14	8D	21	97
C020	2E	DF	2A	96	29	44	44	44	44	8D	15	97	2F	CE	C0	48
C030	96	28	84	F0	08	08	80	10	24	FA	EE	00	AD	00	20	CC
C040	CE	00	2F	08	4A	2A	FC	A6	00	39	C0	6A	C0	A2	C0	AC
C050	C0	BA	C0	C1	C0	C8	C0	EE	C0	F2	C0	FE	C0	CC	C0	A7
C060	C0	97	C0	F8	C2	1F	C0	D7	C1	5F	D6	23	26	25	96	29
C070	81	E0	27	05	81	EE	27	0E	39	4F	CE	1C	00	A7	00	03
C080	8C	1D	00	26	F8	39	30	9E	24	32	97	22	32	97	23	9F
C090	24	35	39	DE	14	6E	00	96	30	5F	93	15	97	15	D9	14
C0A0	D7	14	DE	14	DF	22	39	DE	14	DF	26	39	30	9E	24	96
C0B0	23	36	96	22	36	9F	24	35	20	E8	96	29	91	2E	27	10
C0C0	39	96	29	91	2E	26	09	39	96	2F	20	F0	96	2F	20	F3
C0D0	DE	22	08	03	DF	22	39	BD	C2	87	7D	00	13	27	07	C6
C0E0	A1	D1	29	27	EB	39	C6	9E	D1	29	27	D0	20	D5	96	29
C0F0	20	3B	96	29	93	2E	20	35	8D	38	94	29	20	2F	96	2E
C100	D6	29	C4	0F	26	02	96	2F	5A	26	02	9A	2F	5A	26	02
C110	94	2F	5A	5A	26	0A	7F	00	3F	9B	2F	24	03	7C	00	3F
C120	5A	26	0A	7F	00	3F	90	2F	25	03	7C	00	3F	DE	2A	A7
C130	00	39	86	E0	97	2C	7C	00	2D	DE	2C	96	0D	AB	00	A8
C140	FF	97	0D	39	07	C1	79	0A	C1	7D	15	C1	82	18	C1	85
C150	1E	C1	89	29	C1	93	33	C1	DE	55	C1	FA	65	C2	04	CE
C160	C1	44	C6	09	A6	00	91	29	27	09	08	08	08	5A	26	F4
C170	7E	E0	8D	EE	01	96	2E	6E	00	96	20	20	B0	BD	C2	C4
C180	20	AB	97	20	39	16	7E	C2	E1	5F	9B	27	97	27	D9	26
C190	D7	26	39	CE	C1	BC	84	0F	03	03	4A	2A	F3	EE	00	DF
C1A0	1E	CE	00	08	DF	26	C6	05	96	1E	84	E0	A7	04	09	86
C1B0	03	79	00	1F	79	00	1E	4A	26	F7	5A	26	EB	39	F6	DF
C1C0	49	25	73	9F	E7	9F	3E	D9	E7	CF	F7	CF	24	9F	F7	DF
C1D0	E7	DF	B7	DF	D7	5D	F2	4F	D6	DD	F3	CF	93	4F	DE	26
C1E0	C6	64	8D	06	C6	0A	8D	02	C6	01	D7	0E	5F	91	0E	25
C1F0	05	5C	90	0E	20	F7	E7	00	08	39	0F	9F	12	8E	00	2F
C200	DE	26	20	09	0F	9F	12	9E	26	34	CE	00	30	D6	2B	C4
C210	0F	32	A7	00	08	7C	00	27	5A	2A	F6	9E	12	0E	39	D6
C220	29	7F	00	3F	DE	26	86	1C	97	1C	C4	0F	26	02	C6	10
C230	37	DF	14	A6	00	97	1E	7F	00	1F	D6	2E	C4	07	27	09
C240	74	00	1E	76	00	1F	5A	26	F5	D6	2E	8D	28	96	1E	8D
C250	15	D6	2E	CB	08	8D	1E	96	1F	8D	0B	7C	00	2F	DE	14
C260	08	33	5A	26	CB	39	16	E8	00	AA	00	E7	00	11	27	04
C270	86	01	97	3F	39	96	2F	84	1F	48	48	48	C4	3F	54	54
C280	54	1B	97	1D	DE	1C	39	7F	00	18	BD	E0	84	BD	E1	2F
C290	27	2B	BD	E0	DD	CE	80	20	86	01	A7	02	BD	E1	3A	26
C2A0	0A	A6	02	81	20	27	16	68	02	20	F1	16	4F	CE	E3	DC
C2B0	E1	00	27	0D	8C	E3	EB	27	04	03	4C	20	F3	7C	00	18
C2C0	39	97	17	39	DF	12	8D	BF	7D	00	18	26	F9	8D	10	BD
C2D0	E1	2F	26	FB	BD	E0	DD	96	17	DE	12	39	FF	FF	FF	C6
C2E0	04	D7	21	C6	35	F7	80	05	7D	00	21	26	FB	C6	3D	F7
C2F0	80	05	39	FF	FF	FF	7A	00	20	7A	00	21	7D	80	04	3B
C300	8D	03	7E	C0	00	CE	C2	F6	FF	A0	00	0E	CE	80	04	6F
C310	01	C6	FF	E7	00	86	3D	A7	01	E7	00	39	FF	FF	FF	FF
C320	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF
C330	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF
C340	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF
C350	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF
C360	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF
C370	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF
C380	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF
C390	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF
C3A0	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF
C3B0	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF
C3C0	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF
C3D0	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF
C3E0	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF
C3F0	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF

Here is the complete hex listing for the author's modified CHIP-8 interpreter, to suit the adapted mEK6800D2 kit. As you can see, almost a quarter of the 2708 EPROM is left unused.

ATTENTION ALL SORCERERS

TURN YOUR APPRENTICE INTO A MASTER WITH OUR TWIN 8" DOUBLE DENSITY WIZARD DRIVES.

For immediate connection to your S-100 expansion interface at less than \$3,000.00 you can have the magic of 1 megabyte on-line storage with industry standard CP/M™ operating system.

For larger spells this system is expandable up to 4 megabytes!

You can soon give your sorcerer's crystal ball the advantages of 3D Colour Graphics

Optional Hardware

- Memory expansion S-100 board
- Speech synthesis and recognition
- 240V device controller
- Additional I/O ports
- Hardware clocks

Optional Software

- Microsoft disk extension basic
- C-basic 2
- Fortran
- Cobol
- APL
- QSORT
- NADS
- Selector III-CII
- CP/M™ Utilities
SID, TEX, MAC

Others available on request


JOHN F. ROSE
COMPUTER SERVICES PTY. LTD.

P.O. BOX 817
CROWS NEST
2065
(02) 439-1220

AMA HOUSE
33-35 ATCHISON ST
ST. LEONARDS 2065
TELEX AA27901

CP/M IS A REGISTERED TRADE MARK OF DIGITAL RESEARCH

Microcomputer News & Products

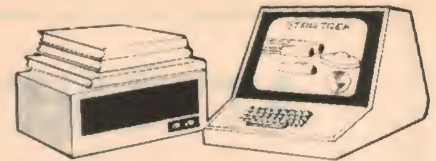

Melbourne's Home Computer Show a roaring success



Peter Alpar from Futuretronics puts the Bridge Challenger through its paces at the recent Melbourne Home Computer Show.

The Home and Small Business Computer Show held in Melbourne in September continued the impressive growth seen at earlier shows. Total attendance over the four days was 17,400, well up on the 14,000 who attended the May show in Sydney and the 6000 who visited last year's Melbourne show.

Some 2000 of those who visited the show were secondary school students, in official school excursion groups. This indicates the degree of interest being generated by computers at secondary school level.

Some 59 exhibitors had stands at the show, displaying the latest personal and small business systems as well as

microprocessor based products for the mass consumer market. A program of seminars was also held on the second day, and these were well attended.

In the second round of the Australian Computer Chess Championships, the Fidelity Electronics Chess Challenger (marketed by Futuretronics) again proved itself superior to all competition. A door prize of a Dick Smith System 80 computer was won by Mr Disseldorp, Pascoe Vale, Victoria.

NEXT SHOW

The next Home and Small Business Computer Show is planned for Adelaide, in March. After that there will be the next Sydney show, to be held in the Westco pavilion at the Showgrounds, from May 22 to 25. Further details regarding both shows are available from the organisers, Australian Seminar Services, 190 Albert Road, South Melbourne 3205. Telephone (03) 690 3833.

DON'T BUY A 6809 CARD YET FIRST CHECK OUT OURS OTHERWISE YOU'LL BE SORRY!

The 6809 is the most advanced 8 bit microprocessor with many 16 bit operations. It deserves more than just being plonked on a PCB with the usual RAM, PROM, I/O and standard Monitor.

PP's 6809 Card has advanced memory mapping and protection hardware with a powerful Monitor to match.

- No more worn out edge connectors — reconfiguration of hardware is done by software, not by switching switches or swapping cards.
- Plenty of addressing capability — 4 x 64K address spaces.
- Memory protection hardware — interrupts to Monitor which prints diagnostics.

- Supports proper operating system — system has privileged control of memory map and I/O.
- Software controlled Baud rates.
- Motorola Exorciser compatible.



Pennywise Peripherals
Pennywise Peripherals

19 Suemar Street, Mulgrave, Vic, 3170.
Phone (03) 546 0308.

ONYX C8000



Computerland has announced the availability of the Onyx C8000, claimed to be one of the new generation of microcomputer systems and probably the most powerful microcomputer currently available. It sports many of the features normally considered by the EDP industry to be essential in a business system: Memory parity, a full 64K memory, run time monitor with start-up diagnostics, an "orderly shut-down" routine, fully integrated 10 megabyte hard disk (20cm Winchester technology), an integrated backup system with 12 megabyte cassette storage, and a comprehensive and powerful operating system (OASIS or PASCAL) with full complement of languages — BASIC, FORTRAN, COBOL and a full line of business and commercial applications packages.

The C8000 has three serial ports and one bidirectional parallel port. One serial port is programmable to support data communications and will interface with most synchronous and asynchronous modems. The 8-bit parallel port has six general-purpose control lines and can be programmed as either an industry standard (Centronics) printer interface or as a DMA controlled bidirectional port for connecting the C8000 to another computer.

UPGRADES TO Z8000

The basic C8000 uses a Zilog Z80A microcomputer. However it can be upgraded at any time by the addition of a 16-bit Z8000 processor, a two-hour field conversion. This gives a system with either 256K or 512K bytes of RAM and the ability to support up to eight user terminals. The original Z80 board is not made obsolete by this upgrading — it becomes an intelligent file management system for the Z8000 host processor.

Further information on the Onyx C8000 system is available from Computerland, 55 Clarence Street, Sydney.

MICRONEWS
CONTINUED



LOOKY VIDEO

FREE \$200 PET PROGRAMS ONLY WITH 8k

PET COMPUTERS
8k — \$1499
16k — \$1750

FREE PET "SOUND" INTERFACE

OHIO COMPUTERS SUPERBOARD II 4k
4k EXPANSION KITS
TRS-80 LIBRARY 100 PROGRAMS & DIRECT INTERFACES
TRENDCOM PRINTER & MANY INTERFACES
MONITOR TV's WITH SOUND
B&W AND COLOUR
NATIONAL PORTAPACKS & NEW MODEL VHS
VIDEO CAMERAS B&W PISTOL GRIP
TRIPOD TYPE
PISTOL COLOUR
PROGRAMMABLE TV GAMES & CARTRIDGES
WIDE RANGE OF VIDEO EQUIPMENT

\$395
\$485
\$67.92
\$345
\$296
\$999

BRUCE FISHER VK3YRF/ATV
DUBBING and EDITING from \$10 per hour
CASH — CARDS — TERMS — LEASING

LOOKY VIDEO
The home TV recorder experts
Video experience since 1969
Write to:
PO Box 347, Richmond, Vic 3121
418 Bridge Rd.
Richmond, Vic 3121
Tel (03) 429 5674

MELBOURNE'S BYTE SHOP

MELBOURNE: 17 ARAWATTA ST., CARNEGIE 3163.

PHONE: (03) 568-4022

SYSTEMS MEMORY

Z80, 8080, and 6800 based.

RAM — 8, 16 & 32K

ROM — 4, 8, 16 & 32 utilizing 2708 or 2716.

INPUT/ OUTPUT

5" mini floppy, 8" Persci dual floppy, 8" IBM compatible floppy; cassette; VDUs; Keyboards; printers; monitor.

SPECIAL PURPOSE

Prototyping boards; digital to analog converters, data acquisition, PROM programmer, speech recognition, speech synthesizer, music synthesizer, interfaces built to your requirement.

HARDWARE

Transformers (suited to S100 bus supply), bridge rectifiers, low profile IC sockets, special components, S100 sockets, guides and chassis.

SOFTWARE

BASICS, PASCAL, FORTRAN IV and COBOL, Macro Assembler, Assembler/Disassembler, Disc operating systems, Word processors, Inventory, Data Base Management, Business Systems.

KILOBAUD

U.S. magazine — understandable for beginners, interesting for experts. New readers only send \$3.00 for a copy now.

Send \$1.00 for quarterly newsletter per annum charge, and \$5.00 for quarterly product and price updates.

MELBOURNE'S BYTE SHOP, P.O. BOX 156, CARNEGIE, VIC 3163

Opportunity Chips

three brand new, fresh off the line chips designed to get you into the market place fast



1 How about a single chip **Keyless Lock** in a 14-pin DIP for around **\$2.63***. Package it your way. We'll even help you with a low cost keyboard to suit. Ask for LS7220.

2 A 14-pin **Hi-in-Low** fully adjustable **Frequency Trip** for Flow Meters, Tachos, Tone decoders or anywhere you need to keep track of pulse rates. Simple to use and only **\$5.89***. We'll call it the FX 701P.

3 This Keyboard programmed **Multi-step Timer** even drives LEDs directly. At **\$6.90*** WD55 is our latest opportunity chip.

* 100 up price +15% sales tax

If you've got an idea that needs a little silicon lubrication to get it moving . . . we'd like to chip in.



daneva control pty.ltd.

70 Bay Road, Sandringham, Vic., 3191. Ph: 598-9207. Telex: AA34439
AGENTS: Sydney: 51-5880. Adelaide: 42-6666. Brisbane: 36-5183.
ACT: 82-4995. Perth: 325-2444. Hobart: 44-1337. N.Z. (63) 85-702.

also available through computer stores and electronic wholesalers

Microcomputer News & Products

S100 SLAVE PROCESSOR

Microprocessor Applications Pty Ltd, a small Melbourne-based firm, have released a new S100 slave interface board. The board may be used for a variety of tasks as it features its own 8085 microprocessor with 4k of usable RAM and 2k of EPROM. An RS232 port is also provided with software-selectable Baud rate.

Initial applications include allowing the board to emulate Burroughs' "polling and select" protocol without affecting the main S100 processor. A "direct connect" adaptor (TDI) is also available.

For further information, contact Microprocessor Applications on (03) 754 5108.

APPLE CORVUS

Corvus Systems has announced an interface which allows Apple II microcomputers to be connected to a 20cm Winchester-technology hard disk drive, for memory expansion to 11 megabytes. The new Corvus 11A system consists of an IMI 7710 disk drive with Corvus intelligent controller and power supply, together with an intelligent module for the Apple. The latter consists of an interface card and associated software.

The system software interfaces with the Apple Disk II operating system to provide complete compatibility with DOS commands and existing DOS applications. This is accomplished by maintaining 82 physical volumes on disk, that are sector by sector compatible with Apple memory volumes. All 82 volumes are effectively "on line" concurrently, such that any application program can utilise the entire data base by simple use of DOS syntax.

The Corvus system supports standard Apple II DOS as well as the recently announced UCSD PASCAL language system.

Interfaces for Tandy TRS80 and S-100 systems are being developed.

Electronic Concepts Pty Ltd has been appointed Australian distributor for Corvus. The 11A disk system will be available through Computerland outlets throughout Australia; also from selected agents.

LOGIC SHOP

Situated in Melbourne at 212 High St, The Logic Shop Pty Ltd has just opened with a range of microcomputer terminals and peripherals from CompuColor, Decwriter, Texas Instruments, QUME and others. Take a look, they are well worth investigating.


BRIGHTON TECHNICAL COLLEGE CHOOSES TEKTRONIX

Victoria's Brighton Technical College has ordered five Tektronix 8002A Microprocessor Development Systems. Valued at \$140,000, the equipment is to be used in support of the government's Microprocessor Aid Program (MAP) which is aimed at increasing the industrial and commercial applications of microprocessor technology.

Initially, the Department of Electrical Engineering at the College will employ the system to train engineers in the use of assembler language and the development of systems covering a wide range of microprocessors. However, the scheme will be kept flexible in order to accommodate the needs of local industry and other users.

The Tektronix 8000 Series Micro Development Labs offer support for a wide range of micros allowing the user flexibility in selection of the right chip for each purpose. The range of micros supported by the 8000 Series is being rapidly increased in line with the continued advances in microprocessor design.

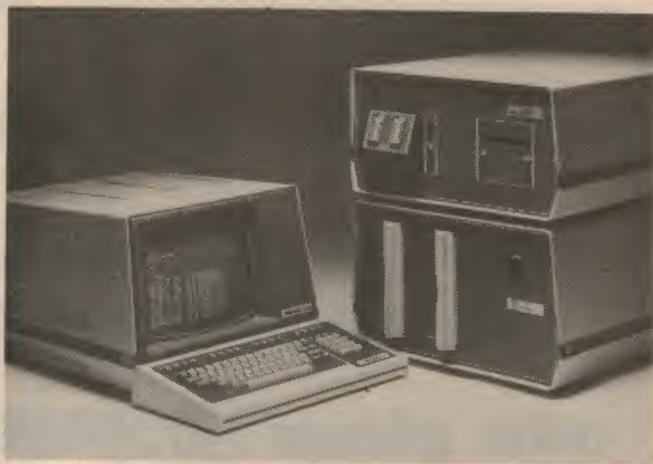Shown is the Tektronix 8002 Microprocessor Development System, of which five have been ordered by Brighton Technical College.



IMS DIRECT MAIL

A software package for the management of mailing lists on small microcomputer systems has been released by IMS Computer Systems, a division of Integrity Management Services Pty Ltd. The package is called the IMS Direct Mail System.

The package caters for any business with a names and address file of clients, prospective clients, users, etc. In addition to having 12 fields covering surname, title, company, position held, address, etc, it contains the date the entry went on to the file plus a 30 digit KEY field. This KEY field allows the user to assign KEY words and place user defined values to each of 20 fields. These fields can then be used, in any combination, to select individuals who satisfy specific selection criteria.

The system can produce reports, write letters and/or prepare labels for those selected. Word processing facilities are included in the package, which comes complete with a comprehensive operating manual for \$500.

The package is written in CBASIC2 and runs under CP/M, the most popular of the operating systems for microcomputers. Hardware which is suitable includes the EDC1, ALTOS, CROMEMCO, VERSATILE 4, SBC1, SUPERBRAIN, etc. IMS can supply the software, the hardware and software system or bureau facilities.

For further information, contact IMS Computer Systems on (03) 51 9156 or (02) 922 6319.

MICRONEWS
CONTINUED



TRS-80® PET® S-100

APPLE® NORTH STAR® MEDICAL & PROFESSIONAL SYSTEMS

*INSTANT SOFTWARE®

OVER 300 PROGRAMS

BUSINESS-HOME-EDUCATION

SCIENCE-GAMES-HEALTH

EASY INSTRUCTIONS

PROFESSIONAL DISKS & CASSETTES

GUARANTEED QUALITY

*TESTED HARDWARE

DEC-LA34 TERMINAL

VERBATIM mini DISKS 1-9\$4-25; 10up \$4

*S-100 BOARDS ASSEMBLED

16K STATIC RAM (2114) \$370

VIDEO 64x16 ETI 640 \$165

EPROM (2708) \$149

VDU \$130

\$1499

\$24 pa.

*SEND FOR FREE CATALOGUE OF SOFTWARE AND HARDWARE-SPECIFY COMPUTER

*NEWSLETTERS-SPECIFY YOUR SYSTEM AND APPLICATIONS

ALL PRICES TAX EXEMPT-ADD 15% WHERE APPLICABLE - F.O.B. HAWTHORN VIC.

SUBJECT TO CHANGE WITHOUT NOTICE

BANKCARD-GIVE NAME NUMBER EXPIRY DATE AND SIGNATURE

MICRODOT® PO. BOX 420 HAWTHORN 3122 AUSTRALIA 03-819 2411



MICROCOMPUTER
APPLICATIONS



TRS-80 Software

LEVEL II CASSETTE

Programme Title	AS	US \$
Cribbage	9.00	7.95
Checkers	8.00	6.95
Fastgammon*	16.00	14.95
Galactic Blockade	9.00	7.95
Pork Barrel	11.00	9.95
Round The Horn	11.00	9.95
Santa Paravia	9.00	7.95
Taipan	11.00	9.95
Accounts Receivable	26.00	24.95
General Accounting	16.00	14.95
Personal Finance	11.00	9.95
Mortgage Calculator	9.00	7.95
Inventory Control	13.00	11.95
Basic Statistics	21.00	20.00
Ham Radio	11.00	9.95
Electronics Asst	11.00	9.95
Ten pin bowling		\$9.00
Kentucky Derby		7.00
Tarot Cards		11.00

TORONTO & ASSOC CONVERSION
OF OSBORNE & ASSOC COMPLETE
BUSINESS SYSTEM

Accts. Receivable	\$150.00
Accts. Payable	\$150.00
General Ledger	\$150.00

SMALL SYSTEM SOFTWARE

Electric Pencil Cassette	\$105.00
Disc	155.00
Air Raid or Barricade	
Or Adventure	16.00 ea
RSM-2 Monitor	28.50
Basic IP Converts LII Into LI	26.00

PITT ST CENTRE

LII Games (Startrek, etc)	\$12.00
LII Basic Instruction Course	32.00
Keno & Game of Life	14.00

HARDWARE

Printer/Typewriter	
Teletype 43	\$1409.00 incl S.T.
Connecting Cable for Ta	
Tandy incl S.T.	30.00
Apparat 16K Memory Kits	103.50
Verbatim Discs 5"	4.86 incl S.T.
Also Tailor Made Systems	500+

Write to:

PITT ST. MICROCOMPUTERS
BOX A344, SYDNEY SOUTH,
PITT ST. 2000

Ph: 235 7229, 569 8228

Tandy Users Club Newsletter, \$10 per annum.
Box 105, Marrickville 2204.

Special : DECEMBER: Ingersoll LCD Calc. \$13.95


We have moved !!

**386 Queens Parade
FITZROY Nth.3068**

new phone: (03) 481 1975

is our new address...

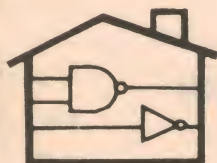*Come and try our
free coffee + friendly
prices*



**Cottage
Computers**

a division of Embryonic Systems Pty. Ltd.

THE SUPERBOARD II

is an excellent choice for
the personal computer
enthusiast

Byte May, 1979

•
**OHIO
SCIENTIFIC
SUPERBOARD II**

\$360 (ex tax)

•
from

COMPUTERWARE

63 Paisley Street,
Footscray, Vic 3011
Tel: (03) 68 4200



SAVE 20 %

WE EXHIBITED THE INCREDIBLE
TI-99/4 HOME COMPUTER AT THE MELBOURNE
"Home & Small Business Computer Show"

Now, before you rush out and buy any brand of Home
Computer get all the facts on "TI BASIC" first.

If you know anything about BASIC, you'll quickly recognize
that TI BASIC is a rich, highly versatile language. In addition
to a full complement of 33 statements, 19 system functions
and 14 commands, TI BASIC features extremely easy-to-use
colour graphics capability (with 16 colours) and simple-to-
access sound and music that allows the playing of tones over
a five octave range and up to three notes simultaneously. You
can control duration and volume of sound. The TI BASIC
graphics sub-program enables you to use the TI-99/4 to create
colourful designs graphs, charts, pictures, gameboards and so
on right on your screen. Combined with the CALL COLOUR
sub-program, the easy-to-use TI BASIC capability makes
creating graphics almost as simple as typing data. You can
create three-dimensional images, the object can be rotated,
magnified several times, and even be re-designed.

Additional features of TI BASIC:

- * Dynamic string variables up to 255 characters.
- * In-line editing with program re-numbering capability.
- * Powerful program debug features, breakpoints and trace.
- * Variable names up to 15 characters.
- * English language error messages.
- * and many more special features.



THIS IS THE TI-99/4 HOME COMPUTER

- I HAVE BEEN DESIGNED BY TEXAS INSTRUMENTS,
- USE THE "TI BASIC" LANGUAGE AND SPEAK
- I USE THE POWERFUL 9900, 16-BIT MICROPROCESSOR
- I HAVE THE EXTENDED 13 DIGIT "TI BASIC"
- I CAN DO COMPLEX SCIENTIFIC CALCULATIONS
- I HAVE POWERFUL PROGRAM DEBUG FEATURES
- I HAVE STRING VARIABLES UP TO 255 CHARACTERS
- I HAVE 128 GRAPHIC CHARACTERS
- I USE A COLOUR VIDEO DISPLAY PROCESSOR CHIP
- I HAVE 16 COLOUR GRAPHICS CAPABILITY
- I HAVE SOUND, 5 OCTAVES/UP TO 3 NOTES
- I HAVE SOLID STATE SOFTWARE
- I HAVE THE SOLID STATE SPEECH SYNTHESIZER
- I HAVE RS-232 INTERFACE
- I WILL HAVE A DISK MEMORY & PRINTER
AND A LOT MORE

TO: DELTA SCIENTIFIC PRODUCT DISTRIBUTION
Distributor for TEXAS INSTRUMENTS
Red Bank Court, St. Albans 3021, Vic. Australia

Please rush me my copy of "PROGRAMMING BASIC WITH
THE TI HOME COMPUTER" plus your 144 page Texas Instru-
ments Product Catalogue. I understand, that I will get a total
value of \$18.50 less full 20% discount. I pay only \$14.80 inclu-
ding postage and packing. This further entitles me to a free
\$15.00 GIFT VOUCHER towards the purchase of the TI-99/4
Home Computer.

NAME:

ADDRESS:



Get the full facts on TI BASIC
by ordering the 306 page book
"Programming BASIC with the
TI Home Computer".
First shipment of books
sold within 3 days.
New shipment arrives
November.
Be early.

DEALER ENQUIRIES FOR ALL TI PRODUCTS INVITED

Microcomputer News & Products

Analex Printer

Bell and Howell has announced an addressable printer interface for connecting the Analex DP-8000 printer with the Commodore PET microcomputer. The interface is supplied in OEM form and attaches directly to the back of the Pet IEEE port. A hard wired cable connects to the DP-8000 input port. The interface also provides an IEEE port for connection of other peripherals.

A new pricing schedule has also been announced for the DP-8000 printer, to encourage the growing OEM market. The new schedule offers attractive OEM discounts starting at \$850 plus tax for quantities of 1-15.

Further details from the Electronics and Instrumentation Division of Bell & Howell Australia Pty Ltd, 55-69 Murray Street, Pyrmont NSW.

New DREAM 6802

J. R. Components, PO Box 128, Eastwood, NSW, have produced a new version of the very successful DREAM 6800 microcomputer published earlier this year in this magazine. Using a new PCB and the new 6802 microprocessor which has its own internal clock, the new design neatly solves the problem of non-availability of the 6875 clock chip. J. R. Components have also produced a 2.5 amp version of the power supply to cope with any likely expansion.

SWTP Distributor for Victoria

G.F.S. Electronic Imports, of 15 McKeon Road, Mitcham, Victoria, have been recently appointed Victorian distributor for South West Technical Products Corporation.

In Brief

● There is a rumour circulating that pioneering US microcomputer firm Im-sai has been declared bankrupt. Also that Processor Technology has ceased manufacturing, for unspecified reasons.

● Cromemco has released a hard disk system using a 20cm Winchester drive, to provide 11 megabytes of storage. As an upgrade facility the HDD-11 system comes in the same case as the System 11, and costs \$6750. Further details from Melbourne's Byte Shop, 17 Arawatta Street, Carnegie, Victoria 3163.

● Patents have apparently been granted to Apple Computer Co in the USA for the switching-mode power supply and video display designs in their Apple II microcomputer. As it is unusual for patents to be either sought or granted for such "run of the mill" circuit subsystems, Apple is particularly proud of the new patents. Both subsystems were designed by Apple's vice-president, Rod Holt, in 1976.

From the clubs ...

Computerland of Adelaide, 131 Pirie Street, has been selected as the venue for the Apple Computer User's club.

First meeting was scheduled for October 23. Membership is open to anyone interested in Apple Computers, not just existing users. There are now over 600 Apple computers in use in Australia. Further information may be obtained from Computerland of Adelaide.

A new microprocessor club has been formed in Manly, NSW. They meet on the second Monday of each month at the Manly Youth Centre, Kangaroo St, Manly (behind the War Memorial Club). They extend an invitation to all people interested in both hardware and software aspects of microcomputers. All age groups are catered for. More information is available from Lionel Hirning on (02) 98 7338 or Ron Bloom on (02) 938 1476.

● The new secretary of the Tasmanian Amateur Computer Society is Richard King, replacing Clive Myers who has resigned. Mail address of TACS is PO Box 474, Sandy Bay, Tasmania 7005. ☺

TRS-80 SOLUTION

HARDWARE	
3 speed modification — a very simply kit	
Blank computer cassettes	\$29.95
Leadless guaranteed no dropout	\$1.80
5 — \$8.00	10 — \$16.00
SOFTWARE	
Sargon (version 2) stocks available December	
Microchess "Still the Best Seller"	\$25.00
Bridge Challenger — Level 2 4K	\$24.00
"Never be without a partner"	\$21.00
Othello Level 1 and 2 4K	\$12.00
Business Package 6 cassettes — level 1 4K "6 pack"	\$29.00
1Q Builder — Vocabulary TRS80L2	\$16.00
Golf and Crossout "2 programmes"	\$9.00
1Q Builder — Pre School TRS80L2	\$16.00
Game Playing with Basic "TRS80 — Apple — Pet" Tape 1	\$12.50
Tape 2	\$12.50
Tape 3	\$12.50
10 Pin Bowling "4 zones and 9 angles"	
TRS80 L1 4K & L2 16K	\$9.00
How to Build a Computer, Controlled robot	\$18.50
Santa Paravia "Become the ruler of a Medieval City"	\$11.00
Graphics TRS80L1 & L2	\$9.00
General Mathematics TRS80 L1 & L2 — Apple 2	\$12.50
Space Trax IV "Trade or Wage War on a Planetary Scale"	
TRS80L2 16K	\$9.00
Oil Tycoon, "Become the world's richest tycoon"	\$9.00
L1 & L2 4K	\$9.00
Complex Matrix Mathematics — Pet	\$18.50
Clone 2 — allows you to copy any programme, display ASCII on screen when loading, shows file name, add axes, copies poorly recorded tapes. A must to protect your programmes by making back up.	\$18.00
Electric Pencil "Michael Schreyer"	
The ultimate word processor L2 16K	\$99.00
First book of Kim Tape 1, 2 & 3	\$12.50
Introductory Engineering Mathematics TRS80 L2 — Apple 2 & Pet	\$12.50
BOOKS	
Basic Basic 2nd Ed. "Every home should have one"	\$11.00
Advanced Basic	\$11.00
Basic from the Ground Up	\$11.00
Basic Workbook	\$7.50
Discovering Basic	\$8.50
Game Playing with Basic	\$10.00
Some Common Basic Programs	\$12.50
The First Book of Kim	\$12.50
Sargon	\$19.00
How to Build a Computer controlled Robot	\$15.00
How to profit from your Personal Computer	\$11.00
An Introduction to Microprocessors	\$11.75
An Introduction to Microprocessors L2	\$12.50
280 Programming for Logic Design	\$12.50
280 Assembly Language Programming	\$13.60
Payroll with Cost Accounting — Osborne	\$20.00
Accounts Payable & Receivable — Osborne	\$20.00
General Ledger — Osborne CB/M	\$20.00
PROGRAMMING AIDS	
Combination Coding/CRT Forms In 50's	2 pads \$8.50
In pad form	10 pads \$30.00
Loose leaf	50 pads \$145.00
Flow chart sheets 280mm x 406mm in 50's	2 pads \$10.00
	10 pads \$45.00
	28 pads \$103.00
Giant print out design sheets 368 x 558mm in 50's	1 pad \$10.50
	5 pads \$37.50
	16 pads \$109.00
SUNDRIES	
Diskettes "Scotch" 5 1/4's	1 — \$8.25
The Best — Don't risk your data	10 — \$7.50
with cheaper disks	50 — \$6.50
Anti static Mat 24" x 20" (A must)	\$70.00
Combination QSL Album & Log Book	\$9.95
Binders for CB Action	\$6.50
Binders for Amateur Radio Action	\$5.50
QSL Cards (SAE for samples)	

DEFOREST SOFTWARE

QUALITY QSL PTY. LTD.

26 STATION STREET, NUNAWADING, VICTORIA 3131
TELEPHONE: (03) 878 9276 (03) 877 6946

Postage is included at no charge, however we suggest certification or registration. DISCOUNTS: any 3 items (min. total \$30) Less 10%, Schools less 10% — Trade Enquiries Welcome.

SOFTWARE FOR

APPLE, PET, TRS80 AND 6800

PIE (PROGRAMMA IMPROVED EDITOR) is a two-dimensional cursor-based editor designed specially for use with memory-mapped and cursor-based CRT's. It is totally different from the usual line-based editors which were originally designed for Teletypes. The keys of the system input keyboard are assigned specific PIE Editor function commands. Some of the features included in the PIE system are: Blinking Cursor; Cursor movement up, down, right, left, plus tabs; Character insert and delete; String search forwards and backwards; Page scrolling; GOTO line number, plus top or bottom of file; Line insert and delete anywhere on screen; Move and copy (single and multiple lines); Append and clear to end of line; Efficient memory usage. The following commands are available in the PIE Text Editor and each is executed by depressing the systems argument key simultaneously with the command key desired.

ALL PROGRAMMA INTERNATIONAL SOFTWARE

AVAILABLE FROM:

J. H. Macgrath & Co Pty

Paris Radio Electronics Ltd
(02) 31 3273

(03) 663 3731

GFS Electronic
15 McKeon Road
Mitcham
Victoria
Australia 3132
(03) 873 3939

PROGRAMMA Software Products




The COMMODORE PET is a completely self contained personal computer. Just plug in, and within a few short hours even the complete novice will be amazed at what can be done. The 8K model is shown. The 16K and 32K models have full size typewriter keyboard and numeric pad. External Cassette, Dual Drive Intelligent Minifloppy and Printers are also available. All models are expandable to 40K and have a built in real time clock. PET FOOD A large range of programs including games, business applications and even a program to teach yourself Basic are available. \$200 WORTH OF PROGRAMS FREE WITH EVERY 8K PET.



We handle the complete TRIO test equipment range. The CS-1352 Dual Trace C.R.O. pictured above features 15MHz bandwidth, 2mV/div, 0.5S to 0.5uS/cm. and AC-DC-Battery operation. \$740 includes rechargeable batteries. PC-29 probes to suit CS-1352 \$32 ea.



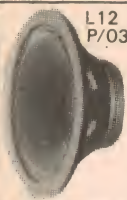The B & K range of Test Equipment includes quality laboratory standard units such as the Model 283 Digital Multimeter shown above — \$211. Other gear includes Signal & Function Generators, Power Supplies, Capacitance meter, Frequency Counters and Semiconductor Testers.



L12 P/03 RCF manufacture a large range of PA, Hi-Fi and Disco sound equipment including speakers (system & components), amplifiers, pre-amps, mixers, microphones, crossovers, and all accessories. For example the L12P/03 (pictured) is a 320mm professional 80HM loud speaker rated at 35 Watts RMS (50 Watts Peak) and with a 75 to 7000Hz response. Cost is only \$57.00 ea.



HO25H02

The range of Plessey Foster speakers include Wide Range, Guitar, Woofers, Mid Range, tweeters and Crossovers. For example the HO25H02 pictured, is a Mid Range Horn 8 ohm speaker with 12W RMS (30W Peak) power handling and a response from 1500 to 14,000Hz. Cost is only \$17.00 ea.



KSN1001



KSN1025

In our range are the Motorola Piezo-Ceramic tweeters. For example, take the two pictured. The KSN1001 A will handle 100W with a response from 4K to 30KHz. The KSN1025 A will handle 150W with a 2K to 30KHz Response. These tweeters feature excellent transient response, low distortion, high impedance, high reliability and light weight. The KSN1001 A is only \$11.00 and the KSN1025 A is only \$21.00 (no crossover is required).



G.E. PAR 38 100W coloured floods. Made in USA. E.S. mount
1 — 11 \$5.50 ea.
12+ \$5.00 ea.
While stocks last.
Red, blue, green, yellow — Please specify colour.

D size NiCad Rechargeable Batteries, Heavy Duty 4 AH cells which comply with US Military specification: \$8.00 ea.
½ D and ¾ D also available. D size Lithium batteries, 3.4V, 10 year shelf life, high stability — \$14 ea.



HANIMEX SAFETY EYE Radar Detector, X and K band, 1030m range, top value. See March 1979 Modern Motor for review. Extra brackets available. \$90.00

SONALERT SC628 6-28 Volts continuous 2900Hz tone \$11.50
AUDITEC Complete range of preamps, mixers, power amps and power supply modules available. 018 High Quality Power Amp, 60W RMS into 4, 35W RMS into 8, 10Hz-20KHz, 0.1% THD, 1V Input, Output fully short circuit proof: \$51.00
CENTRAL DATA 2650 COMPUTER SYSTEM
Computer Board Kit \$285, Built & Tested \$428
S100 Board Kit \$140, Built & Tested \$160
16K Dynamic Memory Board — Built & Tested \$376 (2MHz)
— 4MHz version \$396 (compatible with Cromemco Systems)

— expandable to 64K with just IC's — see ETI October 1979 for review.
SPARKRITE ELECTRONIC IGNITION — Save fuel, up to 10% on 4 cyl, 15% on 6 cyl and 20% on 8 cyl cars (depending on state of tune) and your car will stay in tune longer — \$110.00

All prices include Sales Tax and Road or Rail delivery to your door/nearest railway station. Extra information is available and we invite your enquiries. Please note that all prices, details and predicted availability were correct at time of going to press.

EDIBLE ELECTRONICS

P.O. BOX 1053, RICHMOND NORTH, 3121. PH. (03) 415708




The S100 Slave

Power-on reset, plus 'on board' switch for stand alone use

8 Bit DIP Switches or parallel input via flat cable.

2K EPROM

4K RAM

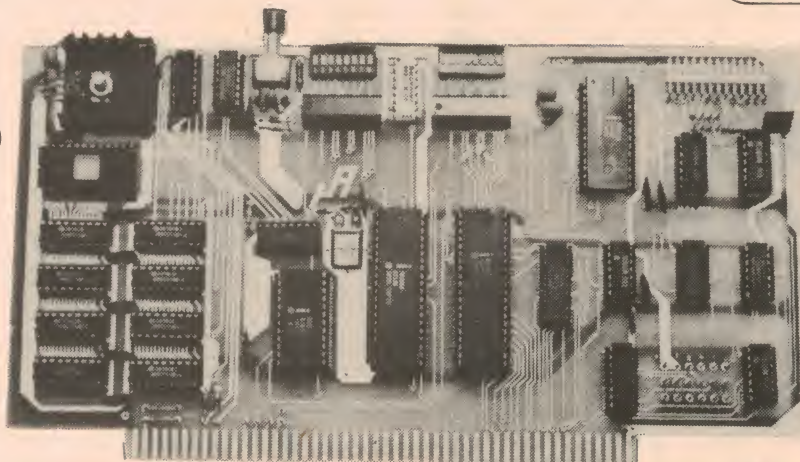

RS232 Cable Connector with power output to drive remote adapters.


Asynch or Synchron Usart Software selectable Baud Rate.

FAST 8085 CPU

Standard S100 Bus

Address selection

Initially designed for the "Versatile" computer this exciting new board is now available for use on any S100 Bus system. This Serial I/O Controller (SIOC) will allow your S100 Bus computer to handle polling and select protocol to a main frame computer! We have software available to allow emulation of Burroughs protocol and more is on the way. But you need not wait for us! Program the slave anyway you want and "unburden" your main processor.

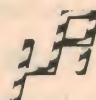


MICROPROCESSOR APPLICATIONS PTY LTD
(03) 754 5108

Maskells Hill Road, Selby, Australia 3159.
"Small computers solving large problems"

Electronic bongo drums

Basic Electronics

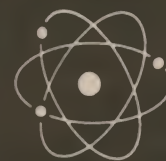

by GERALD COHN

Did you know that a simple circuit can give a remarkably realistic simulation of a set of bongo drums? In this article we show how to make your own electronic bongos for a fraction of the price of the real thing. And you can play them in exactly the same way as with real bongos.

With the advent of synthesizers, it has become possible to simulate just about all musical instruments. Even the magnificent pipe organ has been challenged by its electronic counterparts. But while many instruments are quite difficult to simulate, percussion instruments such as bongo drums are a "piece of cake". You don't need anything as complicated as a synthesizer.

The reason why it is easy to simulate the sound of bongos and other percussion instruments is that their physical behavior is relatively easy to analyse and understand. And having been analysed, it turns out that the electrical analogue is a simple and familiar circuit.

Percussion instruments may be broadly defined as those which are struck, whether by hand, drumsticks or other implements. Rigid objects which are struck forcibly tend to vibrate with the frequency, waveform and duration of the vibration dependent on the type

of material and its shape.

For example, if the object to be struck is a tuning fork it will vibrate at a single frequency and the waveform will closely approximate a sinusoid, or in more familiar terms, a sine wave. The vibration will be sustained for a relatively long time.

At the other extreme, if the object to be struck was a large block of concrete, the resulting vibration would be small and of short duration. In describing the vibration we would say it was heavily "damped". By contrast, the tuning fork has a vibration which is lightly damped.

In between these two extremes fall most percussive instruments. To simulate these, we create an electrical analog: a circuit which resonates in a controlled manner when an electrical impulse is applied to it. This circuit will have a means for setting the frequency of oscillation (or vibration) and a means for controlling the damping of the oscillation.

One possible form of this electrical

analog is the twin-T oscillator. For a set of bongos, two of these oscillators are required. Our circuit uses two twin-T oscillators and very little else.

The name "twin-T" is a reference to the configuration of the two RC phase shift networks in each oscillator. Sometimes this oscillator circuit is also referred to as a "parallel T" oscillator.


Each oscillator can be considered to be a common-emitter amplifier with a feedback network connected between collector and base. In this case, the feedback network is the "twin-T". In our circuit, one "T" is comprised of two 56k resistors in series, together with a capacitor from their junction to the negative rail. The other "T" comprises two .01uF capacitors in series with a 50k pot connected from their junction to the negative rail.

The "twin-T" is actually a nulling network which produces a maximum attenuation at its centre frequency together with a phase shift of 180 degrees. Now if we use this network as the feedback path of a common-emitter amplifier we find that the inherent 180 degree phase shift in the C-E amplifier plus the phase-shift of the twin-T adds up to 360 degrees at the centre frequency.

This means that positive feedback is being applied to the amplifier at the centre-frequency of the twin-T network. Thus we have an oscillator.

The twin-T oscillator may be made to oscillate continuously or it may be adjusted so that it oscillates for a short period, with controlled decay, when fed with an electrical impulse. In our circuit, each oscillator will produce a continuous sinewave output when the 50k potentiometer is set to a minimum.

Increasing the resistance of the 50k pot will cause the amplitude to decrease to the point where the oscillator stops altogether. At this point the oscillator is said to be "quiescent". An electrical impulse applied to either of the two T-networks or to the base of the transistor will then shock the circuit into brief oscillation, and the degree to which the oscillation is sustained will depend upon the setting of the pot. If it is set for maximum resistance, the oscillation will decay very quickly.

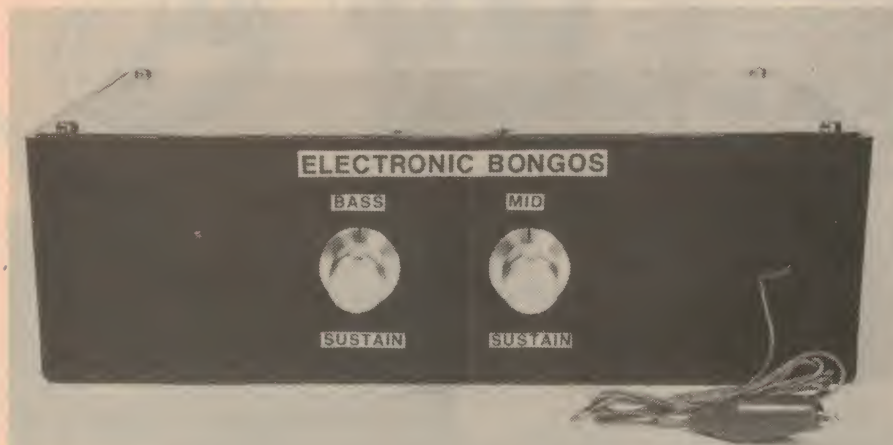

Two potentiometers allow the Bongos to be individually tuned.

HUGE PRICE/TECHNOLOGY BREAKTHROUGH!



**JUST IMAGINE!
A FULL T-R
(transmit/receive)
DISCRIMINATOR
METAL DETECTOR
FOR UNDER
\$300⁰⁰!!!**

find **GOLD** and hidden treasure with **T.R. DISCRIMINATOR** treasure detector

The computerised transmit/receive metal detector
that can actually discriminate treasure
from rubbish - and at an incredibly low price!

★ Most metal detectors can't tell treasure from rubbish - this one can, as the discriminator microprocessor can compare ferrous and non-ferrous metals.

★ Uses an integrated circuit discriminator designed by a brilliant U.S. ex-military engineer.

★ Other discriminator-type metal detectors sell on the Australian market for \$300 - \$480!!

IN AUSTRALIA TODAY

literally millions of dollars simply lies in the ground, waiting to be found...
Not just gold nuggets, but also old coins, artifacts and other treasure!




Make money while you're paying for it - ask about our TERMS

ONLY

\$125⁰⁰

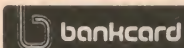P&P \$3 anywhere in Australia
Cat. X-1065



★ The system uses a microprocessor circuit which replaces all the conventional complicated knobs.

★ No this is not a "Toy" type B.F.O. metal detector - it's one of the most sophisticated electronic devices ever offered for the price.

MADE IN THE USA
by the world's largest
metal detector company



DICK SMITH ELECTRONICS

NSW 125 York Street,
147 Hume Highway,
162 Pacific Highway,
30 Grose Street,

SYDNEY. Phone 290 3377
CHULLORA. Phone 642 8922
GORE HILL. Phone 439 5311
PARRAMATTA. Phone 683 1133

263 Keira Street,

WOLLONGONG Phone 28 3800

EXCEPT WHERE NOTED, ALL ITEMS SHOWN IN STOCK AT PRICES GIVEN AT TIME OF GOING TO PRESS.

MAIL ORDER CENTRE: PO Box 321, NORTH RYDE NSW 2113. Ph 888 3200. PACK & POST EXTRA.

ACT 96-98 Gladstone Street,
VIC 399 Lansdale Street,
656 Bridge Road,
QLD 186 Logan Road,
SA 203 Wright Street,
WA 414 William Street,

FYSHWICK. Phone 80 4944
MELBOURNE. Phone 67 9834
RICHMOND. Phone 428 1814
BURANDA. Phone 391 6233
ADELAIDE. Phone 212 1962
PERTH. Phone 328 6944



SHOPS OPEN 9AM to 5.30PM
(Saturday: 9am till 12 noon)
BRISBANE: Half hour earlier.
ANY TERMS OFFERED ARE TO
APPROVED APPLICANTS ONLY
RE-SELLERS OF DICK SMITH
PRODUCTS IN MOST AREAS OF AUSTRALIA.




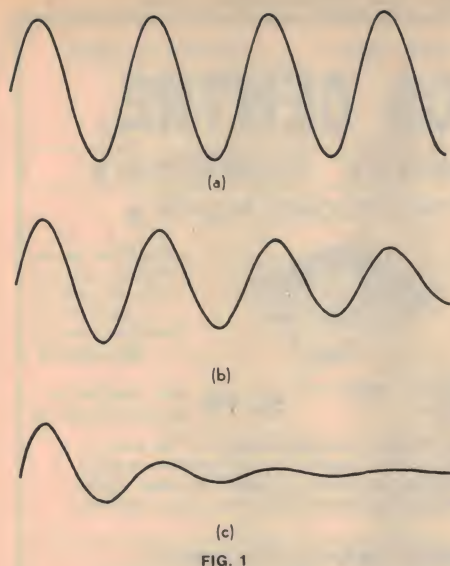


FIG. 1

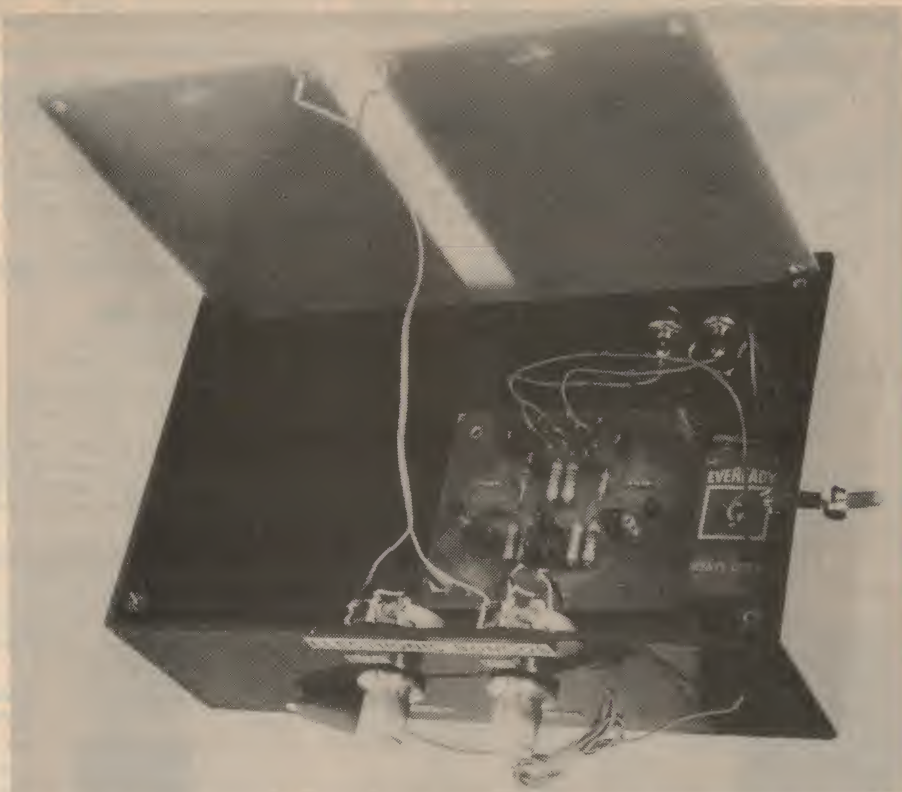The above waveforms show the three modes of oscillation possible with a twin-T oscillator: (a) continuous; (b) lightly damped; and (c) heavily damped.



This photograph shows the internal construction of the unit. The two 47k resistors in series with the touch plates can be seen mounted underneath the touchplate PCB.

On the other hand, if the 50k potentiometer is set so that the circuit is just on the point of oscillation, the result of an electrical impulse will be oscillation which decays very slowly.

Fig 1 shows the modes of operation that are possible. 1(a) shows a continuous oscillation at a constant amplitude, 1(b) shows a lightly damped oscillation and 1(c) shows a heavily damped oscillation.


The electrical impulse to shock the oscillator into the ringing mode is obtained by touching the plates connected to the junction of the T-

networks containing the pots. In some cases the "stray" hum fields will be strong enough for the oscillators to be triggered when the plates are touched, (ie, the hands are used to momentarily inject hum into the circuit).

In most situations, there is not enough stray hum field, so a lead connected to the positive supply rail has been provided. This is held in the hand

or connected to the player's metallic watchband if this proves more convenient. In this case, a DC pulse is injected into the circuit via the player's skin resistance when the respective plates are touched.

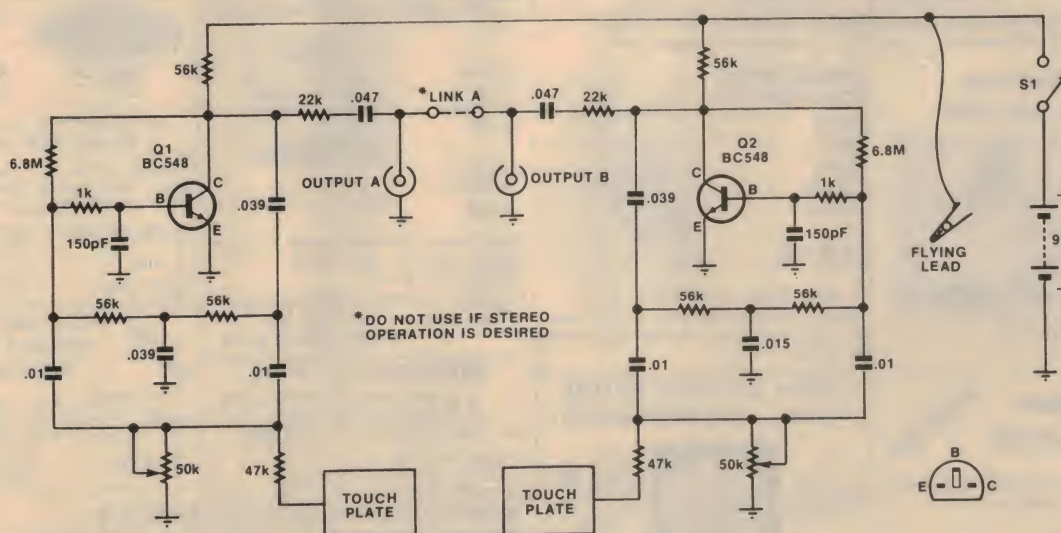47k resistors connect the touch plates to the respective oscillators. These resistors, together with the 1k resistors and 150pF capacitors at the base of each



ELECTRONIC BONGOS

1/EM/-

The circuit consists of two twin-T oscillators. The link allows the unit to be used in the mono mode.

A.C.E. RADIO

136 VICTORIA RD, MARRICKVILLE, NSW 2204

PHONE 51-3845

ELECTRONICS CENTRE

BARGAIN PRICES • PERSONAL ATTENTION • SLICK MAIL ORDER SERVICE • SATISFACTION •

NEW BSR STEREO CHANGER/PLAYERS MODELS

C198 (ILLUSTRATED)
S SHAPE TONE ARM
4 POLE MOTOR
WITH CERAMIC CART.

\$55.00

WITH MAGNETIC CART.

\$65.00



C197
STRAIGHT TONE ARM
2 POLE MOTOR
CERAMIC CART.

\$47.50

PACK & POST: NSW \$2.75, V./SA/Q \$3.75, TAS/WA/NT \$4.75

With all the wanted facilities • Auto or manual operation • Cueing lever • Bias compensator • Adjustable stylus pressure • 33, 45, 78rpm • Plays 7", 10", 12" records • Separate changer and player spindles • Operating instructions • Template for cut-out • Big 28cm turntable • Diamond stylus • 240V AC 50Hz

• BSR BELT DRIVE RECORD PLAYER •

ABSOLUTE
LATEST MODEL P-200

\$95.00

P&P NSW \$3.50
INTERSTATE \$4.50



STYLISH S SHAPE
PICK-UP ARM •
ADC MAGNETIC
CARTRIDGE,
DIAMOND STYLUS
INCLUDED •

ALSO AVAILABLE WITH WALNUT BASE AND
PERSPEX COVER WITH HINGES

\$119

P&P NSW \$5.00
INTERSTATE \$7.50

Specs. 240VAC 50Hz, auto or manual operation • Plays 17, 25, 30cm (7, 10, 12in) records • 33 and 45 rpm, adjustable counter weight and stylus pressure • cueing lever • Bias compensator and anti skate control • Die-cast platter with mat • RCA audio plugs and cable, 3-core power cable and plug •

C-CORE TRANSFORMERS

LOW NOISE • HIGH EFFICIENCY • PRIMARY 240V 50Hz. CONT. RATING

PACK AND POST

V. Q.

MODEL	SEC.V.	AMPS	PRICE	NSW	SA. T.	WA. NT.
JT 266	0-18V	8A	\$22.95	\$2.95	\$3.75	\$5.50
JT 235	260-26V	2A	\$21.95	\$2.95	\$3.75	\$5.50
JT 248	0-10V	10A	\$22.95	\$2.95	\$3.75	\$5.50
JT 249	8.5-0-8.5V	4A	\$23.95	\$2.95	\$3.75	\$5.50
	15VCT	1A				
JT 274	0-10V	10A				
	2x0-12V	1A	\$23.95	\$2.95	\$3.75	\$5.50
JT 353A	0-18V	12.5A				
	30A					
	PEAK		\$41.95	\$3.50	\$5.50	\$7.00



PLAYMASTER STEREO GRAPHIC EQUALIZER

10-OCTAVE \pm 13dB LOW NOISE AND DISTORTION.

COMPLETE KIT **\$97.50** FULLY CONSTRUCTED **\$125**

REF MAY 1979 ISSUE E.A. FOR FULL DATA OR SEND S.A.E.

PACK — POST NSW \$4.50 INTERSTATE \$6.50

SUPER SCOOP



PASSIVE RADIATOR HI FI SPEAKER SYSTEM

Excellent frequency response from the 8 ohm 15 watt 200 mm (8") woofer and 200 mm tweeter with cross-over • modern styling sturdy walnut cabinet • 445H.280 W. 178 DMM.

Pack and Post NSW \$2.75
V. Q. SA. T \$3.75
WA. NT. \$5.50

\$65

PAIR

STEREO CASSETTE DECK FRONT LOAD

SUPER SCOOP • TOP BRAND •

Pack and Post NSW \$2.50 V. Q. SA. T
\$3.50 WA. NT \$4.50

\$99.95

240V AC 50Hz • HiFi Freq. Response • Twin illuminated V-U meters • recording indicator • Tape Counter • Auto stop • Pause • Headphone Jack • 2 mic inputs • Bias/Equalizer switch for normal, FeCr, Cr O2 • Line in/out jacks • woodgrain cabinet 380 w x 240d x 135 h mm.



FM WIRELESS

MICROPHONES



No. 1 Unidirectional

\$34.75

PP \$1.00



No. 2 Omnidirectional

\$26.75

You can't trip over the mic. cable — there isn't any. The signal transmitted by FM microphones is picked up by an FM receiver, operating in the 88-106MHz s.freq. band. Mics can be tuned in this band. Specs. FM modulation. Field strength, 50 UV/M at 50ft max. freq. deviation \pm 75KHz. Electret Condensor Mic. 2 transistors 1.5 VDC.

Miniature hand held model WM-1 Freq 88-95MHz adjustable. Max freq deflection \pm 75kHz. Range approx 50m outdoors. Elec condensor mic size. 10 h x 35 w x 25 d mm, wt 65g.

PACK & POST \$1.00

\$11.95

• SAFETY GEAR •

BOAT • CAR • TRUCK • BUSHWALKER • CAMPER • PILOT
As used by vol. bushfire B. vol coastal P. Civil defence and organisations.

RED ROTATING DISTRESS BEACON

\$9.95

12 VDC
2 AMP



Pack and Post NSW \$1.50
Interstate \$2.50

HONEYWELL STROBOLITE

HAND
HELD
ALSO
FLOATS
UPRIGHT

\$12.95

P.P. NSW \$1.00 INTERSTATE \$1.70

Electronic flashing strobe signal light, uses 2 C size batteries, nominal life 7hrs, flash rate 15-60 per min.



400 OHM HEADPHONES

EX-ARMY
GOOD
WORKING
ORDER

\$2.95
PAIR

P-P NSW \$1.00
INTERSTATE \$1.75



AMERICAN LIGHTWEIGHT 75 ohms.
\$2.95 PAIR P-P NSW \$1.00
INTERSTATE \$1.40

CARBON THROAT MICROPHONES
\$2.95 PAIR P-P NSW 60c
INTERSTATE \$1.00

PLESSEY ROLA SPEAKER SPECIAL

GUARANTEED TOP QUALITY
BRAND NEW BARGAIN

Model C12PX, 15 ohms. 31cm (12in), twin cone. Specs: 30W rms. Reson. Freq. 40Hz, Freq. respon. 35-13,000Hz.

\$19.95 ea. P&P: NSW \$2.00
2 for **\$37.00** INTERSTATE \$2.75
P&P: NSW \$2.75
INTERSTATE \$3.75




SUPER LIGHT SCOOP DIMMER

240VAC 1.8A. Aust. made, approved.
The latest trend in home lighting.

\$4.50 P.P. 90c

PUSH BUTTON PHONE DIAL — WITH MEMORY

TELECOM
APPROVED

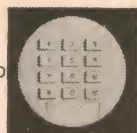

\$43.95

PACK & POST
\$1.25

If wanted number is engaged (including std and isd) unit will re-dial with the push of a single button. Dial dia 100mm. Compatible with telecom type phones.

MINI HOOK-UP WIRE

7 STRAND • PVC COVERED •
9 COLOURS — NO BLACK •
4 x 100m SPOOLS FOR **\$3.95**

P-P NSW \$1.50
V. Q. SA. T \$2.75 WA. NT \$3.50

• OPTO-ELECTRONIC RELAY KIT •

Light dependant switching device with 100s of uses • high sensitivity • rapid and definite relay actuation • operates between 15-20V 40ma • complete with large. 14mm Dia light dependent resistor (LDR) fully assembled P-C Board, 110 x 55 x 15mm, with transistors diodes and all necessary components. The system is suitable to activate or de-activate the relay. Instructions supplied.

P-P NSW 75c TRANSFORMER TO OPERATE UNIT
INTERSTATE \$1.50 240/17V 200MA \$2.50 PP 75c.


\$6.95

BRAND WATT MASTER NEW CEILING FAN MOTORS


200/250VAC 50Hz. Supplied with speed controller. 3 types 55 watt for 36" blades. 75W/48". 90W/56"

\$12.50

P&P: NSW \$3.50
INTERSTATE \$5.50

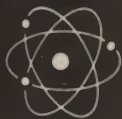

Basic Electronics

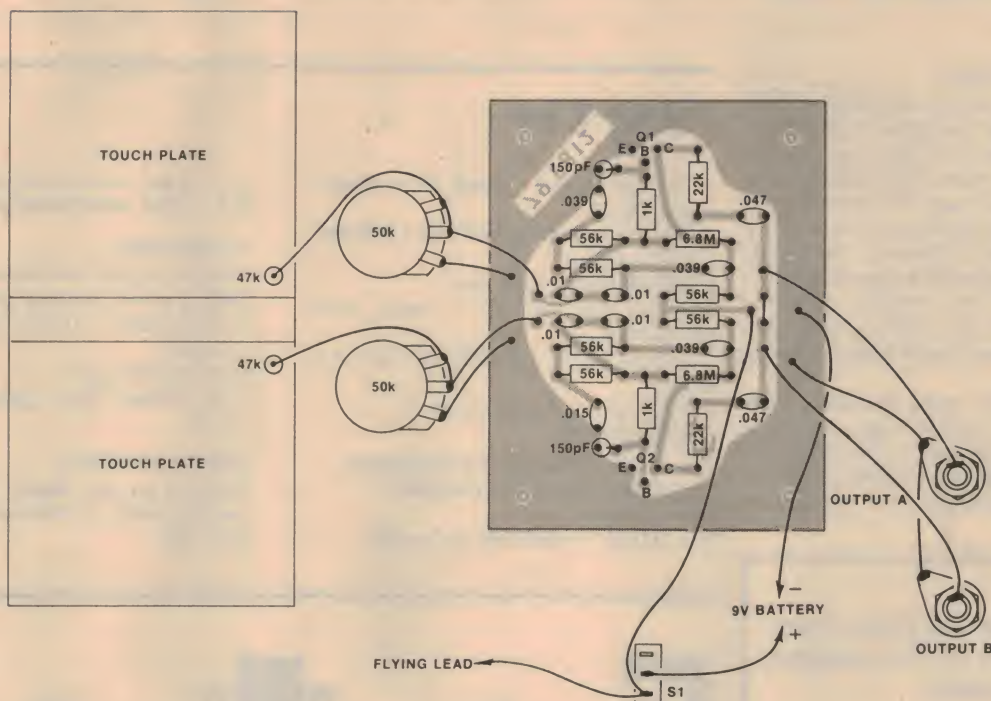

Use this wiring diagram, together with the circuit, as a guide to construction.

transistor are for RF suppression. Without these components, the circuit tends to pick up and detect strong RF signals, usually from the local radio station.

Output from the circuit is in the form of two independent channels, one for each oscillator. There is also a provision on the board for the insertion of a link so that the output can be made mono. When used as a stereo unit you will find that the results can be quite interesting with, say, the bass drum in the right

hand channel and the other drum in the left channel.

So much for the working of the circuitry. Now let's take a look at the construction of the unit. Two printed circuit boards and a plastic utility box make up the unit and the assembly of these should only take a couple of hours at the most. The first of the two boards is a replacement for the lid of the box and forms the touch plates, but more about this later. The other PCB contains all the electronics.

This latter board measures 65 x 83mm (coded 79EB12) and accommodates all the circuitry for the oscillators, with the exception of the pots.


Assembly of the printed circuit board is a simple process and should only take half an hour or so. A component overlay diagram has been provided to assist you in the placement of the components. Take care to insert the two transistors correctly.

We recommend the use of PCB pins for external connections as they make the final assembly task easier and neater.


Once the board assembly is complete, go back and check that all the components are correctly installed and also inspect the solder joints, as a dry joint can be a most frustrating thing when a circuit refuses to work.

Having checked the board put it aside and start on the preparation of the box that is to house the unit. The box that we used for the prototype measures 114 x 197 x 60mm. The aluminium lid that is supplied with the box is replaced by a second printed circuit board that forms the touch plates for the drums, as mentioned earlier.

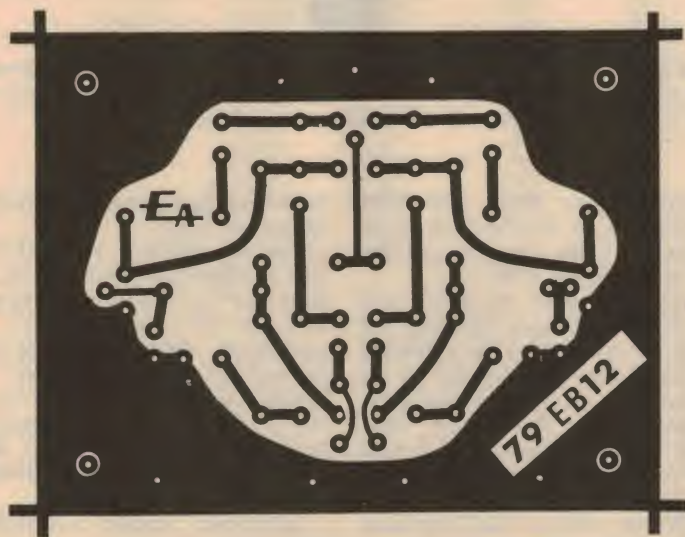Six holes need to be drilled into three sides of the box, two for the pots, another two for the output connectors, another for the power switch and the final hole for the flying lead. The positions of these holes is not critical, and a look at the photographs will show



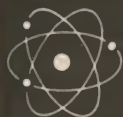A full size reproduction of the printed circuit board artwork.



Basic Electronics

how we placed them.

A further two holes are required for mounting of the oscillator PCB which can be mounted into the base of the box using either nylon PCB standoffs or using screws and nuts. If you elect to use the nylon standoffs you will need to fit rubber feet to the base of the box as the standoffs protrude through the bottom. The use of rubber feet is recommended in any case as they prevent the unit from slipping about while being played.

Now install the pots, power switch and the output sockets into the box, and make connections to the PCB. For those readers that live in close proximity to a radio transmitter, it may prove

We estimate that the current cost of parts for this project is approximately

\$20

This includes sales tax.

necessary to use shielded cable for the connections from the PCB to the pots and output sockets.

The two 47k resistors (shown on the circuit diagram to be in series with the touch plates) are mounted on the underside of the touch plate PCB (see photograph). The wires to the touch plates connect from the free ends of the 47k resistors to the pots and should be approximately 16cm long.

The battery was mounted on the base of the box using double sided adhesive tape. This is available from most hardware stores and is always a handy thing to have around the home.

The negative side of the battery is connected directly to the PCB while the positive side is connected via the power switch. The flying lead is connected to the switched 9V and is terminated with a small crocodile clip.

The flying lead is passed through a small hole drilled in the front of the box and has a knot tied in it to prevent the solder joint being strained.

When all the wiring has been completed check it over to satisfy yourself that there are no errors.

To connect the Bongos to your amplifier you will need a set of shielded

Parts List

1 Printed circuit board 65 x 83mm
code 79EB12

1 Printed circuit board 191 x 108mm
(touch plates)

2 BC548 NPN transistors

RESISTORS ($\frac{1}{4}$ or $\frac{1}{2}$ watt, 5%
tolerance)

2 x 1k, 2 x 22k, 2 x 47k, 6 x 56k, 2 x
6.8M

2 x 50k pots, linear taper

CAPACITORS

2 x 150pF ceramic of polystyrene

4 x .01uF metallised polyester

(greencap)

1 x .015uF metallised polyester

3 x 0.39uF metallised polyester

2 x .047uF metallised polyester

HARDWARE

1 Plastic zippy box 114 x 197 x 60mm

2 RCA panel mount sockets

1 miniature single pole toggle
switch

1 crocodile clip

1 9V battery (type 216) and clip to
suit

MISCELLANEOUS

Printed circuit board pins, solder,
hookup wire, knobs for pots, screws
nuts etc.



This is the artwork for the touch plates that replace the lid (191 x 108mm) on the box. The reproduction is not shown full size but owing to the simplicity of the board we feel that this should not present a problem.

leads. These will be fitted with RCA plugs at one end, to suit the sockets on the Bongos and with plugs to suit the amplifier at the other end.

Now apply power to both the amplifier and the Bongos keeping the master volume control on the amplifier to a low level. The pots should be set fully clockwise so that they have maximum resistance in the circuit. Now slowly rotate one of the pots and note that after some degree of rotation the oscillator starts up. If the pot is turned far enough the oscillator will continue in the sustained mode until the pot is turned back again. Now turn the pot

back and repeat the procedure with the other oscillator.

Having satisfied yourself that both the oscillators work properly, turn the pots one by one so that the oscillators are just on the verge of sustained operation. With the flying lead connected to your watchband (if it is a metal one) or held in the hand touch the plates and note that there is a distinct "bong" sound. The degree to which this sound is sustained can be controlled by the pots.

Set these "sustain" controls to your taste and start to practice. It sounds just like the real thing! Happy drumming!



16K 2001.16	\$1829
32K 2001.32	\$2199
Dual drive floppy disk, huge 340K 2040	\$2099
Tractor feed printer, 2022	\$1699
Friction feed printer, 2023	\$1499
External cassette	\$149

2040



2022




t.b.a.

Give name, number, expiry date and signature. For mail order sales

01

CHEAPER THAN USA!

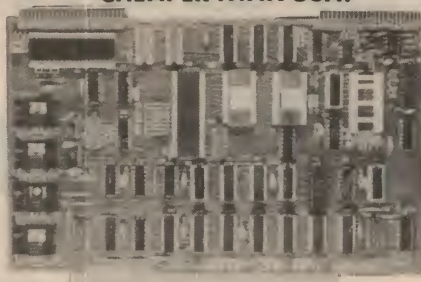

FEATURES —

- Comes with full assembly instructions and card documents.
- Power on jump for automatic execution of monitor program on startup.
- Front panel-less operation allowed by on board 2k monitor which is too good to explain here; 19 commands all unique abbreviations allowed.
- Full \$100 DMA Capabilities.
- Sockets supplied for all major devices.
- Clock speed, 2MHZ Standard, 4MHZ Option.
- I/O Z80 P10 2 x 8 bit programmable parallel I/O.
- RAM 256 Bytes scratch pad (Monitor).
- Onboard 2100 baud Tarbell Cassette Interface (Software Controlled) with cassette recorder remote motor control Test Cassette supplied with CPU Kit contains set up procedures for cassette interface as well as software to allow the cassette interface to read and dump 300 baud CUTS (Kansas City) format.
- Keyboard input direct onto card in parallel ASCII.
- Monitor performs all functions to drive ET1640 VDU as an ASCII terminal. Entry points for cursor control etc.
- The spare socket onboard is to allow the National MM57109 to be fitted which works in conjunction with the CPU to give a full floating point RPN arithmetic unit.
- Functions as a general purpose Z80 single board computer or as the heart of a fully expanded system to 64k Bytes of memory and a multitude of I/O devices.
- Plated thru solder masked printed circuit board with components screened overlay.
- Description Manual Construction manual \$1.00 refundable with purchase.

\$22.50 Number Cruncher Option
Assembled and tested add \$50.00

\$100 Wire Wrap Cards \$34.00

Same spec as for S100 Dynaram except plugs into Motorola Exorciser Bus and same pricing as for Dynaram.

Z80 CPU Technical Description **\$10.00** posted
Z80 PIO Technical Description **\$6.50** posted
Z80 CTC Technical Description **\$6.50** posted
Z80 CPU Programming and Assembly Language
Manual **\$10.00** posted

Prices are inclusive of sales tax; tax exempt institutions deduct six percent

All prices include freight anywhere in Australia.
Allow 10 days for despatch.
Hours of business: Mon. to Fri.: 9am to 5pm. Sat.: 8.30am to 12 noon. Open Thurs. to 9pm.

ZERO


200 MOGGILL ROAD,
TARINGA, 4068
BRISBANE AUSTRALIA.
PHONE 371 6707

ONE

[illegible]

Experiment with digital counters

Basic
Electronics

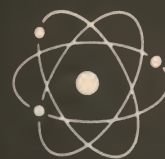

by GERALD COHN

Like to learn more about digital counters and how they work? The best way to do this is to experiment with a low-cost counter IC, the 7490. You can run it through its paces with the simple square wave oscillator we described in the August issue.

by GERALD COHN

The counter that we are going to build is of the decade type, the name decade being derived from the Latin word "decem" which means ten. This means that the counter is capable of counting to 10 before the whole cycle is repeated.

All that we need for the experiment is an easy-to-get 7490 digital counter IC and a handful of other components. The actual "workings" inside the IC consist of four master-slave flip-flops and some additional gating, providing the reset and count control functions. A brief description of flipflop and basic counter operation is provided in the box.

The 7490 is a decade counter device, which counts in a modified binary fashion known as "BCD". There are several ways in which binary numbers can be used in digital counting, one of which is known as BCD or "binary coded decimal". Broadly speaking a code of this sort must use four binary digits or "bits" to represent each decimal

digit. This is because this many bits must be used to provide 10 different value combinations. Four bits actually provide 16 different combinations, but the remaining six combinations are unused.

For those readers that are not so familiar with the binary numbering system, we will go over some of the basic rules of the system. You will find that these are going to prove quite important later on, in particular when you have completed the construction of the project and are ready to use it.

To handle decimal numbers in digital circuits is rather cumbersome, and also demands greater circuit complexity. An alternative is to change the format of the numbers into what is known as "binary". Binary notation uses 2 as its base, in place of the 10 that is used in the decimal system. Binary notation is very well suited to digital circuits, as it involves only two numeral values: 0 and 1. These replace the 10 numeral values (0, 1, 2, ... 9) used in decimal

notation.

This means that many more digits must be used to represent a given number, because each numeral digit position represents a certain power of 2 rather than a power of 10. In place of the units-tens-hundreds-thousands progression of the decimal system, the numeral positions represent units-twos-fours-eights and so on.


In this sense the binary system is clumsier. But each numeral position has only two values, so that it may be represented very simply by a circuit voltage or current switching between two levels — high and low.

Hooking up the 7490 as an experimental counter is a simple task, and if performed with care should only take about two hours. You will probably find that apart from the IC and the LEDs, all the other components will be in your junk box.

The components are all mounted on a small piece of Vero-board, keeping the cost to a minimum. The input stage to the counter consists of an NPN transistor inverter that performs the function of level translation. The reason that level translation is required is that the oscillator used to provide the input pulses uses a 9V supply, whereas the counter circuit operates from a 5V supply.

The 7490 IC that is used in this counter is of the TTL type, and this type of logic is designed to operate from a 5V supply rail. The level translator at the input to the counter will prove to be quite useful, since it will enable the counter to be used with all sorts of equipment operating at various different supply voltages.

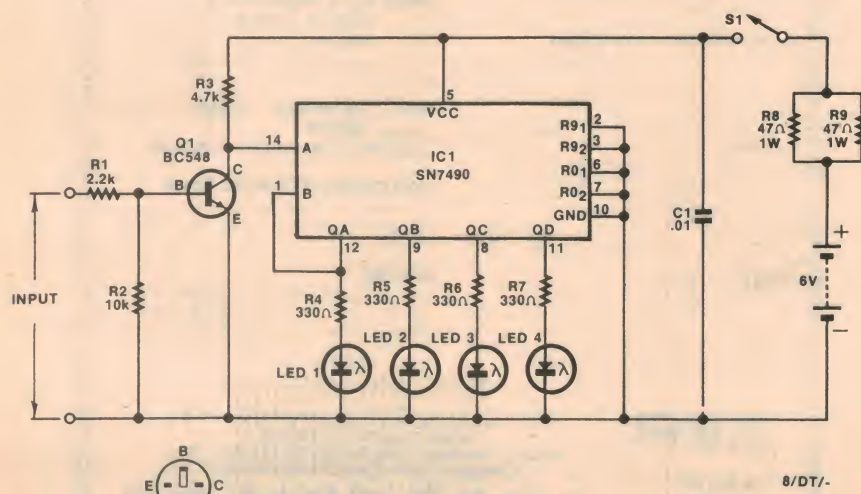The output of the transistor inverter is fed to the input of the counter IC, which is at pin 14. The counter IC features two inputs because it is internally made up of two separate counters, the first of which is a divide by 2 counter and the second being a divide by 5 counter. The output of the



The circuit diagram of the counter. Note the inverting level translator (Q1) at the A input to the IC.

Hioki

PUTS YOU YEARS AHEAD!

On the job, in the lab, or the classroom you want the most advanced equipment you can get. Anything else is time-wasting and cumbersome. So have a look at the Hioki range — particularly these new multimeters.

They have such advanced features, are so sensitive and accurate, that they make the testing jobs easy. Let us demonstrate the advantages.



HIOKI 3204 B Believed to be the world's first production Digital Insulation Tester, the Hioki 3204B offers wide test ranges, high accuracy and a FE liquid crystal display.

Designed to meet Australian requirements, this 500 Volt instrument remains within specified lower terminal voltage limits when connected to low resistance loads. Output voltage is typically 495 Volts into 2 Megohms.

The model 3204B is Semi-Auto Ranging and includes display hold, overreading indication, battery check and overload protection facilities. Measurements facility for AC voltage to 500 Volts included. The instrument is supplied with one lead with probe and one red lead with clip.

Specifications


Reading Ranges and Tolerances			
Function	Range	Lo	Hi
MΩ		1999MΩ	
		1999MΩ	199.9MΩ
			1999MΩ
Ω-kΩ		1999Ω	19.99kΩ
		1999Ω	199.9kΩ
			199.9kΩ
ACV		199.9V - 500 V (Hi or Lo)	
Tolerance			
±2%rdg. ±3dgt.			
500MΩ under: ±4%rdg. ±2dgt.			
501MΩ over: ±5%rdg. ±2dgt.			
±1%rdg. ±0.5%f.s. ±1dgt.			
±1%rdg. ±1%f.s. ±1dgt. (40Hz-70Hz)			

HIOKI 3205 Digital Multi Tester Compact multimeter featuring Semi-Auto Ranging, electronic and fuse protection and approximately 40 hours continuous operation with alkaline batteries. Among the many advantages are overrange indication, auto polarity and automatic battery condition indicator.

Specifications

DC V 0-200mV/2000mV/20V/
200V/1000V 10MΩ
AC V 0-200mV/2000mV/20V/
200V/1000V 10MΩ
Ω 0-200/2000/20k/200k/
2M/20M
DC A 0-200μ A/2000μ A/20mA/
200mA
AC A 0-200μ A/2000μ A/20mA/
200mA

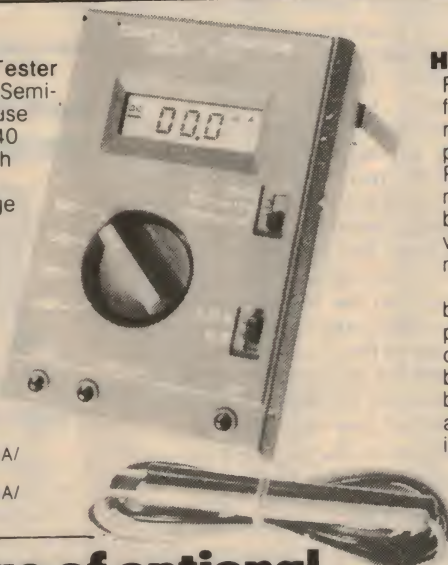A wide range of optional accessories also available




HIOKI 3206 Digital Clamp Tester has FE liquid crystal display, reading hold facility and surge hold for motor start readings. A special 0-20A range provides 0.01A resolution. This Auto Ranging instrument enables current measurements to be made without breaking the circuit. In addition, voltage and resistance measurements can also be made.

The circuit design ensures low battery power consumption providing approximately 100 hours continuous use with alkaline batteries. Overrange indication and battery exhausted warning are among the many features of this instrument.

Specifications

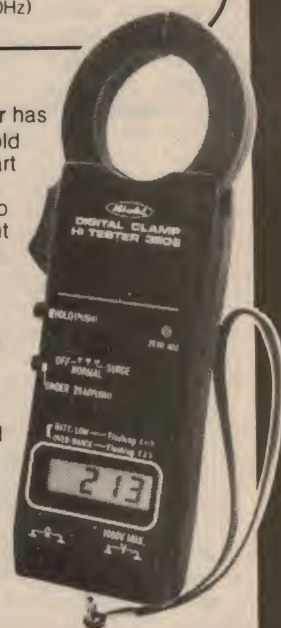AC A 0-19.99 (Push Button)
0-199.9/1000A (Auto)
Surge Current 0-1000A
AC V 0-199.9V/1000V (Auto)
Surge Voltage 0-1000V
0-199.9/1999Ω (Auto)




Hioki Multimeters are available through your favourite stockist or electrical wholesaler. If he does not have the model of your choice ask him to order it for you. For further information contact:—

SYDNEY 6016600
MELBOURNE 3296511 BRISBANE 525231
ADELAIDE 466411 PERTH 4466622

H. ROWE

& CO. PTY. LTD.

SOLE
AUSTRALIAN
AGENTS

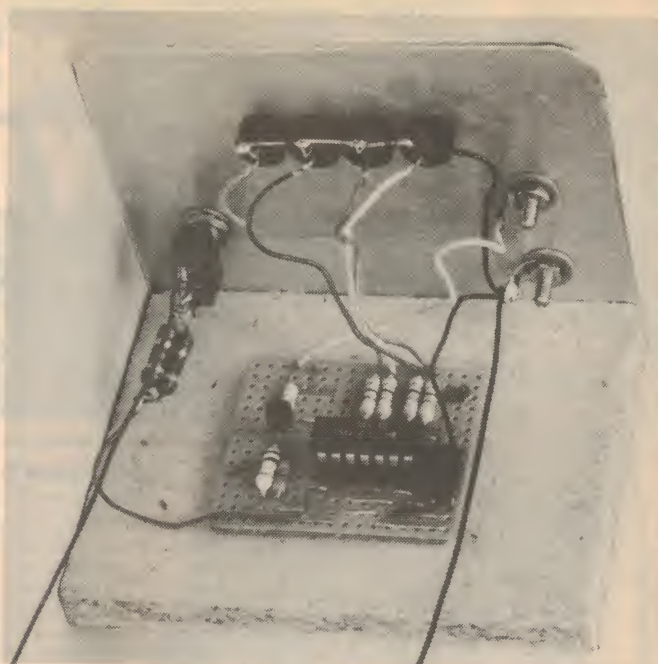

Photographs showing the construction of the unit. The front panel layout appears above, while the rear view of the unit is shown to the right.

divide by 2 counter is fed to the input of the divide by five counter, this being done via a link between pins 1 and 12 of the 7490 IC.

The counter IC also has four other inputs that perform the functions of resetting the counter to either 0 or 9. Since we are not interested in using these reset functions, we ground the inputs. The output of the counter takes the form of four LEDs (light emitting diodes), arranged in such a way that they provide a binary readout. The output can be easily read if you consider a lighted LED to indicate a logic 1, and an unlit LED to indicate a logic 0.

As you can see from the circuit diagram, each of the LEDs has a resistor in series with it. The reason for the series resistor is to limit the amount of current that passes through the LED to approximately 10 milliamps. This is plenty of current to ensure that the LEDs have adequate levels of light output.

Before you start placing components onto the strip board, cut the appropriate tracks as shown in the component overlay diagram. To cut the tracks is a simple matter requiring the use of a small twist drill. The tip of the drill is placed in the hole where the copper track is to be cut and then rotated until the drill has cut away the copper that is not required. The finished result will be a small countersink in the board, with the copper strip milled away.

Once you have cut the tracks that are indicated on the overlay, start to mount the components, again following the layout shown by the component overlay. The first components that should be mounted onto the board are the resistors and the capacitor. These can then be followed up by the transistor. The IC is the last component that is to be mounted, and we suggest that

an IC socket be used for this, therefore enabling the IC to be used again in a future project without any damage resulting from soldering and then removing.

Once the board has been assembled, we turn our attention to the mechanical construction of the project. As can be seen from the photograph, we mounted the prototype onto a piece of particle board, and mounted the LEDs in a front panel that was made from a small piece of aluminium sheet. Also mounted on the front panel are the terminals for the input to the counter, and the power switch. The two 47ohm 1W resistors are mounted on the rear of the power switch, and their purpose is to drop the battery voltage from 6V to approximately 5V, and at the same time limit the amount of current that the circuit can draw. The maximum current drain on the battery will occur when the counter reaches the count of 7, since three of the four LEDs will be lit up. Since this is a BCD counter, this will be the maximum number of LEDs that will be lit up at any one time.

All the holes in the front panel were drilled to a size of 6.5mm, and these are for the mounting of the LEDs, the power switch and the terminal posts. The wiring to the LEDs should be done carefully to ensure that the order of the outputs is correct. The cathodes of the LEDs are wired up to a common bus and then taken to ground, together with the black terminal post. The input of the counter is taken to the red terminal post.

We used a 6V lantern battery for the prototype. It is not essential that this type of battery be used, but we found it to be the best since it is a heavy duty battery. You could also use a battery clip that contains four type AA batteries to obtain a six volt source.

We estimate that the current cost of the parts for this project is approximately

\$6.00

This includes sales tax.

Led lead identification



The cathode is the shorter of the two leads or can be identified by a flat edge on the plastic body.

THE PARTS LIST

- 1 7490 TTL IC
- 1 BC548 NPN transistor
- 2 47 ohm 1/2W resistors
- 4 330 ohm resistors
- 1 2.2k ohm resistor
- 1 4.7k ohm resistor
- 1 10k ohm resistor
- 1 .01uF polyester capacitor
- 4 Red LEDs and bezels to suit
- 1 Piece Vero board, 44 x 40mm

MISCELLANEOUS

Piece of aluminium sheet 7cm x 9cm, piece of particle board 7cm x 9cm, miniature single pole toggle switch, terminal posts (1 red and 1 black), IC socket (14 pin), solder tags, solder, hookup wire etc.

Sabtronics NEW Hand-held Digital Multimeters...

The only thing that beats their performance is their price.

Accurate performance you can rely on, time after time. That's what you expect from a quality DMM. But don't expect to pay as much for it any more. Because now Sabtronics brings you top quality DMMs with more features and better accuracy than other comparable units on the market today. And they cost surprisingly less!

We cut the price. Not the quality.

What you get is a precision crafted unit that features single-chip LSI logic, laser trimmed resistor network and a stable band-gap reference element for better long term accuracy. Basic DCV accuracy is 0.1%. The Model 2035A gives you 32 measurement ranges over 6 functions and the Model 2037A an additional two temperature ranges.

First in features. First in price.

Both models feature touch-and-hold capability with the optional probe — its so convenient, you'll wonder why the expensive models haven't got it yet! And two-terminal input for *all* measurement functions. — this eliminates lead switching and makes your job easier. The Model 2037A even has a built-in temperature measuring circuit with a -50°C to $+150^{\circ}\text{C}$ range (-58°F to $+302^{\circ}\text{F}$) and is supplied complete with the sensor

probe. Of course, auto zero, auto polarity and overload protection are standard. And you get 200 hour operation from a single 9V transistor battery. A low battery indicator warns you of the last 20% of battery life. The large, crisp LCD readouts allow easy viewing even in bright sunlight.

Assembling either kit is simple with our easy-to-follow, step-by-step instructions. And the built-in calibration references allow you to calibrate the unit any time, any place.


We've even eliminated difficult inter-connect wires. All parts mount on the PC board. The only wires you solder are the two battery-snap leads.

Biggest value in small DMMs

To sell hand-held DMMs with all these features at such low prices, we had to sacrifice profits. But we never sacrificed quality or performance.

And you save even more buying direct from our U.S.A. factory. For your convenience, the prices are listed in Australian dollars.

To order, simply send a Bank Draft or International Money Order for an equivalent amount in U.S. funds and we'll ship your kit via

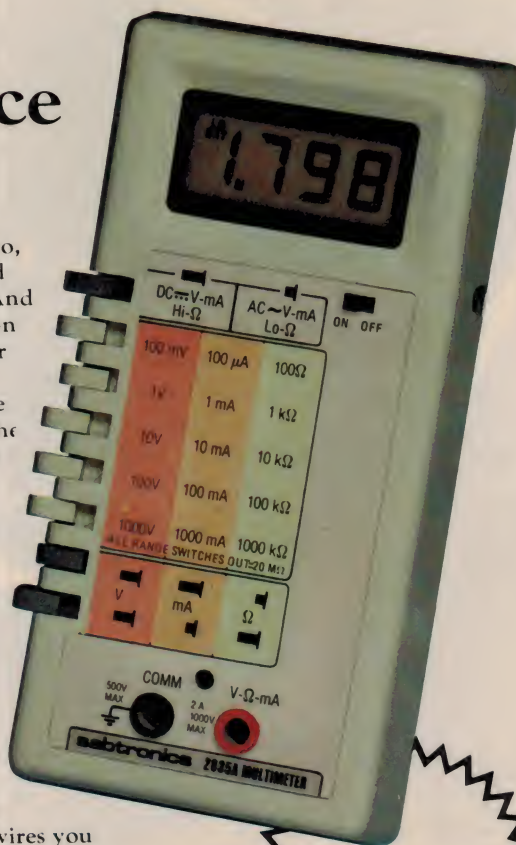

Model 2035A

\$74.95

+ postage & insurance

Insured Airmail. Please allow 4-6 weeks for delivery. Order yours today!

Making Performance Affordable

sabtronics INTERNATIONAL

13426 Floyd Circle M/S 94 • Dallas Texas 75243
Telephone 214/783-0994

BRIEF SPECIFICATIONS:

DC VOLTS: 100 μ V - 1000V, 5 ranges
AC VOLTS: 100 μ V - 1000V, 5 ranges
DC CURRENT: 0.1 μ A - 2A, 5 ranges
AC CURRENT: 0.1 μ A - 2A, 5 ranges
Hi-OHMS: 0.1 Ω - 20M Ω , 6 ranges
Lo-OHMS: 0.1 Ω - 20M Ω , 6 ranges
TEMPERATURE: -50°C - $+150^{\circ}\text{C}$
(-58°F - $+302^{\circ}\text{F}$), 2 ranges
(Model 2037A only).

WEIGHT: 11 oz. (excl. battery)

OVERLOAD PROTECTION: 1000V DC
or ACpeak all voltage ranges; 250V DC
or ACpeak all Ohms ranges; 2A/250V
fuse all current ranges.

Mail to: Sabtronics International, 13426 Floyd Circle M/S 94, Dallas, TX 75243, U.S.A.

Please send via Insured Airmail...

(qty) Model 2035A Hand-held Multimeter kit(s) @ \$A74.95 each	\$A
(qty) Model 2037A Hand-held Multimeter kit(s) @ \$A89.95 each	\$A
(qty) Model THP-20 Touch-and-hold Probe(s) @ \$A19.95 each	\$A
Airmail postage and Insurance for each DMM kit @ \$A9.00 each	\$A
TOTAL	\$A


I enclose a ☐ Bank Draft ☐ International Money Order for the equivalent amount in U.S. dollars, payable to SABTRONICS INTERNATIONAL

Name

Address

(Post Code & Country)

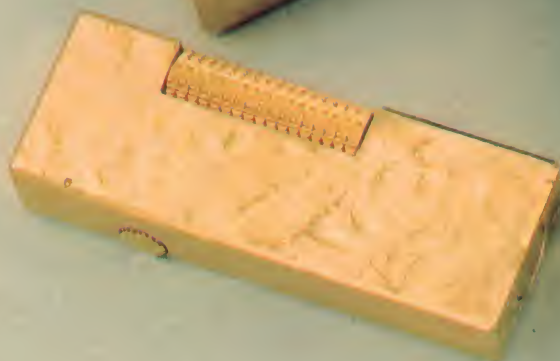NOTE: Prices do not include any tax or duty which may be levied upon receipt of goods.



Now also available in King Size

Dunhill Superior Mild

The new standard of excellence in mild smoking



LONDON · PARIS · NEW YORK

For those who appreciate the finer things

FLIPFLOPS: what they are & how they work.

Apart from logic gates, probably the most basic elements in digital circuits are flipflops. As the name suggests, a flipflop is a bistable device. It has two stable operating conditions, and can be made to switch from one to the other.

A very basic flipflop can be formed by connecting two 2-input NAND gates, as shown in Fig. 1. As you can see, the two gates are "cross coupled", with the output of each being connected to one of the inputs of the other. This forms a regenerative feedback loop, with the result that if the two uncommitted inputs are taken to true (1) logic level, only one of the gates can have a true output; the other must have a false (0) output.

This happens because the output that is true causes both inputs of the other gate to be true, driving the second gate's output false by virtue of the inherent inversion in a NAND element.

Only one output of the flipflop (or "FF") is normally true, and the other is false. The two outputs are logically complementary, in other words — each is the logical complement of the other. By convention one output is usually labelled "Q" and the other "Q-bar".

The FF has two stable states then: one with Q true and Q-bar false, and the other with Q false and Q-bar true. Just which of the two states the FF is in depends upon its previous history.

The main factor that determines the state of the flipflop is any signals which may be applied to the inputs A and B. There are various possibilities here: the FF may have either Q or Q-bar true initially, while either A or B may be

taken true or false independently. With three variables, this gives eight different situations, each of which can be analysed using basic gate principles.

The results are shown in concise form in the "truth table" of Fig. 1. Each pair of lines covers one of the four possible true-value combinations for the two inputs, with the other two lines in each pair covering the two possible initial states of the flipflop.



A simple flipflop of the type in Fig. 1 is known as a "Reset-Set" or R-S flipflop. While an RS flipflop has its uses, there are many applications in digital systems that require a FF to respond only at certain fixed times, as determined by general timing or "clock" signals that are fed throughout the system. To provide for this sort of operation, a number of variations on the basic flipflop have been evolved.

One of these is the so-called T-type or "toggle" flipflop, shown in Fig. 2. This has two inputs, like the RS type, but here the inputs perform entirely different functions. One input is called the toggle or "T" input and the other the "clock" input.

Referring to the truth table of Fig. 2, you can see that if the T input is held false (0 logic level) during the clock pulse, this has the effect of "freezing" the FF in its initial state; ie, no change occurs at the outputs. However if the T input is held true (logic 1) during the clock pulse, the clock pulse forces the FF to "toggle" or change states — regardless of its initial state. If it was set, it will reset; and vice-versa.

The T-type FF is thus capable of only two responses to a clock pulse. It can either remain unchanged, or toggle, depending upon the logic level applied to the T input.

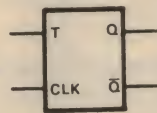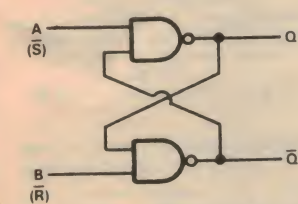Probably the most important type of clocked flipflop is the JK type, which is shown in Fig. 3. This is a very flexible element (and also the type that is used in the counter IC around which this project is built), in that it can be arranged to perform all of the functions performed by the other types.



T	BEFORE CLK PULSE		AFTER CLK PULSE	
	Q	Q̄	Q	Q̄
0	0	1	0	1
0	1	0	1	0
1	0	1	1	0
1	1	0	0	1

Fig. 1 to the left shows the SR flipflop, while Fig. 2 above shows the T-type flipflop and its truth table.

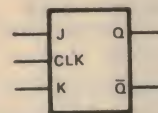


Fig. 3 The most widely used of the flipflop family, the JK type, shown here with its truth table.

J	K	Q (BEFORE)	Q (AFTER)
0	0	0	0
0	0	1	1
1	0	0	1
1	0	1	1
0	1	0	0
0	1	1	0
1	1	0	1
1	1	1	0

The counter could also be powered from a power supply that runs from the mains, and we will consider publishing a power supply project of this type sometime in the not too distant future.

Now that you have completed the assembly of the project, go through and check all the wiring once more, and don't forget the board assembly. If you are satisfied that all is in order, hook up the square wave oscillator that was featured in the August issue, and turn on the power to the counter. Now turn the switch on the oscillator into the 1Hz position and note that the LEDs of the counter's display should start to

follow the binary counting sequence. To check that the sequence does in fact follow the binary notation, refer back to table 1 and check that the sequence of the LEDs corresponds to that shown in the table.

The counter does have some other more practical applications other than flashing a row of lights in a binary sequence. You could for example use it as a frequency divider. If you feed a frequency into the input, you can obtain two different output frequencies; one corresponding to the input divided by two, and the other to the input divided by 10. So if we feed a frequency of

1000Hz into the input, the resulting output frequencies will be 500Hz (1000/2) at output A and 100Hz (1000/10) at output D.

As you can see from the above information, the input frequency is divided down by a factor of 2 each time, and the different output frequencies appear at the outputs of the counter IC.

If you did build the oscillator project, you will soon discover that you can obtain 25 different frequencies, if you use the oscillator together with this counter project.

For those experimenters that feel a little more adventurous, you could

BRASS SHIPS CLOCKS SMITHS 8 DAY 7 INCH DIAMETER \$110

Post A \$1.75; B \$3.00; C \$3.60.

GENUINE EX ARMY WRIST WATCHES

Complete with nylon band \$19.50
Post \$1.10

P.M.G. TYPE TELEPHONES

Standard desk type with magneto bell calling device. Range 30 miles. Uses standard batteries at each phone. Any number can be connected together on single line

\$39.50

(2 TELEPHONE SETS)

\$2 Cartage to Rail. Freight payable at nearest attended Railway Station

RECEIVER No. 210

2-16 M/cs \$65.
Transmitter No. 11 suits 210 \$35.
24 volt Power supply to suit above \$15.
Or complete station with Headphones.
Mic \$110.

EX ABC MAGNETIC RECORDING TAPES 1/4"

PROFESSIONAL QUALITY

5' x 600' \$1.50
7' x 1200' \$2.75
P + P \$1.30
10 1/2' x 2400' \$7.95
P + P A \$1.65 B \$2.75 C \$3.10

COLLINS INDEPENDENT SIDEBAND TRANSCEIVER TRC/75

Fully synthesised transceiver with am, upper, lower and independent sideband operation, 1KHz steps from 2MHz to 29.999MHz 1 microvolt sensitivity, 2.5KHz bandwidth ssb, 6KHz bandwidth AM 1 RW PEP max output Fully automatic tuning of both transmitter and receiver from remote control unit. Complete with automatic aerial coupling unit, mic, headset, etc. 400Hz supply. Ideal for amateur use.
PRICE \$750

COLLINS SYNTHESISED 1 SB RECEIVER

TRC/75 receiver section of transceiver specification as above.
PRICE \$400

TELEPHONE WIRE

1 mile twin (2 miles) genuine ex-Army Don. 8 perfect condition \$45.00 per drum, \$2.00 cartage to rail freight payable at destination.

20X to 60X ZOOM TELESCOPE

With Tripod, \$115.50.
Post A \$2.25, B \$4.10, C \$6.10.

RCA 44BX MICROPHONES

PROFESSIONAL QUALITY \$75
P&P A \$1.80, B \$3.50, C \$4.55,
D \$4.55.

AERIAL CAMERAS

WITH 8" FL 3" DIAM. LENS F24 MARK IV 2.9 LENS STOPS 11, 8, 5.6, 4, 2.9 — \$75
\$2 cartage to rail freight. Payable to nearest attended railway station.

PENTAC LENSES

3" DIAM. 8" FL WITH DIAPHRAGM STOPS 11, 8, 5.6, 4, 2.9 MOUNTED IN METAL HOUSING — \$65
POST: A \$1.85, B \$3.25, C \$4.10

PRISMS

4" SQUARE FACED RIGHT ANGLE PRISMS TOP QUALITY EX AIR FORCE — \$65; OR LENS & PRISM FOR \$120.
POST: A \$1.75, B \$3.00, C \$3.60

SOLENOIDS

200 MA 24 volt, 1/4in push movement.
\$2.50 P+P 80c

NIFE CELLS

1.2 volt, fully charged, 4in x 3in x 1in 4 AH
\$1.50 each P&P 80c

CENTRE DRILLS

15 x 5
64 x 64 Carbon Steel \$3 Doz Post 60c.

ARTILLERY DIAL SIGHTS MK2

Can also be adapted as a Dumpy Level or as base for a telescope has full 360° 5 1/2" diam. gunmetal rotating circle. Adjustable elevation and depression. Has top grade 3/4" diam. object lens. FL 10" with cross hairs, eyepiece, 1/2" right angle prism — height 10" — weight 3 1/2 kgs With leather carrying case. Original cost \$300
Our Special only \$27.50
P&P A \$2.25 B \$4.00 C \$6.00

POSTAGE KEY:

A: NSW
B: Vic, Qld, SA
C: NT, Tas
D: WA

VALVES

BRAND NEW
6SN7 \$1.95 6BM8 \$1.95
5U4 \$1.95 6GV8 \$1.95
EF50 \$1.50 6AK5 \$1.95
2x2 \$1.50 1H6 \$1.50
P+P 80c
6x4 \$1.95
VR65 \$1.50

STC HIGH IMPEDANCE HEADPHONES

3400 ohms, brand new, only \$5.95 pair.
P&P A \$1.65, B \$2.75, C \$3.10

ZOOM SPOTTING SCOPES



30 x 30
LENGTH 12 1/2", HEIGHT
10"
WEIGHT 1 3/4 lb
\$32.50

45 x 40
Length 16in
Height 10in
Weight 2lb
\$49.50

High grade coated lenses
Ideal for pistol and rifle ranges
or general viewing. Zooms in
from very low to high powers
Complete with tripods
POST: A \$1.75, B \$3.00,
C \$3.60

TELESCOPES

25 x 30 \$13.50
P&P A \$1.30

SPY TELESCOPES

8 x 17 mag size of a rifle cartridge extends to 8". Only \$8.95 each, post 60c.

BINOCULARS

PRISMATIC Coated Lenses. Brand new Complete with case.

8 x 30 \$42.00
7 x 50 \$48.95 P&P
10 x 50 \$1.00 A \$1.75
12 x 50 \$3.00 B \$3.00
20 x 50 \$5.00 C \$3.10

SMALL CLIP-ON POCKET TELESCOPE

15X \$7.00, P+P 80c

3" ASTRONOMICAL REFLECTOR TELESCOPE

117X magnification FL 700mm with 5x24mm finder scope and two section hardwood tripod. \$169.25.
Post A \$2.25, B \$4.10, C \$6.10.

C42 set 36 to 60M/Hz with 24 volt power supply headphone mic, leads etc. \$95.
Or 42 set separate \$65.

AIRCRAFT INSTRUMENTS

Directional Gyros.
AN5735-1 Air Operated.
\$35
Sperry Artificial Horizon.
AN5736-1 Air Operated
\$45.
Slip and Turn Indicators
\$17.50.
P&P
A \$1.65, B \$2.75, C \$3.10

MAGNESIUM DRY CELL BATTERIES. Suits PRC25 and dozens of other uses. 15 volts long life. Only \$1.50 each. P & P A \$1.35, B \$2.75, C \$3.60.

ANEROID BAROMETERS

In brass case, made in London, \$39.50
P&P A \$1.65
B \$2.75
C \$3.10

CONDENSER LENS

2 1/2" diam 2" FL \$1.50 each or \$2.50 per pair P&P 80c

IMPELLER PUMPS

New gunmetal body. Stainless Steel Shaft. Neoprene Impeller Up to 15ft Lift, suitable for almost any type of liquid Self priming Ideal boat bilge pump, sillage drains, etc. Approx. size 8" x 5" 3/4" \$35.75, 1/2" \$51.00, 3/4" \$56.50.
P+P A \$1.95, B \$3.50, C \$4.60

Liquid filled compass



With magnified lens sight and degree reader
Only \$7.95 each. Post \$1.30

POLARITY & CURRENT CHECKER

3 volt to 400 volt Simple leads and prods quickly determines positive or negative with illuminated indicators, also checks AC current and intensity, fully insulated only \$4.95, pp \$1.30.

COLLINS COMMUNICATIONS RECEIVER

Type SIJ-4
500kHz to 30mHz
\$350.00

WRIST WATCHES SWISS JAEGER

Le Coultre ex RAAF rated one of the world's best in smart chrome case with black dial. Original cost \$250

SPECIAL \$49.50
Post \$1.30

THEODOLITES

Made by Wilds Microptic, with tripod Model T1, reads down to one minute of ARC \$750.
(Usual Price \$1750).
Model T2 reads down to one second of ARC \$1000 (Usual Price \$3200)
Freight payable at nearest attended R'way Stn.

ZOOM FOCUSING MICROSCOPES

Zoom focusing microscopes, 750X battery and mirror illuminated \$31.75
Zoom 1200X similar to above \$47.95.
P&P A \$1.65, B \$2.75, C \$3.10

DIRECTOR LEVELS

Ex Army No 9 with azimuth horizontal circle and vertical adjustment suits all types of levelling. In leather case \$90.

P + P A \$1.75 B \$3 C \$3.60.

17 PIECE SAE SOCKET SETS

1/2" Square drive ratchet handle, extension bar, T-bar, 13 socket spanners. 3/8" to 1" \$19.50
Post: A \$1.95, B \$3.50, C \$4.60.

24-PIECE METRIC SOCKET SETS

Ratchet handle, 2 extension bars, speed brace, universal joint, 2 plug spanners. 16 socket spanners, 10 to 27mm.
\$24.50
Post: A \$2.25, B \$4.00, C \$5.90.

16MM SOUND PROJECTORS IN GOOD WORKING ORDER

240 volts operated complete with Speaker and Amplifier

SIEMENS \$375

BELL & HOWELL \$195.
\$1 Cartage to Rail. Freight payable at nearest attended Railway Station

SELSYN MOTORS MAGSLIP

TRANSMITTER 3" MK2
\$20.00

Post Packing A \$1.75, B \$3.00, C \$3.10

MAGNIFYING GLASSES

4" Magnifier suspends from neck and rests on chest, leaves hands free ideal for mum or gran, sewing, etc.
\$6.30

4" Hand held \$5.95
3" Hand held \$3.80
2 1/2" Hand held \$2.65
3 1/4" Rectangular \$4.25
4" Magnifier on stand leaves hands free \$10.75
Illuminated 10 x power magnifier \$6.60
Postages \$1.30 extra

Deitch Bros.

70 OXFORD STREET, SYDNEY 2010

SORRY NO COD


Flipflops in counters

The JK flipflop has two main inputs in addition to the clock input, and as you can see these are labelled "J" and "K". If the J input alone is held true, the FF will set; if the K input alone is held true, the FF will reset; if both the J and the K inputs are held true together, the flipflop will toggle with the applied clock; and if both are held false, the flipflop will "freeze".

If you now refer to the diagram of Fig. 4, you will see that we have reproduced the circuit of the 7490 IC. Note that it uses JK type flipflops.

Closer examination of the schematic will reveal that the first FF in the counter chain is in fact not connected to the other FFs. The device is actually a dual counter in that the first stage is a divide-by-2 stage, while the other three FFs form a divide-by-5 stage. To use this device as a divide-by-10 stage, we must connect the two internal stages in cascade. This is done by connecting the output of the first stage to the input of the second stage (ie pins 12 and 1 are connected together).

The device also features some special reset inputs, but we shall leave these from the discussion as they are not used in this project. The pulse train that is to be counted is fed to the input of the first stage, ie. pin 14. The output from the device is in a four bit binary pattern, actually not pure binary, rather BCD or "binary coded decimal". The outputs are labelled QA to QD, with QA being the least significant bit (LSB), and QD being the most significant bit (MSB).

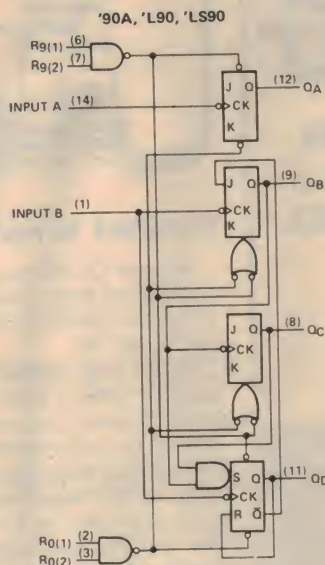

COUNT	OUTPUT			
	Q _D	Q _C	Q _B	Q _A
0	L	L	L	L
1	L	L	L	H
2	L	L	H	L
3	L	L	H	H
4	L	H	L	L
5	L	H	L	H
6	L	H	H	L
7	L	H	H	H
8	H	L	L	L
9	H	L	L	H

Fig. 4 to the right shows the circuit of the 7490 IC. Two separate counters exist in the package, the first a divide by two, and the second a divide by five. Fig. 5 above shows the truth table for the outputs of the 7490 counter.

The resulting output from the counter will appear as shown in Fig. 5. Here you can see the BCD code that is output, and also the decimal equivalent of the BCD number.

For those readers that wish to learn a little more about flip-flops and electronic counters we refer you to the Electronics Australia handbook "An Introduction To Digital Electronics".

build up several of these counters and interconnect them to obtain counts that are increasing in decade steps. In other words, if you use two of these counters, you can count up to 100, and with three you can count up to 1000, and so on. To connect one counter to another, all that has to be done is to take the output of the first counter (output labelled QD), and feed this to the input of the next, and so on.


By cascading counters in this way you can obtain count lengths that are as

long as you could want them. All that is required is to build several of these, one for each decade. If for example you want to be able to count to one million, you will need to build six of these counter modules and then interconnect them the way that was described in the last paragraph. The number of applications for a counter of this type is almost endless. All that you need to do is come up with some more ideas, other than those that have already been described here.

In an early issue we hope to show you how to hook up a digital display to your counter, so you can read the count in both binary and decimal form. Apart from being an extremely practical and fun project, it also goes a long way in teaching you some of the basics that are involved in electronic counting.

Incidentally, a little message to all you beginners out there. This is your section of the magazine, and we would welcome suggestions for projects and ideas that you would like to see designed and published. You are the people that know what you want, and you could greatly simplify our task in project selection if you let us know.

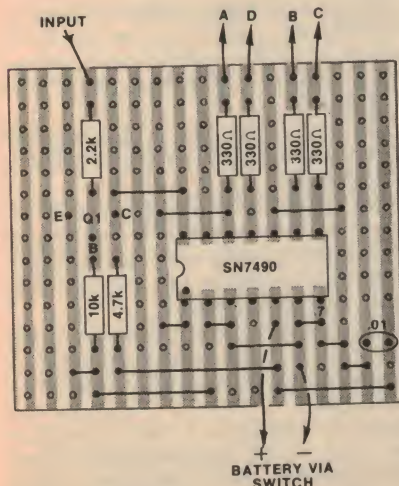In the meantime, we hope that you have lots of fun with the counter, and if you have any novel ideas for the use of the counter, let us know so that we can pass some of these along to other readers.



The component overlay diagram. Note the cuts in the copper tracks.

AUSTRALIAN MARITIME COLLEGE

MARINE RADIO OFFICERS

A two year full-time course, leading to an Associate Diploma in Marine Radio-communications, will commence in February 1980 for those wishing to become Marine Radio Officers.

The course will be conducted in 1980 in Sydney. Students will then transfer to Launceston in 1981 for the final year of the course.


Entry requirements are passes at HSC level in mathematics, an approved science subject and, preferably, English.

For further information please write to:

The Admissions Officer,
Australian Maritime College,
PO Box 986,
Launceston, Tas 7250

MICRO POWER

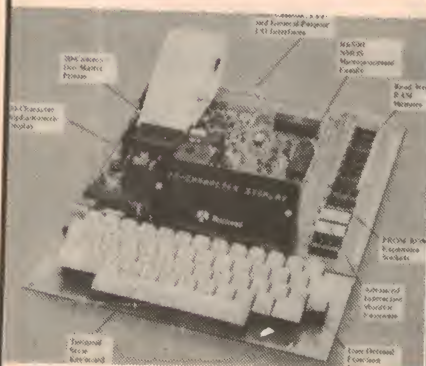**MICROCOMPUTER
WITH PRINTER
THAT'S ROCKWELL
MICROPOWER**



For more on AIM 65 and how you can develop programs in assembly language or BASIC, write



**General
Electronic
Services
Pty Ltd**

99 Alexander Street, Crows Nest,
N.S.W., 2065. Phone: 439-2488.
Telex: 25486 A/B Servo

ADELAIDE: 42-6655
BRISBANE: 277-4311
CANBERRA: 80-4654, 82-3581
NEWCASTLE: 69-1625
PERTH: 325-5722
MELBOURNE: 598-9207
DWELL PTY LTD 487-3111



Letters to the editor

Project errors?

In your October editorial you refer to complaints from readers about errors in projects. I believe you have a record to be proud of.

Since first reading "Radio & Hobbies" in 1954, I have built many of your projects and have never had a problem not of my own making. The same cannot be said of projects I have attempted from other magazines. This is true not only in respect to errors and omissions, but the thoroughness of design (component tolerances, for example).

Keep up the good work!

G. Derrett,
Beacon Hill, NSW.

COMMENT: Thanks for the bouquet, G.D. However, we must admit that despite a fairly elaborate checking procedure, occasional errors do slip by.

NZ attitude to FM

In researching an article, I came across an "Electronic Australia" series on FM radio, written just after approval was given to restart FM transmissions in Australia. The first of the article talked of the FM "hiatus" in Australia and described how, for many, FM broadcasting had become "a pipe dream, which they would (eventually) be too old to enjoy!"

That is still the situation in New Zealand and I, too, am beginning to despair of ever having FM broadcasting in this country. The history of attempts to introduce FM broadcasting to NZ is a sorry one of indifference and procrastination, which has not been helped by frequent political interference in broadcasting.

The first event to impede the introduction of FM radio was the short-sighted decision of the NZ Post Office to allocate most of the international FM band to two-way radio use. Although the Post Office was to have the band cleared by 1980, they have now relaxed this to 1982! Subsequent events which have delayed FM radio include the introduction of colour TV, and the establishment and networking of a second Government run TV channel throughout the country.

A 1973 report which recommended the fragmentation of the one Government broadcasting organisation into four corporations contained an interesting reference to FM Radio, which

admitted its technical advantages, but dismissed it with the statement: "but the submissions to the committee did not reveal the existence as yet of any large body of opinion pressing for the change (from AM to FM)". Thus the public not only has to know about FM without having any transmissions to judge it by, it also has to show the administrators of broadcasting the advantage of high quality transmission methods!

The original "Electronics Australia" article wound up with the words "and what of NZ? There has been consistent minority pressure in that country for a VHF FM service — and no less consistent rejection of the idea by successive governments."

At a public hearing in 1969 there were 33 submissions, nine of which were presented in person. Most favoured the introduction of FM, with the exception of the government broadcasting organisation! Hardly minority pressure!

Your article went on to suggest that on the basis of the Australian decision, this might strengthen the case for FM radio in NZ. I have to tell you no such luck!

Keith Macdonald ZL2AWM,
Silverstream, NZ.

Hearing aids

Four hundred dollars seems a lot to have to pay for a small battery operated mono amplifier.

The price ICs are today, it's not surprising one can buy a calculator from as little as \$6 and a good one for less than \$100; or a pretty complicated solid-state electronic watch for about the same price.

Yet, if one is deaf, it's usually a good deal more than \$100 for just a simple mono amplifier.

It doesn't seem fair since they use the same parts. The people who most need them are the people who can least afford them and they're not a luxury like watches and calculators.

I'm sure if they were cheaper a lot more deaf people would be buying them and making life more pleasant for their relatives.

Seems to me it's a very lucrative racket that needs exposing and since your magazine is quite popular I hope it does just that.

P. Truscott,
Mosman, NSW.

Oldest reader?

Thinking back through the past, I reckon that I may now be the oldest reader of "Electronics Australia" and the journals from which it emerged.

I bought the first edition of "Wireless Weekly" in 1912 or 1913, as published from the old Bulletin office in George St. I've been building radio sets ever since.

The only station on the air at the time was the ship's station that came on at 1:00pm. I thought it wonderful to pick it up on my first crystal set.

Down through the years I've enjoyed reading "Wireless Weekly" through to "Electronics Australia". I'm now 82 and my eyesight is failing but I still make some of your projects to while away the time. My last project was the digital clock with the National module 1002B. I made the aluminium cabinet and finished it in gold and brown.

R. Barton,
Caringbah, NSW.

Computer contest

I think that it is not good that you make a big thing on your cover about "Win a Computer" when you have to own one already to be able to enter. The rules say you have to write the program so it will go into "Level 1 Basic", and they want it on a cassette which only a computer can make. How do I get to know "Level 1 Basic"?

Your cover should also have said "competition for TRS-80 owners only". Joke's a joke, but either the ad or the competition is not fair.

P. Brown,
North Adelaide, SA.

COMMENT: We agree that entrants would have to understand Basic (see article in the same issue) but there are lots of readers who do — students, hobbyists, teachers, professionals — and who have access to a computer using Basic. Being on display in Tandy stores, the TRS-80 is fairly readily accessible for reference. The cassette was not a pre-requisite for success, merely "desirable to assist the judges".

BASIC ELECTRONICS

Basic Electronics begins with the electron, introduces and explains components and circuit concepts, and progresses through radio, audio techniques, servicing, test instruments, etc.

Available from:
"Electronics Australia", 57 Regent St, Sydney. **PRICE** \$3.50 OR by mail order from "Electronics Australia", PO Box 163, Beaconsfield 2014. **PRICE** \$4.10.

MEGASPARK

Australia's best Electronic Ignition Systems

**NOW OFFERS THE ELECTRONICS AUSTRALIA
DWELL EXTENDED ELECTRONIC IGNITION
IN KIT FORM.**

E.A. KIT — \$35.00

WIRED AND TESTED — \$47.50

MEGASPARK TRANSISTOR

IGNITION READY TO INSTALL — \$45.50

PACK AND POST. ADD \$1.50

Write or phone for details

ENSON EQUIPMENT

PO BOX 355, NARRABEEN NSW 2101


PHONE: (02) 913 8386



One-Second Desoldering with SODER-WICK

1. Hold Soder-Wick on termination with hot soldering tip. Wicking action soaks up solder.

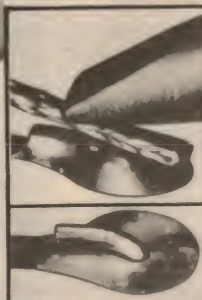2. Remove tip and braid. Termination is left clean and free of solder.



Soder-Wick is a specially treated copper braid which soaks up molten solder like a sponge. Desolders a P.C. pad in a second or so: acts as a heat sink to protect circuits and components.

From your Components supplier or ring:

Royston Electronics

(02) 709 5293 (07) 44 0131
(03) 543 5122 (08) 42 6655
(002) 34 2233 (09) 381 5500

SW-2

RADIO DESPATCH SERVICE

THE SPECIALIST STORE

869 GEORGE STREET, SYDNEY, NSW 2000. (NEAR HARRIS STREET)
PHONES: 211 0816, 211 0191

SPECIAL COMPUTER COOLING FANS



Muffin fan 4 5/8" square.
240V \$24.

NOTE: We keep all PC Boards for EA & ETI projects.
Write or call.

MAIL ORDER CUSTOMERS

\$1 packing plus 5% of order value up to \$80
and thence a flat \$4 for postal items.
Carrier — freight on.

TEXAS INSTRUMENTS

TI 59 CALCULATOR PRICE: \$247.00 plus s/tax.
TI PC100 PRINTER PRICE: \$213.57 plus s/tax.

	Excl	Incl
	S Tax	S Tax
TI-30 Student Pack	20.00	22.10
TI-58C	109.00	120.70
TI-5025M	73.85	81.76
Little Professor	15.00	16.57
Data Man	21.00	23.25

FM Transmitter

HF65 FM TRANSMITTER 60-148 MHz
Will run 5w output with heat sink Ideal for signal testing or for a miniature transmitter which could be received on a standard FM receiver. Kit HF65 — \$9.90.

Distributors For

XCELITE Tools

OPEN: MON-FRI 8.00 am-5.30 pm

Thursday late night shopping until 8.30 pm, Saturday 8.00 am-11.45 am.



REVIEWS OF RECENT

Records & Tapes

CLASSICAL • POPULAR • SPECIAL INTEREST

Liona Boyd: "fine Spanish music"

LIONA BOYD plays music by Albeniz, Barrios, Sor, Satie, Debussy, Tarrega, Payet, Barnes. *Liona Boyd, classical guitar.* CBS Stereo Disc SBR 235975.

The record sleeve refers to the artist on this disc as "The First Lady of the Guitar"; however sexist the argument, it seems to be justified as I cannot recall any other serious guitarist on the distaff side — not among the true professionals, anyhow. Miss Boyd (who would seem to be most toothsome as well), is a young Canadian, whose teachers include Julian Bream, Narciso Yepes and Alirio Diaz — a formidable team indeed. Her playing is so sure, clean and competent that I find it difficult to believe her teachers had a hard task.

About the music: Augustine Pio Barrios, a Paraguayan Indian guitarist, who died in 1944, wrote 19th century music of beauty and charm; Carlos Payet is a composer-guitarist-physician in El Salvador and his music, also, is of

straight-forward appeal. Miss Boyd's transcriptions of Debussy ("The Little Shepherd") and Satie (Gymnopédie No. 1) are sensitive, delicate and work exceedingly well as plucked by her. A Fantasy by Canadian Milton Barnes, written for Miss Boyd and based on an Amerindian folk song is of limited interest. Musically, the best (and not unexpectedly) are the three Waltzes by Fernando Sor, Tarregas' "Recuerdos de la Alhambra" and Albeniz' "Granada" and "Asturias".

It is in fine Spanish music written for the instrument that the classical guitar comes into its own; it is in such music that Miss Boyd gives of her best — and her best is pretty good! My only reservation about this record is in the sound which appears to have been recorded with some bass-bias. Apart from this — and it may well be that others' ears will react differently — all of it is in good taste, the Albeniz is played with agreeable restraint and the Tarrega is as gorgeous as I've yet heard. (P.F.)



are sufficient to be worthy of notice and there are passages in which the piano sound is preferable; others in which the strings seem much more convincing. The contrapuntal final Presto impresses me much more powerfully in this version; on the other hand, the Poco Sostenuto is diminished by percussiveness. As for the Variations, I find the sonority and tone colours of the pianos to be quite definitely preferable to the over-rich orchestral sound that Brahms so often favoured.

Preferences will, needs, be personal ones and dictated by one's taste; one thing stands out: these are important works of considerable beauty, quite apart from their historical curiosity. I can recommend this recording on every count. (P.F.)

☆ ☆ ☆

BRAHMS: Hungarian Dances Complete. Michel Beroff and Jean-Phillippe Collard, piano duet. *World Record Quadrasonic Disc QR 05890.*

Twenty-one Nocturnes from Chopin ... 21 Hungarian Dances from Brahms, and they are all here, on one disc, delightfully played on two pianos. This is really much more fun than hearing the more usual orchestral arrangements, let alone all the other arrangements for various palm-court ensembles. The authenticity of "Hungarian" is, of course, irrelevant; Brahms was not an ethno-musicologist and he wrote these dances to entertain — did not even allot them an opus number!

The Beroff-Collard duo lack the Kon-

Brahms: four hands, two pianos

BRAHMS: Sonata F minor; op 34b, after the Quintet op 34, for two pianos; Variations on a Theme by Joseph Haydn, op 56b, for two pianos. Alfons & Aloys Kontarsky, pianos. *DG Stereo Disc 2531 100.*

This release was actually timed to coincide with the current Australian concert tour, their second, by the Kontarsky brothers. The playing is quite brilliant and, as one has come to expect from them, always musicianly and very stylish. The quality of their playing is matched by the recorded sound; the two pianos blend and balance so well that one might almost suspect the duo to be performed on one instrument, at four hands (the record cover somewhat oddly, refers to "two pianos, four hands" — how many hands would you expect?)

It was not at all uncommon in the 19th century to arrange major chamber works or even full orchestral ones for two pianos or, more usually, one piano at four hands; at first, I expected these works to be such arrangements and I would not have been surprised had they been made, with or without Brahms' approval, by someone else. The surprising thing is that these two-piano works are undoubtedly by Brahms; op 34b in fact precedes the Quintet op 34 and op 56b may or may not have been written before the orchestral version. In any event, we are here faced by two major compositions, authentically Brahms' and both of them as good as unknown in recent times.

The Piano Quintet op 34 is very well known and a justly admired work. The work for two pianos is, in all essentials, identical; all the same, the divergencies

Reviews in this section are by Paul Frolich (P.F.), Neville Williams (W.N.W.), Jamieson Rowe (J.R.), Leo Simpson (L.D.S.), Norman Marks (N.J.M.), Greg Swain (G.S.), and Danny Hooper (D.H.).

tarskys' relentless accuracy and earnestness, which is rather fortunate for this music; they score with greater liveliness and temperament and communicate their joy in happy music-making to the listener. The recording (HMV, originating in the Salle Wagram, Paris) combines agreeable acoustics and good piano tone for any occasion of twenty-one times total pleasure. (P.F.)

Avant-garde sound

REVERBERATIONS TWO. Ron Nagorcka: Sanctus. James Penberthy: Hymn for the Death of Jesus. Scherzo ("Devils up there"). Felix Werder: Holy Thursday. Douglas Lawrence, organ. Move Stereo disc MS 3025 (Move Records, PO Box 266, Carlton South, Vic 3053).

Recorded in St Patrick's Cathedral, Melbourne, this record has remarkably fine sound and contents that are as avant-garde as one could wish for. Side 1, Nagorcka's piece for organ, didjeridu (their spelling and it seems more sensible than the traditional one), voices and electronics is described by the composer as "... the coming together of an organist, a didjeridu player, an electronic technician and a group of untrained singers to produce a sonic object according to the general specifications of a simple score."

Reverberations two

Douglas Lawrence



I do like "sonic object" — a novel term, but one which is quite descriptive of a near-monodic event. At over 20 minutes, the experience may seem a bit long; all the same, there is interest here, there is tension (though without resolution) and some sections of the sound produced are deeply satisfying. Felix Werder's brief piece for organ shows this composer from a new angle; it is nervously charged music and the sleeve notes fairly refer to "... scatter techniques and constant nuance of tempo and colour". As always, Werder makes few concessions to the lazy listener and I regard this as one of his most successful essays in terse self-expression.

The two pieces by James Penberthy are for organ solo and combine strict notation and aleatoric sections. The adaptation of these recent compositional techniques to organ music are, to my ear, very successful

Christmas with Move Records

THE MESSAGE OF CHRISTMAS in Song and Story. Stereo, Avant Garde AVS-117.

An unusual record, this, appropriate for those who have the time to relax and ponder the Christian implications of Christmas.

A female voice is used for the narration and the first impression is one of affectation, even tension. But the impression gives way to acceptance and the realisation that it is probably a deliberate part of the presentation.

All through, the story is punctuated by snippets of Christmas songs from many lands, often in the appropriate language and backed by national instrumental sounds. Israel is represented, along with Mexico, Germany, Spain, India, Ireland, the Ukraine, Norway, the Cameroons, Switzerland, Greece and Chile. There are Gregorian chants and a negro spiritual.

Diction is excellent but, on the rear of the album is a sheet containing both narration and lyrics. The recording quality is clean and the record should be enjoyed, as I said, by those who have the time and inclination to listen. (WNW).

☆ ☆ ☆

15 FAVOURITE CHRISTMAS CAROLS. Organ, Brass and Tubular Bells. Move MS-3019.

This one is also different from the usual run of Christmas albums but for another reason — one that will appeal to some and alienate others. Normally simple carols have been selected and arranged to use the resources available to arranger and conductor Christopher Willcock: Douglas Lawrence playing the organ of St Patrick's Cathedral, Melbourne; Dal Barbare, tubular bells and glockenspiel; the Festival Brass Ensemble.

Carols presented are: While Shepherds Watched — Unto Us Is Born A Son — Sussex Carol — We Three Kings — Hark The Herald Angels — Sing Aloud On This Day — It Came

and I found some of the eventuating tone clusters both interesting and beautiful. Penberthy, in these works, seems to have progressed considerably from earlier organ pieces of his. Nagorcka, 30 years his junior, had also written for organ before and it might be noted that Move Records recorded a piece of his, and one of Werder's, on a previous occasion, with similarly spectacular results. (P.F.)

(Still to be reviewed: "Full Spectrum"; works of Percy Grainger and others performed by Barry Coningham using digitally controlled sound sources).



Upon The Midnight Clear — Es Ist Ein Ros Entsprungen — Once In Royal David's City — First Noel — Coventry Carol — Silent Night — O Come All Ye Faithful — Angles From The Realms — God Rest You Merry Gentlemen.

Recording organ, bells, brass and glockenspiel is not an easy assignment and I could not classify the sound quality as anything more than average. Best you sample it for yourself. (WNW).

☆ ☆ ☆

COME TO BETHLEHEM. Johnny Pearson, his Chorale and Orchestra. Stereo, Avant Garde AVS-118.

Different again is this English recording, which substitutes contemporary carols for the traditional, with some of them, not surprisingly, employing a mild up-tempo beat:

Hallelujah, Hallelujah — Lord Give Us Lasting Faith — Lord of Lords, King of Kings — Star Of The East — Mary, Mary, Pray For Us — Come To Bethlehem — Cantate Domino — How Could There Be A Fairer One — Christmas Prayer — Jesus Christ The Holy Infant — Christmas Prayer — Asleep To The World — Glory To The Lord In Heaven.

The sound quality is a trifle "edgy" in complex passages but, otherwise, the tracks are a pleasant mix of instrumental, solo voice and chorale, and of Christmas/devotional themes which will be new to most. (WNW).

☆ ☆ ☆

All three albums are distributed in Australia by Move Records, Box 266, Carlton South, Vic 3053.

SCHOENBERG: Pierrot Lunaire, op. 21. Yvonne Minton, mezzo-soprano; Pinchas Zukerman, violin & viola; Lynn Harrell, cello; Michel Debost, flute & piccolo; Antony Pay, clarinets; Daniel Barenboim, piano; conducted by Pierre Boulez. CBS Masterworks Stereo disc 76720 (with full texts).

Written in 1912, this music remains as revolutionary and prickly as ever it was — the compiler of the English-language notes rightly states that this is a work one never "gets used to". On this occasion, we have a recording made in

"timbre, clarity, presence"

APPALACHIAN SPRING, Aaron Copland. **THREE PLACES IN NEW ENGLAND**, Charles Ives. Played by the St Paul Chamber Orchestra, conducted by Dennis Russel Davies. Stereo from Digital Master, Sound 80, S80-DLR-101. (From P. C. Stereo, PO Box 272, Mt Gravatt, Qld 4122.)

The notes explain that Appalachian Spring is the current title for a composition "Ballet For Martha", composed circa 1944 for Martha Graham. Although more commonly heard as a ballet suite for full orchestra, it is played here in its sparse original scoring — but a happy episode by way of a quaker wedding in the hills of Pennsylvania.

"Three Places In New England" (or "New England Symphony" or "Orchestral Set No. 1") composed between 1903-1914 involves an enlarged chamber orchestra. It opens with a gentle nocturne ("The St Gaudens in Boston Common"), which is followed by "Putnam's Camp, Redding, Connecticut" — a fantasy on a Revolutionary Army camp, with Stravinsky-like clashes of harmony and rhythm.

"From the Housatonic at

Stockbridge" retains the mood, but in a different setting.

The two sides, 25 minutes and 18 minutes respectively, were non-interrupted performances, as for direct cut, but captured instead on a 3M digital mastering system. The quality is very clean, with soft passages that are likely to be compromised, not by the recording itself, but by ambient noise on the home — from a fan, a ticking clock, or distant traffic.

Indeed, Norman Eisenberg of "High Fidelity" magazine has nominated this as a disc especially suitable for judging instrumental timbre, clarity and presence.

The music, if you don't know it? Copland: instant, simple appeal; Ives: takes longer. (WNW).



heard before and I'll confess to a preference for Mary Thomas' methods which, I think, are closer to the composer's intentions. However, the quality of Minton's vocal effort is quite splendid and possibly easier on many listeners' ears; equally, all the instrumental playing is of a wonderful clarity and precision and Boulez direction is certainly firm and consistent. Although the lavishly produced album includes full texts, in three languages, it is worth noting that other recorded versions of this work had space left for additional music. However, the quality of the recording is what matters more and that is certainly excellent. (P.F.)

☆ ☆ ☆

TCHAIKOVSKY: Piano Trio in A minor, op. 50. Yuval Trio. CBS Masterworks Stereo disc 76698.

In some five decades of concert-going, I've heard this work just once and on record, also, I'd encountered it but once before. It is rather a mystery that this should be so: the music is delightful, characteristically Slavonic and among Tchaikovsky's happiest creations. It was written in 1882, to commemorate the death of Nicolai Rubinstein, founder of the Moscow Conservatory, a supporter of the composer's and an outstanding pianist of his day; therefore one need not cavil if the piano is a little more prominent than in some other trios — it is never oppressively dominant.

If the music is very lovely — in three movements: elegiac and allegro; tema con variazioni, andane co moto; and allegro risoluto — the performance and recording are worthy of it. The Yuval Trio brings three outstanding Israeli musicians together in a remarkably fine reading; the only legitimate objection might be their omission of the eighth variation (a fugue) because it is, in the words of pianist Jonathan Zak

SCHOENBERG — cont.

a Paris church two years ago as one of the "manifestations" connected with the inauguration of the acoustic research centre at the Centre Georges Pompidou — a cause closely connected with Boulez.

Comparisons are neither easy nor, perhaps, very relevant; I've only heard this work twice before on disc, once "spoken" by Alice Howell and once sung by Mary Thomas. In live performance, I know Marilyn

Richardson's splendid readings; what Yvonne Minton gives us, presumably at Boulez' direction, is very different. In this performance, there seems to be a determination (shared by all the participants, except perhaps Barenboim) to avoid emotional excesses, to play down the romantic and expressionist elements and to present the work as starkly and uncompromisingly as possible.

Miss Minton's singing is much further removed from the usually accepted "speech" sounds than I've

MICRO-80

MONTHLY MAGAZINE FOR TRS-80 USERS

\$30 SOFTWARE FOR ONLY \$2.00*

(it would cost at least \$30 to buy each months' software on cassette)

PROGRAMS

- Games
- Education
- Business
- Utilities

WRITTEN FOR

- Level 1
- Level 2
- Disc Basic
- Machine Language

*12 month subscription rate — single copies \$2.50 ea.

TO:

MICRO-80: PO BOX 213, GOODWOOD, SA 5034

PLEASE SEND ME:

- ☐ 12-MONTH SUBSCRIPTION FOR \$24.00
STARTING FROM (Dec 79's issue 1)
- ☐ CURRENT ISSUE FOR \$2.50
(MAKE CHEQUE PAYABLE TO MICRO-80)

Name:

Address:

Post Code:

"somewhat weak". The recording is yet another of the 1977 series made on the occasions of the Israeli Music Centre's opening in Jerusalem; it is distinguished by good sound from both piano and strings and Tchaikovsky, who doubted the validity of this combination, would be duly gratified to hear the result, I believe. (P.F.)

☆ ☆ ☆

VIVALDI: Four Solemn Concertos for Violins. Chamber orchestra conducted by Claudio Scimone. World Record Club stereo, R 03505.

A record for anyone who enjoys the characteristic music of Antonio Vivaldi, the famous "red monk". The four concerti played are all of ecclesiastic origin: that in C major (RV581) for the feast of La Santissima Assunzione di Maria Vergine, in D major (RV212) for the feast of the Tongue of St Anthony of Padua, in B-flat major (RV579) known as the Concerto Funebre, and in F major (RV286) for the Solennita di San Lorenzo. All are rather more contemplative than secular works like the

well-known Four Seasons, but still very satisfying and enjoyable.

The performance here is sensitive and warm, and the recording is also excellent.

If you're at all partial to Vivaldi, well worth a hearing. (JR).

☆ ☆ ☆

SONGS AND POEMS OF AUSTRALIA. Stereo, Harbour MLF-281. Distributed by 7 Records.

I would guess that this album has been designed primarily as a keepsake for tourists, overseas relatives, etc. It is packaged in a colourful double-fold jacket, with typical colour pictures of Australia, an outline map, a flag and a few relevant facts.

The album itself contains songs sung by the Hawking Brothers: Waltzing Matilda — The Wild Colonial Boy — Eumerella Shore — The Lime Juice Tub — Click Go The Shears — Botany Bay — The Queensland Drover — South Australia.

Interspersed with the songs are poems read by Ken Sparks and Terry

Devotional or sentimental?

EVERLASTING KIND OF LOVE. Lynn. Stereo, Day Spring DST-4010. (From Word Records Australia, 18-26 Canterbury Rd, Heathmont, Vic 3135)

Lynn is introduced in the jacket notes as "a very special kind of person ... a striking, lovely young christian" — a statement which is certainly supported by her portrait. Although an obviously capable vocalist, she nevertheless stays well inside the dynamics of the backing — ranging from full orchestral strings to soft rock. For much of the time, the words are submerged by the instrumental but, fortunately, the lyrics appear in full on the inner sleeve.

The title song is "Everlasting Kind Of Love" and the other tracks carry on the same general theme: More Of You — Make Me Smile — It's A New Day — I've Never Been Loved Like This Before — Heed The Call — No Greater Love —



Satisfaction Guaranteed — I Love You — Break Out.

One must accept the sincerity of the artist and the fact that younger people in particular will like the sound but, to many others, the lyrics will be seen as sentimental imitations of secular love songs. Maybe it's me, but I had much the same reaction, a few months back, to Jamie Owens-Collins' "Love Eyes" (July, 1979).

You'd better hear this one for yourself. (WNW).

**PAIA 8700 MICRO COMPUTER/CONTROLLER
PRACTICAL DOWN TO EARTH MICRO COMPUTER
SYSTEM BASED ON THE MOS
TECHNOLOGY 6503 MICROPROCESSOR CHIP
SPECIAL PRICE TO E.A. READERS**



**ALL ENQUIRIES: MAIL ORDER DEPT.
GPO BOX 4000
SYDNEY 2001.
TELEPHONE: 02-663-3911**

TELEX®

**QUALITY PRODUCTS FOR
AUDIO PROFESSIONALS**



36 SERIES

CONTINUOUS CARTRIDGE PLAYER

For background music, message repeating, broadcasting, public address, uses N.A.B. cartridge.



MC SERIES

TELEX/MAGNECORD CART MACHINE

The finest broadcast cart unit available. It runs cooler and costs less. Now available I.E.C. and N.A.B.



CS SERIES

TELEX COMMUNICATION HEADSETS

A variety of professional quality headsets for outside broadcast, cameramen, two way radio. Available single and dual muff.

AVAILABLE FROM

**AUDIO TELEX COMMUNICATIONS
PTY. LTD.**

SYDNEY 1 Little Street, Parramatta, 2150
Tel: 633 4344

MELBOURNE 7 Essex Road, Mt. Waverley, 3149
Tel: 277 5311

BRISBANE 394 Montague Road, West End, 4101
Tel: 44 6328

Records & tapes — continued

Another side of Burt Bacharach

WOMAN. Burt Bacharach and the Houston Symphony Orchestra. Stereo, AM (Festival) L-36843.

A difficult album to classify, this. The music was composed, arranged and conducted by Burt Bacharach and there are nine tracks in all: Summer of '77 — Woman — Riverboat — Magdalena — New York Lady — There Is Time — The Dancing Fool — I Live In The Woods.

Although the title majors on the Houston Symphony, 11 guest musicians have been added, plus five vocalists. As a result, the sound ranges from traditional orchestral, through touches of jazz and blues, to rock. And therein lies my difficulty in trying to visualise



who will like or dislike the end result. Really, I think that it's an album that will appeal most to Bacharach fans who may tend to respond and analyse, rather than merely listen. Certainly the album is being hailed overseas as a response to the danger of his becoming musically "type cast".

The sound quality and production is excellent but you had still better judge for yourself. (W.N.W.)

McDermott: Kimberleys — Cattle Camps — Clancy Of The Overflow — Long Time I Remember — Retired Territory Drover — Ruby's Pie — Northern Plains — The Camp Cook, Southern Home.

The sound is clean and full and the general style a compromise between "City and the bush" — not too rough, not too much polish. As I said, a keep-sake, in the same general class as mulga wood ashtrays (WNW).

REGINALD DIXON Recalls The Hits of World War II. Stereo. World Record Club WRC — R 04454.

As I remember it, the first record I ever bought was a 2/6d Regal Zonophone featuring Reginald Dixon playing "Teddy Bear's Picnic" and "Blaze Away". He's been "blazing away" ever since, the very epitome of the old-time Wurlitzer organist, with their endless array of popular tunes, and their ability to embellish, im-

provise, bridge and modulate with seemingly effortless ease.

That is well illustrated here with 12 tracks containing three melodies in each, strung together in traditional style. Please don't ask me to list them but you'll know them. And listen to the way he pulls every trick of the console to summon and blend voices without the least suspicion of a pause.

Technically, my pressing had an irregularity on the outer edge which upset the playing of the first few grooves but, hopefully, it was an isolated fault. And the sound is rather zizzy on the high pitched pipes; you can ease that back with the tone control, if you want to be reminded of one of the big-name artists of the thirties. (W.N.W.)

☆ ☆ ☆

THE MINSTREL SHOW. Stereo, 7 Records MLR-277.

The jacket names Eddie Foy Jr, Harold Adamson and David Burns, but gives no other information about the when and where of this recording. However, it follows the traditional minstrel show format with Mr "Locutator" and Mr Bones and their traditional jokes, a couple of featured instrumentalists and, of course, old-time songs. As a recording and as a minstrel show, I could only rate it as "average". (W.N.W.)

☆ ☆ ☆

NEW FROM



**THE NEW
MODEL
LM-353—
\$127.50**

**A Serviceman's Multimeter
with LCD Display.**

3-1/2 digits
3 digits + 100%
over-range
0.5% Accuracy

PORTABLE

BATTERY OPERATED—
Providing up to 100
hours of operation.

FEATURES

- Measures VDC, DCmA, ohms, low ohms, VAC and ACmA.
- Automatic polarity, decimal and overload indication.
- No zero adjustment and no full scale ohms adjust.
- Large LCD display for easy reading.
- Input voltage protection
- Size: 1.9"H x 2.7"W x 4.0"D.
- Parts and labour guaranteed for one year.

A Portable, Dual Trace Oscilloscope with Big Performance and a Low, Low Price.

\$627.00



**The New MS-230 Miniscope
with 30MHz Bandwidth!**

Portable Battery Operated With Rechargeable Batteries & Charger Unit

FEATURES

- Dual trace — 2-channel; separate, chopped or alternate modes.
- 30-megahertz bandwidth.
- External and internal trigger.
- Time Base — 0.05 microseconds to 0.2 Sec/div — 21 settings.
- Battery or line operation.
- Line synchronization mode.
- Power consumption less than 50W.
- Vertical Gain — 0.01 to 50 volts/div 12 settings.
- Size: 2.9"H x 6.4"W x 8.5"D.
- Weights only 3.5lbs with batteries.



For further information, contact:

Non-Linear Systems (Aust.) Pty Ltd

61 Lothian Street, North Melbourne, Vic. 3051. Phone 329 9951 or your closest distributor.

Vic.
Radio Parts Group
Pty Ltd
Ph. (03) 329 7888

N.S.W.
Radio Despatch
Service,
Ph. (02) 211 0191

N.S.W.
University Graham
Instruments
Ph. (02) 53 0644

QLD
L. E. Boughen
& Co.,
Ph. (07) 35 1277

QLD
Electronic
Components (Old)
Ph. (07) 371 5677

S.A.
Pratronics
Pty Ltd
Ph. (08) 212 3111

*Plus 15 per cent sales tax if applicable.

THE WIND IN THE WILLOWS, by Kenneth Graham. Adapted and produced by Tony Robertson. Stereo, two-record set. World Record Club WRC R-05547, R-05548.


First published in 1908, "The Wind In The Willows" was not received very warmly at the time. However, the highly fanciful stories, built around such animal characters as Ratty, Mole, Badger, Mr Toad and Otter, gradually built up a following, to become something of a classic.

In this two-record set, the stories have been re-scripted for sound recording, with Patricia Wymark as the narrator and other experienced people in the character roles. The seven episodes are: The River Bank — The Open Road — The Wild Wood — Dulce Domum — Toad's Adventures — Like Summer Tempests Came His Tears — The Return Of Ulysses. All these are presented in stereo with sound effects (cars, trains etc) as nearly as possible reminiscent of the era.

I guess that their major appeal will be partly nostalgic and partly to teachers and others involved with primary school-age children.

Technically, the sound quality is average only, adequate for the purpose but not without some suggestion of "crushing", probably in the original tape master. But don't let this put you off if you're partial to goings-on in the wild wood yonder! (WNW).

The Australian CB SCENE

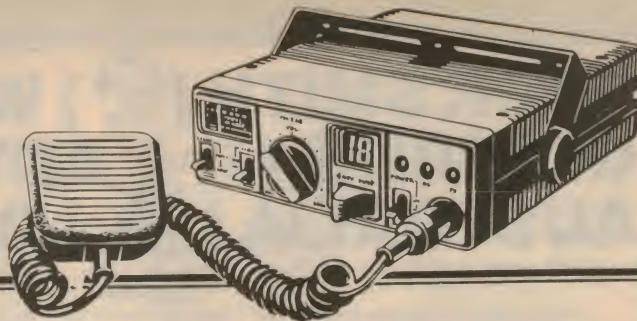

FIRST US-STYLE REACT TEAM SET UP IN SYDNEY

According to a letter from its newly elected President, the first REACT team has been formed in Australia and has established a liaison with the International organisation in the United States.

REACT is an acronym for Radio Emergency Associated Citizens Teams and, as such, is probably the best known — if somewhat controversial — CB volunteer aid group in the Americas. Figures published a few years back credit REACT with about 1400 24-hour stations monitoring and active on the U.S. emergency channel 9. They are manned by more than 40,000 "hard core" members, with at least as many again licensed CBers having had some kind of REACT training.

REACT is primarily concerned with assisting motorists in need of routing information, or faced with mechanical problems, or in need of emergency help from ambulance, fire or the police. They operate from vehicles and/or fixed locations and handle about 50,000 calls per month, nationwide.

Unlike many other CB groups, REACT is not particularly concerned with the social aspects of CB-ing, DX-ing, card-swapping, etc. They are a fairly loose organisation of "teams" averaging about 25 members involved primarily in community service activities.

Unfortunately, some such teams have attracted a good deal of criticism for excessive zeal and the assumption of a right to order their fellow citizens around. In extreme cases, according to reports, this has gone as far as marked cars, uniforms and acting out the role of highway police.

It will not be surprising if moves to set up REACT teams in Australia are not met with opposition based on this image.

The first such group in Australia is the Waratah State REACT Team (NSW) 4380, with Peter W. Herman NBR 695 as President. Their postal address is P.O. Box M447, Sydney Mail Exchange, 2012.

Enclosed with the announcement is a letter from REACT International, which reads as follows:

Dear Peter:

We are delighted to acknowledge the establishment of your REACT team

as the first official REACT Team in Australia!

We are enclosing all necessary information for immediate activation of your team. Your membership cards and other materials for each of your members has been shipped separately and should be arriving very soon.

Your official REACT Team charter is being made up and will be received some time later.

I think that you should be aware of the fact that we have already received correspondence from CREST concerning your Team operation. They are very concerned about REACT developing in Australia when it is not under their auspices. We should point out to you that you are established as a local team and have no authority to represent REACT except in your local team area. Of course, when new people

want to start REACT in Australia we will refer them to you for consultation and co-ordination.

Very frankly, we are still hopeful that CREST will choose to affiliate as National REACT organisation, and in that case all existing REACT Teams will be part of that body. We don't know when or if that will ever happen.

In any case, you are now the only official REACT team in Australia. We will keep you informed as to when and if additional teams are established. We of course expect that you will want to assist in that effort and we are enclosing additional team applications for that purpose.

If we can help you in any way unique to your team's needs, please let us know. Your interest and cooperation will help to build REACT in Australia in the months ahead.

Best wishes for the success of your team. You know we stand behind you.

REACTively,
Gerald H. Reese
(Managing Director)

NCRA: National Citizens Radio Association

I would like to thank "Electronics Australia" for the support being shown for the NCRA and for CB operators generally, in providing this space in your magazine. It is much appreciated.

For those readers who are not quite sure what NCRA is, the following brief details may be of interest:

The NCRA is a National Organisation made up of the constituted Divisions of the ACT, NSW, Victoria, Western Australia, Queensland and Tasmania. Each Division is made up of and represents the clubs within the State which are affiliated with it. To affiliate, a club pays the State Division a once only \$10.00 registration fee, and \$2.00 per financial member per year. Of this, 50% is forwarded to the National body, and this, except for donations, etc, is the only income of the organisation. Clubs are represented on the State Council by sending along two delegates to each Council meeting, where State policy is formulated. In turn, each State sends along two delegates to the National Council.

The Government has officially recognised the NCRA as the spokesman for the CB operators of Australia and, as such, the NCRA was a member of the WARC '79 Preparatory Group. Many NCRA submissions were accepted in the re-write of the RB 14. The 1982 proposed cut-off of 27MHz is still a priority issue with the NCRA, and the time is coming when the CB operators will be faced with an issue which, to a great many of them, will be as important as legalisation itself was.

At the Annual General Meeting of the NCRA, held in Canberra last September, the first "CB Merit Award" was presented. It is a National award which will be presented each year to the person considered by NCRA as having contributed most to CB in that year. There was only one nomination for the inaugural Award, and who else could it have been than Mike Hurst-Meyers, past National Director of the NCRA and past National Director of CREST.

(Mrs) Jan Christensen,
National Liaison Officer, NCRA.

'DICK SMITH () WILL MATCH () ANY GENUINE () ADVERTISED PRICE IN AUSTRALIA () ON YAESU () GEAR'

That's right! If someone advertises Yaesu for lower than our advertised price, take a copy of the advert to your nearest Dick Smith store. We will guarantee to match — and better any genuine advertised Australian Yaesu price! You can't lose!

INTRODUCING:

- Digital frequency display
- 320 channels 144 – 148MHz
- Auto or manual scanning
- Keyboard entry of frequency
- Memory with back-up
- Any repeater splits
- 12.5kHz scanning steps
- 4 bit CPU for frequency control

Cat D-2888

\$358⁰⁰

Price includes NiCad battery pack.

The Yaesu FT-207R 2 metre hand held

This is the transceiver you've dreamed of. Gone are the horse-and-buggy days of crystal controlled hand-helds. This new Yaesu uses a four-bit microprocessor to give you more features, more control than you'd imagine possible. If you really want to get into 21st century amateur radio, the Yaesu FT-207R is the transceiver to take you there.

Expensive? no, not when you remember you're holding a computer in the palm of your hand. A computer ready to go to service for YOU.


The Yaesu FT-207R. 21st century amateur radio.



We welcome



or offer easy terms with

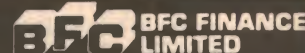

Some other fine Yaesu products from Dick Smith. . .

FT-901D: all HF bands, all modes, 180W input.

For the discerning amateur who wants the best technology available today. Vox, FM unit, RF speech processor, digital frequency display, RF negative feedback, crystal filter... you name it, the 901D has it! Outstanding value. Cat D-2854 **\$1266.00**

FT901D Options:

FC-901 Antenna tuner Cat D-2855 **\$265.00**

DC-DC Converter Cat D-2856 **\$75.00**

Memory Unit Cat D-2858 **\$149.50**

FT-101Z all HF band transceiver. 180W DC input.

A worthy successor to the FT-101E. All the features of the previous model, but with 6146B finals, selectable AGC, front panel VOX control, Rx/Tx clarifier, and fully compatible with the FT-901 series of accessories. Superb! Cat D-2862 **\$849.00**

(For accessories refer above to FT901)

FT-7B: Up-rated mobile HF transceiver. 100 W.

Now a massive 100 watts with AM, USB & LSB, the FT-7B is a force to be reckoned with. Designed for mobile use (single knob tuning makes it a breeze) but makes a great base station, too. 13.5V operation, a superb performer. Cat D-2868. **\$649.00**

FT-625R: 6 metre, all mode transceiver.

The sunspot cycle is nearing its peak. Don't miss the chance of some rare DX! The 625R will get it for you. ALL modes, so you aren't going to miss any of the action. Cat D-2886. **\$795.00**

FT-227RB: 2 metre mobile transceiver.

Here's a chance to go 2m mobile and save. We've reduced the price of this unit by \$46.00! Simplex, repeaters, etc etc, all easily accomplished! 1W or 10W output. Cat D-2891 **\$399.00**

CPU2500RK: The ultimate 2 metre transceiver!

Central processing unit (CPU) controls the action. And there's plenty of that. 800 channels from 144-148MHz, LED readout, dual gate front FET front end, 25 watts output... it really is a brilliant piece of gear. Call in for a test drool! Cat D-2889 **\$549.00**

FRG-7: listen to the world! 0.5 - 30MHz coverage.

This extremely sensitive communications receiver is used by monitoring services throughout the world. It runs from mains or 12 volt, is a delight to use. Cat D-2850 **\$395.00**

YAESU MOBILE ANTENNAS

The greatest mobile system you'll find: Buy the gutter mount base and 2 metre stub and you're on the air immediately on 2m. Then, as you need them, buy the whips for the HF bands you want to operate on. It's as simple as that. Now there's no excuse not to go mobile — with Yaesu mobile antennas from Dick Smith Electronics.

RSE-2-M
Gutter mount
Cat D-4100
\$32.50

RSE-2A
2 metre stub
Cat D-4102
\$10.95

RSL-145
6 & 2 metre antenna
Cat D-4104
\$23.95

RSL-3.5
80 metre antenna
Cat D-4110
\$19.95

RSL-7
40 metre antenna
Cat D-4112
\$19.95

RSL-14
20 metre antenna
Cat D-4114
\$20.95

RSL-21
15 metre antenna
Cat D-4116
\$20.95

RSL-28
10 metre antenna
Cat D-4118
\$20.95

DICK SMITH ELECTRONICS

SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RESELLERS



AMATEUR RADIO

by Pierce Healy, VK2APO



Amateur radio clubs — their aims and activities

On a worldwide basis amateur radio can be likened to a club with ever increasing membership; a club whose keynote is to foster the widest possible communication between all members at all levels, technical, social, educational and the goodwill which comes from sharing a common interest.

The fraternity of amateur radio is made up of individuals and large and small groups throughout the world, meeting under various names which can be embraced by the term "club" — an association of people united in pursuance of a common interest. It is through the aims and activities of such individuals and clubs that continuing progress is made at the grassroots level in the fields of technical and social discourse.

Australia has the oldest national amateur radio society in the world — the Wireless Institute of Australia — founded in 1910. Throughout the country there are clubs fostering local needs by providing a venue for meeting others with the same basic interest. A warm welcome is extended to visitors dropping in on such gatherings.

To promote such aims and activities, and as a service to all interested in amateur radio, here is a brief summary of those clubs who accepted the invitation to be included in these notes.

The details given are: club name, call sign and postal address. Contact may be made on air as most clubs hold nets on which inquiries may be made, or from the address given. The repeater (R) call signs given are for the two metre band and licensed through the respective clubs. Regular meetings provide lectures and classes for those wishing to obtain their amateur licence.

AUSTRALIAN CAPITAL TERRITORY
ACT Division WIA, Inc: VK1WI, VK1RAC, VK1RGI. Secretary, PO Box 46, Canberra, ACT 2600.

NEW SOUTH WALES

Australian National Amateur Radio Teleprinter Society: VK2TTY. Secretary, PO Box 860, Crows Nest 2065.

Blue Mountains Amateur Radio Club: VK2AUX, VK2NCM. Secretary, PO Box 54, Springwood 2777.

Central Coast Amateur Radio Club: VK2AUX, VK2RAG. Secretary, PO Box 238, Gosford 2250.

Crestwood Amateur Radio Club: VK2BFZ. Secretary, 16 Turon Avenue, Baulkham Hills 2135. Telephone 639 0267 or 638 6970.

Hunter Branch WIA, NSW: VK2AWX, VK2RAN. Secretary, 49 Valaud Crescent, Highfields 2289.

Illawarra Amateur Radio Society: VK2AMW, VK2RAW. Secretary, PO Box 1838, Wollongong 2500.

Jesmond & Districts Electronic and Communication Club: VK2BHZ. Secretary, John Murphy, at clubrooms rear of Regal Theatre, Moore Street, Birmingham Gardens, Saturday 1pm to 5pm.

Liverpool and District Amateur Radio Club: VK2AZD. Secretary, 42 Waratah Cres, Macquarie Fields 2564.

Mid South Coast Amateur Radio Club: VK2RMU. Secretary, PO Box Milton, 2538. Telephone (044) 55 1077.

Museum of Applied Arts and Sciences Amateur Radio Club: VK2BQK. Secretary-general, MAASARC, 659-695 Harris Street, Broadway, Sydney 2007.

North West Amateur Radio Group: VK2RMI (Moree). Publicity Officer, David Grant, 19 Delander Cres, Moree 2400.

St George Amateur Radio Society: VK2LE, VK2RLE. Secretary, PO Box 77, Penshurst 2222. Telephone 531 3295 (Bus), 521 7303 (AH).

University of New South Wales Amateur Radio Society: VK2BUV. Secretary, UNSWARS, PO Box 1, Kensington 2033.

Westlakes Radio Club: VK2ATZ, VK2RWR. Secretary, Box 1 PO, Teralba 2284. Telephone (049) 59 1588.

Wagga Amateur Radio Club: VK2WG, VK2RWG. Secretary, PO Box 71, Koorringal 2650.

VICTORIA

Eastern and Mountain District Radio Club: VK3ER, VK3BNW. Secretary, PO Box 87, Mitcham 3132.

Geelong Amateur Radio Club: VK3ATL, VK3RGL. Secretary, PO Box 520, Geelong 3220.

Geelong Radio and Electronics Society: VK3ANR. Secretary, PO Box 962, Geelong 3220. Telephone (052) 21 3658.

Gippsland Gate Radio Club: VK3BJA. Secretary, PO Box 98, Dandenong 3175. Telephone (03) 772 7985.

Moorabbin and District Radio Club: VK3APC. Secretary, PO Box 88, East Bentleigh 3165.

RAAF Laverton Amateur Radio Club: VK3ARC. Secretary, PO Box 326, Laverton 3028.

Shepparton and District Amateur Radio Club: Secretary, PO Box 692, Shepparton 3630.

Southern Peninsula Amateur Radio Club: VK3BSP, VK3VKR. Secretary, 7 Spensley Street, Rosebud 3939.

Swan Hill and District Radio Club: VK3BSH, VK3RSH. Secretary, PO Box 682, Swan Hill 3585. Telephone (050) 37 2591.

QUEENSLAND

Brisbane VHF Group: VK4IF, VK4RBC, VK4RBN. Secretary, PO Box 911, Fortitude Valley 4006.

Dalby and District Amateur Radio Club: Secretary, 19 Twine Street, Dalby 4405. Telephone (074) 62 2596.

AMATEUR RADIO

Gold Coast Amateur Radio Society:
VK4WIG, VK4RGC. Secretary, PO Box 588, Southport 4215.

Townsville Amateur Radio Club:
VK4WIT, VK4RAT. Secretary, PO Box 964, Townsville 4810.

SOUTH AUSTRALIA

Wireless Institute SA Division:
VK5WI, VK5RAD, VK5RHO, VK5RMN.
Secretary, PO Box 1234, GPO, Adelaide 5001.

Telecommunications Division

COURSES IN TELECOMMUNICATIONS

at
RMIT TECHNICAL COLLEGE

The Telecommunications Division conducts Full-time and Part-time (Day & Evening) courses at Electronics Mechanic and Electronics Technician level in the following areas:

Communications —

CB Radio and Broadcasting

Digital Electronics —

Microprocessors, Computers

Industrial Electronics —

Electronic Control Systems

Television —

Colour TV Servicing, TV Studios

Other Courses offered by this Division include 35 mm and 16 mm Motion Picture Projection, Post-trade and Post-technician subjects, Advanced Audio, Video Tape Recorders, TV Antennae, Remote Controlled TV, etc.

Applications close on 18 January

Further Information is available from the Telecommunications Division, Telephone 341 2358.

RMIT Technical College, 80 Victoria Street, Carlton 3052. Telephone 347 7611.

RMIT
THE DOOR TO
GREATER
OPPORTUNITY
SINCE 1887.

1392

South Coast Amateur Radio Club:
VK5ARC. Secretary, PO Box 333, Morphet Vale 5162.

WESTERN AUSTRALIA

The West Australian VHF Group Inc:
VK6WH. Secretary, PO Box 189, Applecross 6153.

Perth Radio League of Western Australia: Secretary, PO Box N1102, GPO, Perth 6001.

TASMANIA

North West Branch Tasmanian Division WIA: VK7NW, VK7RNW. Secretary, PO Box 194, Penquin 7316. Telephone (004) 25 3770.

NORTHERN TERRITORY

Alice Springs Community College Radio Club: VK8AR, VK8RCA. Secretary, PO Box 2935, Alice Springs 5750.

Darwin Amateur Radio Club: VK8DA. Secretary, PO Box 37317, Winnellie 5798.

INTERNATIONAL NEWS

Amateur radio teletype offers a definite advantage by providing hard copy of interesting events relating to amateur radio. Several ART groups transmit regular news sessions for local and overseas information.

From the Australian National Amateur Radio Teleprinter Society here is an extract from a broadcast by the British Amateur Radio Teleprinter

Group of the Radio Society of Great Britain made on September 23, 1979.

"Russian amateurs may use top band: An announcement in the newspaper 'Sovetskiy Patriot' on May 16 last has been translated by HB9BRQ as follows: 'Amateur radio stations and novice radio stations are permitted to operate on CW in the band 1850 — 1950kHz, on SSB between 1875-1950kHz and with AM on 1900-1950kHz. The highest power that can be used is 10 watts, with five watts maximum for novices.

"Novice stations may only establish communication with another novice station. For these stations the prefix 'EZ' will be used. The number of the prefix will be composed in the usual system.

"It is hoped that the use of this band will encourage the development of radio sport as well as a wide attraction of youth into amateur radio."

"RAYNET — is the abbreviation given to the Radio Amateurs' Emergency Network in the United Kingdom set up to handle emergency traffic for police and a number of other organisations in times of emergency and disaster where normal communications have failed."

"RAYNET has over 2000 members who it is stated are highly skilled in the art of communication, and is, outside the USA, the largest such organisation in the rest of the world."

"The national RAYNET committee wants to obtain information about similar organisations in other countries to ensure that complete information

The video cassette you buy today...
can only be as good
as the service you get tomorrow.

It's not like purchasing a simple television set, which requires little or no intricate adjustments on installation. When you buy a video cassette recorder, the expert service that comes immediately with it is absolutely essential for good performance. And it is equally self-assuring to know the service will always be there when you need it. That's why people come to VIDEO TECHNICS. Because we're more than just a store for videocassette recorders and a range of electronic equipment. We're service experts, too.

SPECIAL

Universal TV Video Monitor. Ideal as display unit for dream 6800, Sorcerer, TRS-80, Apple, CCTV, or any composite video signal. Features 240v AC or 12v DC. Video input via quality BNC socket. Can be switched over as TV receiver. Priced at \$149. See our complete range of video equipment and other special items such as clock timers, full length features and many more.



BUY FROM THE
SERVICE EXPERT



VIDEO TECHNICS

The Carousel Centre, Shop 17-18, 530 Oxford Street, Bondi Junction.
P.O. Box 50, Bondi Road, Bondi 2026 NSW 2022 Telephone 3872555.
Third floor, Equitable Life Building, 301 Coronation Drive, Brisbane
4064 Telephone 36-1257.

AMATEUR RADIO

can be given of public service given freely by amateurs at international IARU and other conferences. Such information should be sent to E. W. Yeomanson, G3IIR, 32 Gaynesford Road, Forest Hill, London, SE 23 2UQ, England as soon as possible."

(Comment: It would be no surprise if, on a population basis, national or amateur, the area covered and the scope of emergency and community service work done by WICEN — the Wireless Institute Civil Emergency Network — surpasses the claims made for Raynet. — VK2APQ).

GOSFORD FIELD DAY

The 23rd annual field day of the Central Coast Amateur Radio Club will be held at the Showground, Showground Road, Gosford, NSW, Sunday February 17, 1980.

A full program of radio and non-radio events and attractions have been arranged for the enjoyment of amateurs, their families, and friends.

See January and February issues of these notes for further details.

WARC 79

At the time of compiling these notes (mid October) a few details of the World Administrative Radio Conference, which commenced on September 27, had been received. These were preliminary decisions and may yet be amended.

The conference (organised by the ITU) will deliberate for 10 weeks. In addition to the 147 delegations, 38 international organisations have sent observers, including the International Amateur Radio Union. The delegates and observers number over 1900.

The first plenary meeting was addressed by Mr M. Milli, Secretary-General of the ITU. Mr Milli referred to the expansion of the ITU since the previous conference in 1959 and the vast technical achievements made since then. He drew attention to the need to use the radio spectrum in the most efficient and economic way.

In regard to the conference he made these points.

"With its 1800 participants, its 14,000 proposals amounting to nearly 5000 pages, and co-ordinated documentation in several volumes totalling nearly 3000 pages, no term seems adequate to designate the largest conference ever

IONOSPHERIC PREDICTIONS FOR DECEMBER

Reproduced below are radio propagation graphs based on information supplied by the Ionospheric Prediction Service Division of the Department of Science. The graphs are based on the limits set by the MUF (Maximum Usable Frequency) and the ALF (Absorption Limiting Frequency). Black bands indicate periods when circuit is open.

14MHz EAST		01	02	03	04	05	06	07	08	09	10	11	12	13	14	15	16	17	18	19	20	21	22	23
EAST AUST TO BARBADOS (SR)																								
JOHANNESBURG																								
McMURDO SOUND																								
NEW DELHI																								
NEW YORK																								
RIO DE JANEIRO																								
TOKYO																								
VANCOUVER																								
WELLINGTON																								
WEST AFRICA																								
WEST EUROPE (SR)																								
WEST EUROPE (LR)																								
ADELAIDE TO SYDNEY																								
BRISBANE TO MELBOURNE																								
PERTH																								
SYDNEY																								
DARWIN TO SYDNEY																								
MELBOURNE TO PERTH																								
SYDNEY																								
21MHz GMT		15	16	17	18	19	20	21	22	23	24	01	02	03	04	05	06	07	08	09	10	11	12	13
EAST AUST TO BARBADOS (SR)																								
JOHANNESBURG																								
McMURDO SOUND																								
NEW DELHI																								
NEW YORK																								
RIO DE JANEIRO																								
TOKYO																								
VANCOUVER																								
WELLINGTON																								
WEST AFRICA																								
WEST EUROPE (SR)																								
WEST EUROPE (LR)																								
ADELAIDE TO SYDNEY																								
BRISBANE TO MELBOURNE																								
PERTH																								
SYDNEY																								
DARWIN TO SYDNEY																								
MELBOURNE TO PERTH																								
SYDNEY																								
28MHz EAST		01	02	03	04	05	06	07	08	09	10	11	12	13	14	15	16	17	18	19	20	21	22	23
EAST AUST TO BARBADOS (SR)																								
JOHANNESBURG																								
McMURDO SOUND																								
NEW DELHI																								
NEW YORK																								
RIO DE JANEIRO																								
TOKYO																								
VANCOUVER																								
WELLINGTON																								
WEST AFRICA																								
WEST EUROPE (SR)																								
WEST EUROPE (LR)																								
ADELAIDE TO SYDNEY																								
BRISBANE TO MELBOURNE																								
PERTH																								
SYDNEY																								
DARWIN TO SYDNEY																								
MELBOURNE TO PERTH																								
SYDNEY																								

organised under the auspices of the ITU."

The conference elected Mr Roberto J. P. Severini from Argentina as chairman. Delegates from the USSR, Cameroon, Switzerland, China, Italy and USA were elected vice-chairman.

Mr E. J. Wilkinson of Australia was elected vice-chairman of Committee 6 — Regulatory Allocations Committee.

Taking a very active role at the conference is another Australian, Mr Richard Butler, deputy-secretary general of ITU.

AMATEUR RADIO COURSE

The University of New South Wales Amateur Radio Society's vacation study course for the full and novice examinations, to be held by the P & T Department early in 1980, will commence on Friday December 14, 1979 at 7.00pm, at the Wireless Institute Centre, 14 Atchison Street, Crows Nest, Sydney, NSW.

This will be the society's seventh annual course and will cover Morse code, theory, and regulations for the three types of amateur licence.

The course is to be held on Tuesday, Thursday, Friday and Saturday evenings from 6.00pm to 9.00pm for six weeks.

The cost, which includes all text books, is \$22 for the AOCP and NAOCP and \$5 for the Morse code only section.

Those wishing to enroll should attend the WIC at 7.00pm Friday December 14.

Additional information may be obtained from Michael Katzmann, VK2BEA, telephone (02) 665 8014 after 6.00pm.

This is an excellent opportunity for beginners or those wishing to upgrade their knowledge in the field of amateur radio.

WOULD YOU LIKE TO JOIN THE RANKS OF AMATEUR RADIO ENTHUSIASTS?

The Institute conducts Courses for the A.O.C.P. or L.A.O.C.P. with the benefit of expert guidance throughout your studies.

PERSONAL CLASSES for 1980 will commence on Tuesday, February 5th, at 6.00pm at Crows Nest, and will continue for three terms to December in readiness for the February 1981 examinations.

CORRESPONDENCE COURSES may be commenced at any time.

For further information, write to:

The Course Supervisor, W.I.A.
PO Box 123,
St Leonards, NSW 2065

Radio clubs and other organisations, as well as individual amateur operators, are cordially invited to submit news and notes of their activities for inclusion in these columns. Photographs will be published when of sufficient general interest, and where space permits. All material should be sent to Pierce Healy at 69 Taylor Street, Bankstown 2200.

SHORTWAVE SCENE

by Arthur Cushen, MBE



Test transmissions from Africa Number One: new French relay base in Gabon

The recent test transmissions from Africa Number One, a new Radio France International relay base in Gabon, have been heard world-wide. Listeners in both Australia and New Zealand also heard the broadcasts, which featured a competition with a Peugeot motor car as first prize!

The test transmissions from the four 500kW transmitters located at Moyabi-Moanda, Gabon, were received on a variety of frequencies; in fact 18 channels were tested during the period. The two test transmission periods, 0400-1200 one week and 1300-2100GMT the following week, resulted in many listeners in Australia and New Zealand hearing these broadcasts.

The station offered prizes including a Peugeot car to the winners of a lottery which would be drawn after the series of tests were completed. Listeners were asked to send details of their reception on a postcard, including name, address, frequency of reception, interference and details on the particular broadcast being heard. The transmissions were in Arabic, French and English, but later other European languages were added to the schedule.

The address of the station was given as Africa One, Mail Box Number One, Libreville, Gabon.

Africa Number One is the name of the holding company which owns the transmitters at Gabon and is leasing them to Radio France International for their world-wide services. The test transmissions were beamed to South America, Europe, North Africa and East Africa and reception in New Zealand covered frequencies from 9595kHz up

to 21525kHz. The channels which have been assigned to the station are as follows: 9595, 11720, 11755, 11910, 11945, 11950, 15125, 15200, 15270, 15325, 15415, 17820, 17835, 17895, 21475, 21495, 21525 and 21635kHz.

NSB EXTENDS SERVICE

The Nippon Shortwave Broadcasting Company has, for many years, broadcast on short-wave with a commercial program. The first program is mainly Japanese, but the second program includes English.

An extension of the schedule has been noted on 6115kHz when JOZ6 is received with an English broadcast from 0900-0930GMT. The program then continues in Japanese. The English program consists of commercial announcements and talks, as well as popular English recordings.

The broadcasts on NSB are regularly received in 3925, 3945, 6055 and 9595kHz. These four channels have been in use for many years and provide fair reception during our evening listening period.

The Nippon Shortwave Broadcasting commenced operation in the early 1950s and one of our early verifications was from JJ2KY operating on 3925kHz with the power of 500W.

RADIO NEW HEBRIDES

The recent change in status of broadcasting in the New Hebrides has resulted in a new verification being printed, and this will be issued shortly. Many reports are being held by the station pending the printing of the new card. The station is also installing new transmission equipment, which should give better reception of the signals in

Australia and New Zealand.

Formerly known as the New Hebrides Broadcasting Service and Radio Vila, the organisation is now known as Radio New Hebrides. The address is PO Box 49, Port Vila, New Hebrides. Broadcasts are well received on 3945kHz to closing at 1100GMT daily except Sunday, when close down is 1000GMT.

A new medium-wave transmitter has already been noted on 1125kHz and this frequency seems to replace 1422kHz. French has been noted to 1000GMT, and the local Bislama program follows to closedown.

ENGLISH FROM ALGIERS

Radio Algiers has been observed by Stewart Forsyth of Christchurch, NZ, with a new program in English 2000-2030GMT on 11810kHz. According to "DX Post" in Adelaide the station also broadcasts on 7145, 9610 and 11740kHz. According to the WRH Newsletter the transmissions in French from Algiers are erratic and have been observed on 7195, 9509, 11633, 11810 and 15160kHz.

Further observations show that as well as the unannounced 11810kHz carrying the English broadcast at 2100GMT, another frequency, 11615kHz, is also heard with the same program. News is broadcast up to 2015 when disco music is featured up to 2030GMT. The out-of-band frequency of 11615kHz has suffered some side band interference from All India Radio on 11620kHz.

TRANS WORLD RADIO

Trans World Radio at Monte Carlo has been looking for a new outlet in the 31-metre band. The latest channel is 9495kHz, which is in use with English up to 0800GMT. Broadcasts are well received on this frequency and requests for reports have been noted in the transmission with the address of the London office being given. This address is 175 Tower Bridge Road, London SE12AS, England.


Another new frequency for Trans World Radio is 11795kHz, which is still

Notes from readers should be sent to Arthur Cushen, 212 Earn Street, Invercargill, NZ. All times are GMT. Add eight hours for WAST, 10 hours for EAST and 12 hours for NZT. In areas observing Daylight Saving Time add a further hour.

GET VICOM'S INTERNATIONAL LINE-UP

AIRCRAFT RECEIVER Model 747

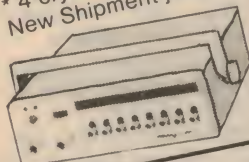- * 16 Channels
- * AC/DC Operation
- * 4 crystals supplied
- New Shipment just arrived!




\$199

All the big names in international communications gear right here!

Like Icom, Leader, Kenwood — to drop only a few of our top names. At Vicom, you'll find not only Australia's largest range of communications gear — but all the best-known names in this field from around the world. Check out our international Line-up today!

TR DIP METRE SCOOP PURCHASE — \$89

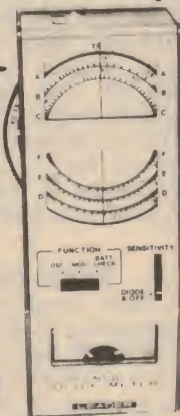Normally \$132
Freq. 1.5-250 MHz
Modulation 2KHz
Sine
Power 9 volts
2mA Max.



LEADER

NEW! KENWOOD R-1000 COMMUNICATIONS RECEIVER

- * AM/SSB/CW
- * 200 KHz-30MHz




Introductory Price \$498

VHF & UHF POCKET RECEIVERS

- * 10 channel scanners
- * 12 channel units
- * prices from \$78 & ST

BEARCATS TOO!

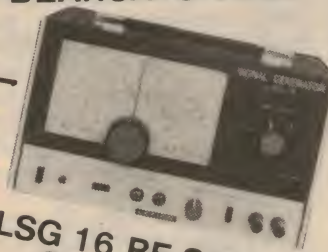

LSG 16 RF SIGNAL GENERATOR

100KHz-100MHz Solidstate RF signal generator. Suited for aligning the IF circuits in AM, FM and TV sets.


\$119

PORTABLE VIDEO CAMERA

— What the home video market was missing!

- * Black & white with 4:1 zoom.
- * Built-in split image focus.
- * Fade out control.
- * Built in condensor mike.
- * Light weight.

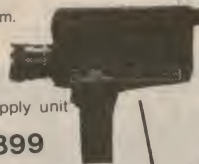Includes its own power supply unit. Write or call today!



\$399

OVER 2100 SOLD!
Yes, more than 2000 IC22S have been sold in Australia! Surely a mark of success for this superb rig.

IC22S 2MFM: STILL \$299

27MHz Marine Transceivers

AC516 ANA incl. one channel — \$126.00
MARINE ANTENNAS ALSO AVAILABLE!

Coax Relays

CX-2L 1.8-170 MHz, 100 w pep — \$45.00
CX-2H 1.8-450 MHz, 200 w pep — \$69.00

SWR/PWR Meters

VC2 Popular twin meters, 3-150 MHz — \$35.00
SWR200 Osborn, 3-200 MHz — \$86.00
CN620 Daiwa, cross-needle type, 1.8-150 MHz — \$99.00
CN630 Daiwa, 140-450 MHz, direct read — \$135.00

Cameras

EX-803 B&W, handheld with 4:1 300m — \$414.00

Plugs & Sockets

BNC Plugs \$2.80

BNC Jumper leads \$6.20
BNC Chassis Sockets \$2.80
BNC "T" adaptor \$5.60

2m Bi-Linears

MR900E Tono, 80-90w incl. Rx preamp — \$289.00
MR1300E Tono, 120-B&W incl. Rx preamp — \$350.00

Kenwood Transceivers

TS520S HF transceiver — \$635
TS120S Solid state 100w — \$735.00
TS120V Solid state 10W — \$600.00
TS180S Solid state 10w — \$1240.00
Call us today for a good deal.

Microphones

VM-1 Noise cancelling, hand ptt, low z — \$10.00

Coaxial Cable

RG58AU mil spec. 30m reels — \$13.00
RG213/U mil spec. per metre — \$1.40

ICOM Gear

IC701 transceiver NOW — \$1199.00
IC22S 2m transceiver — \$299.00
IC551 6m transceiver — \$799.00
IC280 2m fm remotable — \$450.00
IC502 6m ssb portable — \$239.00
IC202S 2m ssb portable — \$318.00
IC211 2m all mode — \$847.00

Morse Keys

HK702 Deluxe Key with marble base — \$41.00
HK708 Economy Key — \$23.00
HK706 Operator's Key — \$25.00
MK701 Manipulator (side-swiper) — \$45.00
PALOMAR 1C Keyer — \$149.00

Baluns

AS-BL Asahi 50 ohm for beams — \$34.00
BL50A 50 ohm 4 KW. 1:1 for dipoles — \$32.00

Radio Teletype Terminal

O-7000 Tono RTTY CW/Baudot/ASCII — \$839

Duncan Baxter VK3LZ
Custom Service Manager

Sydney 635 6399
Adelaide 43 7981
Rockhampton 28 2843

Perth 321 3047
Newcastle 69 1222
Gold Coast 32 2644
Geelong 78 9660
Melbourne 836 8635

Perth 446 3232
Brisbane 48 6601
Townsville 72 2633

Vicom

68 Eastern Road,
South Melbourne,
Victoria, 3205.
(03) 699 6700

Launceston 44 3882
Brisbane 38 4480
Adelaide 272 8417
Kalgoorlie 21 1906
Wellington (NZ) 287 946
Wagga 21 2125

SHORTWAVE SCENE

being used with transmissions to South East Europe and the Middle East. An Armenian program has been observed on this channel at 1845GMT.

ETHNIC RADIO

Ethnic radio in Australia has been extended with the opening of repeater stations in Newcastle and Wollongong which relay the 2EA Sydney program. Both of these stations operate with a power of 100W on medium-wave. Wollongong, on 1485kHz, and Newcastle, on 1584kHz, have both been verified by the writer, with reception in New Zealand best just before sign-off at 1400GMT. 2EA's schedule shows that it operates from 2000-1400GMT and broadcast in 41 languages. The address of the station is Radio 2EA, GPO Box 21, Sydney 2001.

The two present stations which have operated for some months are to increase power. 2EA Sydney is to move from 801 to 1386kHz early in the New Year with an increase of power to 5kW, while 3EA, the Melbourne station, will move from 1116 to 1224kHz with the power increased to 5kW.

A further ethnic station is projected for Brisbane. 4EB will be operated by Ethnic Broadcasting Association of

Queensland with 250W power and should come into service this month.

NEW GREEK FREQUENCIES

Broadcasts of the Voice of Greece to North America have been heard on the new frequency of 9650kHz from 0200GMT. This channel replaces 9655, which suffered interference from Radio Moscow and from Radio Kiev during the transmission period 0200-0355GMT. The signals from Athens are also observed on 9515 and 11730kHz. The transmission is all in Greek, except for English news 0215-0225GMT.

Another new channel is 7205kHz, broadcasting to Australia in Greek from 2100GMT. This signal has been well received, but during our mid-summer period could be a little difficult to hear, due to the low frequency. The transmission is 2100-2150GMT and is also heard on 9640 and 9760kHz.

ISRAEL FREQUENCIES

A new frequency for the Israel Broadcasting Authority has appeared on 21600kHz with a relay of the Home Service of 1900GMT. Another relatively new channel is 15615kHz. Consistent signals on 21600kHz are received on Saturdays and Sundays from 0535-0600GMT, but a program in Russian relayed on 25620kHz at the same time is subjected to severe jamming. The higher frequency of 29705kHz seems to be free of any jamming and provides fair reception.

LISTENING BRIEFS EUROPE

FINLAND: Helsinki is broadcasting to North America with English 0330-0400GMT. Two frequencies are used, 9675 and 11755kHz, with the latter channel giving the best reception.

SPAIN: The broadcast in Spanish to Australia and the Philippines, which for some months has been using 9790kHz, is now heard on 11920kHz 0730-1000GMT. The transmission is best received on 11730kHz, which carries the service from Madrid up to 1100GMT, while 9520kHz carries the same transmission.

BELGIUM: Brussels has two daily transmissions in English 1705-1750GMT on 6010 and 17740kHz to Africa. English to the Americas is 0015-0100GMT on 6080 and 9685kHz. There is a DX program on the second and fourth Sunday of each month at 1735GMT to Africa, and on Monday at 0045GMT to North America.

ANDORRA: Adventist World Radio has been carrying out test transmissions over Radio Andorra on 6215kHz 2000-2100GMT. This daily transmission has English for the first 30 minutes and then at 2030GMT on Monday French, Wednesday Arabic, Thursday Greek, Friday Dutch and German and Sunday Swedish. According to the BBC Monitoring Service, the transmissions on Tuesday and Saturday are in English for the full hour.

EAST GERMANY: Radio Berlin International has made a frequency change for its English transmission at 0330GMT. The new channel is 11975kHz which replaces 11970kHz. English broadcasts to Europe are: 1915-2000GMT on 6080, 6115 and 7185kHz; 2030-2115 on 7260; and 2130-2215 on 6080 and 6115kHz.

AMERICAS

COLOMBIA: Ecos del Combeima in Ibague, which was using 4785kHz, has been noted on the new frequency of 6025kHz by Ray Crawford of Invercargill, NZ. The station operates 24 hours a day, and has been heard around 0800GMT with typical Spanish programming and identification announcements after each recording. ☺

BRIGHT STAR CRYSTALS PTY LTD

35 EILEEN ROAD, CLAYTON, VICTORIA, 546 5076
(ALL MAIL TO:— P.O. BOX 42, SPRINGVALE, VIC. 3171)

INTERSTATE AGENTS

• ROGERS ELECTRONICS
ADELAIDE Phone 42 6666
• HOSE & EQUIPMENT
SYDNEY 666 8144

B.S.C. TELEX AA36004

• DILMOND INSTRUMENTS
HOBART 47 9077

• WESTEST ELECTRONICS
PERTH 337 6393

• FRED HOE & SONS PTY. LTD.
BRISBANE 277 4311

C-MOS CLOCK FREQUENCY GENERATORS

Supply Requirements:

5 - 12 V Dc at 6 MA. No load

Output Drive:

50 MA Model - 6 & 22
5 MA Model - 13

Stability:

Better than 1-PP/M

Operating Temperature Range:

0-60°C

Supply voltage to be nominated by user

Output frequency:

Nominated by user

Maximum Crystal Frequency:

5 Volt Supply - 5MHz max 12 Volt - 9MHz max

Crystal Frequency:

Required frequency X number
counters
Frequency X 2x

NUMBER OF COUNTERS

Model BSC 6 - 14
BSC 13 - 16
BSC 22 - 28 Stages
BSC 11 - 14

BSC 11 has varicap

Fine and Course trimming for higher
setting accuracy

Crystal Locked:

for maximum stability

Output Options:

2' through 2¹⁰

FORMULAR for crystals frequency:-
(Required output frequency X 2x to
give a crystal frequency of 2 to 8MHz
ie. 100Hz X 2¹⁴ = 6553.6)

Output: Square wave 0 - 99 supply
volts 1 - 20 MA Max
Supply voltage 5 - 12 Volts Dc

Stability: ± 003% / 0-60°C

P.C.B. Dimensions.

	length	width	height
BSC 6	43 mm	27 mm	20 mm
BSC 13	52 mm	40 mm	26 mm
BSC 22/11	54 mm	48 mm	26 mm

If the module you require is
not listed then please in-
quire.

We have many others.



Model BSC 11



Model BSC 6



Model BSC 13/22

Australian Radio DX Club

A non-profit, hobby group, now in our 15th year, serving shortwave DXers throughout Australia. Our monthly magazine "Australian DX news" is packed with up-to-the-minute news on club activities, station schedules, technical articles, reception and QSL notes. Comprehensive new-member kit. A full range of membership services available — stationery, report sheets and special publications. Shortwave, medium wave and utility DXing covered. Regional branches throughout Australia. Write now, enclosing a 30c stamp for further information to ARDXC, PO Box 67, Hightett, Victoria 3190 or PO Box 79, Narrabeen, NSW 2101.

New Products

Beckman 3020 Digital Multimeter

Beckman Instruments, Inc have entered the digital multimeter market with a range of three instruments which have liquid crystal displays. The instruments are rugged and fully protected, and have guaranteed long-term accuracy. Battery life is up to 2000 hours and should last two years under normal use.

We reviewed the Beckman model 3020 which comes in a high-impact-resistant ABS plastic case with a large recessed selector switch and a 3½ digit liquid crystal display. The case measures 174mm long x 93mm wide x 46mm deep and it weighs about 450 grams including the battery.

The model 3020 has many features common to other digital multimeters such as AC and DC voltage measurements from 200mV to 1500V and resistance measurements up to 20 megohms. Other features which are not so common include AC and DC current measurements up to 10 amps and the "Insta-ohm" facility.

The "Insta-ohm" facility operates when the 3020 is switched to any resistance range and causes a small "ohm" symbol to appear on the display whenever there is continuity between the probes. This is a very useful aid in rapid circuit testing.

Range and function selection are performed by a single large rotary switch which has easy-to-read and unambiguous markings. A tilting bail is fitted for convenience of use.

Overload of the meter is indicated by a flashing "OL" display. Maximum input voltage is 1500VDC or 1000V RMS. Low battery voltage is indicated by flashing of the decimal point.

A special diode test function is included in the resistance ranges. It provides a constant 5mA current through the diode under test and the display gives the resulting voltage across the diode.

A very worthwhile feature of this DMM is the low open circuit voltage between the test probes when using the resistance measurement ranges. The voltage is less than 250mV which means that it won't turn on a silicon junction, so in-circuit resistance measurements can be readily made — something you certainly can't do with the traditional analog multimeter.


DC voltage accuracy of the 3020 is stated to be within $\pm 0.1\%$ of reading plus one digit. We have few voltage

standards which are specified to within those limits but our limited checks indicated that the 3020 certainly meets this specification. Beckman specify this accuracy for a period of one year for temperature limits of 20 to 30 degrees Celsius.

AC voltage accuracy is quoted for three frequency ranges, with the accuracy reducing for the higher frequencies. Over the range from 45Hz to 2kHz, the accuracy is stated to be

enables one to measure the true average DC voltage even with quite large AC signal components present. The quoted figure for the normal mode rejection ratio is 60dB at frequencies above 49Hz. We were able to quickly verify this by using a simple arrangement of a transformer in series with a 10 volt regulated DC supply. Even though the peak voltage of the AC voltage exceeded the average DC voltage there was no change in displayed DC voltage — again well within specifications.

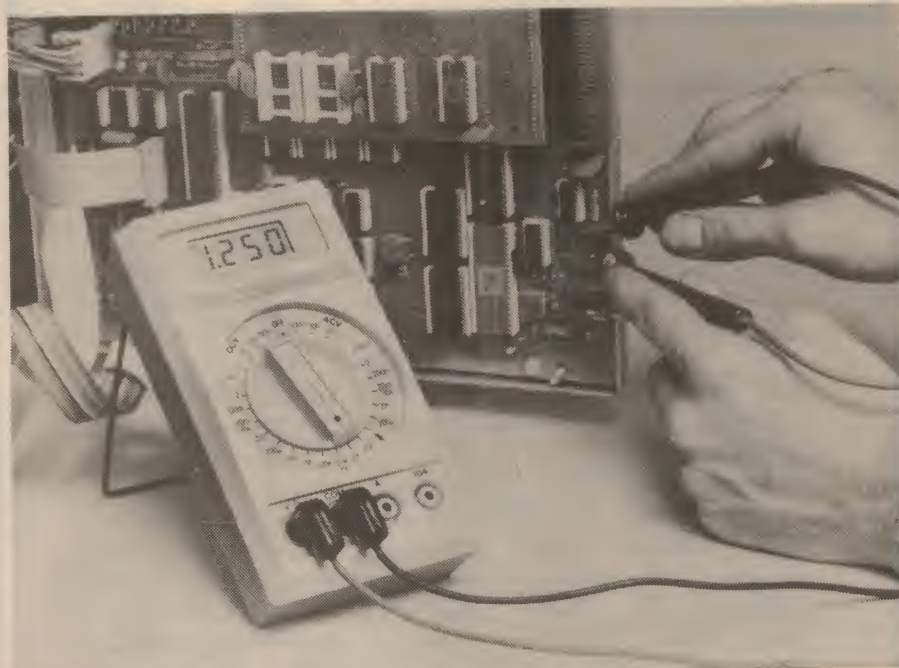In summary, the overall performance of the Beckman model 3020 is very good. The only quibble which we had was that the detent action of the range selector could have been more positive.



within $\pm 0.6\%$ of reading plus three digits; from 2kHz to 5kHz, the figure is $\pm 1\%$ of reading plus five digits; and from 5kHz to 10kHz, the accuracy is specified to be within $\pm 2\%$ of reading plus nine digits. Our tests confirmed that the model 3020 was well within this specification.

The more advanced digital multimeters, including the Beckman 3020, feature high AC rejection on the DC voltage range. This very useful feature

Accessories which are available for the model 3020 include a 50kV high voltage probe, an RF probe for measurements up to 200MHz and 2A, 20A and 200A AC current clamps.

The 3020 has a list price of \$179 while the model 3010 is \$139 and the model 3030, which features true RMS readings, is \$199. Further inquiries should be addressed to Warburton O'Donnell Ltd, 372 Eastern Valley Way (PO Box 182), Chatswood, NSW 2067.



ELECTROCRAFT PTY LTD

68 WHITING ST, ARTARMON TELEPHONE 438-4308 Ext. 6

E.T.I. Metal detector kit.	\$55.00
ROTATORS CDE 44	\$165.00
ROTATORS. CROWN. Load 17kg wind test to 70mph includ 70' 3-way cable	\$99.00
UHF TM13 Beam Antenna 465 to 480Mhz	\$28.75
1/4 Ground Plane 27Mhz Antenna	\$32.00
5' Rod CB Antenna Base 12' lead & plug	\$14.00
Topix Gutter mount CB middle loading Antenna	\$14.50
Low Pass CB filters 75 ohm	\$10.91
Cobra 138xLRA 18Ch AM/SSB Deluxe. digital readout	\$162.00
CABLE Coaxial double screened 75 ohm.	
CABLE 2045 Times 3.5dB loss	47cm
\$56.00 152m roll	
CABLE 2560 Times 3.00 dB loss	59cm
\$63.75 152m roll	
CABLE 50ohm CB Coaxial	37cm
\$36.00 100m roll	
CABLE 300 ohm Ribbon slotted plain	19cm
\$12.00 100m roll	
CABLE 300 ohm open wire	70cm
\$14.00 30.4m roll	

MAST HEAD AMPLIFIERS	
Hills 300 ohm 12dB gain	\$40.00
Hills 300 75 ohms 20dB gain	\$54.00
Kingray MH20. 20dB gain 75-300 ohm	\$74.97
Kingray MH20. WN. 20dB gain with Atten of 20dB on ch 3 to 5A	\$81.00
75 to 75 ohm 40-880Mhz. IN LINE AMPS. Ecraft	
1.75 D16 16dB gain	\$45.00
2.75 T12 12dB gain 2 outlets	\$52.79
3.75 T10 10dB gain 3 outlets	\$53.70
4.75 T10 10dB gain 4 outlets	\$54.19
1.75 D25 25dB gain	\$53.55
2.75 D21 21dB gain 2 outlets	\$60.44
3.75 D19 21dB gain 3 outlets	\$61.35
4.75 D19 21dB gain 4 outlets	\$61.84

MASTS 2.4m — 3m — 4.5m — 6.7m
MASTS Telo Guyed 6m to 30m
Coaxial plugs lots of 10 60c each

TES Field Strength Meter	
VHF-UHF 41-65. 65-110. 155-280. 470-840Mhz	\$257.60

TELEVISION AERIALS	
HILLS 215-8EL	\$25.30
CY7 Colinear 300 ohm	\$31.00
CA16 Phased Array	\$48.00
2010 Airways anti ghost	\$58.56
TL3 Log Periodic 10 EL	\$39.29
TL4 Log Periodic 11 EL	\$46.48
EFC2 75 ohm anti ghost	\$42.96
EFC3 75 ohm anti ghost	\$62.41
EFC4 75 ohm anti ghost	\$78.64

CHANNEL-MASTER CITY ANTI GHOST	
3110-300 ohm	\$27.96
3111-75-300 ohm	\$41.98
3617A 28 EL Crossfire World's highest gain antenna 11 14dB	\$134.98

FM AERIALS HILLS	
FM1 300 ohm	\$11.55
FM3 75 ohm	\$28.55
353 300 ohm	\$14.72

MATCHMASTER HIGH GAIN	
FMG/2 6.2dB	\$24.23
FMG/6 8.7dB	\$45.74


Are you ready for UHF. We have the largest range of VHF & UHF Masthead and Distribution amplifiers in Australia. Distributors and wholesalers required in all States.

**PLEASE INCLUDE POSTAGE
WITH ALL ORDERS
TRADE ENQUIRIES WELCOME**

We are specialists
30 years in the antenna business.
Hours: 8am to 5pm. Sat 9am to 12 noon.

New Products


Hitachi 'Scopes

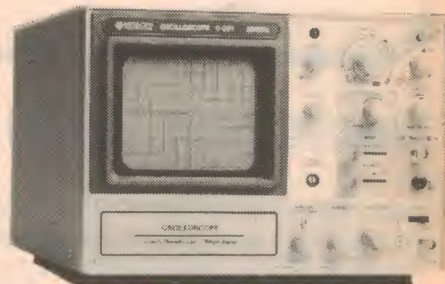

Pictured above is the Hitachi model V-301 oscilloscopes which is one of four recently released onto the Australian market. The V-301 is a single-trace model with 30MHz bandwidth. Other models in the range are the V-151, single trace, 15MHz; V-152, dual trace, 15MHz and V-302, dual trace, 30MHz bandwidth.

The V-152 is anticipated to be the most popular model and will sell for \$540 plus sales tax where applicable. All enquiries should be directed to the distributors, Standard Components Pty Ltd, 10 Hill Street, Leichhardt, NSW 2040.

Christmas Novelty

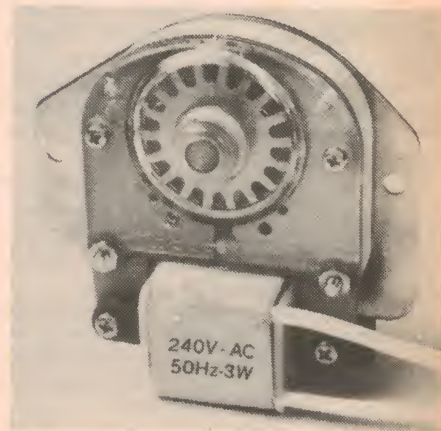

Buried in A.C.E. Radio adverts is a bargain which has an automatic appeal for the festive season — a motor-driven microswitch rated at 110-250VAC, 10A. It switches every four seconds and can be wired to flash lights long-on short-off, or vice versa. Alternatively it could control two separate strings. \$2.50 + 50c P&P. A.C.E. Radio, 136 Victoria Rd, Marrickville 2204.

"ELECTRONICS AUSTRALIA" PROJECTS & CIRCUITS NO. 2

Available from "Electronics Australia", 57 Regent St. Sydney PRICE \$3.00. OR by mail order from "Electronics Australia", P.O. Box 163, Beaconsfield. 2014. PRICE \$3.60.

*HAPPY
CHRISTMAS to ALL*

Phone 7476472

FROM: ELECTRONIC AGENCIES
115-117 PARRAMATTA RD,
CONCORD 2137

I would like to thank all my valued customers for the great deal of support they have given me during the past year — the first year of "Bill Edge's Electronic Agencies."

A note of thanks must also go to my suppliers who were prepared to back me when I was starting up — with special thanks to Dick Smith, The Pak Electronics and Radio Dispatch Service — without whose support getting started may have been difficult.

All The Best

To All,

Bill Edge

*Electronic Agencies
7476472*


Ultrasonic rangefinder

Just released by Peter Shalley Communications, this new electronic rangefinder uses ultrasonics to measure distances from 50cm to eight metres at the press of a button.

Operation of the "Contact" rangefinder is quite simple. The user simply aims it at the target (eg the wall of a room) and depresses the ranging key. The distance from the rear end of the unit to the target is then read off a 3-digit LED display.

Accuracy of the unit is around the 1% mark, which should be adequate for most situations. An in-built 8-digit calculator allows the user to calculate areas, volumes etc. In short, the Contact rangefinder should prove invaluable to anyone who needs instant rangefinding for calculations and cost estimates.

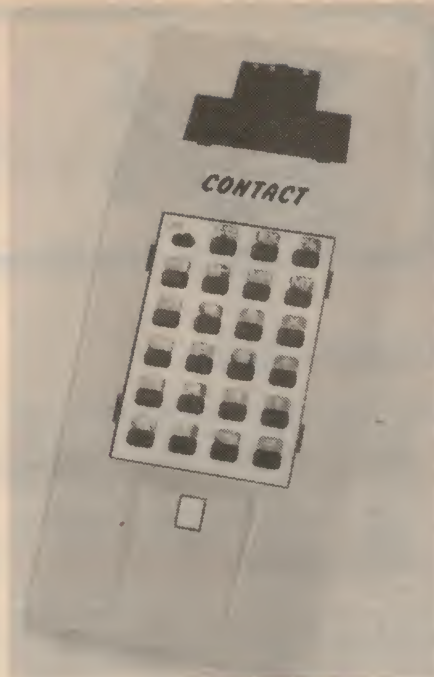For further information contact Peter Shalley Communications, 554 Pacific Highway, Killara, NSW 2071. Telephone 498 2611.



This 24-page colour booklet on kit building is now included in all Jostykit electronic kits sold in Australia. Entitled "Jostykit Kit Guide", the booklet provides valuable basic information for the beginner. It tells you which tools to buy, shows how components are mounted on a PC board, gives information on soldering, illustrates the resistor colour code, and has colour photographs of just about every type of electronic component you can think off.

The Jostykit kit range comes from Denmark and includes audio amplifiers, radio tuners, RF preamplifiers, car burglar alarms etc. The range is imported by Vicom, 68 Eastern Rd, South Melbourne 3205. Telephone (03) 699 6700.

TASMAN ELECTRONICS

12 Victoria St. Coburg, Vic. 3058. Phone (03) 354 5062

ELECTRONIC COMPONENTS
TRANSISTORS
IC's
RESISTORS
CAPACITORS

PLUGS & SOCKETS
TRANSFORMERS
SANKEN MODULES
ILP MODULES
POTENTIOMETERS
DIODES, ETC

WIRE & CABLE
AUDIO LEADS
MULTIMETERS
CALCULATORS
INSTRUMENT CASE
POWER SUPPLIE

MUSICAL INSTRUMENTS
RECORDS, CASSETTES
SPEAKERS AND
SPEAKER KITS
STYLII, BATTERIES
VALVES

T.V. AERIALS
AND ACCESSORIES
HI-FI PRODUCTS
JOSTY KITS
PROJECT PC BOARDS
BOOKS, PLUG PACKS

MAIL ORDERS
WELCOME—
COME AND SEE
US — our
prices are the
"BEST IN TOWN"

printed circuits

- Accurately machine printed etched
- Phenolic & fibreglass-gold tin plated
- EA R & H ET Philips Mullard available
- Specials to your drawing
- POSTAGE small 80c large \$1.10.

	\$		\$		\$
79PG9	3.00	ET146	2.50	79PS11	2.80
ET573	2.80	79MD9	2.80	ET606	3.00
79QM9	3.00	ET577	2.80	ET473	3.50
79RR8	4.20	79PS10	2.80	79R18	2.80
79BT9	2.60	79SF10	2.50	79AL9abc	4.20
79AC9	3.50	79TT7	2.60	79W9	2.80
ET576	4.20	79SF9	2.60	ET731	3.00
ET730	3.50	ET574	2.80	ET575	2.20
ET252	3.00	ET814	2.80	ET725	3.50
79WF8	3.20	79SR8	2.80	79TRF5	2.50
79PS6	2.80	79UT8	3.00	79M8	2.80
ET451	2.50	79FR6	3.50	ET148	2.50
6,800	8.50	ET472	3.00	ET724	2.20
79UPS6	2.50	79CL7	4.80	79KB7	2.80
ET144	3.50	79SA5	8.00	ET651	4.50
79R05	3.00	ET254	2.50	ET471	5.50
77EQ2A	3.50	79EQ2C	2.50	79EQ2B	4.00
		ET249	—		2.50
		ET253	—	ET594	2.50
ET320	2.20	ET253	—	ET470	3.20
ET595	2.80	7905	—	79A3	3.00
491	4.50	559	3.80	721	3.00
79PS3	2.60	78SE3	4.00	79PB2	3.20
79P1B	280	79P1A	2.80	78C1B	2.80
79C1A	3.00	558	2.50	557	3.00
142B	4.00	142A	8.00	79UP1	5.00
79S1	4.50	79W3	2.60	79CL1	2.60
791T2	5.00	78SB12	3.00	78S12B	2.20
78S12A	5.50	781M12	3.00	78UP10	7.00
78N10	2.60	78C11	3.10	78DT10D	2.00
78DT10C	2.50	78DT10B	2.80	78DT10A	6.50
ET813	3.50	ET143	2.80	ET141	4.20
ET812	2.80	ET593	3.20	ET490	2.80
ET556	6.00	78DB11	2.80	78UP9	6.00
78BBd9	3.50	555	4.00	650C	2.60
650B	2.60	650A	4.00	138	3.80
718	2.60	553	3.00	811	3.30
590B	8.00	590A	8.00	78MC10	4.00
78E09	2.50	ET605	7.00	ET391B	2.50
ET391A	2.50	ET551	3.00	ET641	ON/AP
ET591C	2.20	ET550	2.80	ET592	4.50
78UT9	16.00	78MX9	3.30	78T9	2.30
78UM8	2.60	78CL8	3.00	ET638B	3.00
ET638A	4.00	ET248	2.30	ET318	7.00
ET591	4.00	ET810	2.80	78TM8	2.80
78TSC7	2.50	78PT7	2.50	78VBG7	3.50
ET137B	2.80	ET137A	3.50	ET139	2.50
ET717	3.50	ET587	7.00	ET640	16.50
78F6B	3.50	78N	2.80	78A06	2.80
246	4.00	489B	2.50	489A	2.80
78CD4	2.60	78PS5	2.50	78C5	3.20
78UP5	5.00	ET140D	4.00	ET140A	14.00
ET1140P	5.50	ET136	2.50	ET487B	7.50
ET487A	750	ET588 20	10.00	78NG4	3.00
78UT4	4.00	78EK3	3.30	78T3	3.60
78B2	3.00	781A2	2.60	ET450B	2.60
ET450A	2.80	ET716	4.00	ET715	3.00
ET486	3.20	ET245	2.50	78C2	3.00
78AF2	3.00	78S3	2.60	78CF1	2.80
77CB12	2.60	77PH12	2.60	77PM12	3.50
ET135	3.00	ET586	2.80	77MX11	2.50
775C11	3.80	77PS11	2.50	77UP6A	3.00
77MX11	2.50			77PS11	2.50
ET604	2.50	ET585, R	3.00	ET635	2.80
ET713	3.00	ASC11	2.80	77UP11	6.50
77TS9	3.00	ET603	3.00	ET583	2.50
ET134	2.60	77AL8	2.50	77T10	2.50
77DVM9	2.80	ET065	2.50		3.20
ET067	2.20	ET063	2.50	ET083	2.20
ET072	2.50	ET085	2.00	ET084	2.50
ET485	2.80	ET484	3.00	ET581	2.50
ET481M	2.50	ET582B	2.60	ET582A	3.00
ET547	2.50	ET317	2.50	ET712	2.50
77D7	2.50	7787	2.80	77DL7	6.00
77UP6	3.50	77TTY7	3.00	77QB7	3.20
ET631/2	4.50	ET481PS	3.00	ET444M	2.00
ET444S	3.00	ET316	2.50	ET549A	2.50
ET548	3.20	77TTY6	2.50	HMS276	6.00

ALL SILICON 30/60w PA PORT AMP

6 1/2"W x 8 1/2"D x 3 1/4"H 12 — 16V. two inputs 5 & 100mV. 125. 250. 500 ohm output only. No. 763A \$70 ea. 240V operation \$33 extra. Freight collect.

COILS and IF's All \$2.50 ea plus post 60c 3/4"W x 3/4"D x 2"H

MAIL cheque or money order
(add postage) direct to:—

RCS radio pty ltd

651 FOREST RD BEXLEY.
NSW 2207 587 3491

DC REGULATED POWER SUPPLY

LABORATORY SPECS AT AN
AFFORDABLE PRICE!



MK-IV
6 AMP
10 AMP
PEAK

Rec. Retail
\$74.95 inc. Tax

IDEAL FOR VHF 25
WATT BASE STATIONS

SPECIFICATIONS:

- AC Input Volts 240/50Hz
- DC Output Volts 13.8V
- Output Current
at 50% Duty Cycle 6 Amps
- Output Current Peak .10 Amps
- Voltage Regulation1% at
Rated Load
- Ripple & Noise .5 MV P-P at
Rated Load
- Short Circuit Protected
- Primary Circuit Fuse
- "On" Neon Indicator
- Power Switch
- Screw-on or Push-in Terminals
- Rubber Feet
- Dimensions . 130mm x 75mm
x 200mm
- Weight 3.0kgs
- S.E.C. Approved
- P. & T. Approved

"IT'S A FACT"

TRANSWEST POWER SUPPLIES
GIVE YOU BETTER VALUE FOR
YOUR MONEY THAN ANY OTHER
BRAND

Manufactured By:

TRANSWEST TRADING CO.,
PERTH, W.A.

P.O. Box 80, Osborne Park, W.A. 6017
Phone (09)444 0505 Telex 94100

Distributed By:

RADIO PARTS GROUP,
562 Spencer St., West Melbourne,
Victoria.

I.F.T.A. AUSTRALIA,

1 Greville St., Randwick, N.S.W.

OTHER STATES: TRADE AND
DISTRIBUTOR ENQUIRIES WELCOME



Books & Literature

Amateur Radio

**THE BEGINNERS' HANDBOOK OF
AMATEUR RADIO** by Clay Laster
W5ZPV. Published 1979 by Howard
W. Sams, Indianapolis, USA. Stiff
paper covers, 384 pages 214mm x
137mm, freely illustrated. Price in
Australia \$14.20.

As an American publication, this
book understandably presents amateur
radio from the American viewpoint and
pre-supposes that the reader will be
preparing for an FCC-style examina-
tion. However, this is only a minor dis-
advantage in a book which is basically
an up-to-date theory course for aspir-
ing amateurs.

Tutorial chapters include (ab-
breviated): Communication Theory —
Electricity and Magnetism — Vacuum
Tubes — Semiconductors — Power
Supplies — Amplifiers — Oscillators —
Transmitters — Receivers — Transmis-
sion Lines & Antennas — Com-
munications — Practices and
Procedures.

Ostensibly, the book is aimed at
aspirants to the US Novice amateur
licence but my impression is that, with a
little rounding out for the local
syllabus, a reader with this material un-
der his/her mental belt would be well
on their way to a limited or full licence.
Well worth looking at. Our review copy
came from McGills Newsagency, 187
Elizabeth St, Melbourne 3000. (W.N.W.)

GE SCR Manual

SCR MANUAL, FIFTH EDITION,
GENERAL ELECTRIC. Semiconductor
Products Department, Syracuse, New
York. 1977. Paper back, 687 pages, 210
x 135mm, 697pp. Price \$3.00.

The fifth edition is a revised and up to
date version of the well known fourth
edition. The new edition encompasses
not only SCRs, but also TRIACs, PUTs,
UJT's and other associated components.

The manual begins with a description
of Thyristors, their operation, chip
structure and construction. The second
chapter gives the graphical symbols
used within the manual along with their
V-I characteristics. Terminology, an im-
portant facet for understanding these
devices, is given comprehensive treat-
ment.

To successfully design a circuit using
SCRs the ratings and characteristics

must be understood. The SCR Manual
excels here in that all the relevant
specifications are discussed to a depth
suitable for design work.

Triggering methods are discussed in
chapter four and it is here that the UJT,
PUT, DIAC and other devices are dis-
cussed. The design information is quite
adequate for their use in SCR
applications.

Examples and suggested circuits are
given for many applications in later
chapters. Topics covered include full
wave control, feedback systems and
power supplies. Waveforms are usually
given. Full descriptions of circuit opera-
tion aid the reader in understanding
the circuits.

A short chapter at the end of the
manual is devoted to specifications of
diodes and thyristors. A useful supple-
ment to a well written and informative
manual.

For the Engineer, Technician and
hobbyist alike, this manual will prove
invaluable. The only real fault with the
manual is the binding. After the book is
opened a few times it starts to fall apart.
(J.C.)

Computers

**THE WAY THINGS WORK BOOK OF
THE COMPUTER,** published by
George Allen & Unwin Ltd, London.
Soft covers, 137 x 213mm, 245pp,
many illustrations. Recommended
retail price \$9.95.

The original version of this book was
published in German, in 1969. It ap-
parently became so popular that an
English translation was made, and the
English edition was first published in
1974. This is the most recent reprinting.

Basically, the book is an en-
cyclopedia, covering the fields of com-
puting, information science and
cybernetics. It seems to be written
primarily for the technically inclined
lay person, although there is sufficient
mathematics thrown in to make it of
potential value to the professional
engineer or scientist as a reference.

The text is clearly written and quite
readable, which is a little unusual in a
translation from another language. It is
also well served by illustrations, most of
which are diagrams with pickout in a
second colour (red).

Because of the very broad range
covered, the treatment of some of the
topics seems to me a little unsatisfying.

Electronics: the FUN WAY!

At last, there's a book that treats electronics as the really enjoyable hobby it is!

It's called 'Dick Smith's Fun Way Into Electronics' – and it's the ideal introduction to electronics for all ages – from 5 to 95.

Dick Smith's Fun Way uses a unique 'breadboard' wiring system that needs no soldering – so it is **safe** and each project has easy, step-by-step instructions that anyone can follow.

There are twenty exciting projects to build, from continuity checkers to radio transmitters – even a beer-powered radio receiver!

Electronics is fun. Have fun with Dick Smith's Fun Way into Electronics.

- **SAFE**
- **SIMPLE**
- **ECONOMICAL**
- **FUN!**
- **ONLY \$4.95**
- **NOW AVAILABLE**

SCHOOLS, COLLEGES, BOOK SHOPS, NEWSAGENTS, ETC: Ask about our incredible discounts for bulk orders (10 copies or more) of this book. You'll be pleasantly surprised!



And to help you get started:

Save money with 'Fun Way' kits! The components used in the Fun Way book are all common, easy-to-get types. But you can save by buying the kits from Dick Smith: We have assembled two kits which contain brand new, guaranteed components. You save up to 1/3 on the cost of individual components!

SAVE MONEY - BUY THE KIT:

KIT 1: FOR PROJECTS 1 - 10

Build the first ten projects with these components – even includes the baseboard to assemble them on. You can make light flashers, Morse communicators, transistor checkers, continuity indicators, etc etc.

Contains: One particle board, 28 self tapping screws & washers, 1.7m wire, speaker, battery clip, 23 resistors, light dependent resistor, one diode, two LEDs, two transistors, 7 capacitors.

\$6 90

Cat K-2600

KIT 2: FOR PROJECTS 11 - 20

This kit contains slightly more specialised components which, with the components in kit 1, will enable you to make the last ten projects, including radio receivers & transmitters, audio amplifiers, etc.

Contains: 10 capacitors, one variable capacitor, one potentiometer, one resistor, one signal diode, one integrated circuit, one ferrite rod aerial, one crystal earphone, one audio transformer and 70cm hook-up wire.

\$7 50

Cat K-2610

DICK SMITH ELECTRONICS

NSW 125 York Street,
147 Hume Highway,
182 Pacific Highway,
30 Grose Street,
263 Kaira Street.

SYDNEY. Phone 290 3377
CHULLORA. Phone 642 8922
GORE HILL. Phone 439 5311
PARRAMATTA. Phone 683 1133

WOLLONGONG Phone 28 3800

ACT 96-98 Gladstone Street,
VIC 399 Lonsdale Street,
656 Bridge Road,
QLD 166 Logan Road,
SA 203 Wright Street,
WA 414 William Street,

FYSHWICK. Phone 80 4944
MELBOURNE. Phone 67 9834
RICHMOND. Phone 428 1614
BURANDA. Phone 391 6233
ADELAIDE. Phone 212 1962
PERTH. Phone 328 6944

EXCEPT WHERE NOTED, ALL ITEMS SHOWN IN STOCK AT PRICES GIVEN AT TIME OF GOING TO PRESS.

MAIL ORDER CENTRE: PO Box 321, NORTH RYDE NSW 2113. Ph 888 3200. PACK & POST EXTRA.

bankcard
welcome here

SHOPS OPEN 9AM to 5.30PM
(Saturday: 9am till 12 noon)
BRISBANE: Half hour earlier.
ANY TERMS OFFERED ARE TO
APPROVED APPLICANTS ONLY
RE-SELLERS OF DICK SMITH
PRODUCTS IN MOST AREAS OF AUSTRALIA.



NEW BOOKS

NEW — NEW — NEW

Latest editions of some of the most popular books on the subject:

A.R.R.L. Handbook 1979 edition	\$13.95
World Radio TV Handbook 1979	\$15.95
R.S.G.B. Handbook Volume 1	\$21.85
R.S.G.B. Handbook Volume 2	\$18.90
R.S.G.B. Test Equipment for the Radio Amateur	\$19.55
Reference Data for Radio Engineers (New Edition) I.T.T.	\$39.95
Radio Handbook (William Orr) 21st Edition	\$26.50
Master OP-AMP Applications Handbook (Harry W Fox)	\$13.50

Adam Osborne Books

Introduction to Microcomputers, Osborne	
Vol. 0 — Beginners Book	\$12.55
Vol. 1 — Basic Concepts	\$12.55
Vol. 2 Some Real Microprocessors — New Edition, Loose-leaf w/out Binder	\$19.00
With Binder	\$28.00
Vol. 3 Some Real Support Devices — New Edition, Looseleaf w/out Binder	\$19.00
With Binder	\$28.00
6800 Programming for Logic Design	\$13.50
8080 Programming for Logic Design	\$12.55
Z80 Programming for Logic Design	\$13.50
Z80 Assembly Language Programming	\$13.80
6800 Assembly Language Programming	\$15.85
8080A/8085 Assembly Language Programming	\$13.50

New Books from T.A.B.

Antenna Construction for Ham, CB & SWL	\$7.50
Beginners Guide to Microprocessors	\$7.50
Beginners Guide to Computers & Microprocessors with Projects	\$8.50
Giant Book of Amateur Radio Antennas	\$10.95
Master Handbook of Digital Logic Application	\$10.75
Master Handbook of Ham Radio Circuits	\$11.75
Master Handbook of 1001 Practical Electronic Circuits	\$12.50
Master Handbook of 1001 More Practical Electronic Circuits	\$15.95
Master Tube Substitution Handbook	\$6.75
Microphones — How They Work — How To Use	\$7.95
Microprocessor Microprogramming for Computer Hobbyists	\$11.75
Miniprocessors: From Calculators to Computer	\$7.95
Pictorial Guide to Tape Recorder Repairs	\$6.75
The Power Supply Handbook — Editors of 73 Mag.	\$9.95
Towers' International FET Selector	\$6.75
Towers' International Transistor Selector	\$8.50
303 Dynamic Electronic Circuits	\$8.50
Transistor Ignition Systems (Automobile)	\$7.95
Complete Handbook of Public Address Sound Systems — Everest	\$10.75
Complete Handbook of Videocassette Recorders — Kybett	\$7.50
How to Build Your Own Working Robot Pet — DaCosta	\$8.50
How to Select & Install Your Own Speakers — Crowhurst	\$7.50

Microprocessor Books

Basic Primer — Waite & Pardee	\$12.70
The 8080A Bugbook — Microcomputer Interfacing and Programming — Rony, Larsen, Titus	\$15.00
8080/8085 Software Design — Rony, Larsen, Titus	\$13.60
How to Build a Microcomputer and Really Understand It — Creason	\$13.30
M6800 Microprocessor Applications Manual	\$12.50
Microcomputer — Analog Converter Software and Hardware Interfacing — Titus, Rony, Larsen	\$13.60
Microcomputer Primer — Waite & Pardee	\$11.30
Microprocessor Cookbook — Hordeski	\$7.50

Just a few of the thousands in stock. Call in or write. Prices subject to fluctuation. Correct at time of going to press.

If the book you require is not listed below, it can be ordered from us.

Using the 6800 Microprocessor — Poe	\$9.90
The Z-80 Microcomputer Handbook — Barden Jr	\$12.70

American Radio Relay League

Hints and Kinks for the Radio Amateur	\$7.20
The Radio Amateur's VHF Manual	\$7.20
A.R.R.L. Antenna Handbook	\$8.80
Understanding Amateur Radio	\$8.80
The Radio Amateur's License Manual	\$6.20
A Course in Radio Fundamentals	\$7.20
Specialized Communication Techniques for the Radio Amateur	\$7.20
FM & Repeater for the Radio Amateur	\$8.80
Single Sideband for the Radio Amateur	\$7.20
Ham Radio Operating Guide	\$7.20
Electronic Data Book	\$7.20
Solid State Design for the Radio Amateur	\$12.80
Learning to Work with Integrated Circuits	\$4.00
Getting to Know Oscar from the Ground Up	\$6.20

Howard W. Sams Books

Video Tape Recorders (Harry Kybett)	\$13.50
How to Use Videotape Recorders (H. Kybett)	\$8.95
Logic and Memory Experiments Using TTL ICs — Book 1 (Larsen & Rony)	\$14.20
Logic and Memory Experiments Using TTL ICs — Book 2 (Larsen & Rony)	\$14.20
IC OP-AMP Cookbook (Walter C. Jung)	\$17.50
TTL Cookbook (Lancaster)	\$12.95
TV Typewriter Cookbook (Lancaster)	\$13.50
The Cheap Video Cookbook (Lancaster)	\$7.95
CMOS Cookbook (Lancaster) 1977	\$14.25
Active Filter Cookbook (Lancaster)	\$19.95
IC Timer Cookbook (Jung)	\$13.50
Transistor Substitution Handbook	\$7.95
Audio Cyclopeda — Tremaine	\$54.00
Design of Active Filters. With Experiments — Berlin	\$10.75
Design of Op-Amp Circuits With Experiments — Berlin	\$11.80
The 555 Timer Applications Sourcebook With Experiments — Berlin	\$8.50
How to Buy & Use Minicomputers & Microcomputers — Barden Jr	\$14.20
IC Converter Cookbook — Jung	\$18.40
Semiconductor General-Purpose Replacements	\$19.00
TTL Cookbook — Lancaster	\$12.70

Other Titles

World DX Guide — 1st Edition (Ed. Jens M. Frost)	\$9.95
73 Dipole and Long-wire Antennas (Edward M. Noll)	\$6.75
73 Vertical, Beam and Triangle Antennas	\$7.50
Basic Television — Principles and Servicing — 4th Edn (Bernard Grob)	\$18.75
The Truth About CB Antennas (William I. Orr & Stuart D. Cowan)	\$7.00
Simple Low-cost Wire Antennas for Radio Amateurs (Orr & Cowan)	\$9.40
Beam Antenna Handbook — New 5th Edition (William I. Orr & Stuart D. Cowan)	\$7.80
Better Shortwave Reception — New 4th Edition (William I. Orr & Stuart D. Cowan)	\$5.85
All About Cubical Quad Antennas — 2nd Edition (William I. Orr)	\$5.60
The Radio Amateur Antenna Handbook (William I. Orr & Stuart D. Cowan)	\$10.00
Amateur Radio Theory Course — Ameco	\$7.80
Electronic Projects for Musicians — Anderson (Guitar Player Pubs)	\$9.95
Home Recording for Musicians — Anderson (Guitar Player Pubs)	\$13.25
Ham & CB Antenna Dimension Charts, Noll	\$3.90
A Guide to Amateur Radio — Hawker	\$13.00
Metal Detecting in Australia — Webster	\$4.50
Radio Data Reference Book — Giles	\$9.35
Towers' International Op-Amp Linear-IC Selector — Towers	\$18.10

BOOKS & LITERATURE

It is also beginning to show its age here and there: quite significant space is devoted to electro-magnetic relay logic and thermionic valve circuitry, while I could find no mention of bubble memories or CCD devices.

Still, there is a lot of interesting and informative reading, particularly for those interested in the broad concepts of information theory and cybernetics. So at the quoted price of \$9.95 it is really quite good value for money.

The review copy came from the local office of the publisher, who advise that copies should be available from all major book stores. (J.R.)

ICs for Old-timers

GETTING ACQUAINTED WITH THE IC by Rufus P. Turner. Published 1978 by Howard W. Sams Inc, Indianapolis, USA. Stiff paper covers, 112 pages 215mm x 136mm, illustrated by circuits and diagrams. Price in Australia \$7.00.

If you're an old-timer who has never faced up to these new-fangled integrated circuits, or a "new-timer" who hasn't faced up to much at all, this new book by Rufus P. Turner should be a most useful acquisition.

Part 1 provides a highly readable introduction to ICs, which sets out what is necessary with clarity and economy.

In Part 2 he describes a whole series of bench style experiments with a type 741 op-amp — an inexpensive and universal type. This should constitute a very meaningful exercise in instrumentation relative to ICs.

This done, the reader is invited to assemble up to 41 small projects, which are simple only because they are centred on a single 741. In reality, the constructor is utilising about 20 in-built transistors and sundry in-built resistors. Many of the projects are useful gadgets in their own right. Recommended.

Our review copy came from McGills Newsagency, 187 Elizabeth St, Melbourne 3000. (W.N.W.)

BASIC Primer

BASIC PRIMER, by Mitchell Waite and Michael Pardee. Howard W. Sams Inc., Indianapolis, 1978. Soft covers, 137 x 216mm, 240pp, many illustrations. Price \$12.70.

A further copy of this book has been received from Technical Book and Magazine Company, of 289-299 Swanston Street, Melbourne, Victoria 3000. A full review was given in the August 1979 issue, which in summary concluded that it is a good introduction to BASIC for the beginner, although not especially good value for money. (J.R.)

MAIL ORDERS BY RETURN

PLEASE ADD 90c per parcel postage (Vic)
\$1.70 per parcel interstate

TECHNICAL BOOK & MAGAZINE CO.

295-299 Swanston St., MELBOURNE 3000. Ph. 663 3951.

BOOKS

GOOD ENOUGH TO GO TO BED WITH

DICK SMITH'S AMATEUR HANDBOOK

122
PAGES

For the beginner, novice and even the established 'Ham' this book by Dick Smith will give a wealth of information on the Australian Amateur Radio scene. Chapter after chapter of facts about antenna, procedures, exams, equipment etc, etc. Even if you're not a Ham you will find this an interesting book into this fascinating hobby.

Ideal
Christmas Gift

\$6⁹⁵

B-2320

METAL DETECTING IN AUSTRALIA

94 pages of exciting information on how to use metal detectors for finding gold, coins, artifacts etc. Written by a man who has 25 years of gold prospecting experience in Australia. Recommended for the serious prospector!

Ideal
Christmas Gift

\$4⁵⁰

B-4520

DICK'S 'FUN WAY INTO ELECTRONICS'

'Fun Way Into Electronics' has been written by Dick Smith for the person who knows nothing about electronics, but would like to learn.

20 exciting projects (from a simple transmitter to a beer powered radio, among others) with precise instructions and clear illustrations enable you to learn step-by-step the 'Fun Way Into Electronics'



72
PAGES

Ideal
Christmas Gift

\$4⁹⁵

B-2600

BOOKS FOR MICROCOMPUTER ENTHUSIASTS

AN INTRODUCTION TO MICROCOMPUTERS
By Osborne - takes you from square 1 through to a thorough understanding of microcomputer technology

- Vol 0 The beginner's book
- Cat. B-2339 \$9.50
- Vol 1 deals with basic concepts
- Cat. B-2340 \$9.95
- Vol 2 discusses use of real products
- Cat. B-2342 \$27.50
- Vol 3 contains useful information on support systems
- Cat. B-2343 \$17.50

HUGE STOCKS NOW IN! THE WIA AMATEUR RADIO CALLBOOK (1979 Edition)

Yes, we now have large stocks of the new up-dated 1979 edition. Contains the call signs, names and addresses of almost all the amateur operators and SWLs in Australia and PNG, plus loads of data and information - don't delay get your copy NOW!

Ideal
Christmas Gift

\$2⁹⁵

B-2317



BOOKS FOR BEGINNERS

BASIC ELECTRONICS

E A publication 128 pages 23 chapters ideal for beginners
Cat. B-3620 \$3.50

BASIC TRANSISTOR COURSE

Kenian - 218 pages Explains all about transistors
Cat. B-1567 \$7.50

FUNDAMENTALS OF SOLID STATE

Rowe - 120 pages An introduction to semiconductors
Cat. B-3621 \$3.50

ELECTRONICS A PRACTICAL INTRODUCTION

B Brown & P Carr approx 93 pages A really superb book for the beginner. SPECIAL NOTE A PCB (exclusive to Dick Smith Electronics) has been prepared for use with projects in this book
Cat. H-8902 \$6.95

PROJECT ELECTRONICS HANDBOOK

ETI Publications - 74 pages 26 easy to build projects
Cat. B-3652 \$4.75

DICK'S OWN CB BOOK - NOW IN ITS 3rd PRINTING....

A huge 128 pages of information and facts concerning the CB radio scene in AUSTRALIA by the leading authority Dick Smith

Cat. B-2325

\$3⁹⁵

BOOKS FOR AMATEURS

AMATEUR RADIO TECHNIQUES

Hawker - 300 pages Covers HF, VHF, CW, SSB, NBFM, AM plus many more subjects

Cat. B-2040 \$8.25

VHF - UHF MANUAL

Evans & Jessop Covers frequencies above 30MHz plus micro waves

Cat. B-2054 \$17.00

ARRL ANTENNA HANDBOOK

Theory plus practical designs
Cat. B-2204 \$8.75

RADIO AMATEURS HANDBOOK 1979

ARRL - The latest and only amateurs 'bible'

Cat. B-2219 \$13.95

ALL BOOKS IN STOCK AND PRICES CORRECT AT TIME OF GOING TO PRESS

DICK SMITH ELECTRONICS

SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RESELLERS



INFORMATION CENTRE

BASS DOESN'T BACH: I have successfully constructed the Playmaster 25/25 amplifier together with the Dick Smith 3-53L speaker kit. The system has proved excellent and has, in fact, altered our family lifestyle (for the better). I have however one small problem. I am a fan of J.S Bach, and am in real trouble with very low frequency reproduction of the pipe organ. On some passages all the speakers rattle, and distort the music horribly. Would you give some thought to this problem, bearing in mind that I have a zero knowledge of electronics. (R. H. Bendigo, Vic).

● For a lover of classical organ music, we would have advised the larger system, the 3-75L, using a 30cm woofer. Having said that, however, we wonder whether the speaker systems have been assembled correctly: rigid, airtight and wired as per instructions. We are puzzled by your statement that all the speakers rattle. The low frequency notes should affect only the woofers. If the others are rattling, there may be something amiss with the divider network.

It is possible, of course, that you are simply pushing the speakers and amplifier beyond their capabilities. This would be a very real possibility if you are trying to operate the system at high

volume, with the bass boost control advanced beyond "level". A still further possibility is that of acoustic feed-back between the pickup and the loud speakers, perhaps via the floor. Leave the system set in the condition that produces apparent overload, stop the turntable and simply rest the stylus on the stationary record. If a gentle tap on the playing deck produces a sustained "dong" rather than a dull "thud", you have an acoustic feedback problem which will tend to push the system towards overload. Mount the player on a thick foam pad or find another spot for it where the feedback is less evident.

If you feel that everything is in order but you crave for more of everything — particularly Bach bass — it may just be that your family has reached more rapidly than usual the condition that faces most hifi enthusiasts: the hankering for a bigger, better, and more expensive system!

POWER FETs: I was interested to read your article in the September issue, on the design problems of a 100 watt amplifier. Why don't you consider the use of Power FETs? They seem to have many advantages over bipolar transistors and are available in Australia, if somewhat costly. All the reviews on the

commercial versions of Power FET amplifiers have been more than favourable. And there are an awful lot of published designs for amplifiers using bipolar transistors, Darlington or otherwise. (P. L., Maylands, WA).

● At the present time, Power FETs with sufficiently high voltage and current ratings to enable use in a high power amplifier are prohibitively expensive and not really an economic proposition. As soon as the prices come down to a reasonable figure, you can look forward to seeing a FET power amplifier circuit in the pages of this magazine.

COMBINATION LOCK: After assembling the above combination lock I had difficulty in getting it to work. After checking the circuit, I found the connection between IC3-13 and IC2-8 and between IC5-3 and IC2-9 different from the wiring diagram and the PCB. Could you please advise me which is right. (EN, Whyalla Norriw, SA.)

● Although there is a difference between the wiring diagram and the circuit diagram as you mention, it only involves two of the inputs of gate IC2d being swapped around. The circuit will work either way, however, as IC2d is a simple NAND gate. The only suggestion we can make as to why you are having difficulty with the circuit is that you may not have realised that a digit not in the code must be entered before the correct combination so as to reset the circuitry. This scheme was used in preference to a separately labelled reset key, and has the advantage of making the code harder to crack.

THUNDERCLAP: Having constructed the Playmaster series of hifi components (and hoping that the Octave Analyser will be available soon for construction) I've had only one real problem which has occurred in the Playmaster 40/40 amplifier. With only the speakers hooked up, and all inputs disconnected, every time a light switch is turned on or off, a resulting clap of thunder is emitted from the loudspeakers.

If the light switch is rapidly turned on and then off, only a click can be heard. Would installing a mains line filter help the situation? (H. G., Bulleen, Vic).

● To determine whether a mains filter is desirable you must first find out whether the interference is entering

RADCOM QUALITY COMPONENT

105 ELDRIDGE ST., BANKSTOWN
PHONE: 709-4706

Air spaced variable capacitors

10pF-25pF-50pF-100pF
250pF ALL AT \$2.50
500pF at \$5.00

All preferred values of capacitors

All preferred values of resistors

PLUGS CONNECTORS AND ACCESSORIES IN STOCK

High voltage fixed capacitors, all types of toggle and wafer switches.

Multi-tapped transformers

0-15v 1 AMP \$5.00
0-15v 2 AMP \$9.30

TRY US FOR THE HARD TO GET COMPONENTS

STOCKIST FOR

silicon valley

If you are unable to complete an "Electronics Australia" project because you missed out on your regular issue, we can usually provide emergency assistance on the following basis:

PHOTOSTAT COPIES: \$2 per project, or \$2 per part where a project spreads over multiple issues. Requests can be handled more speedily if projects are positively identified, and if not accompanied by technical queries.

METALWORK DYELINES: Available for most projects at \$2 each, showing dimensions, holes, cutouts, etc., but no wiring details.

PRINTED BOARD PATTERNS: Dye-line transparencies, actual size but of limited contrast: \$2. Specify positive or negative. We do not sell PC boards.

PROJECT QUERIES: Members of our technical staff are NOT available to discuss individual projects, either in person at our office or by telephone.

REPLIES BY POST: Limited to advice concerning projects published within the past two years. Charge \$2. We cannot provide lengthy

answers, undertake special research or discuss design changes.

BACK NUMBERS: Available only until our stocks are exhausted. Within three months of publication, face value. Four months and older, if available, \$2. Post and packing 60c per issue extra.

OTHER QUERIES: Technical queries outside the scope of "Replies by Post" may be submitted without fee, for reply in the magazine, at the discretion of the Editor.

COMMERCIAL, SURPLUS EQUIPMENT: No information can be supplied.

COMPONENTS: We do not deal in electronic components. Prices, specifications, etc., should be sought from advertisers or agents.

REMITTANCES: Must be negotiable in Australia and made payable to "Electronics Australia". Where the exact charge may be in doubt, we recommend submitting an open cheque endorsed with a suitable limitation.

ADDRESS: All requests to the Assistant Editor, "Electronics Australia", Box 163, Beaconsfield, 2014.

the amplifier via the mains cord or via the speaker leads. Disconnect the speakers and connect a pair of headphones instead. Now switch the lights on and off and listen for the interference. If the interference is still present, then the path would appear to be the mains cord and so a mains filter would be of use.

On the other hand, the more likely result is that the interference path is via the loudspeaker leads. This makes us wonder whether you have omitted the two 0.1uF capacitors which are connected between the earth return lines and the chassis, at the speaker terminals.

PLOP ELIMINATOR: Having constructed graphic equalisers, dynamic range enhancers and other audio equipment, I feel that a "plop" eliminator would be very useful when tape recording records with damaged grooves. Such a unit would also be ideal for eliminating, or at least reducing annoying clicks and plops when copying old 78s.

As many types of ICs are now available, and commercial plop eliminators are quite expensive, a pro-

ject of this nature should be a practical proposition.

Have you published any information along these lines as yet, or do you have anything planned for the near future. (R.B., Burrendah, WA).

● We have never published information on constructing a plop eliminator. However, the idea is an excellent one, and we shall keep it in mind as a possible future project.

Notes & Errata:

INDUCTANCE-CAPACITANCE METER (June 1979, File No 7/CM/12): It was mentioned in this article that a 0-50uA or 0-100uA meter could be used with appropriate component changes. However, unless major changes are made it will not be possible to obtain full scale deflection on the 100uA meter when measuring capacitance.

DECISION DATA PRINTER (p90, November, 1979): The price of \$2395 given for the Decision Data Model 6540 serial printer is incorrect. The correct price is \$2700 plus sales tax.

RS-232C interface . . . ctd from p84

interface, and you don't want to modify it — can't you make up a current loop/RS-232C adaptor? Yes, you can. In fact a circuit designed for this very purpose is shown in Fig. 4.

As you can see, it is again quite simple. Opto-couplers are used on the current loop side, while the RS-232C side uses a simplified version of the circuitry in Fig. 3. Apart from the opto-couplers, all components are readily available low-cost items.

The electronics side of Fig. 4 should cost you around \$5, apart from a wiring board and a suitable power supply. The

power supply can be quite modest, as it only has to supply +12V at around 80mA and -12V at around 90mA.

You may find that the dearest part of the interface is the DB-25 socket, and the matching plug. These are not cheap, unfortunately.

Well, I hope that the "mysteries" of RS-232C are now quite clear to you. It's really not very complicated, and you can provide your microcomputer with a simple RS-232C interface at very low cost. Why not do so, and give yourself the added flexibility?

join our

Gold Rush

with the

RED BARON

...not only the best — but the **EASIEST!**

2 Coils
8" & 12"

Lifetime
Warranty

revolutionary
new S.P.D.
(Synchron-
ous Phase
Discrimination)
circuitry
enables
Discrimination
at VLF depths!

the professionals

This is the unit that
WILL DISCRIMINATE
AND CANCEL

GROUND MINERALIZATION **\$660**
AT THE SAME TIME! *+ freight*

**ORDER NOW BY MAIL
OR CALL AT SHOWROOMS**


ELECTRON 2000

44 Brown Road,
Broadmeadow.
N.S.W. 2292
Or Phone 69 1222 (049)

NEW...

DIGITAL HANDHELD MULTIMETER ...

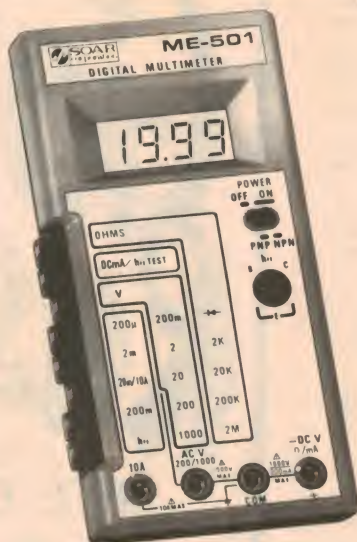USHERS IN A DYNAMIC GENERATION OF MULTIMETERS



SPECIFICATION

ME-501A

VOLTS: DC — 200MV 1000V
ACCURACY 0.8%
AC — 1000V
ACCURACY 1%
DCMA — 200UA 10%
ACCURACY 1.2%
RESISTANCE: 2K 2M
TRANSISTOR HFE CHECKER: 10%

ME-501A FR. \$70 TAX PAID

ME-501B

Same as ME 501A plus continuity checker.

Available From:

NSW: RADIO DESPATCH;
M. DE LAUNAY;
DAVID REID.
VIC: ELLISTRONICS;
ARLIN; TECH SCIENTIFIC.

SA: PROTRONICS;
WA: RESERVE
QLD: WILBER

Also Available:

ME-521 DX-3.5 DIGIT LED
ME-522 3.5 DIGIT LED
ME-523-3.5 DIGIT LED
* NEW
MC-545-4.5 DIGIT LED

DOT MATRIX IMPACT PRINTER MODEL 8300

The model 8300 serial dot matrix printer features 125 characters per second print speed and one line buffer memory.

1. Print speed : 125 CPS (50Hz/60Hz)
60 LPM (50Hz/60Hz)
2. Interface : 8-bit parallel-standard
RS-232C/TTY-option
3. Data buffer : 1 line
4. Code : ASCII (96 characters)
5. Character font : 7 x 5 dot matrix (7x9 option)
6. Number of columns : 80 column
7. Character spacing : 10 CPI (Enlarged character printing is available)
8. Line spacing : 6 LPI
9. Paper width : Width: from 4.5 inch to 9.5 inch (including sprocket margin)
10. Number of Copies : Original+3 copies nominal (max. total thickness 0.013 inch)
11. Paper feed method : Pin feed
12. Ribbon : 13mm width, purple color
13. Operating temperature : 10°C — 35°C (50°F — 95°F)
14. Operating humidity : 10% — 80% (Non condensed)
15. Power input : 115VAC ± 10%/60HZ
220 or 240 VAC ± 10%/50Hz available
16. Power Consumption : Printing 100W
Non printing 7W
17. Dimension : approx. 449 (W) x 375(D) x 185(H) mm
18. Weight : approx. 10Kg

—The above specifications may be changed without prior notice.—



**AMPEC ENGINEERING
CO PTY LTD**

1 Wellington Street, Rozelle 2039
PO Box 132, Rozelle 2039. Phone (02) 818 1166

MARKETPLACE

FOR SALE

CRITICS' SELECTIONS OF BEST MIND — stimulating games from USA for Commodore PET and TRS-80. Send SAE for list. Softronics Micro Systems, Box 238, Lindfield, NSW 2070. PET Sales & Programs.

TRS-80 General Ledger Accounting System Level 1, uses 2k memory. Listing \$10, Cassette \$13.95. Micro-Basic 80, 9 Myers Crt, Doncaster, Vic, 3108.

OBSOLETE STOCK

We have a quantity B/W TV Games with to external handcontrols, AC Adaptor and Circuit Diagram \$14.50

Colour TV Games with two external handcontrols and Circuit Diagram \$18.00.

100mW Speakers, 75 Ohm \$0.60ea, Fiber Optics, 5 meters 0.040" \$4.50 2 meters 0.060" \$2.90, 5 meters 0.060" \$7.20, Glass Lenses \$0.60, Siemens UUA170 \$1.20, UUA180 \$1.20, 723C \$0.80, LM 340T-24 \$0.65, LM-340T-18, \$0.65, LM-340-15 \$0.65, 2N5777 Photodarlington transistor \$0.80ea or \$45.00 per 100 Siemens LD242 Infrared Led \$1.00, Siemens Magenta Resistor \$1.50 ea, Siemens photo-voltaic cell in miniature glass cell \$1.50 ea, Augat 28-pin IC Socket \$0.80 ea or \$6.50 per 10 or \$50.00 per 100

Post & pack \$1.00 per order
DELTA DESIGN LABORATORY
P.O. Box 147, St. Albans 3021

Japanese Transistors & IC's

Catalogue — Send 40c (Aust) stamp

CTV Transistor prices:


2SC 1106	\$3.10	2SC 1325	\$5.60
2SC 1114	\$6.00	2SC 1413	\$6.50

Min Order \$10 plus \$1.50 post. Bank Cheques, money orders in Australian dollars.

N. NAKAGAMI

457-22 Hasama-cho
Kasugai, Aichi-ken JAPAN 487

TIME CLOCKS SANGAMO

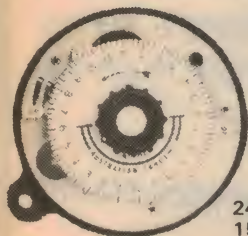

LESS
DAY OMIT
DEVICE
\$13.50

WITH
DAY OMIT
DEVICE
\$16.00

240V 50 cs
15A Contacts

Used tested and guaranteed
PACK & POST N.S.W. \$2.00
Vic. & Qld., S.A. \$2.90, W.A. \$3.40

CLOCK DISPOSAL CO.

P.O. Box 147
LINDFIELD, N.S.W. 2070

ELECTRONIC ORGANS Build your own! Send 45c stamp for fullest details of the SCHOBBER (USA) organ kits. Schober Organs (Aust), PO Box 22, Guildford NSW 2161 (Established 21 years.)

KEYBOARD KITS — Popular ASR-33 Format, ASCII output 53 keys and ASCII logic IC's all mount on same PCB. Three user definable keys, easy to follow instructions Keyboard kit \$59.60, or assembled and tested \$68.00, optional mounting frame \$8.20. PCB edge contour \$2.00, post and pack free in Aust. For more info contact CANNY COMPUTING, PO Box 65, Nth Carlton, Vic Ph. 347 5513.

COMPUTER PERIPHERALS for sale, all in used condition most complete with all manuals. Potter LP 1000 line printer \$1000, BRPE110 paper tape punch \$600, GNT paper tape reader (8-level ISO) \$500, Singer model 10 workstation (ASCII Flexowriter) \$700 Contact BABER ENTERPRISES 2 Monomeeth drive, Mitcham, Vic. 3132 (03) 873 3223.

DEVICES M19 8 CHANNEL POLYGRAPH, 3 pressure amplifiers, 1 ac high gain amp, 1 dc high gain amp, blood pressure, Hg strain gauge transducer amp and ecg amp. Selective filtering on all channels, patch panel connector to outputs and displays. Service and instruction manuals. Enquiries to Cortek Instruments (02) 438 3744.

BOOMERANG TAPE RECORDING CLUB full details, 9 x 4 SAE PO Box 118, Wellington, NSW 2820.

SORCEROR SOFTWARE

Programs include MIMIC musical game, MORSE code, HEX conversions, OHMS law, RENUMber, PIANO and HAM exams. Budget priced from one dollar each. Send 20c stamp for list

BANDSPREAD

35A Carnarvon Road
Roseville 2069

Computer Salesman

(Microprocessor based systems)

Capable sales oriented person required to manage home/hobby/small business division of our company.

Duties will include obtaining and evaluating new products, marketing and ensuring continuity of supply of hardware and software. Responsibility will be to our Technical Director.

The ideal background will be from sales engineering of small business systems. Computer programmers or academics would probably have insufficient commercial experience; however if you think you may be suitable, please apply.

Good salary and conditions.

Contact: Mr Gary Johnston,

Marketing Manager,

Dick Smith Electronics Pty Ltd

PO Box 321, North Ryde, NSW 2113.

Telephone (02) 888 3200

DISPLAY ADVERTS IN MARKETPLACE are available in sizes from a minimum of 2cm x 1 col rated at \$11 per col cm.

CLASSIFIED RATES \$2 per line per insertion payable in advance. Minimum two lines.

CLOSING DATE is six weeks prior to the on-sale date. Issues are on sale the first Monday of each month.

ADDRESS all classified orders, copy, enquiries, etc, to: The Advertising Manager, **ELECTRONICS AUSTRALIA**, Box 162, Beaconsfield 2014.

L.C.R. BRIDGE, Precision B&K (Denmark) comparator type. Mint condition \$165. Details Wentworth Electronics, 77 Wentworth Ave. Wentworthville NSW 2145 Ph. (02) 636 4686.

COMPUTER CASSETTES: QUALITY "PECOS" C-10 BLANKS \$4.50 for package of four or \$10.95 (leaderless) plus 90c postage & packaging. Quantity discounts available on request. Please make Cheque/Money Order payable to PECOS, P.O. Box 382, Royal Exchange, Sydney 2000.

AMIDON TOROIDS — REFER ARRL HANDBOOK. T200-2, \$6ea. T106-2/6, \$3ea. T50-2/6/10/12, \$1.20ea. T25-2/6/10/12, 70c ea. Orders over \$10 less 10%. P&P 80c. Closed Xmas + 3 weeks. SAE for information. U.S. Imports, Box 157, Mortdale, NSW 2223 Tel (02) 579 3848.

NEGATIVE AIR IONIZER, Medicor (Hungary) Bion 79 improved personal model helps many respiratory complaints, migraine headaches, fatigue in air conditioned buildings, nervous tension etc. Reduces pollution from dust, smoke, bacteria, odours & vehicle exhausts. \$87.50 posted. Wentworth Electronics, 77 Wentworth Ave. Wentworthville NSW 2145. Ph. (02) 636 4686.

Amateur Radio Manager

A capable person, preferably with the AOCP or AOLCP license, is required to supervise our efforts to market Amateur radio equipment and accessories in Australia.

Whilst we expect the suitable person to have a thorough technical background, preference will be given to applicants who have a proven track record in sales administration.

Please note that we will consider a semi-retired person in this instance for a part-time position.

Duties will include the evaluation of new lines, ensuring constant supply of existing lines, training sales staff and resolving technical problems regarding the equipment sold.

The appointee will be responsible to the Managing Director through the Technical Director.

Excellent salary and conditions await the right person.

Apply in writing to:

Jim Rowe,

Dick Smith Electronics Pty Ltd,
PO Box 321, North Ryde, NSW 2113
Phone (02) 888 3200


Complete confidence assured.

SYN-1 Single Board Computer . \$210.00

KTM-2 CRT/TV Keyboard terminal module \$349.00

BAS-1 8K BASIC ROM for SYN-1 . \$149.00

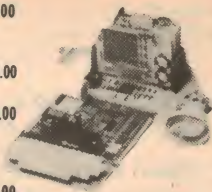BUFFERED MOTHERboard for SYN-1, KIM-1 or AIM-65 systems . . \$179.00




16K-8 fully tested memory board
WRITE PROTECT
and **BANK switching**
for SYN-1, KIM-1 or
AIM-65 systems . . \$360.00

EPROM

Programmer and EPROM/ROM Board MEMORY mapped EPROM programming will program up to 16K per command firmware in PROM included. For SYN-1, KIM-1 or AIM-65 systems

\$345.00

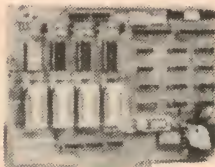

AUTOMATIC TELEPHONE DIALER PROM
dialling 32 numbers plus other options .

\$180.00



PRESETTABLE COUNTER 5 digits suitable for counting, batching and numerical control .

\$150.00



DIGITAL TACHOMETER
\$120.00



STEPPING MOTORS wide range for N.C. Control, Plotters, Variable speed, Servo Control etc. From . \$49.50



STEPPING MOTOR DRIVING CIRCUITS for 3 or 4 phase in Mode 1 phase 2 phase 1-2 phase excitation. From \$12.00

THUMB WHEEL SWITCHES — \$2.20ea.
PROXIMITY TRANSDUCERS — \$15.00ea.



Mail orders add \$3.50 for postage and packaging

G.C.S.

67 Blackshaw Avenue,
MORTDALE 2223.
Telephone: 570 1225
(Trade enquiries invited)

Marketplace

DEFROST SOFTWARE — 26 Station St., Nunawading, Vic., 3131 (03) 878 9276. Any order of 3 or more items less 10%. Schools less 10% *3 Speed modification for TRS80 1/2 speed, normal and double speed a very simple kit only 4 connections to keyboard easily reversible. \$29.95. *Electric Pencil for Level 2 16K. The ultimate word processor. \$100. *Clone II. Allows you to copy ANY program, displays ASCII on screen while loading, copies poorly recorded tapes. Protect your programs by making back-up tapes. \$18. *Business Package L1 4K includes 6 programs. \$29. *Golf Crossout L1 4K, L2 16K, \$10. *Bowling L1 4K, L2 16K, \$10. *Santa Paravia become the ruler of a medieval city L1&L2, \$10. *Space Trek IV, trade or wage war on a planetary scale L2 16K, \$10. *Oil Tycoon, becomes the world's richest tycoon L1 & L2, \$10. **BOOKS:** An introduction to microprocessors 'o'. The beginner's book numerous illustrations and photographs, \$11.75. An introduction to microprocessors 'I'. A best seller tells you everything you need to know on computer applications, \$12.50. Some common basic programs, 76 programs covering financial math, statistics and general interest programs. Every program has been tested and sample programs and source listings are published along with sample runs, \$12.50. Payroll with Cost Accounting — 'Osborne', \$20. Accounts Payable — 'Osbourne', \$20. General Ledger — 'Osborne', \$20. Z80 Programming for logic design — A must for the serious programmer, \$12.50. Z80 Assembly language programming — The best, \$13.60. MAIL ORDER — POST FREE.

PAPER TAPE READER. Siemens Model 108A 30 Char/Sec. Excellent condition \$65. Ken Ryan, P.O. Box 50, Croydon, NSW 2132. Phone (02) 799 3000.

ORGAN PARTS — Two 44 note manuals complete, 13 note pedals, Swell pedal, stop tabs — \$250 the lot. (02) 913 9636.

INTERESTED IN HAM RADIO?

W1A. study materials now available. Novice Kit: Texts and Morse tapes \$15.00 complete. 500 objective questions (novice to full call technical) \$2.50. Post Included.

R. Wilson P.O. Box 109 Toongabbie 2146.
Voluntary produced solely for the good of amateur radio.

WANTED

WWII 122 Transceiver, For restored Blitz. (02) 53-5581.

READER SERVICE

FRONT PANELS. Repeater and Mimic panels. Labels. Nameplates. Scales etc Machine engraved to your specifications in metals or plastics. From Commercial & Industrial Engraving 9 Napier St, Westmead 2145. Phone (02) 635 8537.

Z80 — 8080 AND SC/MP Programs Disassembled from listing \$20 per K (Hex or Octal) or from E-Proms 2708-2716 or 5204 \$10 per K. TRS-80 Basic or machine code programs to your requirements. Also machine code programs for above processors. Write to Micro-Assistance P.O. Box 49, Sandy Bay, Tasmania 7005.

IF YOU PROGRAM MICROPROCESSORS, THESE SHEETS ARE FOR YOU

Writing microprocessor programs on blank or plain ruled paper is messy and time consuming. To make the job easier, Electronics Australia has produced custom-designed programming sheets for use with virtually any microprocessor system. The sheets feature columns for a 4-digit address, up to six digits of instruction code or data, labels, mnemonics, and comments. There is space for 46 lines per sheet, and the sheets are provided with space for program title, data and sheet number. All for less than 5 cents per sheet, posted!

PRICED AT \$2.00 FOR 50 SHEETS (plus 40c for postage anywhere in Australia)

Available only from Electronics Australia, 57 Regent St, Sydney (PO Box 163, Beaconsfield, NSW 2014)

NEW from etone

380mm (15") loudspeakers, 100mm (4") voice coils, 9.5kg ceramic magnet structure, edgewound aluminium ribbon, high efficiency.

150mm (6") loudspeakers, 40 watts RMS, multiple driver array.

Details from **ETONE**

53 STANLEY STREET,
PEAKHURST, N.S.W. 2210

L.E. CHAPMAN

122 PITT RD, NTH CURL CURL
MAIL ORDERS BOX 156, DEE WHY, NSW 2099
TEL.: 93 1848

SPECIAL TRANSISTORS

AD161-162 \$2.50 pair
2SC901A \$1.50 each
BC548B 10 for \$1
Diodes OA636 50 cents each

Speakers: 8 ohm, 3 inch \$2.50
5 x 4 47 ohm \$4.50


Speakers: 5 x 4 1500 ohm CT \$4.50

Power Leads: 240 volt, suit most tape recorders, radios, etc. \$1 each.

TV Stick Rectifiers 20SC \$1.00

Philips TV Colour TV Convergence Boards \$3 each

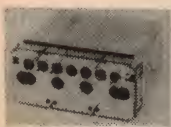TV Demodulator Units, complete with TCA IC \$1 each



455KC IF Transformers for valve radios. \$1 each, also aerial and OSC coils, 75 cents each.

Transistor Miniature Speaker and Drive Transformers. \$1 pair.

Car Radio Suppressors 3 for \$1

Philips TV Yokes AT10721-00 \$5 each

Test Prods suit most meters \$1 pair

Tape Recorder Motors, 240v, heavy duty, reel-to-reel \$5 each

Slide Pots, 250K-50K 3 for \$1
Dual 500K 3 for \$1
1 Meg 3 for \$1
2 Meg 3 for \$1
Including Fancy Gold Knobs.

RESISTORS

150 ohm, 5W, 20c
10 ohm, 5W, 20c
47 ohm, 5W, 20c
12 ohm, 3W, 20c
2.5 ohm, 3W, 20c
33 ohm, 3W, 20c
8 ohm, 10W, 25c
4000 ohm, 10W, 25c
1000 ohm, 5W, 20c
330 ohm, 10W, 25c
220 ohm, 5W, 20c
5 ohm, 5W, 20c
220 ohm, 10W, 25c
950 ohm, 3W, 20c
115 ohm, 5W, 20c
10 ohm, 5W, 20c
1k ohm, 5W, 20c
5000 ohm, 5W, 20c
6.8k ohm, 3W, 20c
330 ohm, 10W, 25c
6800 ohm, 10W, 25c
1500 ohm DUAL, 21W, 50c
50 ohm, 5W, 20c
330 ohm, 5W, 20c
1k ohm, 5W, 20c
820 ohm, 5W, 20c
12 ohm, 10W, 25c
470 ohm, 7W, 20c
4700 ohm, 4.5W, 20c
5000 ohm, 10W, 25c

ELECTROS

470uF 25V 5 for \$1
400uF 10V 5 for \$1
47uF 63V 5 for \$1
350uF 16V 2 for \$1
27uF 160V 5 for \$1
25uF 63V 10 for \$1
22uF 160V 10 for \$1
47uF 16V 5 for \$1
47uF 200V 5 for \$1
2200uF 10V 10 for \$1
68uF 16V 10 for \$1
1000uF 25V 5 for \$1

CAPACITORS

0.0039uF 1500V 20c ea
6N8 1500V 20c ea
0.0068uF 1500V 20c ea
1200PF 400V 10 for \$1
0.068uF 400V 5 for \$1
2200PF 630V 10 for \$1
0.47uF 250V 10 for \$1
0.10uF 400V 5 for \$1
0.082uF 160V 10 for \$1
26k 250V 10 for \$1
0.041uF 400V 10 for \$1
0.033uF 250V 5 for \$1
0.027uF 100V 20 for \$1
220uF 10V 10 for \$1

SPEAKERS

MSP 9 x 6 15 ohm \$6.00
9 x 6 8 ohm 6.00
12 watt 8 inch dual cone 8 ohm 9.00
7 x 5, 15 ohm 5.50
7 x 5, 8 ohm 5.50
6 inch dual cone, 8 ohm 5.00
6 inch single cone, 15 ohm 5.00
6 inch dual cone, 27 ohm 8.50
5 inch dual cone, 27 ohm 5.00
5 inch single cone, 3.5 ohm 3.50
5 inch single cone, 8 ohm 3.50
5 inch single cone, 15 ohm 3.50
4 inch dual cone, 4 ohm 6.00
6 inch dual cone, 3.5 ohm 6.00
4 inch single cone, 15 ohm 3.00
4 inch single cone, 27 ohm 4.50
5 x 3, 27 ohm 3.50
5 x 3, 47 ohm 3.50
7 x 5, 3.5 ohm 5.50
12 watt 8 inch dual cone, 3.5 ohm 8.50
5 x 7 single cone, 27 ohm 6.50
3 inch, 8 ohm 2.50
6 x 4, 8 ohm 2.50
6 x 4, 15 ohm 2.50
6 x 9, 27 ohm 6.50
6 x 9, 47 ohm 6.50
3 inch, 8 ohm 2.50

SPEAKERS SPECIAL

\$1 pair 2 1/4 inch
5 x 3, 8 ohm
2 for \$3
SPECIAL
8 x 4, 15 ohm, \$4
8 x 4, 8 ohm, \$4
2 3/4 inch, 8 ohm, \$1.50
6 x 9, 3.5 ohm, \$6
2 inch, 8 ohm, 2 for \$1
6 inch dual cone, 4 ohm, \$5

SPECIAL

100 mixed resistors, all useful, \$2
100 Mixed capacitors, fresh stock, \$2

AUDIO LEADS

3.5m to 3.5m, 7ft, 75c
3.5m to 6.5m, 7ft, 75c
6.5m, 7ft, 50c

MICRO SWITCH

5A, 250V AC, 75c each

TUNING CAPS

2 and 3 gang, \$1 each
min 2 gang, 50c

FUSES

0.5A, 2A, 3.25, 10 for \$1
In line fuse holders, 30c
RCA jack plugs and sockets, 40c pair

PILOT LIGHTS

Screw in 6.3V, 10 for \$10.50
12V, 10 for \$1
24V, 10 for \$1

100 Mixed Resistors, all useful \$2.00


Transistor Specials AD149 \$3.50 pair

Special! 100 mixed capacitors — fresh stock, all useful.

\$2.00


SUPER SPECIAL

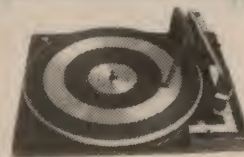BSR RECORD, CHANGER. Cuing device 11in turntable, brand new. \$35, P&P NSW \$2.50; Interstate \$3.50. WA \$4.50.



ICS TBA 760, TBA 540, 7400, TDA 1005, TCA 750, TCA 420K, TBA 720, \$2.50 each.

6 Position Push Button Switch, \$1.

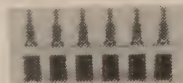

SPEAKER SYSTEMS
INCLUDING TWO 6x4 SPEAKERS
5 Watts RMS \$7 each
Pack & Post NSW \$1.50
Interstate \$2.50 For Singles or Pairs



SPEAKER SYSTEMS

15 watt RMS including 2 6in dual cone, each cabinet \$16 each. P&P NSW \$2.50; Interstate \$3.50. WA \$4.50.



TRANSISTOR EAR PIECES PLUGS AND LEADS, 3 FOR \$1 PICK UP ARMS MONO COMPLETE WITH CARTRIDGE, \$4.50
PICK UP ARMS STEREO COMPLETE WITH STEREO CARTRIDGE, \$6.50


TV TUNER VALVE TYPE



\$2.50
Including valves
P&P \$1.00
Interstate \$2.50

SUPER SPECIALS

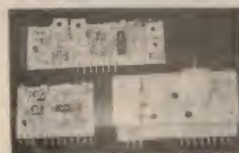FM STEREO TUNER KITS
SETS OF 3 MODULES INCLUDE FM TUNER, DECODER & IF/DETECTOR. CIRCUIT DIAG. SUPPLIED: CAN BE USED WITH AMP MODULES.
ONLY \$18! PP \$1



VORTEX DECKS

COMPLETE WITH HEADS & CIRCUIT FOR AMPLIFIERS FOR THE DECK.

ONLY \$25!

SPARE ERASE HEADS for above \$2 ea
PP NSW \$2.50 INTERSTATE \$3.50
WA \$4.50



24V MOTORS

REVERSIBLE
only \$2.50 each



VU & BALANCE METERS




STEREO VU
\$3



12 Kn 100uA
\$2

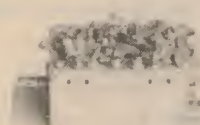PHILIPS
TV TUNER
Transistor
NT3024
NT3030
NT3032
Colour—PP \$1
\$10 ea



**Don't let your valuable issues
go astray**

ELECTRONICS AUSTRALIA BINDERS

These attractive binders finished in brown plastic with gold lettering will keep your back issues of Electronics Australia neat and tidy.



*** HOLDS
12 ISSUES**

Available from
Electronics Australia,
57 Regent St, Sydney. PRICE: **\$4.50**
or by mail order from Electronics
Australia, P.O. Box 163, Beaconsfield 2014.
PRICE **\$5.50** NSW; **\$6.50** other states;
or 6 for: **\$28.00** NSW; **\$30** other states.

*Magazines prior to April 1971 will need to be trimmed to fit binder

ADVERTISING INDEX

ADVERTISER	PAGE
A & R Soanar	2, 78
AGS Electronics (Aust.) Pty Ltd	43
ASP Microcomputers	82
Ace Radio	106
Adaptive Electronics Pty Ltd	82
Alfred Dunhill International Ltd	facing 113
Ampec Engineering Co Pty Ltd	20, 140
Audio Engineers Pty Ltd	48
Audio Telex Communications Pty Ltd	121
Australian Maritime College	115
Australian Radio DX Club	130
Brewco Electronics	12
Bright Star Crystals	130
Byte Shop, The	109
Cash-More Enterprises Inc.	76
Chapman L. E.	143
Classic Radio	38
Clock Disposal Co.	141
Coates, H. F. & Co Pty Ltd	142
Computerware	100
Daneva Control Pty Ltd	98
Danish Hi-Fi	41
David Reid Electronics	75
Deitch Bros	114
Delta Scientific Product Distribution	87, 100, 141
Dick Smith Electronic Group	14, 30, 31, 33, 46, 67, 88, 104, 124, 135, 137, 141
Dwell Pty Ltd	92
Edible Electronics	102
Electrocraft Pty Ltd	132
Electron 2000	139
Electronic Agencies	132
Electronic Development Sales Pty Ltd	29
Elmeasco Instruments Pty Ltd	19
Embryonic Systems Pty Ltd	100
Enson Equipment	117
Etone Pty Ltd	142
Fairchild Australia Pty Ltd	85
Ferguson Transformers Pty Ltd	69
General Electronic Services Pty Ltd	116
Hagemeyer (Aust.)	IBC
Home Talkie Co of Aust.	26
Imark Pty Ltd	59
Instant Software	99
John F Rose Computer Service Pty Ltd	73, 95, facing 73
Lafayette Electronics	37
Logic Shop, The	93
Looky Video	97
Micro-80	120
Microprocessor Applications	102
National Panasonic (Aust.) Pty Ltd	OBC, facing 32
Nobaru Nakagami	141
Non-Linear Systems (Aust.) Pty Ltd	122
Paris Radio Electronics	101
Pennywise Peripherals	96
Philips	6, IFC
Pitt Street Microcomputer Centre	99
Plessey Components	35
Quality QSL Pty Ltd	101
RCS Radio	133
Radcom Pty Ltd	138
Radio Despatch Service	117
Radio Parts Group	36, 45
R.M.I.T.	126
Rod Irving Electronics	22
Rowe H & Co.	111
Royston Electronics	117
SM Electronics	92
Sabtronics International	facing 112
Scope Laboratories	70
Sontron Instruments	97
Stewart Electronics	80
Stotts Technical College	53
TEAC Aust Pty Ltd	In Centre Magazine
Tandy International Electronics	8
Tasman Electronics	142
Technical Book & Magazine Co.	136
Texas Instruments Australia Ltd	facing 72
Transwest Trading Co	134
University Graham Instruments Pty Ltd	76
Vicom International	17, 56, 129
Video Technics	126
Warburton Franki	23, 64
Wireless Institute of Australia	127
Zero One Electronics	109

SUBSCRIPTION SERVICE



**ELECTRONICS
Australia**

Subscription Rates
\$18.00 per year
within Australia.
\$A21.00 per year
elsewhere.

Make sure you receive every copy of the magazine by ordering it from your newsagent or the publisher. For publisher subscriptions post this coupon, with your remittance, to Electronics Australia Subscription Dept., John Fairfax & Sons Ltd, GPO Box 506, Sydney 2001. Subscription will start with first available issue.

Name
Address
Postcode Enclosed is for years

REAL HI-FI

AND IT'S ALL IN OUR COLOUR CATALOGUE

The truth is, JVC have always produced real hi-fi components and we believe this current range represents JVC's finest range ever. Here are some real innovations and performance features to whet your appetite:— Quartz locked turntables with uncanny accuracy; Receivers/Amplifiers, some with built-in SEA Graphic Equaliser and DC, class A/B amplification; Cassette deck with JVC automatic computerised tape tuning; Computer designed

speaker systems; Separate but matching JVC components designed to compliment one another; perfectly. And all this real hi-fi know-how is yours ...merely for the asking.



**If you think they look different,
wait till you've heard them!**

FREE OFFER COLOUR HI-FI CATALOGUE

Just fill out this coupon and we'll fill you in on what's available and new in terms of JVC hi-fi entertainment...and it's all FREE!

Name _____

Address _____

Postcode _____

WT1323/EA/79

I am especially interested in...

- ☐ Cassette Decks
- ☐ Matching Systems ☐ Amplifiers
- ☐ Speakers
- ☐ Turntables
- ☐ Receivers

Just address your envelope to...
JVC Hi-Fi Advisory
Service,
Post Office Box 307,
North Ryde,
N.S.W. 2113

JVC

the right choice



Shoot for instant replay and the family video album.

National Portable Video Home System

Make the good times last; keep your memories on video cassette. Watch a child growing up. Check your golf swing. The uses of portable video are as varied as your lifestyle. Simply connect the recorder and camera to your imagination.

You record in full colour and playback up to three hours on one cassette. This portable National system works off mains power, re-chargeable battery or car or boat battery. You can dub in a voice track or background music and you can hold a still frame for close inspection.

This camera is easy to operate and features a built-in microphone, control unit for various light conditions, zoom lens and an electronic viewfinder that doubles as a monitor for instant replays on location. If your shot isn't to your satisfaction, you simply shoot again. There is no processing. It's instant. For home showings, just connect the video recorder to your TV set.

National: Setting the pace in today's video world.



National

There's so much more to National.

For further information, write to National VHS PO Box 278, Kensington NSW 2033.

QMSH 2330